

# Stacking Power MOSFETs

## NMOS Configuration

By Kendrick De La Pena

Updated: 08/07/2014

# Test 3

- NMOS Configuration
- MOSFET:
  - STP8NM60
- Calculated Capacitance Values:
  - 50pF, 100pF, 150pF, 200pF
- Max Voltage:
  - 2500 V
- Changes:
  - Fabricated a new board

# Test 3 – Calculations

$$C_{gs} = 440 \text{ pF}$$

$$C_{gd} = 10 \text{ pF}$$

$$V_d = 500 \text{ V}$$

$$V_{gs} = 20 \text{ V}$$



$$A_v = 25$$

$$\begin{aligned} C'_{gs} &= C_{gs} + A_v * C_{gd} \\ &= 440 \text{ pF} + 25 * 10 \text{ pF} \\ &= 690 \text{ pF} \end{aligned}$$

$$\begin{aligned} V_{gs} &= V_d * C_2 / (C_2 + C'_{gs}) \quad \text{Solve for } C_2 \\ C_2 &= [(V_{gs} / V_d) * C'_{gs}] / [1 - (V_{gs} / V_d)] \\ &= [(20 / 500) * 690\text{p}] / [1 - (20 / 500)] \\ &= 28.75 \text{ pF} \end{aligned}$$



*To ensure the MOSFETs turn on, increase  $C_2$  to **50 pF***

# Test 3 – Simulation & Values

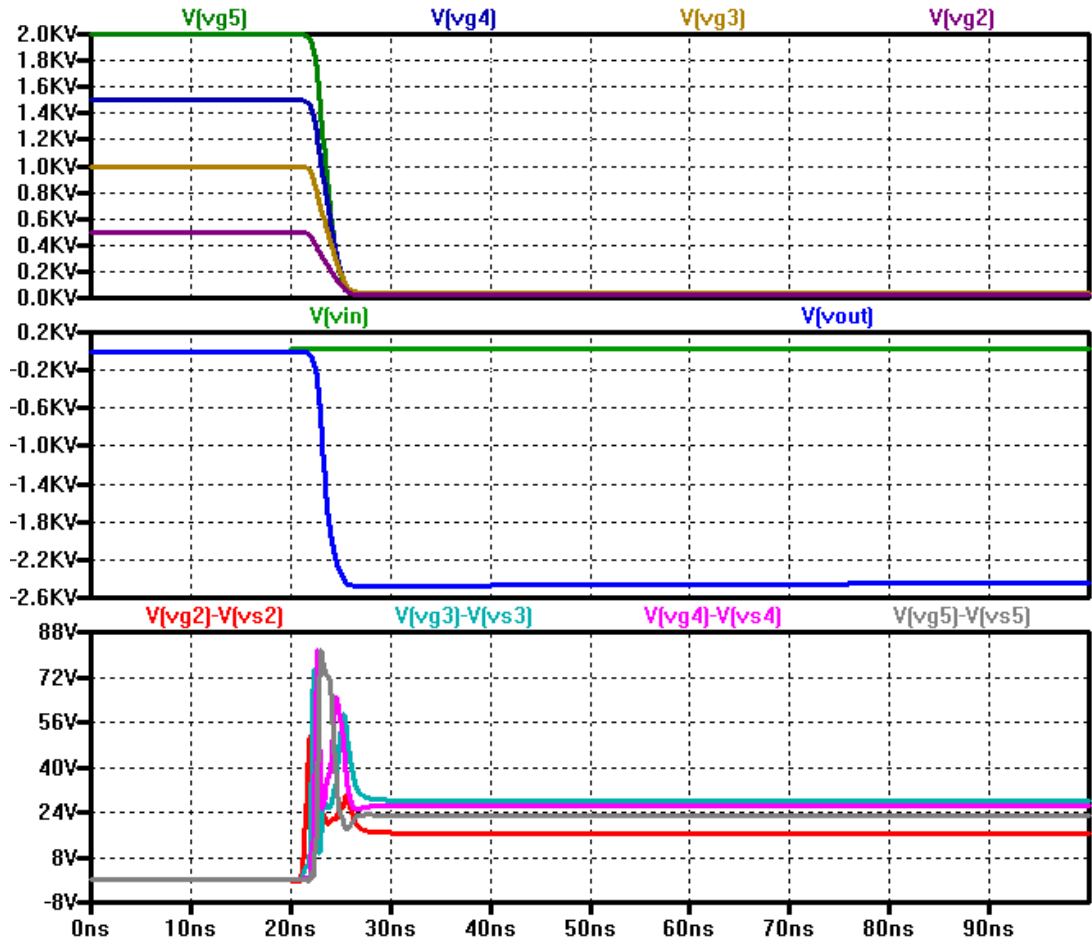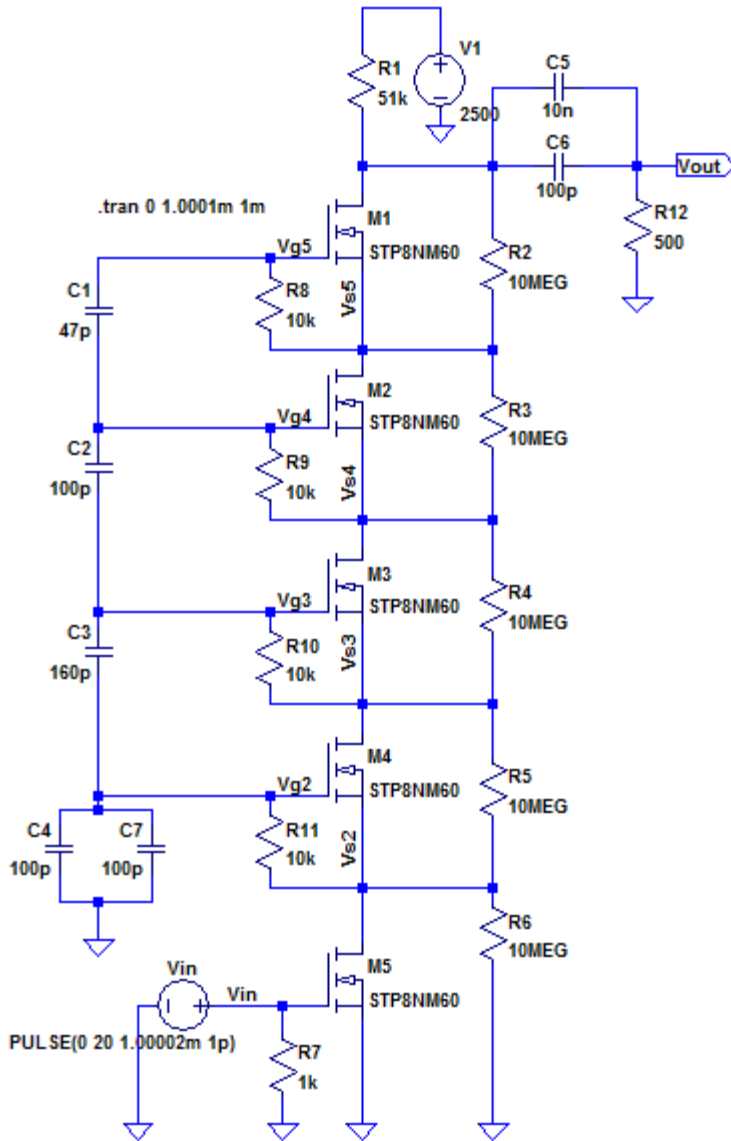


- \*Values reflect components available
- \*Simulation are the same as the previous test

# Test 3 – PCB Layout

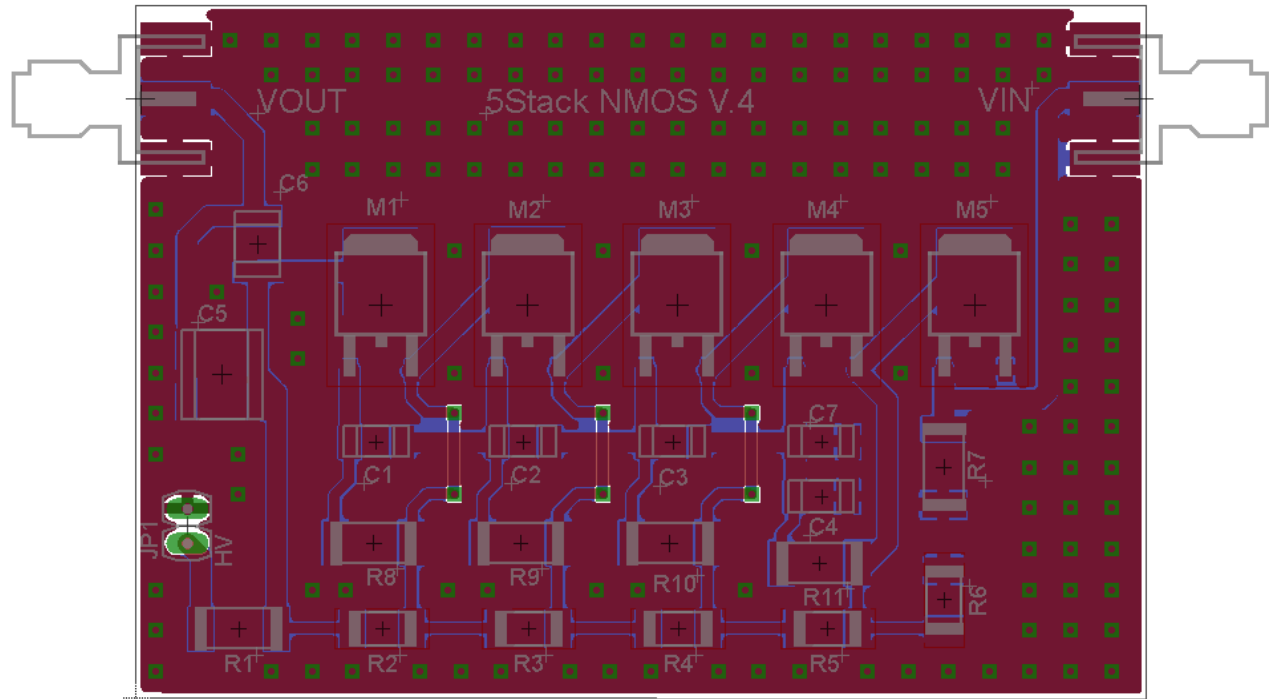
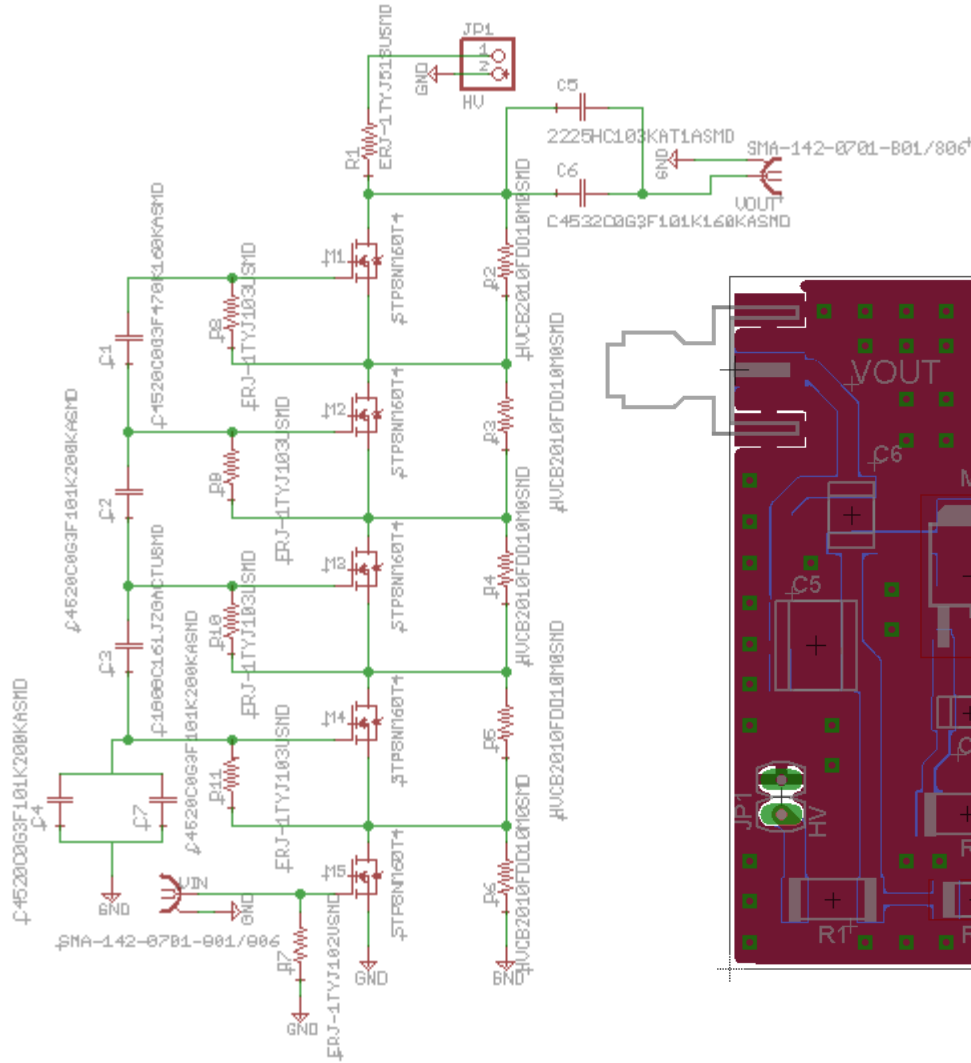


# Test 3 – Chip

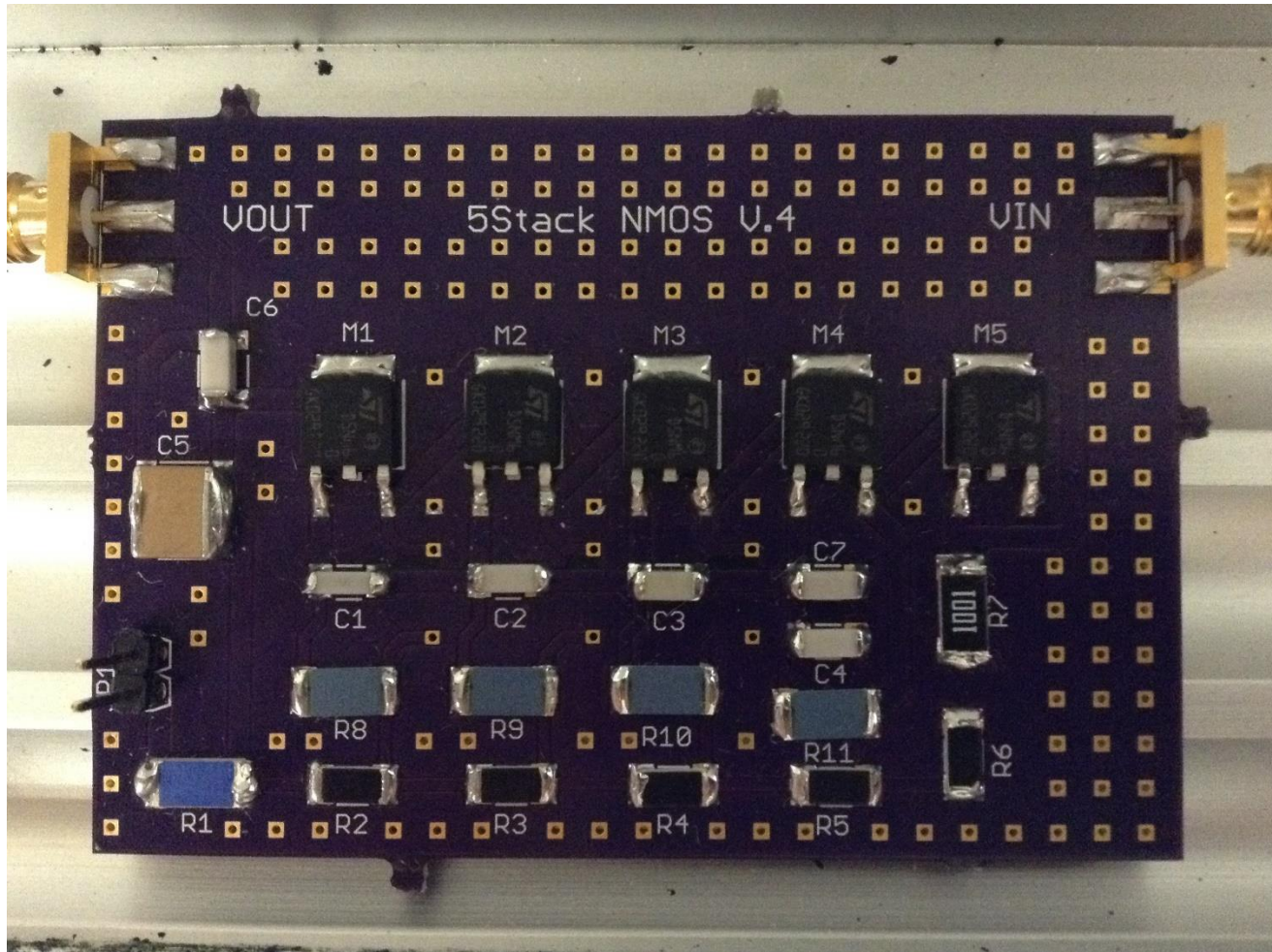
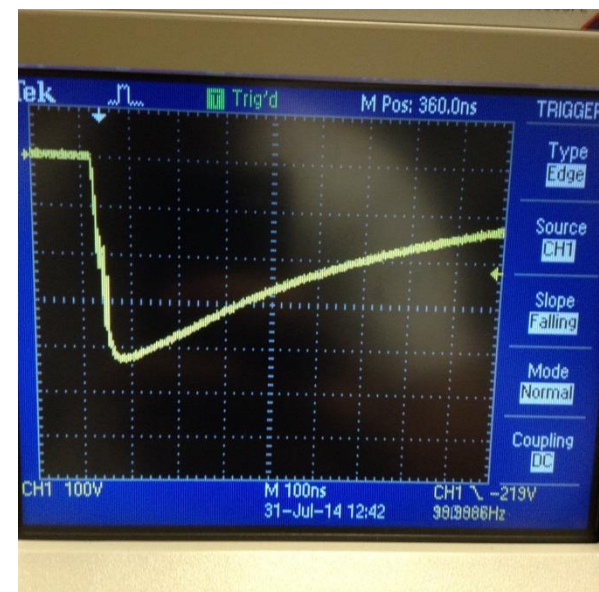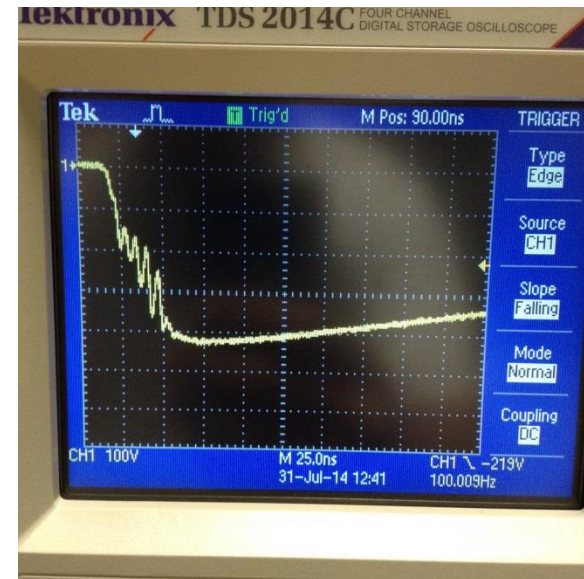
# Test 3 – Sample 1 Results

- $V_{in} = 504\text{ V}$
- Switching =  $420\text{ V}$ , or 83.3%
- Voltage Across (Difference):
  - M1:  $468\text{ V}$  (-36)
  - M2:  $342\text{ V}$  (-126)
  - M3:  $235\text{ V}$  (-107)
  - M4:  $135\text{ V}$  (-100)
  - M5:  $64\text{ V}$  (-71)
- Ringing still occurs, but much less than previous test
- More voltage is switching as well
- PC board needs to be reworked to eliminate the oscillation



# Test 3 – Sample 2 Results

- $V_{in} = 754 \text{ V}$
- Switching = 580 V, or 76.9%
- Voltage Across (Difference):
  - M1: 700 V (-50)
  - M2: 522 V (-178)
  - M3: 370 V (-152)
  - M4: 235 V (-135)
  - M5: 132 V (-103)

