

Stacking Power MOSFETs

PMOS Configuration

By Kendrick De La Pena

Updated: 08/07/2014

Test 1a – IFR9640

- PMOS Configuration; 5 Stack PMOS
- MOSFET:
 - IFR9640, $V_{DS} = -200$ V, $R_{DS(on)} = 0.5$ Ohms
- Capacitance Values:
 - 150 pF, 300 pF, 450 pF, 600 pF
- Max Voltage:
 - 1000 V

Test 1a – Calculations

$$C_{sg} = 1200 \text{ pF}$$

$$C_{dg} = 81 \text{ pF}$$

$$V_d = 500 \text{ V}$$

$$V_{sg} = 20 \text{ V}$$

$$A_v = 25$$

$$C'_{sg} = C_{sg} + A_v * C_{dg}$$

$$= 1200 \text{ pF} + 25 * 81 \text{ pF}$$

$$= 3225 \text{ pF}$$

$$V_{sg} = V_d * C_2 / (C_2 + C'_{sg}) \quad \textit{Solve for } C_2$$



$$C_2 = [(V_{sg} / V_d) * C'_{sg}] / [1 - (V_{sg} / V_d)]$$

$$= [(20 / 500) * 3225 \text{ pF}] / [1 - (20 / 500)]$$

$$= 135 \text{ pF}$$


*To ensure the MOSFETs turn on, increase C_2 to **150 pF**

Test 1a – Simulation & Values

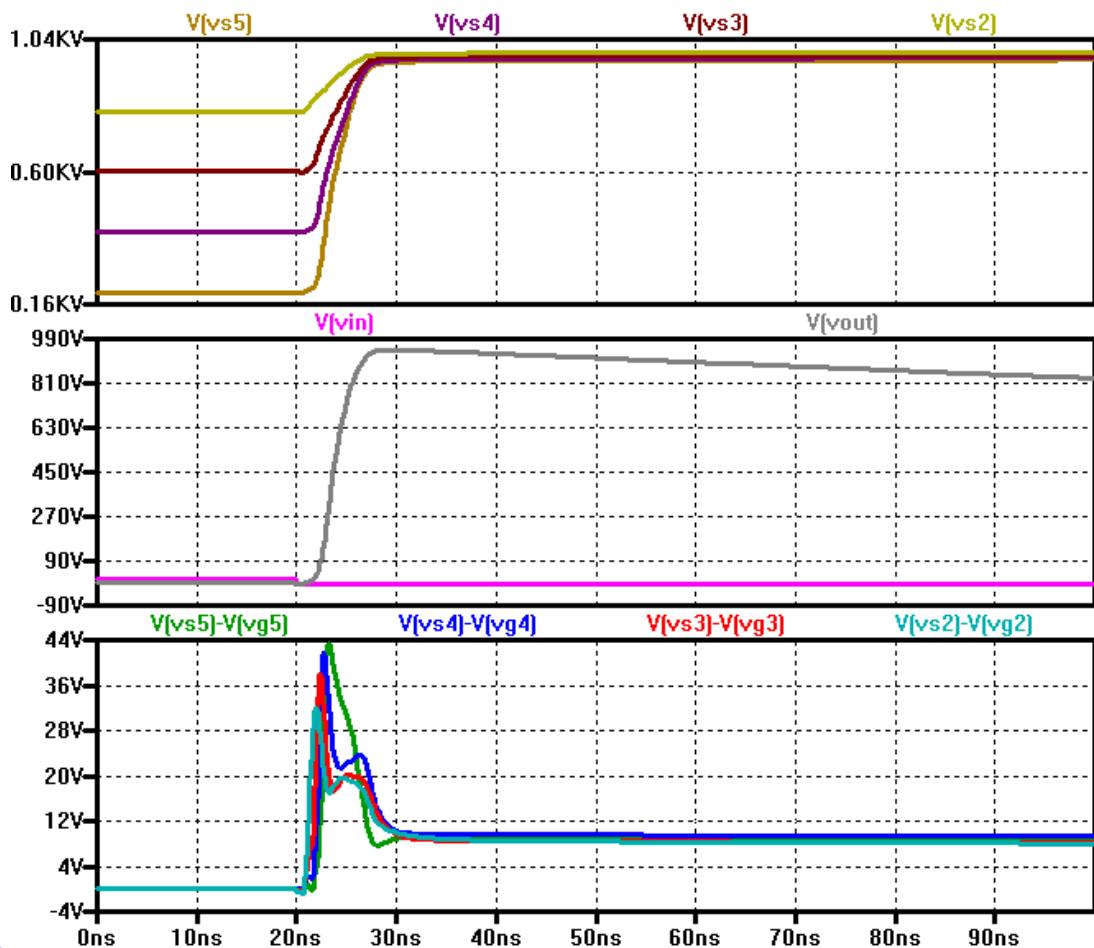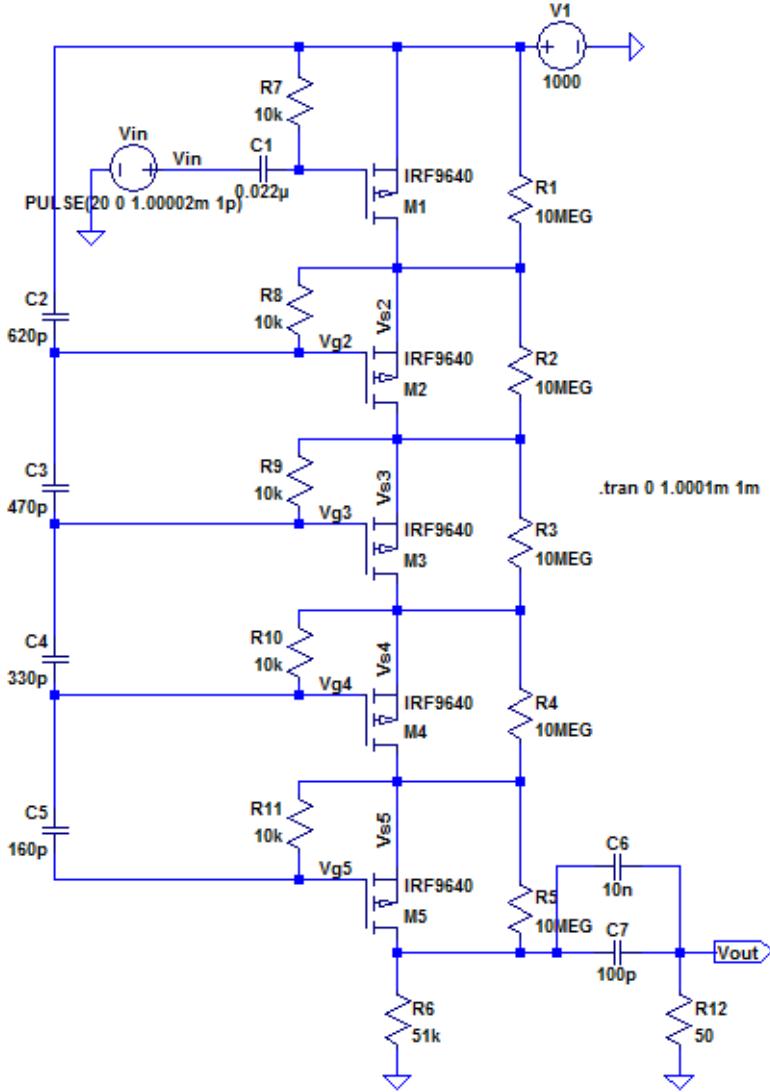


*Values reflect parts available

Test 1a – PCB Layout

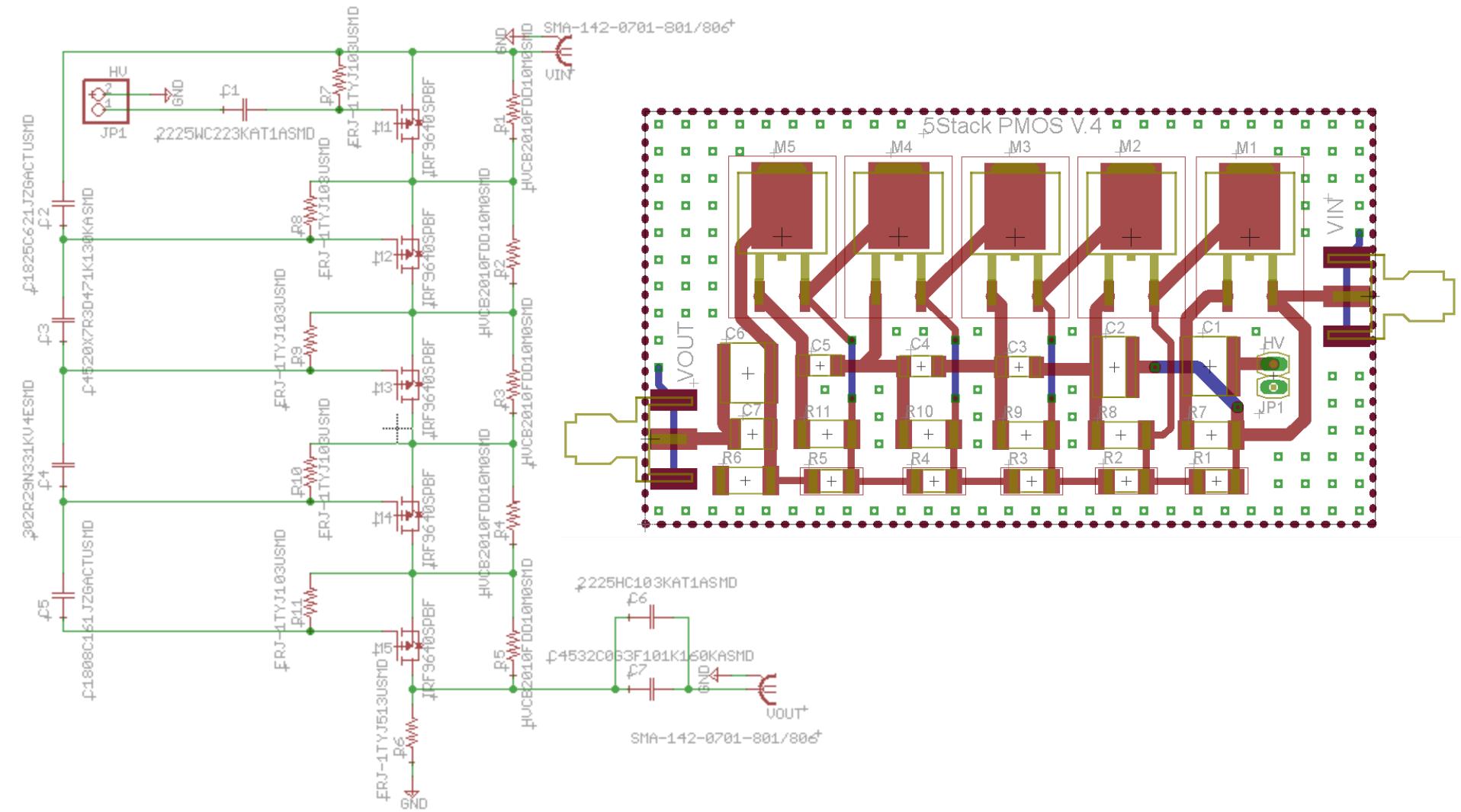


Test 1a – Chip

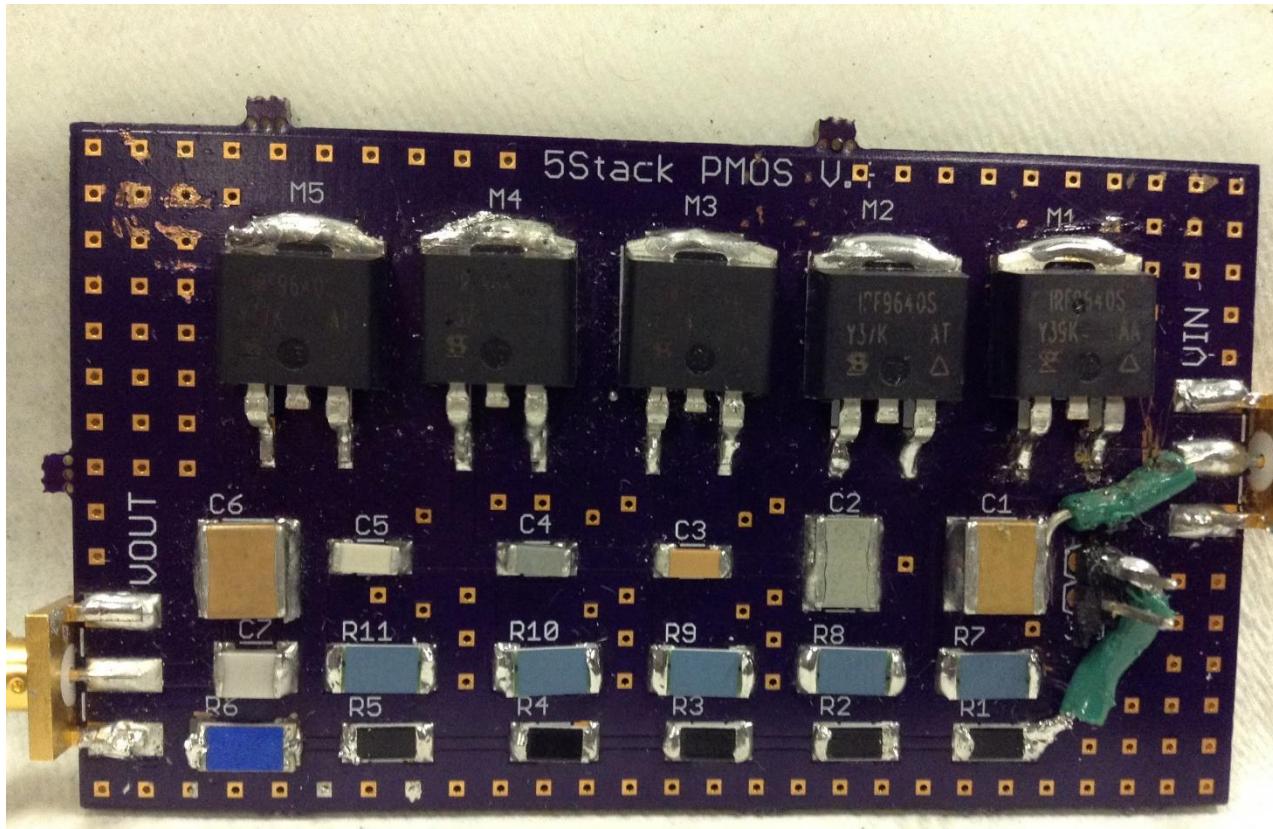

* The VIN and HV were switched in the PCB and needed to be rewired

Test 1a – Setup

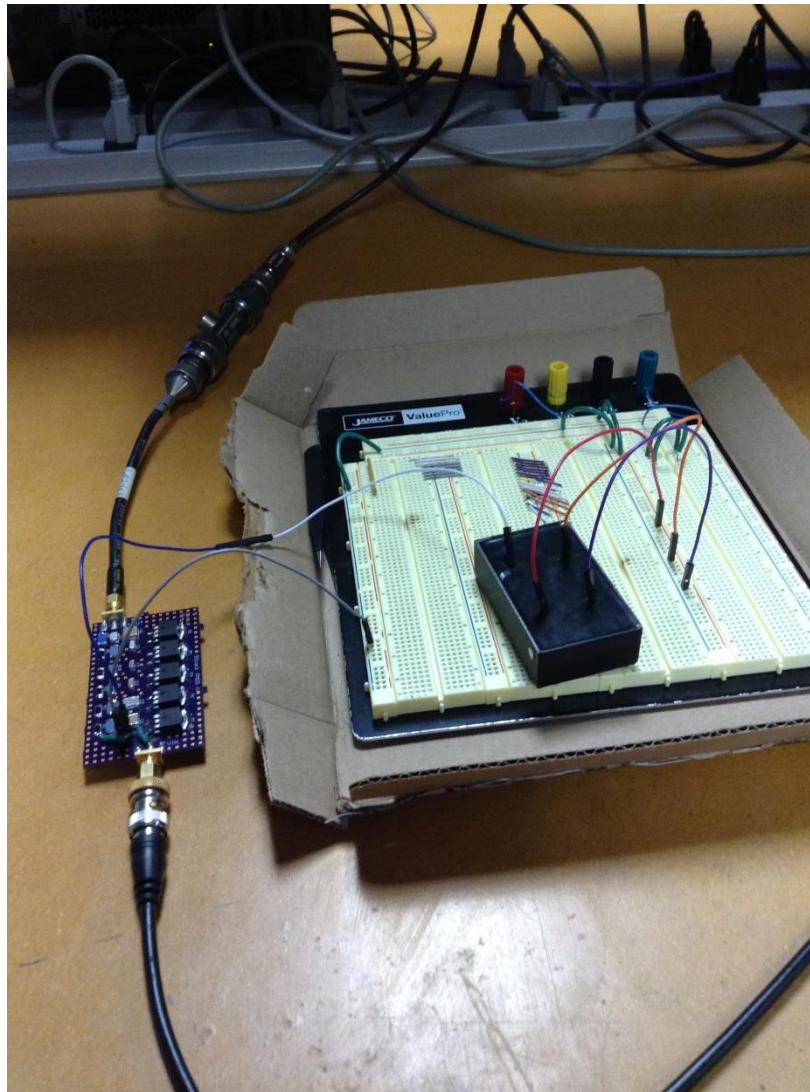

Test 1b – FQD4P40

- PMOS Configuration; 5 Stack PMOS
- MOSFET:
 - FQD4P40, $V_{DS} = -400$ V, $R_{DS(on)} = 3.1$ Ohms
- Calculated Capacitance Values:
 - 50 pF, 100 pF, 150 pF, 200 pF
- Max Voltage:
 - 2000 V

Test 1b – Calculations

$$C_{sg} = 845 \text{ pF}$$

$$V_d = 500 \text{ V}$$

$$C_{dg} = 26 \text{ pF}$$

$$V_{sg} = 20 \text{ V}$$

$$A_v = 25$$

$$C'_{sg} = C_{sg} + A_v * C_{dg}$$

$$= 680 \text{ pF} + 25 * 15 \text{ pF}$$

$$= 1055 \text{ pF}$$

$$V_{sg} = V_d * C_2 / (C_2 + C'_{sg}) \quad \textit{Solve for } C_2$$



$$C_2 = [(V_{sg} / V_d) * C'_{sg}] / [1 - (V_{sg} / V_d)]$$

$$= [(20 / 500) * 1055 \text{ pF}] / [1 - (20 / 500)]$$

$$= 44.0 \text{ pF}$$


*To ensure the MOSFETs turn on, increase C_2 to 50 pF

Test 1b – Simulation & Values

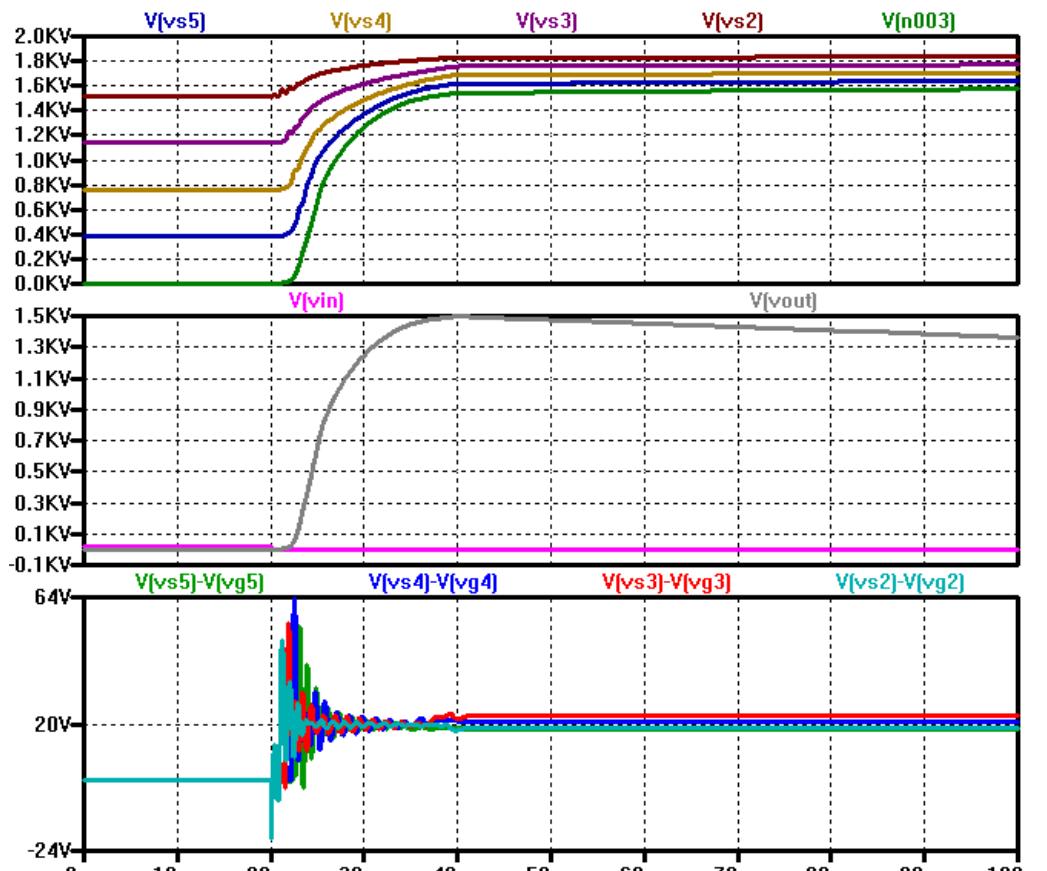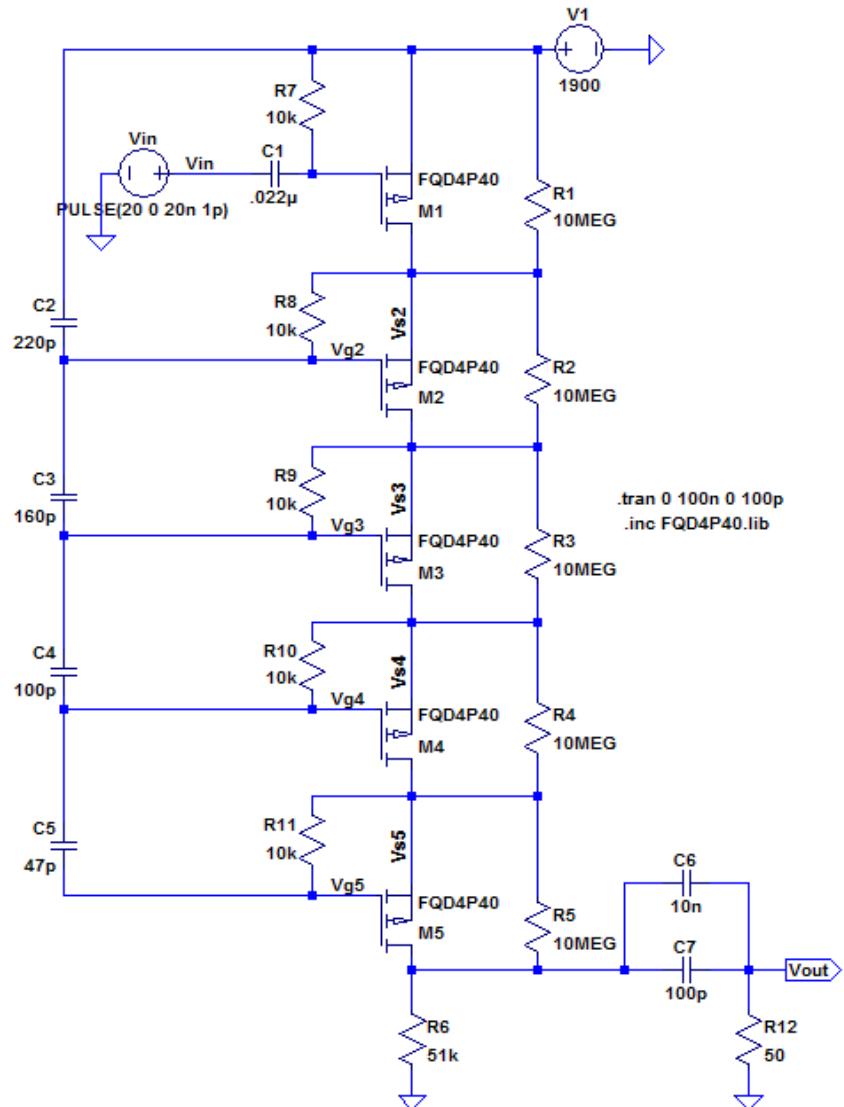


*Values reflect parts available

Test 1b – PCB Layout

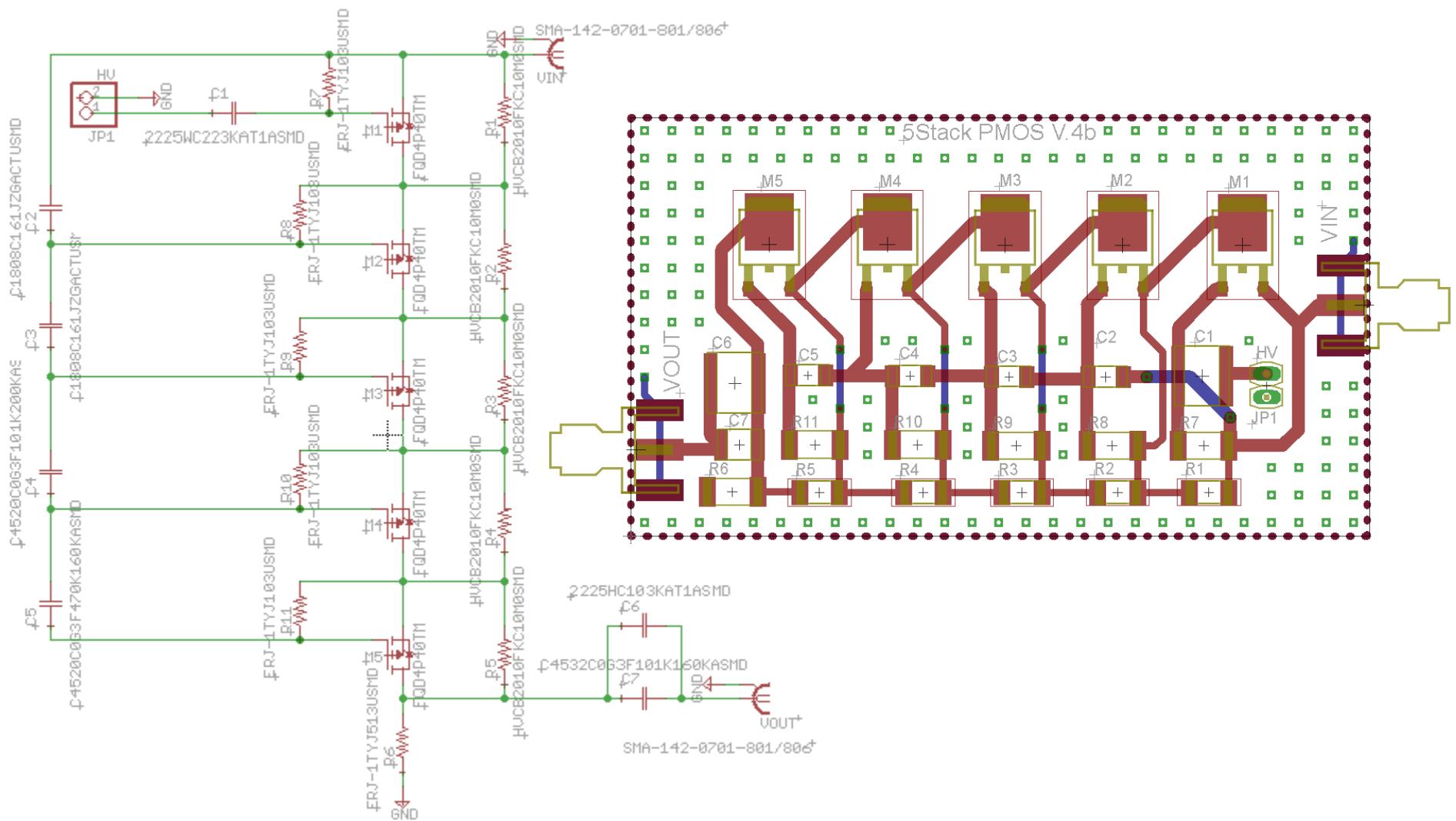

Test 1b – Chip

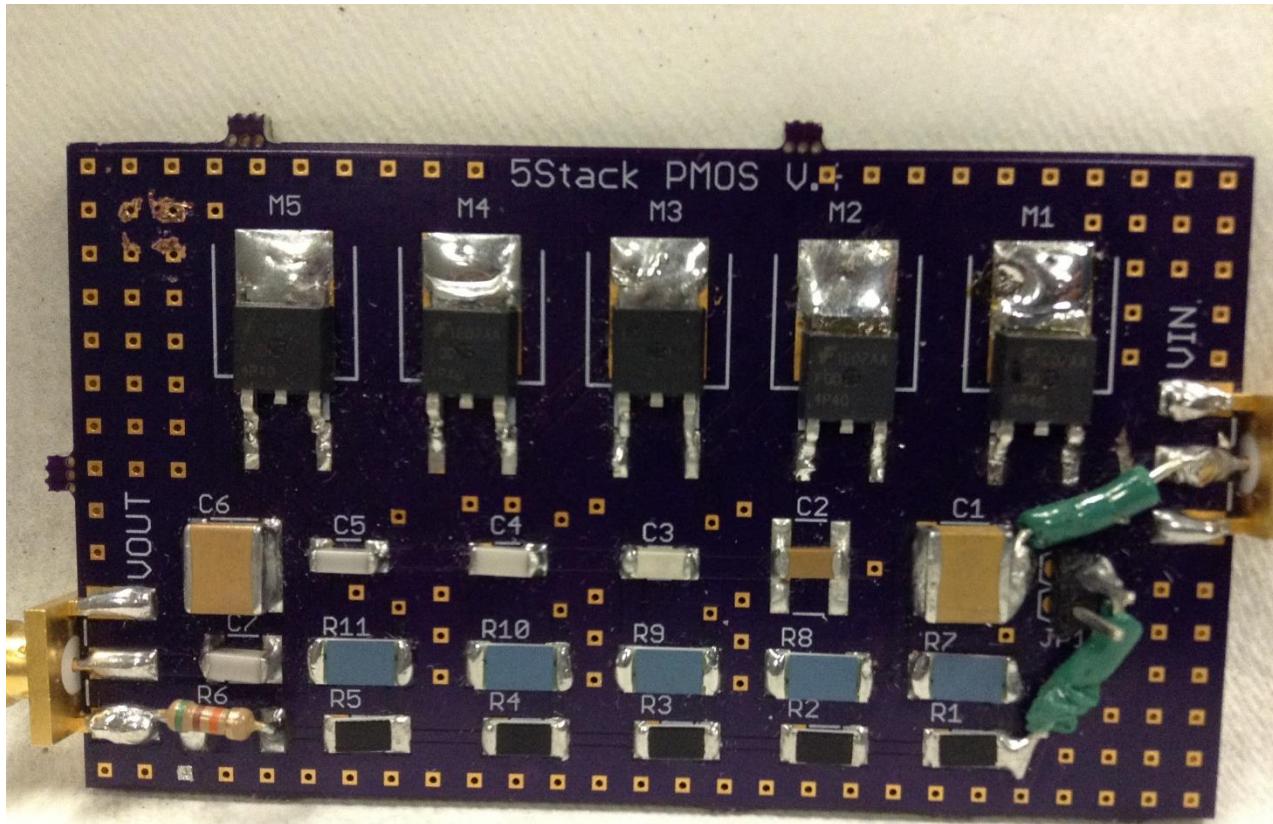

* The VIN and HV were switched in the PCB and needed to be rewired

Test 1 – Conclusion

- No results were able to be gathered from either type of MOSFET
- The first MOSFET that is attached to the high voltage repeated blew up while testing
- An extra capacitor near the high voltage is needed in the design
- The board will be re-fabricated appropriately to accommodate changes