

# Low Voltage Op – Amp

**On Semiconductor's 500nm process, C5 with two polysilicon layers and 3 levels of metal with a lambda of 300nm.**

Shadden Abdalla

EE 420 Final Project, May 2019

---

*The following report details the design and simulation of a low voltage op amp that operates with VDD from 2V - 5V while driving 100pF maximum and 1k minimum load.*

**The requirements followed** are DC open-loop gain > 66 dB under all load and VDD condition, gain-bandwidth product > 1 MHz, CMRR > 90 dB at 100 kHz, PSRR > 60 dB at 1 kHz, Slew-rate with maximum load > 1V/microsecond.

**The op-amp design goals** were to have as high of a gain as possible, while maintaining a phase margin of 90 degrees for optimal stability and a first order step response mirroring that of a RC circuit. The design aimed to use smaller device sizes for a faster and more concise design and layout, minimal power dissipation and a minimum current.

**Some trade-offs** made in this design to preserve the design goals were the reduction in PSRR in order to reduce power dissipation and the gain. Decreasing the current increases the gain and in turn, the PSRR, however it makes the circuit unstable. The only way to decrease the current without reducing stability is to also reduce device sizes throughout the biasing circuit and the op-amp and change the compensation capacitance or splitting it. The CMRR value was not as high as possible, as explained in the next paragraph. Due to time constraints, I was not able to redesign the entire circuit properly and improve stability.

**If I had more time to improve my design**, I would aim to reduce device sizes even more, and reduce the amount of current from the biasing circuit because that would reduce power dissipation. Reducing the current will reduce the power since current is added up by each branch and multiplied by the VDD value. I would also increase the output resistance of the PMOS differential amplifier in order to increase the common mode rejection ratio and increase the performance of the differential amplifier. The CMRR value of my circuit met requirements, however, I was able to increase it even more by increasing the output resistance of the PMOS differential amplifier but choose not to in order to preserve the stability of the circuit (due to time constraints). Reducing the sizes and increasing the current will improve the gain of the circuit and improve the PSRR. In a future design I would reduce sizes, which is optimal for design and for chip layout.

## Result Tables

### DC Open Loop Gain

Power Supply Voltage (V)	Normal Load: 1k & 100pF	Larger Load: 100k & 100p
2	72 dB	78 dB
3	68.4 dB	74 dB
4	66 dB	71 dB
5	64 dB	68 dB

### Gain Bandwidth Product

Power Supply Voltage (V)	Normal Load: 1k & 100pF	Larger Load: 100k & 100p
2	4.967MHz	4.72MHz
3	4.48MHz	4.37MHz
4	4.48MHz	4.37MHz
5	4.429MHz	4.37MHz

### CMRR at 100kHz

Power Supply Voltage (V)	No load (in units of dB)	Normal Load: 1k & 100pF (in units of dB)
2	93.412	95.494
3	109.512	95.629
4	94.84	104.84
5	87.169	93.47

**PSSR Plus at 1kHz**

Power Supply Voltage (V)	Normal Load: 1k & 100pF	Larger Load: 100k & 100pF
2	87.86 dB	77.11 dB
3	79.38 dB	75.6 dB
4	76.1489 dB	72.7 dB
5	72.761 dB	69.9 dB

**PSSR Minus at 1kHz**

Power Supply Voltage (V)	Normal Load: 1k & 100pF	Larger Load: 100k & 100pF
2	58.3 dB	59.0 dB
3	53.8 dB	54.6 dB
4	50.64 dB	51.57 dB
5	47.85 dB	48.9 dB



<b>Slew Rate at Maximum Load</b>	3.22V/us
----------------------------------	----------

**Power Dissipation**

Power Supply Voltage (V)	Power Dissipation
2	286 uW
5	1.06mW
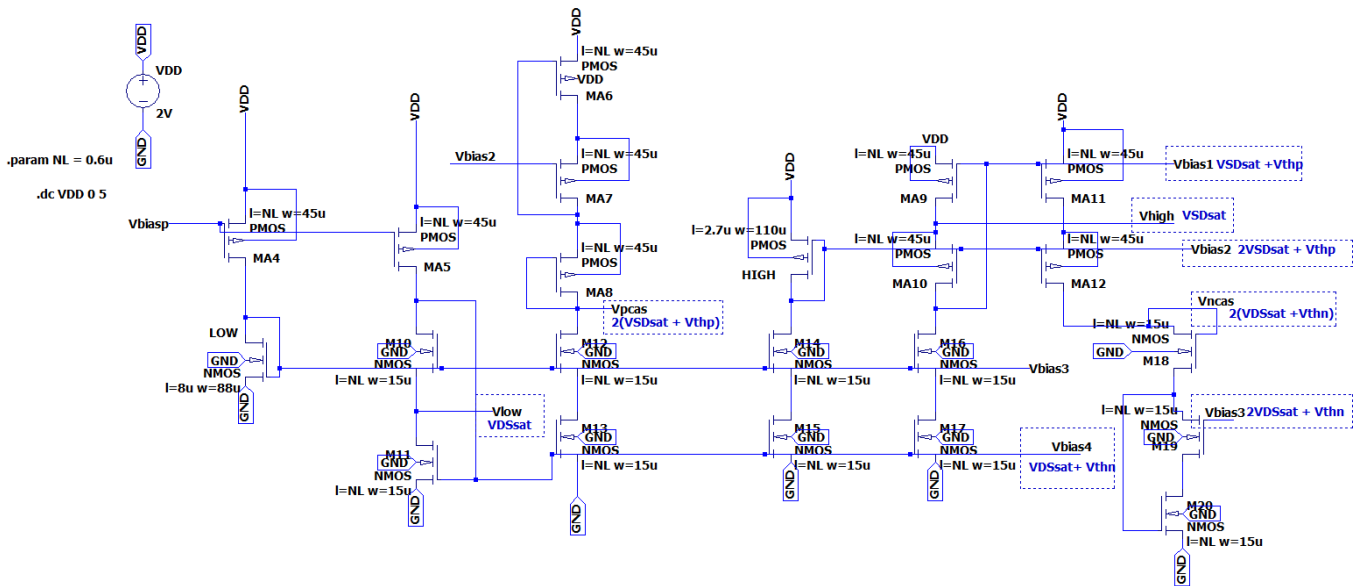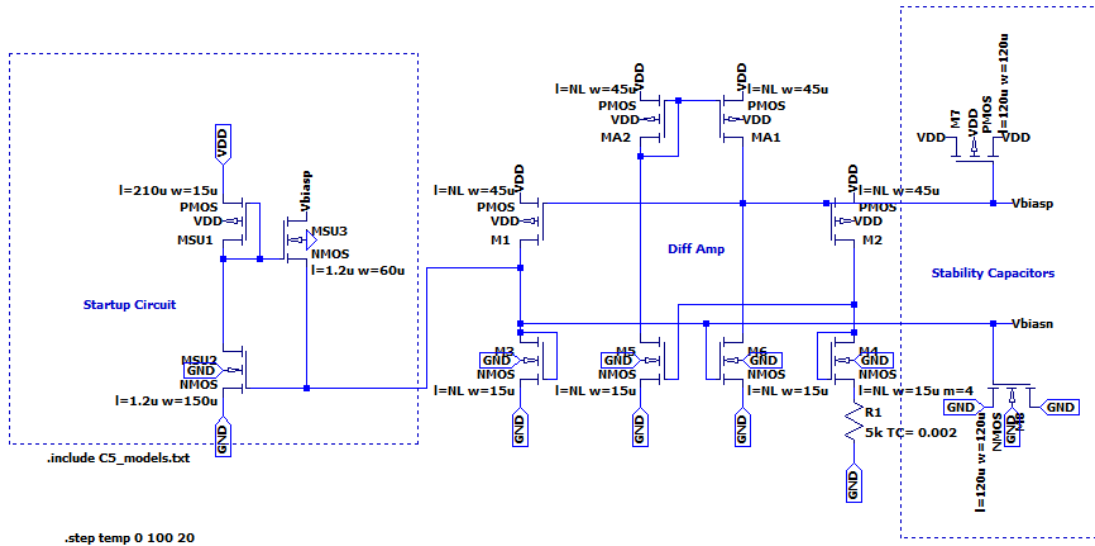
## Part 1: Biasing Circuit

The Biasing Circuit topology I choose is below:



**Folded Cascode Topology:** It is best when generating bias voltages because diode connecting the NMOS devices allows the PMOS current source to set the gate potentials of the NMOS current source that is diode connected beneath the two PMOS devices. This way, we can connect the currents and allow them to be at the same potential between the two sources. Current stealing is used with these connections.

I designed this circuit to follow a **VDSsat of 5% of the lowest VDD**, to follow 5% of 2V, at 100mV. Once the VDSsat was designed to 100mV. The voltages on the biasing circuit that correspond to VDSsat are Vhigh and Vlow. Since VDSsat is related to the other voltages, perfecting those values should give the accurate biasing voltages in the rest of the circuit. I changed the sizes of two transistors in the biasing circuit to change Vhigh and Vlow to 100mV, and those changes led the other voltages to align with my calculations. In order to increase VDSsat, the length should be increased since the length is directly proportional to VDSsat and the width is inversely proportional to VDSsat. Increasing the width will decrease the value. This is based on the VGS equation and its relation to VDSsat.

$$VDSsat = VGS - Vthn$$


$$VDSsat = \frac{\sqrt{2ID}}{\sqrt{KP} \frac{w}{L}} + Vthn - Vthn$$

$$VDSsat = \sqrt{\frac{2 * ID * L}{KP * W}}$$

From this equation, it is deduced that the length of the MOSFET is directly proportional to the VDSsat value and the width of the MOSFET is inversely proportional.

Vlow corresponds to VDSsat and Vhigh corresponds to VSDsat.

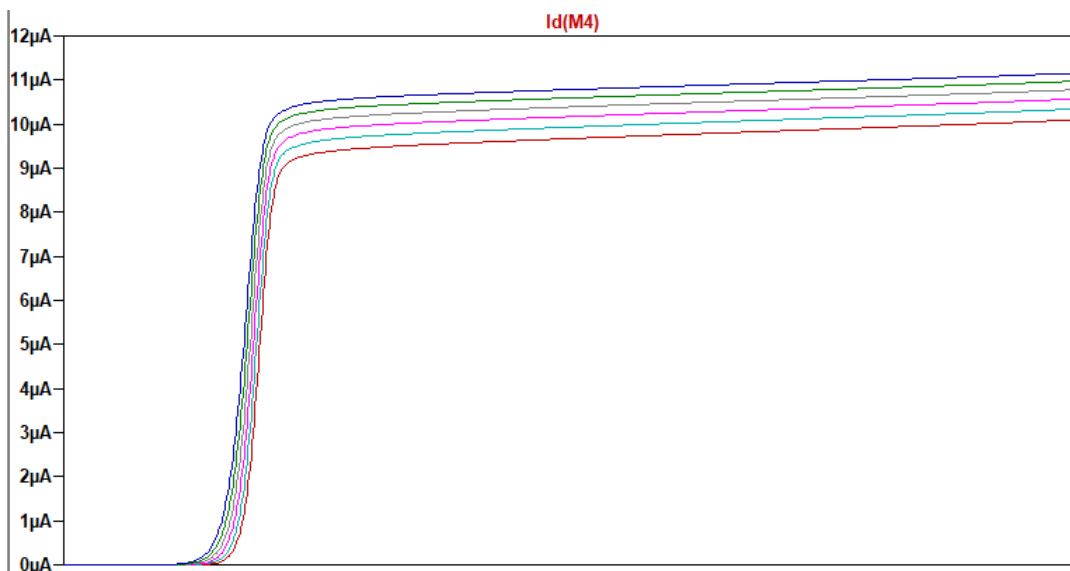
### Current over Varying Temperature: 10uA



The current used in my biasing circuit ranges from 9.93uA to 10.4uA from 2V-5V. I was able to flatten the current and make it constant over a range of voltage by increasing the strength of my startup circuit. The current value I choose was 10uA. Decreasing the current gives a better gain, and decreases the power dissipation. Decreasing the current creates a skewed step response, even


if the phase margin is accurate, and I would like to try a topology of that sort in a future project. The current can be easily increased and decreased by changing the resistor value in the Beta Multiplier Circuit. Increasing the resistance decreases the current, while decreasing the resistor increases the current.

**Startup Circuit:** The three transistors in the startup circuit are used to turn the circuit on, and act as a switch. These transistors work with the gate voltages of the transistors in the circuit, and when some of them are at VDD, and MSU1 turns off, the other two transistors will be on, and send current into the gates of the transistors that have gone to ground and turn them back on. Once the current is stable, MSU3 turns on.

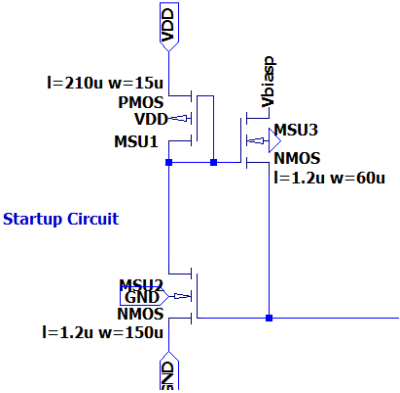


The current can be easily increased and decreased by changing the resistor value in the Beta Multiplier Circuit. Increasing the resistance decreases the current, while decreasing the resistor increases the current.

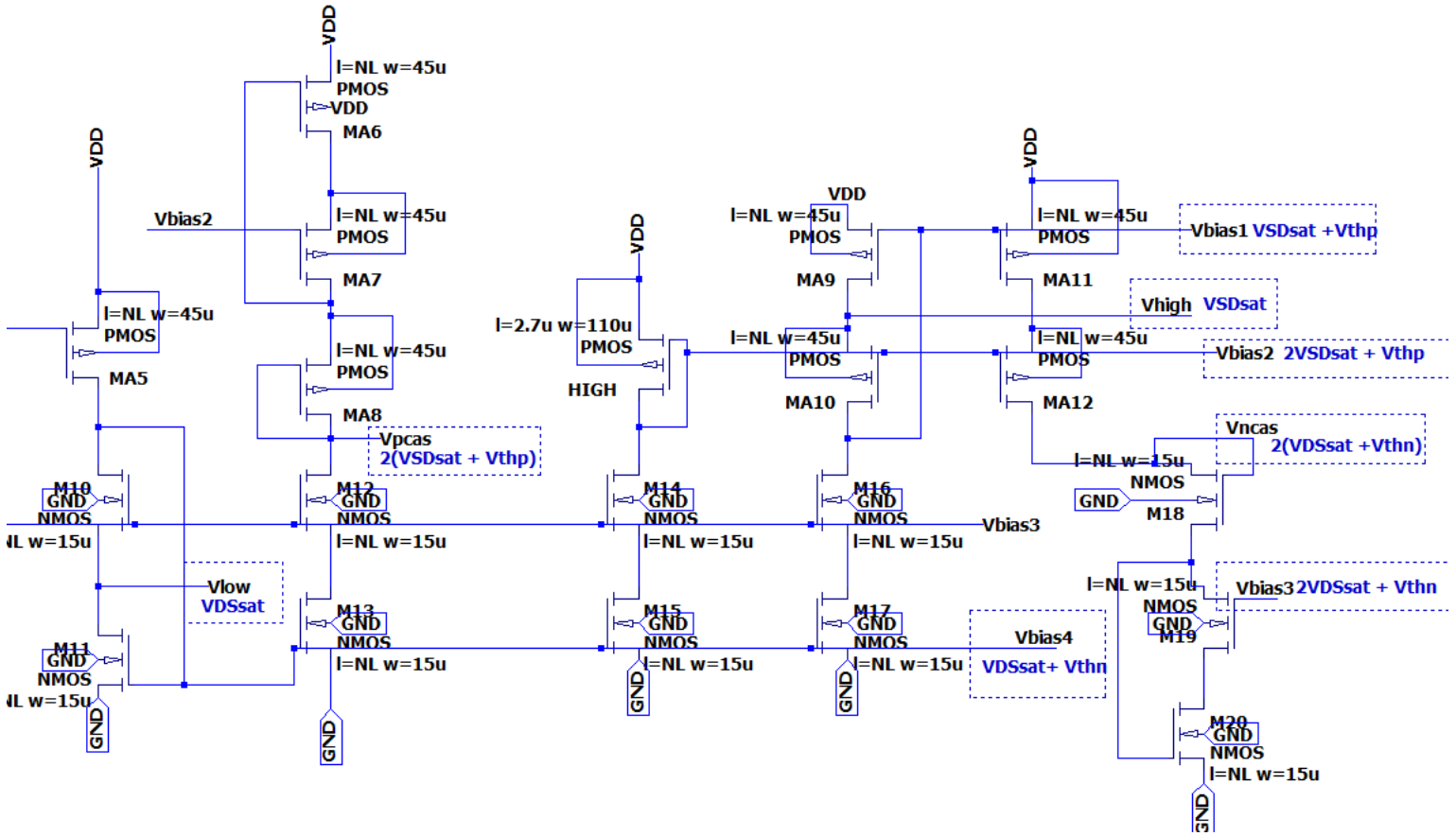I designed the biasing circuit to follow the calculations of what the voltages should be in the circuit. Below is a photo showing the values of the biasing voltages.



Below are the voltages simulated from the current reference.

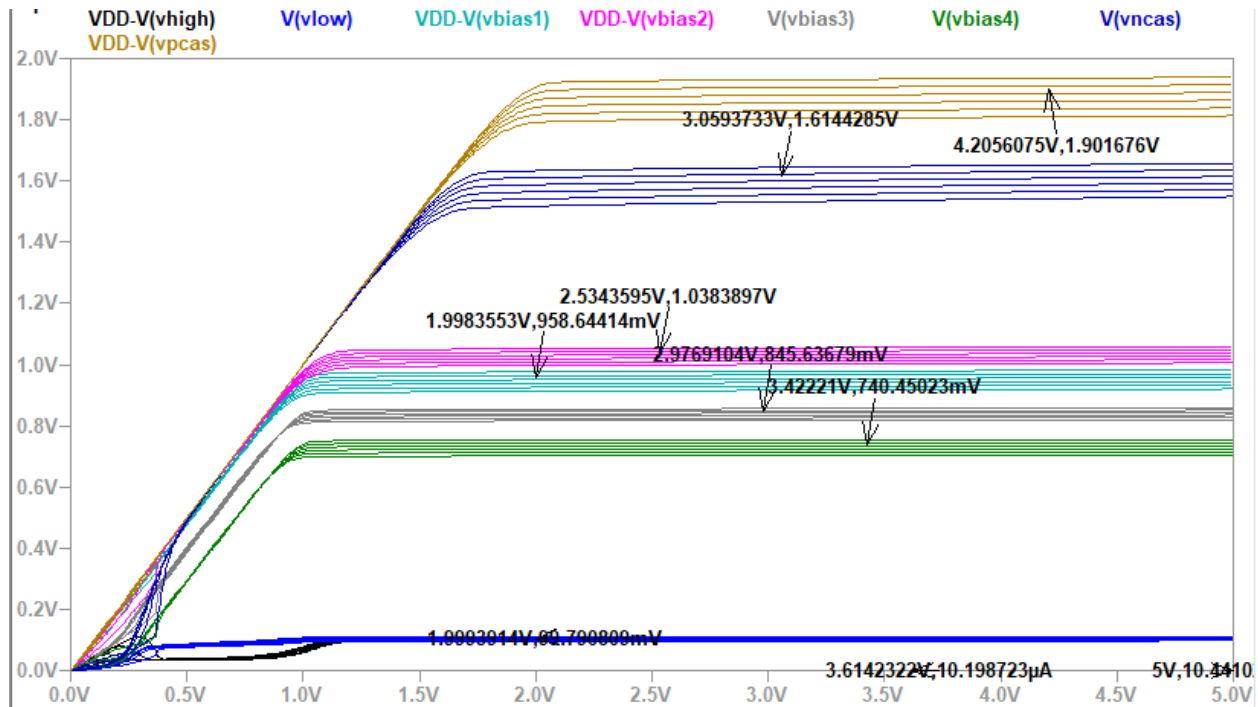Biasing voltages over varying temperatures from 0- 100 degrees Celsius with increments of 20 degrees, showing that the circuit works under all temperature conditions.



$$V_{thn} = 0.667$$

$$V_{thp} = 0.9214$$

$V_{high} = V_{DSsat}$  is set to  $99.8\text{mV}$  in my biasing circuit, which is about  $100\text{mV}$ , at 5% of  $2\text{V}$ .

$V_{low} = V_{DSsat}$  is set to  $99.9\text{mV}$  in my biasing circuit, which is about  $100\text{mV}$ , at 5% of  $2\text{V}$ .

The calculations used are below:

$$V_{bias1} = V_{DSsat} + V_{thp} = 0.098\text{V} + 0.9214\text{V} = \mathbf{1.02\text{V}}$$

$$V_{bias2} = 2V_{DSsat} + V_{thp} = 2 * 0.098 + 0.9214 = \mathbf{1.121\text{V}}$$

$$V_{bias3} = 2V_{DSsat} + V_{thn} = 2 * 0.098 + 0.667 = \mathbf{0.863\text{V}}$$

$$V_{bias4} = V_{DSsat} + V_{thn} = 0.0998 + 0.667 = \mathbf{0.7668\text{V}}$$

$$V_{ncas} = 2(V_{DSsat} + V_{thn}) = 2 * (0.099 + 0.667) = \mathbf{1.532\text{V}}$$

$$V_{pcas} = 2(V_{DSsat} + V_{thp}) = 2 * (0.0999 + 0.9214) = \mathbf{2.04\text{V}}$$

$$V_{low} = V_{DSsat} = \mathbf{0.0998\text{V}}$$

$$V_{high} = V_{DSsat} = \mathbf{0.099\text{V}}$$




The biasing voltages from LTSpice compared to calculations:

Voltage Name	From LTSpice (V)	From Calculations (V)
Vbias1	0.960	1.02
Vbias2	1.04	1.121
Vbias3	0.845	0.863
Vbias4	0.739	0.7668
Vncas	1.60	1.532
Vpcas	1.89	2.04
Vlow	0.100	0.0998
Vhigh	0.100	0.099

The voltages from my circuit are very similar to the calculated voltages.

---

## Part 2: Op-Amp Design

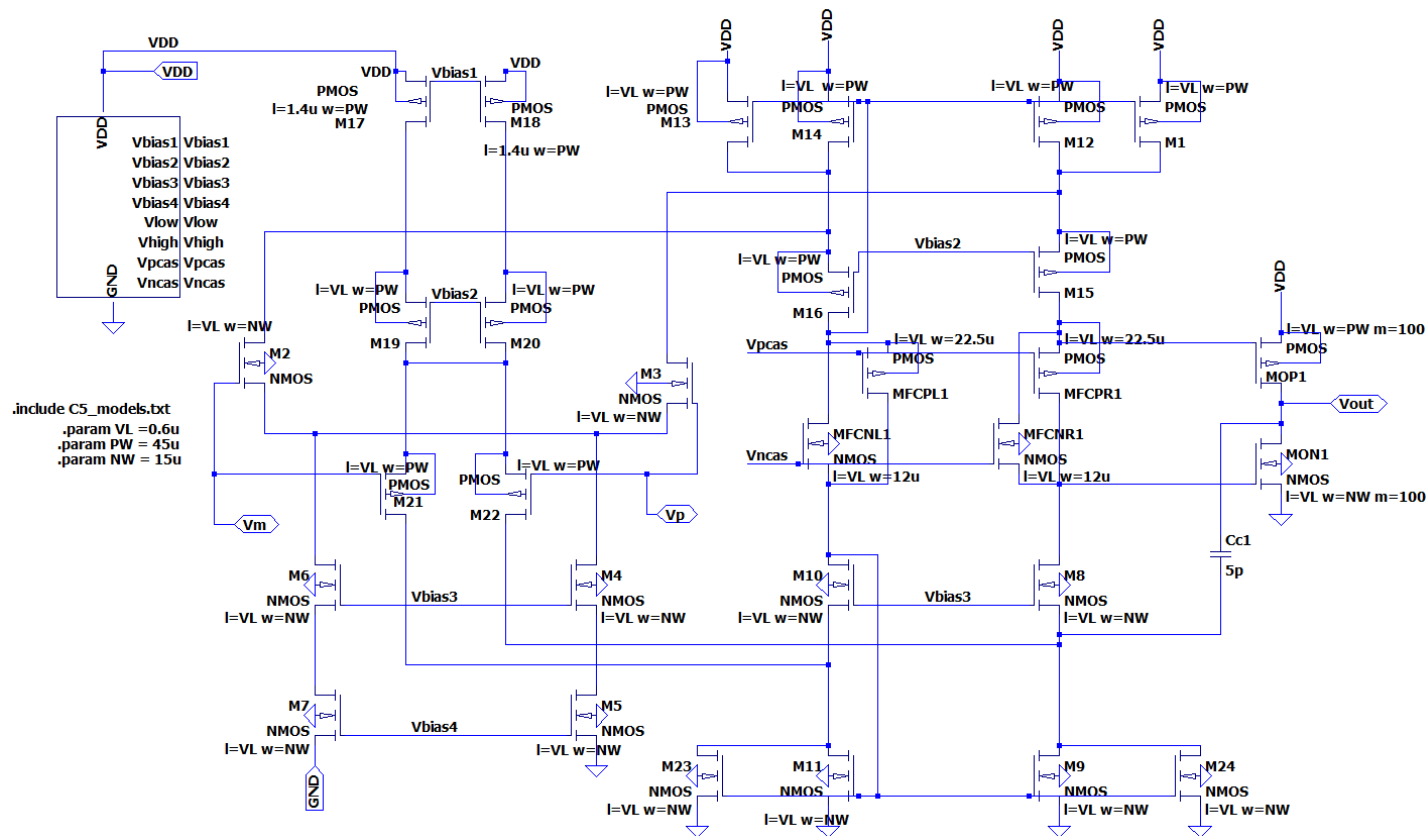


The op amp design I choose is a two stage op-amp with an output buffer, since this op amp should be capable of driving a load with a resistor and a capacitor. It is a wide swing, folded cascode op amp with a class AB output buffer and a PMOS differential amplifier stage. I choose a wide swing topology in order to increase the input common mode voltage with the PMOS diff amp addition, and the NMOS additions to sink the larger current supplied by the PMOS. The PMOS diff-amp topology with the NMOS sinking transistors is useful because it allows the sourcing and sinking currents to be very similar. If the PMOS attempts to source more current than the NMOS can handle, the PMOS will enter triode until the current decreases to match what the NMOS is willing to sink. This topology is also useful because the floating current sources minimize offset from the input, assisting the common mode range. The common mode range of this circuit is large enough to go almost 1V above VDD and almost 1V below VDD. Decreasing VP to a negative voltage also works with this topology. If the voltages on VP and VM differ greatly and extend beyond the common mode range, the gain will decrease. This is prevented using this differential amplifier topology. Using this topology allows us to increase the unity frequency and gain bandwidth product by decreasing the compensation capacitor, Cc. In this case, I increased the compensation capacitor in order to create a more stable circuit. Decreasing the compensation will make the circuit faster but it will reduce stability. The larger the gain is,


the more likely the op amp will feedback properly. I based the compensation capacitor value on the unity frequency equation, where the unity frequency is inversely proportional to the compensation capacitor. The gain can be increased in this op amp by increasing the output resistance on the MOSFETs connected to VPCas and VNCas. Increasing the ratio of length to width can increase the gain by decreasing the gm value of those transistors. The two output transistors making a push pull amplifier, creating the output stage are large in order to stabilize the circuit as well. The push pull amplifier increases the output swing of the circuit. The sizes are not too large in order to create practicality when laying out a circuit on a chip, but are larger than the respective other sizes in the design.

**My goal** when designing the circuit was to minimize sizes as much as possible to create the most efficient and concise layout. The sizes I used are the same as the ones in the current reference and biasing circuit, lengths of 0.6u (minimum length) and PMOS widths of 45u, and NMOS widths of 15u. The purpose of this circuit is to have as large of a gain as possible while the stability is optimal by giving a phase margin of 90 degrees, since the phase shift at unity gain is -90. The step response is thus a first order response. I wanted to reduce the current and power as much as possible while having an optimal phase margin and gain. Once those conditions were set, I worked on improving the CMRR and PSRR, however, my goal is a large gain, a very stable circuit, low power dissipation and lower current input.
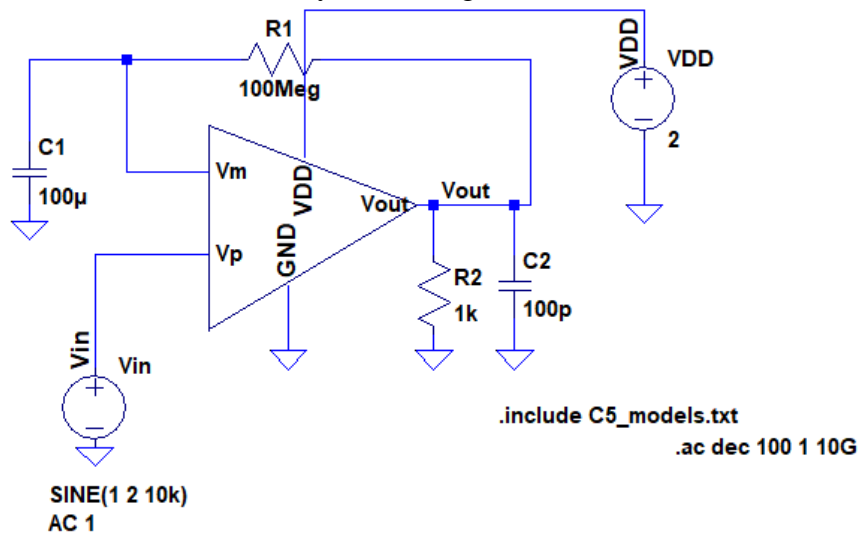
## Project Condition 1: DC open loop gain of > 66dB

The DC open loop gain of my amplifier is about 72dB, with a phase margin of 90 degrees. The gain could be decreased by decreasing the current.



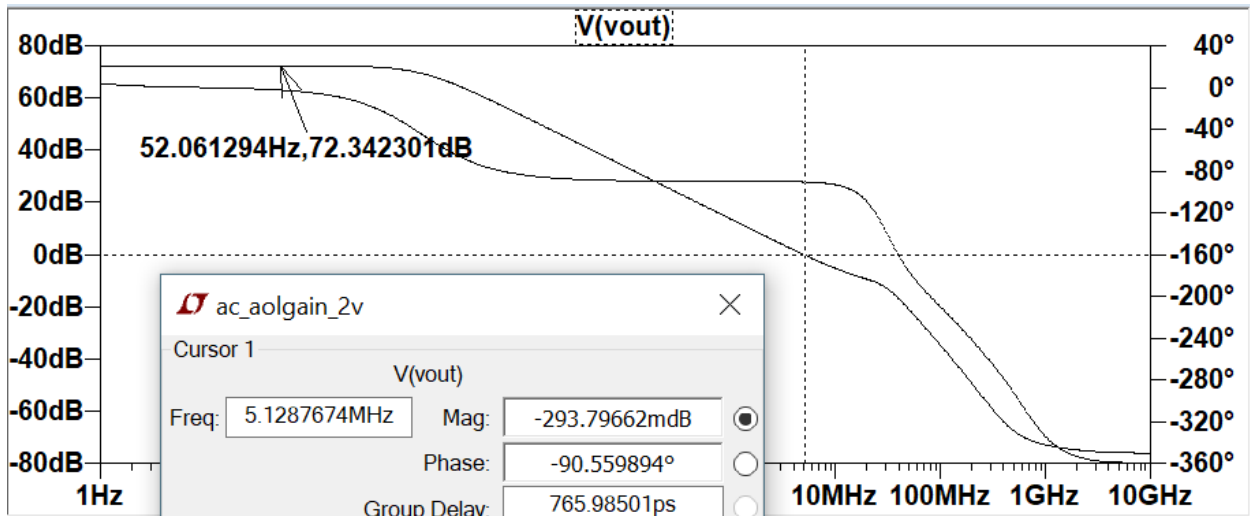


**Gain of 72dB with a phase margin of 90 degrees.**

The low frequency gain is found by:

$$A_v = g_{mn} * (R_{ocasn} || R_{ocasp})$$

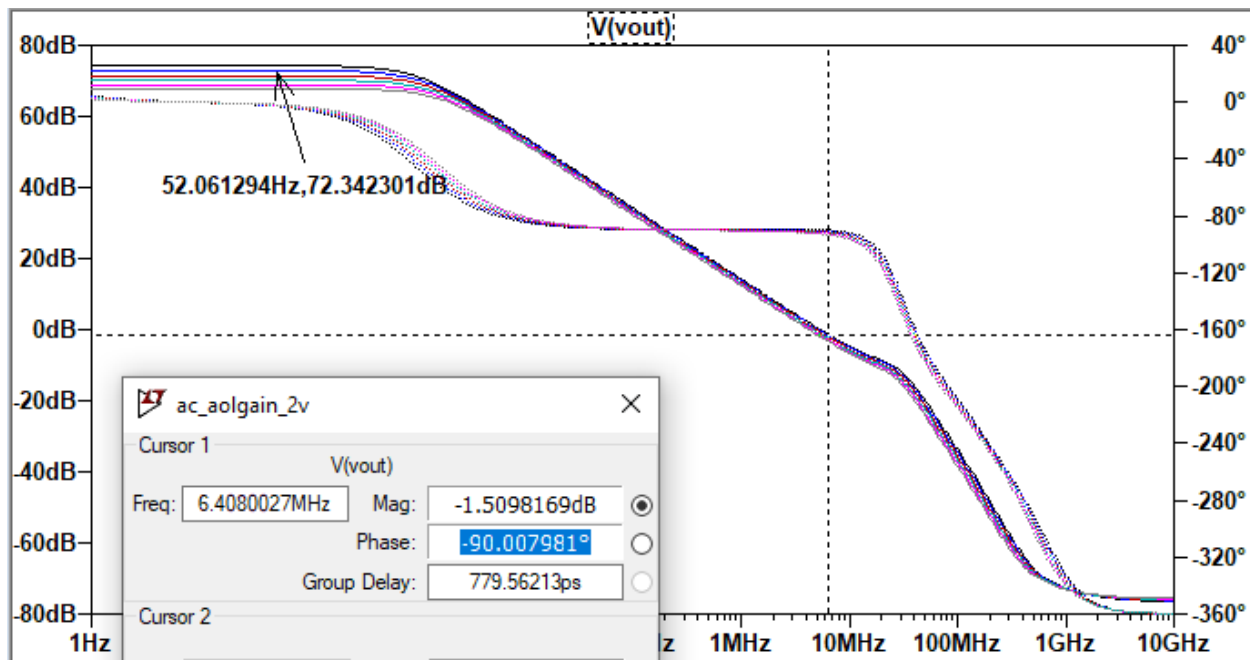**The gain and phase margin also stay the same at varying temperature.**





## Project Condition 2: Gain Bandwidth Product > 1MHz at 5.12MHz

Two specifications are satisfied here, a gain over 66dB and a gain bandwidth product over 1MHz, at 5.12MHz.
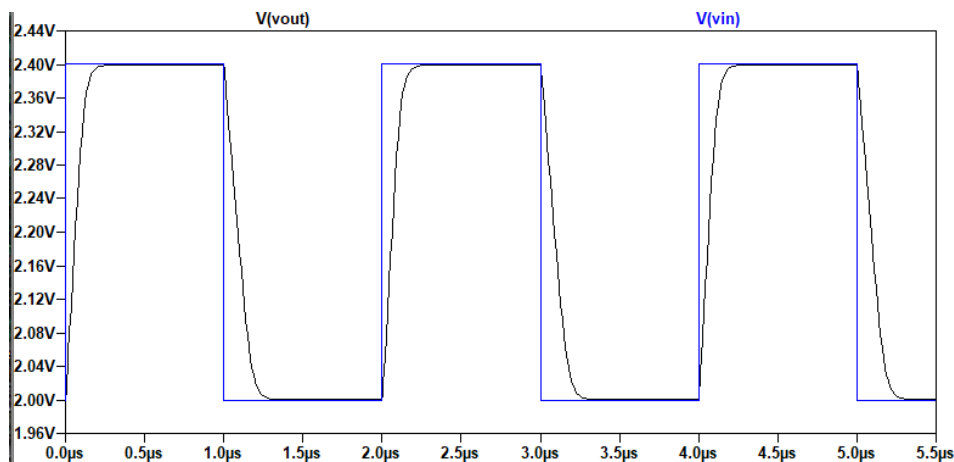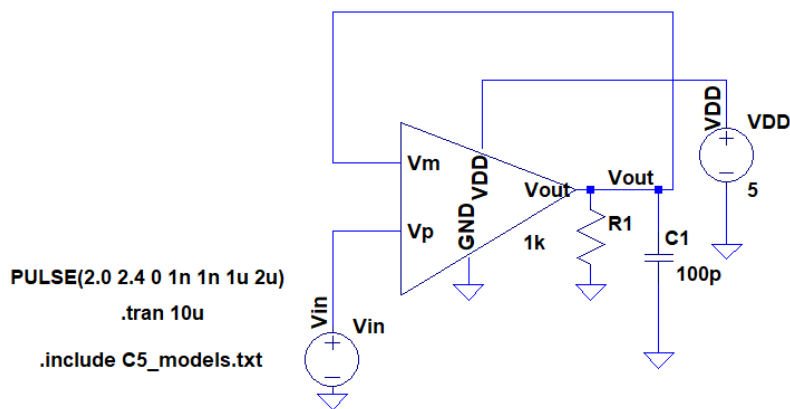
### Phase Margin


The ideal phase margin in this case is 90 degrees in order to create an optimal step response that acts as an RC circuit, giving off a first order response.

**Step Response:** since the phase margin is 90 degrees, the step response is a first order response, like an RC circuit.




## Step Response at Varying Temperature of 0-100 degrees Celsius

VDD of 5V

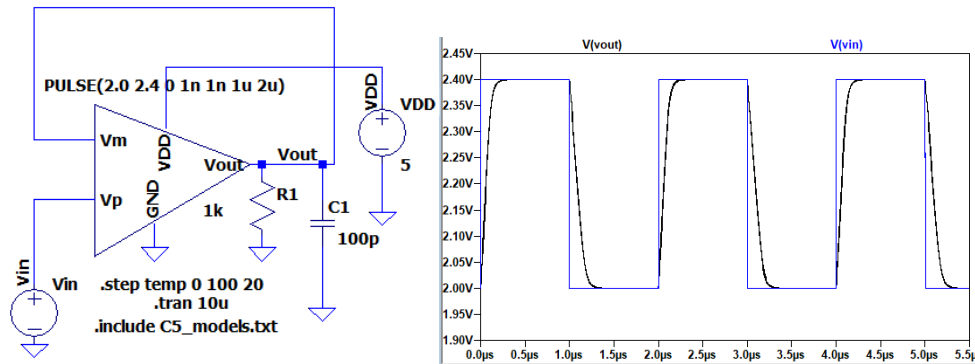


 **VDD of 2V- step response with varying temperatures.** This step response shows the same output as the original step response. The gain decreases with increasing temperature but the difference is very small.


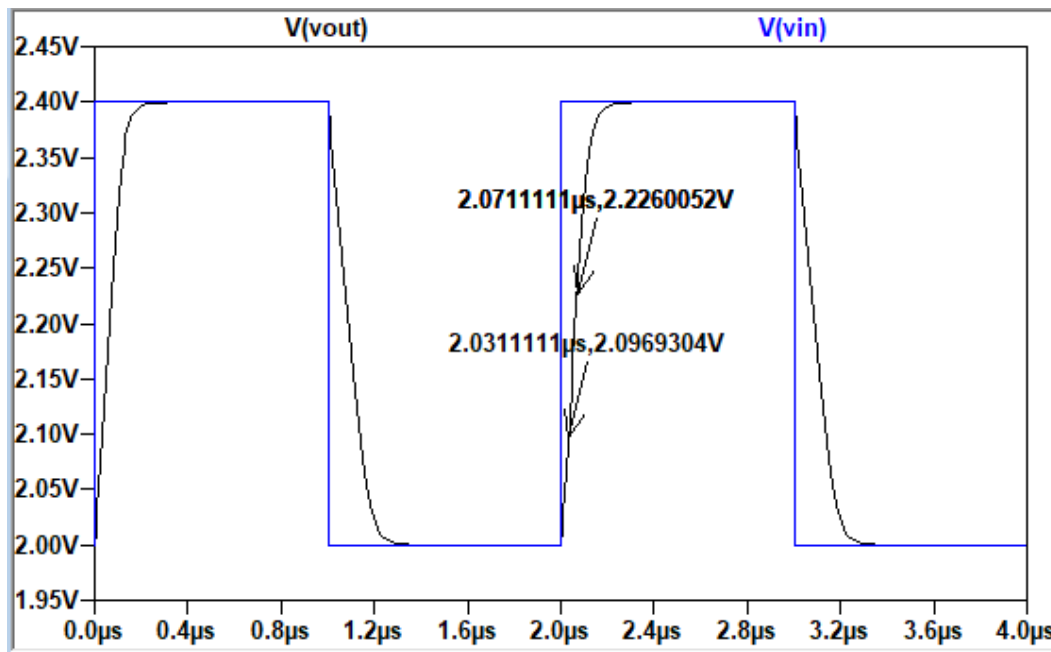
### Project Condition 3: Slew Rate with maximum load > 1V/ microsecond, satisfied at 3.22V/us



Using the same step response circuit from above, I measured the slew rate by finding the slope of the line as  $V_{out}$  increases. The step response looks like the response from an RC circuit, a first order response, because the phase margin is 90 degrees.



$$\text{Slew Rate} = \frac{\text{change in voltage}}{\text{change in time}} = \frac{2.226V - 2.0969V}{2.0711\mu s - 2.0311\mu s} = \frac{0.1291V}{0.04\mu s} = 3.2275 \frac{V}{\mu s}$$


---
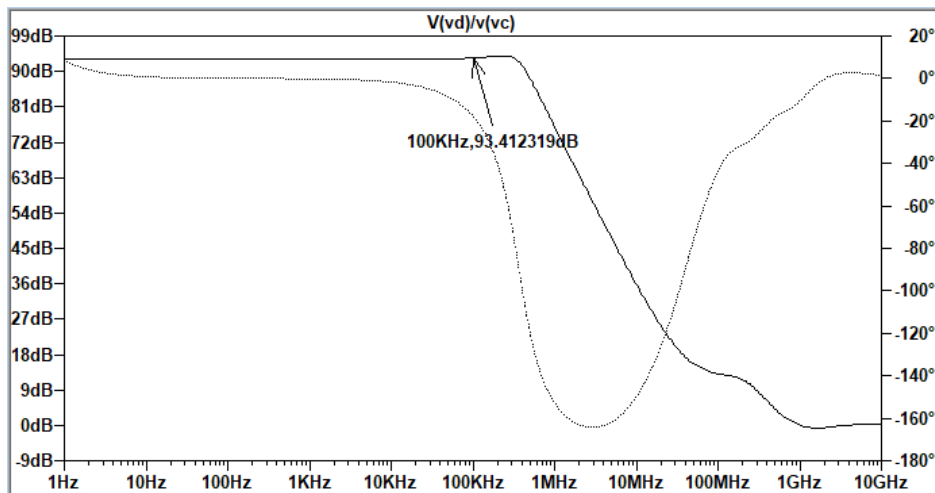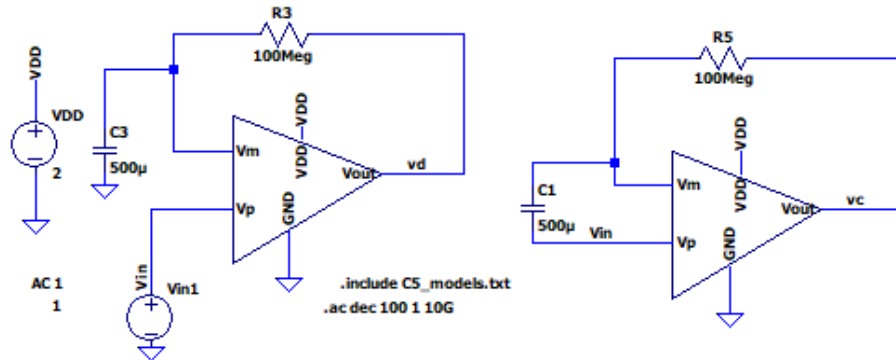
## Project Condition 4: CMRR > 90dB at 100kHz, satisfied at 93.4dB



The CMRR was 93.41dB which was above the requirement. At first, I had a lower CMRR of about 70dB. The common mode signal is just noise, so the common mode rejection ratio is how well the circuit's differential amplifier rejects noise. The noise affects the positive and negative terminal's voltages to vary so increasing the CMRR is crucial for a good circuit. By understanding the CMRR equation, I deduced that increasing the length of the PMOS differential amplifiers current biasing source would **decrease gm** and in turn **increase the output resistance**. Increasing the output resistances increases the CMRR.

$$\text{The equation for } gm = \sqrt{2 * Kpn * \frac{W}{L} * ID}$$

Increasing the length decreases the gm because the length is inversely proportional to the gm.


$$r_o = \frac{1}{gm}$$



Once gm goes down, the ro goes up and the CMRR increases based on the equation for CMRR below.

$$\text{Common Mode Gain} = A_c = \frac{V_{out}}{V_c} = \frac{-1}{2 * R_o} = \frac{-1}{2 * g_m * R_o}$$

$$\text{CMRR} = 20 * \log \log \left| \frac{A_d}{A_c} \right| = 20 * \log(g_m(ro_{17} || ro_{18}) * 2(g_m R_o))$$

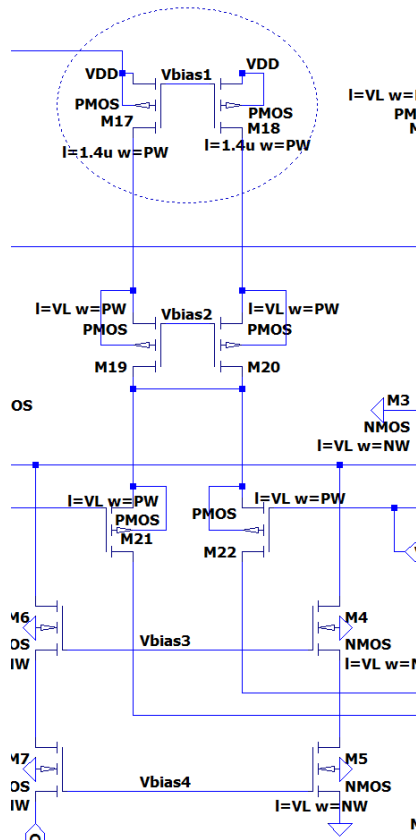

The usual length was 0.6u and was increased to 1.4u.



## Project Condition 5: PSRR > 60dB at 1kHz

**PSSR PLUS satisfied, at 87.74dB at 1kHz.**

The power supply rejection ratio measures how well the op amp rejects noise on the power supply voltages, VDD and GND, where the CMRR checks the voltages on VP and VM.


The compensation capacitor has a lot to do with PSRR since at higher frequencies, the compensation capacitor has a transistors gate and drain short together which sends the noise from VDD to the output. The ground noise does not affect the op amp ideally, but it does show up in practical circuits at the output. At high frequencies the compensation capacitor, ground noise does not appear.

 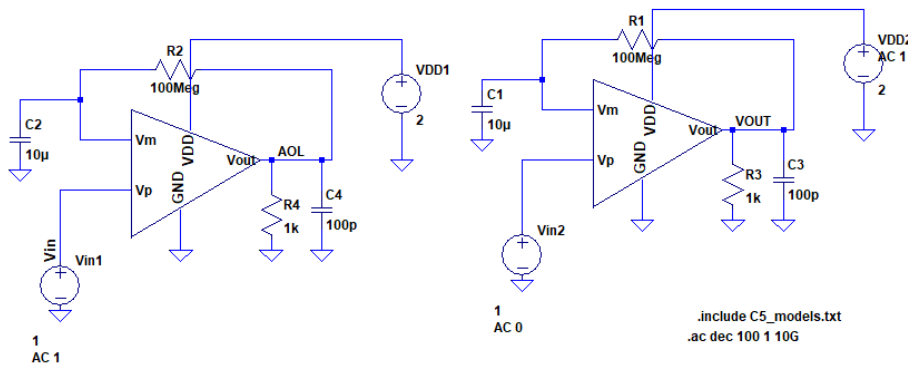
$$PSRR+ = \frac{Aol(f)}{\frac{Vout}{V+}}$$



## PSRR Minus

Slightly below 60dB at 1kHz, at 58.4dB

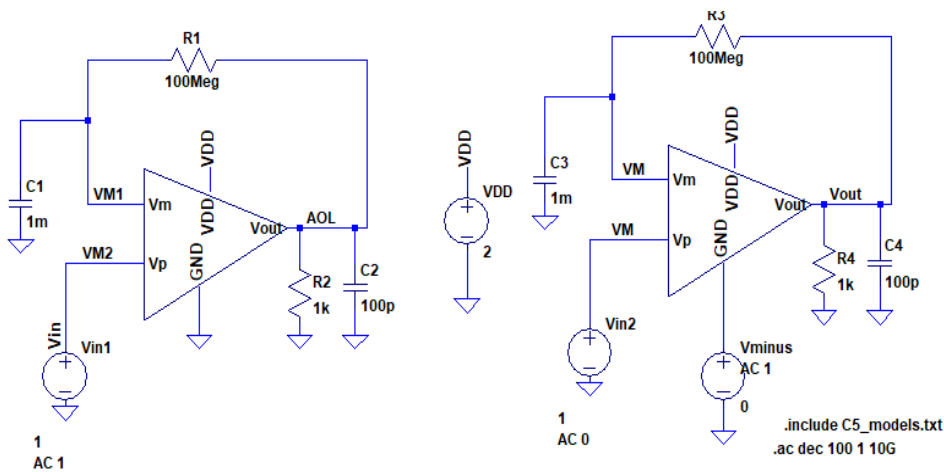

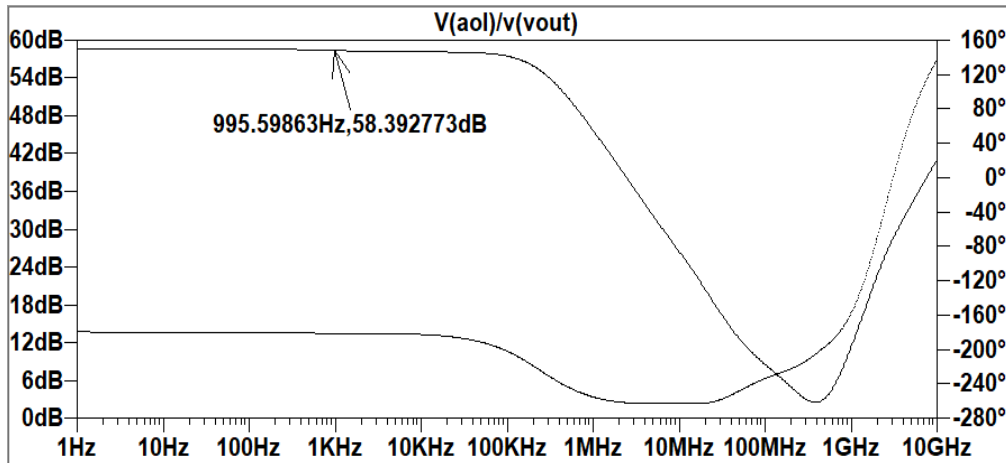



At higher frequencies, the PSRR is still at 58dB before dropping, whereas for the PSRR plus, the signal falls earlier, before 1kHz. Because of the compensation capacitor, at higher frequencies the ground noise contributions to the output signal decrease.

The PSRR minus is slightly below the requirement, because of a tradeoff I choose in this design. Increasing the gain will increase the PSRR, however the stability of the circuit decreases. My priority in this design is to have a stable circuit. **More discussion on PSRR and CMRR tradeoffs is found in the first few pages.**
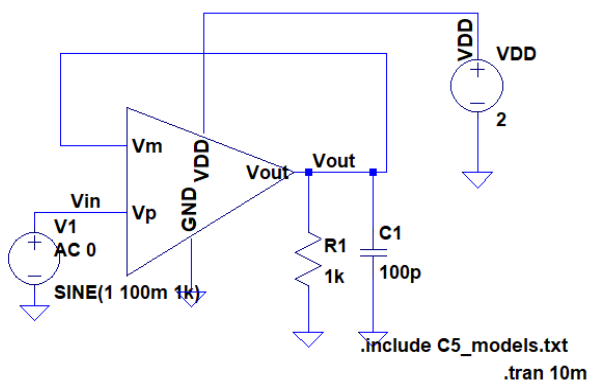
## Testing Closed Loop Gain using a Voltage Follower



The closed loop gain of a voltage follower is 1. A voltage follower is very unstable and testing it with a feedback increases the stability when testing the open loop gain. Testing it with a load of 1k and 100pF shows the gain to be 1.



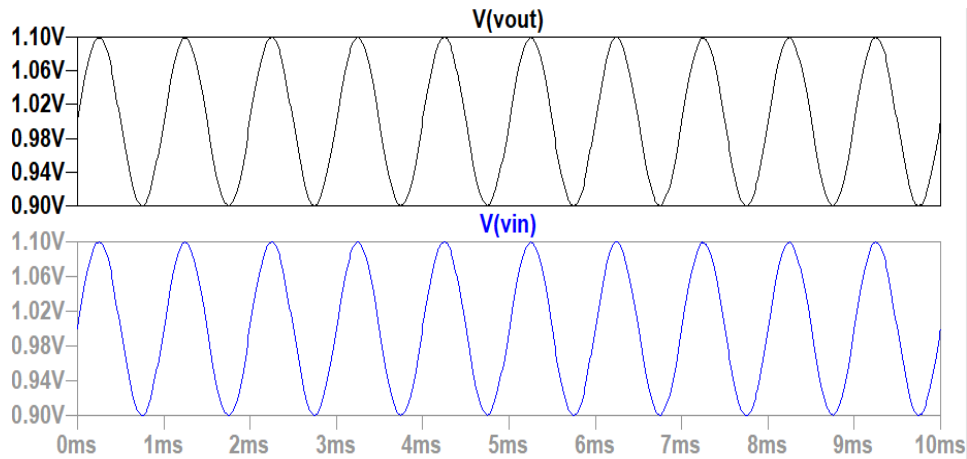

 
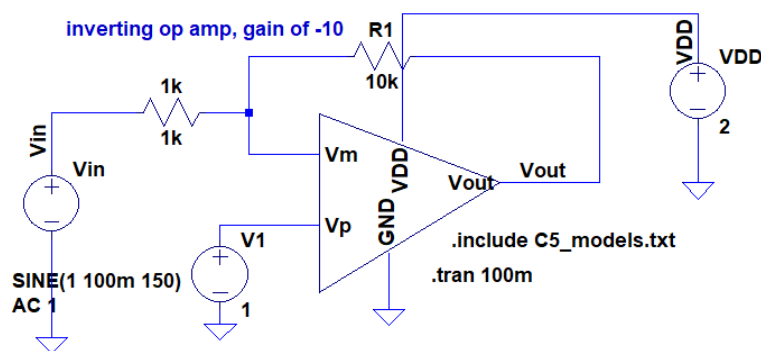
## Testing Closed Loop gain using an Inverting Op-Amp

Testing the closed loop gain shows a gain of 10, and that the op amp works.


 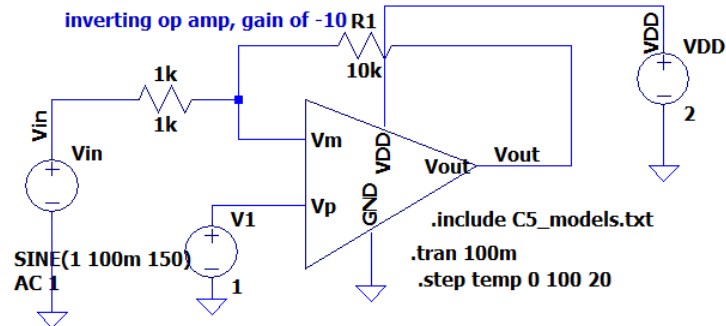
## Closed Loop Gain Over Varying Temperatures


Gain remains the same, 10, over varying temperatures.



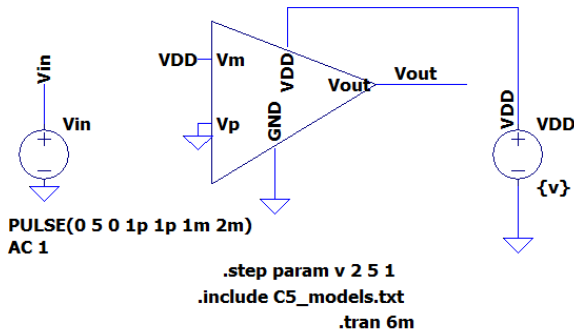
## Power Dissipation

One of the goals of this op amp design is to dissipate as little power as possible while operating properly. The current was reduced in order to lower the power dissipation of the circuit. To find the power dissipation, all the currents were added through each branch and multiplied by the VDD value.

The power ranges from 287.85uW at 2V to 1.06mW at 5V. The power dissipation is not optimal, however, for such a large gain and precise phase margin, the power dissipation of the circuit is enough.



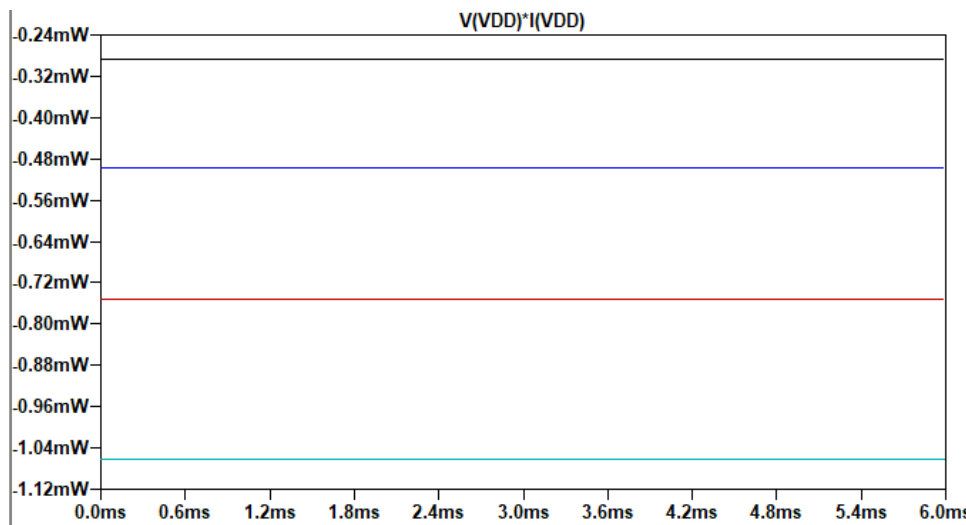This response shows VDD of 2V at the top and increases the voltage as it moves further down.



## Input CMR as a Function of VDD

The common mode range (CMR) is the range at which the inputs of the op amp can operate, since the inputs are forced through feedback to be similar values. If the voltages on VP and VM go outside of the CMR, the gain can fall. The common mode voltage is the average of the voltages on the inputs of the op-amp. In order to maintain that range we must know the minimum and maximum input voltages. We can find those values using the VCMmax and VCMmin equations.

$$VDS \geq VGS - V_{thn}$$

$$VD \geq VG - V_{thn}$$

$$VD = VDD$$

$$VD \geq VG - V_{thn}$$

Let  $VG = V_{cmmax}$

$$V_{cmmax} = V_{DD} + V_{thn} = 2V + 0.667 = 2.667V$$

The VCMmax equation shows that the input can be 667mV larger than the power supply voltage.

### Find VCMmin

$$V_{cmmin} = V_{GS} + 2 * V_{DSsat}$$

$$V_{SD} \geq V_{SG} - V_{thp}$$

$$V_D \leq V_G + V_{thp}$$

$$\text{Let } V_G = V_{CMmin}$$

$$V_{CMmin} = V_D - V_{thp}$$

$$V_D = V_{SDsat}$$


$$V_{CMmin} = V_{SDsat} - V_{thp} = 0.100V - 0.9214V = -0.8214V$$

The VCMmin equation shows that the input can drift 821mV below power supply voltage.

The common mode range is the range between these two voltages with respect to VDD.


 
### VCM Min Simulation

This simulation shows that when the input voltage in the positive terminal is more than 800mV below VDD, the circuit still operates correctly. I tested it with a negative voltage to show the full operation. The gain is still above 66dB and the phase margin is still 90 degrees.



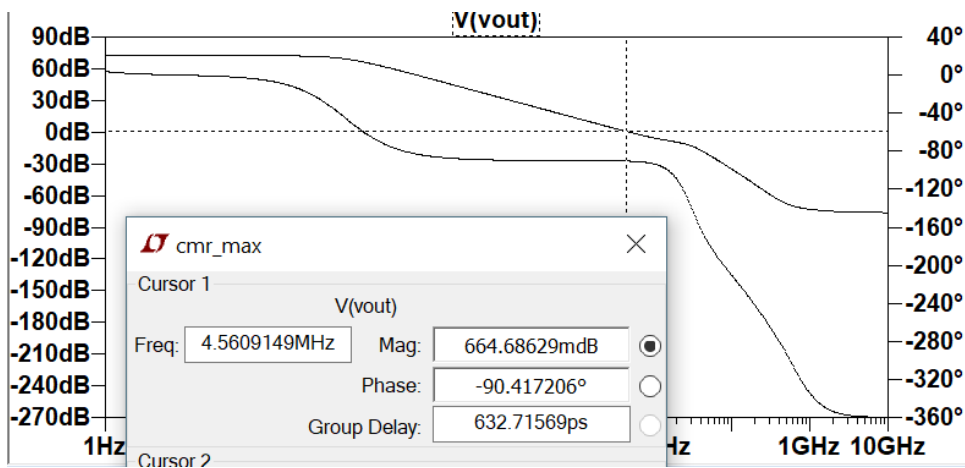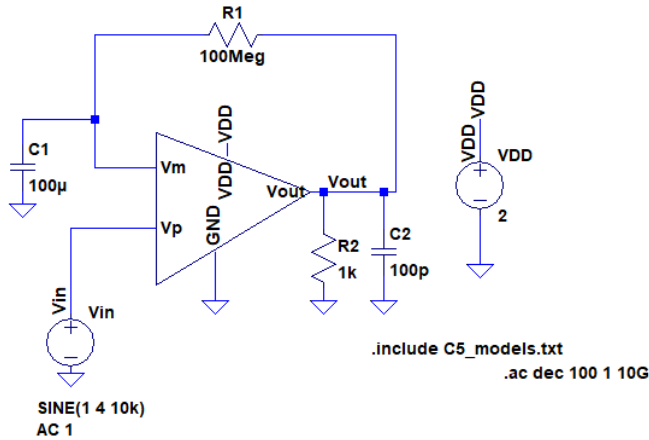
### VCM Max Simulation

CMR max tested with an input voltage double the power supply voltage.



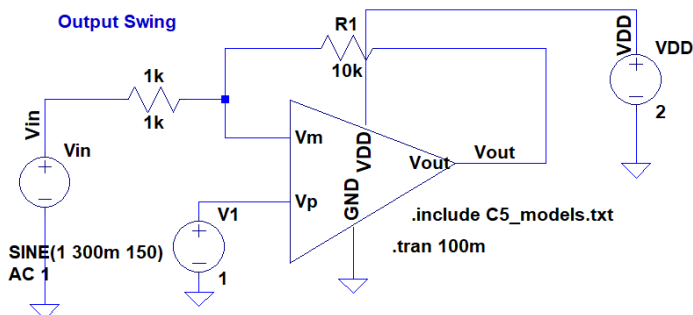
## Output Swing

In order to measure the output swing, a sine wave with a large amplitude is sent into the op-amp in order to find where the output clips. The amplitude I choose was 300mV and the output was 2V again, showing that the output swing is from 0-2V.





 

Overall, the op-amp worked and satisfied the requirements. More information about trade-offs and future project improvement can be found at the beginning of the report.