

### Chapter 1, Solution 16


(a)

$$i(t) = \begin{cases} 30t \text{ mA}, & 0 < t < 2 \\ 120 - 30t \text{ mA}, & 2 < t < 4 \end{cases}$$

$$v(t) = \begin{cases} 5 \text{ V}, & 0 < t < 2 \\ -5 \text{ V}, & 2 < t < 4 \end{cases}$$

$$p(t) = \begin{cases} 150t \text{ mW}, & 0 < t < 2 \\ -600 + 150t \text{ mW}, & 2 < t < 4 \end{cases}$$

which is sketched below.

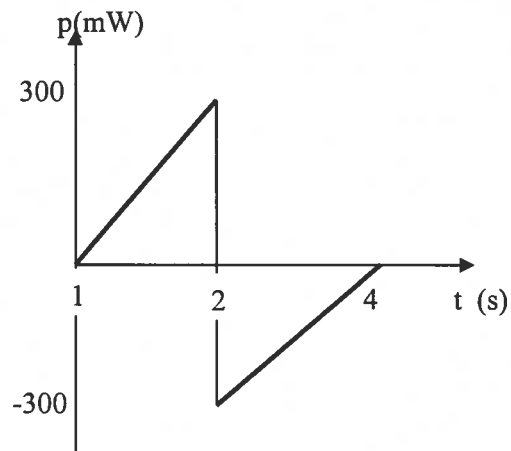

(b) From the graph of  $p$ ,

$$W = \int_0^4 p dt = \underline{0 \text{ J}}$$

**Chapter 1, Solution 18**

$$p_1 = 30(-10) = \mathbf{-300\ W}$$

$$p_2 = 10(10) = \mathbf{100\ W}$$

$$p_3 = 20(14) = \mathbf{280\ W}$$

$$p_4 = 8(-4) = \mathbf{-32\ W}$$

$$p_5 = 12(-4) = \mathbf{-48\ W}$$

**Chapter 1, Solution 20**

$$p_{30 \text{ volt source}} = 30(-6) = -180 \text{ W}$$

$$p_{12 \text{ volt element}} = 12 \times 6 = 72 \text{ W}$$

$$p_{28 \text{ volt element with 2 amps flowing through it}} = 28 \times 2 = 56 \text{ W}$$

$$p_{28 \text{ volt element with 1 amp flowing through it}} = 28 \times 1 = 28 \text{ W}$$

$$p_{\text{the 5I}_o \text{ dependent source}} = 5 \times 2 \times (-3) = -30 \text{ W}$$

Since the total power absorbed by all the elements in the circuit must equal zero,  
or  $0 = -180 + 72 + 56 + 28 - 30 + p_{\text{into the element with } V_o}$  or

$$p_{\text{into the element with } V_o} = 180 - 72 - 56 - 28 + 30 = 54 \text{ W}$$

Since  $p_{\text{into the element with } V_o} = V_o \times 3 = 54 \text{ W}$  or  $V_o = 18 \text{ V}$ .

**Chapter 1, Solution 26**

(a)  $i = \frac{0.8\text{A} \cdot \text{h}}{10\text{h}} = \mathbf{80\text{ mA}}$

(b)  $p = vi = 6 \times 0.08 = \mathbf{0.48\text{ W}}$

(c)  $w = pt = 0.48 \times 10\text{ Wh} = \mathbf{0.0048\text{ kWh}}$

Chapter 1, Solution 3

$$(a) \quad q(t) = \int i(t) dt + q(0) = \underline{(3t + 1) \text{ C}}$$

$$(b) \quad q(t) = \int (2t + s) dt + q(v) = \underline{(t^2 + 5t) \text{ mC}}$$

$$(c) \quad q(t) = \int 20 \cos (10t + \pi / 6) + q(0) = \underline{(2 \sin(10t + \pi / 6) + 1) \mu\text{C}}$$

$$(d) \quad q(t) = \int 10e^{-30t} \sin 40t + q(0) = \frac{10e^{-30t}}{900 + 1600} (-30 \sin 40t - 40 \cos t) \\ = \underline{-e^{-30t} (0.16 \cos 40 t + 0.12 \sin 40t) \text{ C}}$$