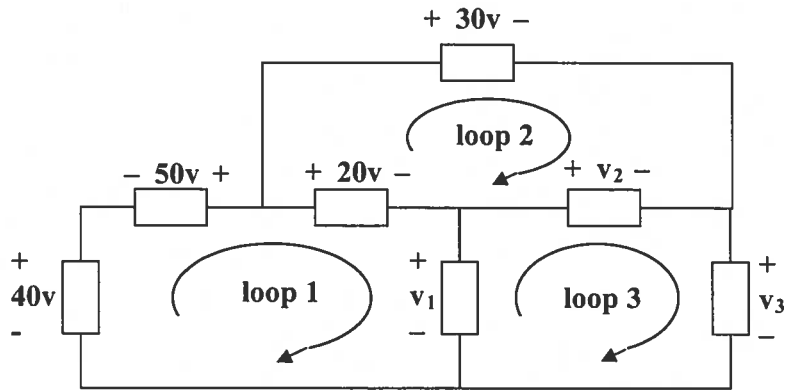


Chapter 2, Solution 12



For loop 1, $-40 - 50 + 20 + v_1 = 0$ or $v_1 = 40 + 50 - 20 = 70 \text{ V}$

For loop 2, $-20 + 30 - v_2 = 0$ or $v_2 = 30 - 20 = 10 \text{ V}$

For loop 3, $-v_1 + v_2 + v_3 = 0$ or $v_3 = 70 - 10 = 60 \text{ V}$

Chapter 2, Solution 18

Applying KVL,

$$-30 - 10 + 8 + I(3+5) = 0$$

$$8I = 32 \quad \longrightarrow \quad I = \underline{4A}$$

$$-V_{ab} + 5I + 8 = 0 \quad \longrightarrow \quad V_{ab} = \underline{28V}$$

Chapter 2, Solution 22

Find V_o in the circuit in Fig. 2.86 and the power absorbed by the dependent source.

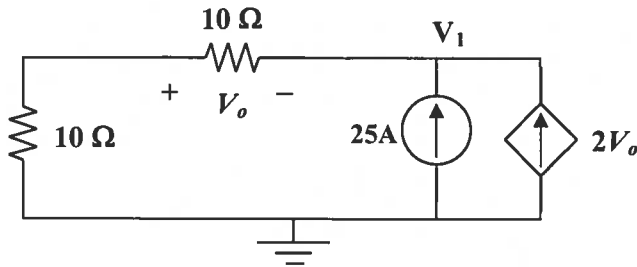


Figure 2.86
For Prob. 2.22

Solution

At the node, KCL requires that $[-V_o/10] + [-25] + [-2V_o] = 0$ or $2.1V_o = -25$

$$\text{or } V_o = -11.905 \text{ V}$$

The current through the controlled source is $i = 2V_o = -23.81 \text{ A}$
and the voltage across it is $V_1 = (10+10) i_0$ (where $i_0 = -V_o/10$) $= 20(11.905/10)$
 $= 23.81 \text{ V}$.

Hence,

$$P_{\text{dependent source}} = V_1(-i) = 23.81 \times (-(-23.81)) = \mathbf{566.9 \text{ W}}$$

Checking, $(25 - 23.81)^2(10 + 10) + (23.81)(-25) + 566.9 = 28.322 - 595.2 + 566.9$
 $= 0.022$ which is equal zero since we are using four places of accuracy!

Chapter 2, Solution 24

$$(a) \quad I_0 = \frac{V_s}{R_1 + R_2}$$

$$V_0 = -\alpha I_0 (R_3 \parallel R_4) = -\frac{\alpha V_s}{R_1 + R_2} \cdot \frac{R_3 R_4}{R_3 + R_4}$$

$$\frac{V_0}{V_s} = \frac{-\alpha R_3 R_4}{(R_1 + R_2)(R_3 + R_4)}$$

$$(b) \quad \text{If } R_1 = R_2 = R_3 = R_4 = R,$$

$$\left| \frac{V_0}{V_s} \right| = \frac{\alpha}{2R} \cdot \frac{R}{2} = \frac{\alpha}{4} = 10 \longrightarrow \alpha = 40$$

Chapter 2, Solution 42

$$(a) \quad R_{ab} = 5 \parallel (8 + 20 \parallel 30) = 5 \parallel (8 + 12) = \frac{5 \times 20}{25} = 4 \, \Omega$$

$$(b) \quad R_{ab} = 2 + 4 \parallel (5 + 3) \parallel 8 + 5 \parallel 10 \parallel 4 = 2 + 4 \parallel 4 + 5 \parallel 2.857 = 2 + 2 + 1.8181 = 5.818 \, \Omega$$

Chapter 2, Solution 46

$$\begin{aligned} R_{eq} &= 12 + 5 \parallel 20 + [1 / ((1/15) + (1/15) + (1/15))] + 5 + 24 \parallel 8 \\ &= 12 + 4 + 5 + 5 + 6 = 32 \Omega \end{aligned}$$

$$I = 80/32 = 2.5 \text{ A}$$