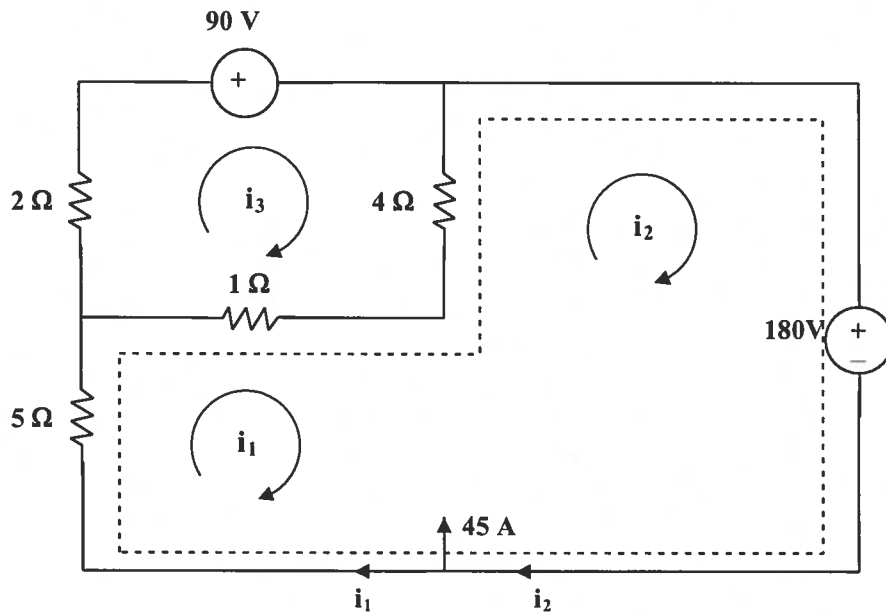


Chapter 3, Solution 44



Loop 1 and 2 form a supermesh. For the supermesh,


$$6i_1 + 4i_2 - 5i_3 + 180 = 0 \quad (1)$$

For loop 3, 
$$-i_1 - 4i_2 + 7i_3 + 90 = 0 \quad (2)$$

Also, 
$$i_2 = 45 + i_1 \quad (3)$$

Solving (1) to (3),  $i_1 = -46$ ,  $i_3 = -20$ ;  $i_o = i_1 - i_3 = -26 \text{ A}$

Chapter 3, Solution 50

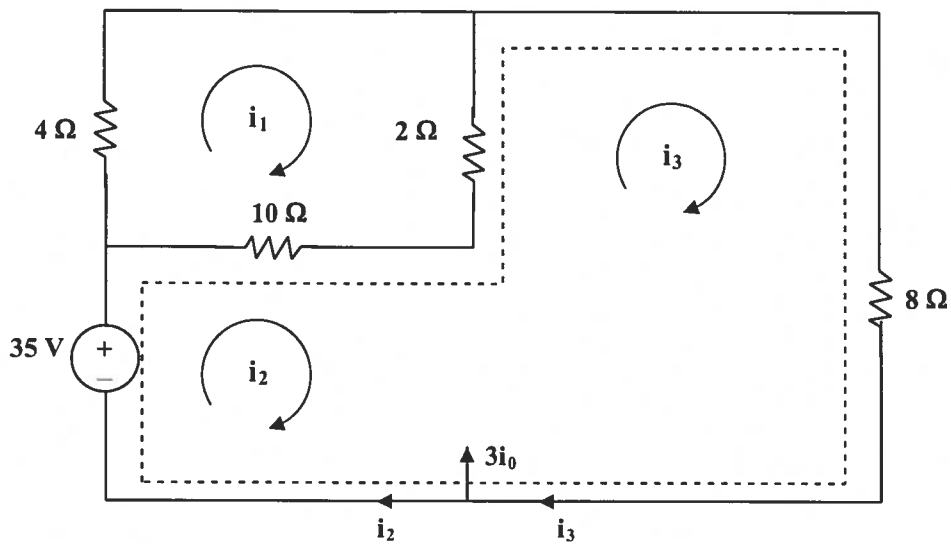

For loop 1,  $16i_1 - 10i_2 - 2i_3 = 0$  which leads to  $8i_1 - 5i_2 - i_3 = 0$  (1)

For the supermesh,  $-35 + 10i_2 - 10i_1 + 10i_3 - 2i_1 = 0$


or  $-6i_1 + 5i_2 + 5i_3 = 17.5$  (2)

Also,  $3i_0 = i_3 - i_2$  and  $i_0 = i_1$  which leads to  $3i_1 = i_3 - i_2$  (3)

Solving (1), (2), and (3), we obtain  $i_1 = 1.0098$  and

$$i_0 = i_1 = \mathbf{1.0098 \text{ A}}$$

Chapter 3, Solution 56

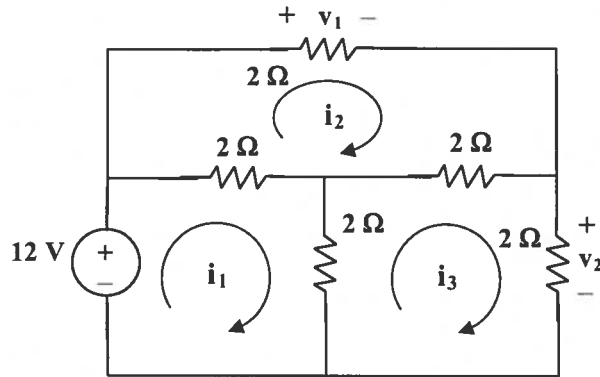

For loop 1,  $12 = 4i_1 - 2i_2 - 2i_3$  which leads to  $6 = 2i_1 - i_2 - i_3$  (1)

For loop 2,  $0 = 6i_2 - 2i_1 - 2i_3$  which leads to  $0 = -i_1 + 3i_2 - i_3$  (2)

For loop 3,  $0 = 6i_3 - 2i_1 - 2i_2$  which leads to  $0 = -i_1 - i_2 + 3i_3$  (3)

In matrix form (1), (2), and (3) become,

$$\begin{bmatrix} 2 & -1 & -1 \\ -1 & 3 & -1 \\ -1 & -1 & 3 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 6 \\ 0 \\ 0 \end{bmatrix}$$

$$\Delta = \begin{vmatrix} 2 & -1 & -1 \\ -1 & 3 & -1 \\ -1 & -1 & 3 \end{vmatrix} = 8, \quad \Delta_2 = \begin{vmatrix} 2 & 6 & -1 \\ -1 & 3 & -1 \\ -1 & 0 & 3 \end{vmatrix} = 24$$

$$\Delta_3 = \begin{vmatrix} 2 & -1 & 6 \\ -1 & 3 & 0 \\ -1 & -1 & 0 \end{vmatrix} = 24, \text{ therefore } i_2 = i_3 = 24/8 = 3\text{A},$$


$$v_1 = 2i_2 = 6 \text{ volts}, \quad v_2 = 2i_3 = 6 \text{ volts}$$

### Chapter 3, Solution 75

\* Schematics Netlist \*

```

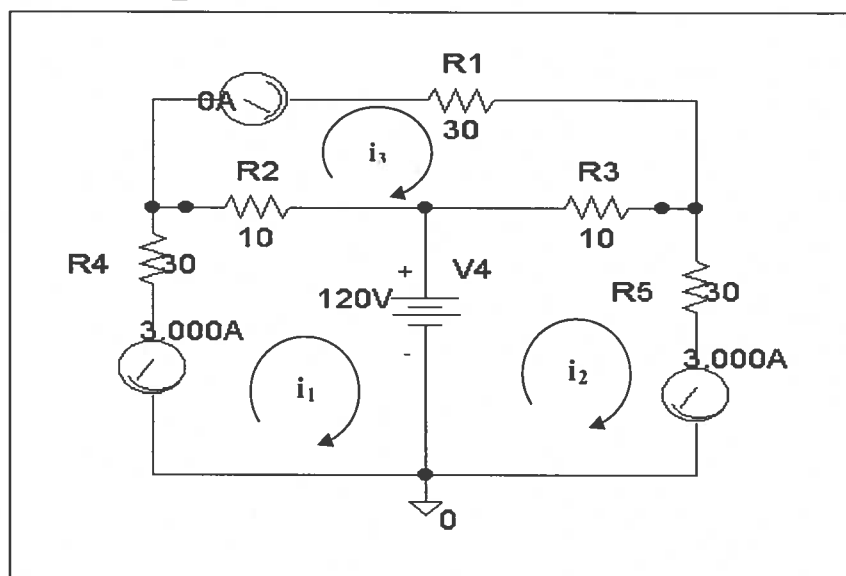R_R4      $N_0002 $N_0001 30
R_R2      $N_0001 $N_0003 10
R_R1      $N_0005 $N_0004 30
R_R3      $N_0003 $N_0004 10
R_R5      $N_0006 $N_0004 30
V_V4      $N_0003 0 120V
v_V3      $N_0005 $N_0001 0
v_V2      0 $N_0006 0
v_V1      0 $N_0002 0
    
```



Clearly,  $i_1 = -3$  amps,  $i_2 = 0$  amps, and  $i_3 = 3$  amps, which agrees with the answers in Problem 3.44.

### Chapter 3, Solution 88

Let  $v_1$  be the potential at the top end of the 100-ohm resistor.

$$(v_s - v_1)/200 = v_1/100 + (v_1 - 10^{-3}v_0)/2000 \quad (1)$$

For the right loop,  $v_0 = -40i_0(10,000) = -40(v_1 - 10^{-3})10,000/2000$ ,

$$\text{or, } v_0 = -200v_1 + 0.2v_0 = -4 \times 10^{-3}v_0 \quad (2)$$

Substituting (2) into (1) gives,  $(v_s + 0.004v_1)/2 = -0.004v_0 + (-0.004v_1 - 0.001v_0)/20$

This leads to  $0.125v_0 = 10v_s$  or  $(v_0/v_s) = 10/0.125 = -80$