

**Chapter 5, Solution 10.**


Since no current enters the op amp, the voltage at the input of the op amp is  $v_s$ . Hence

$$v_s = v_o \left( \frac{10}{10+10} \right) = \frac{v_o}{2} \quad \longrightarrow \quad \frac{v_o}{v_s} = 2$$

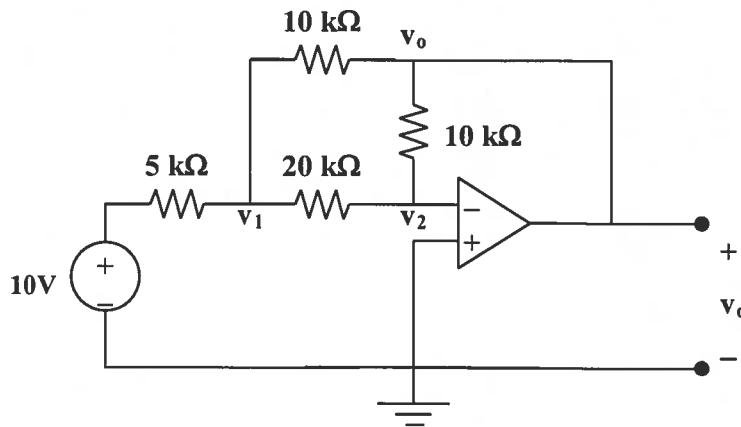**Chapter 5, Solution 14.**

Transform the current source as shown below. At node 1,

$$\frac{10 - v_1}{5} = \frac{v_1 - v_2}{20} + \frac{v_1 - v_o}{10}$$




$$\text{But } v_2 = 0. \text{ Hence } 40 - 4v_1 = v_1 + 2v_1 - 2v_o \rightarrow 40 = 7v_1 - 2v_o \quad (1)$$

$$\text{At node 2, } \frac{v_1 - v_2}{20} = \frac{v_2 - v_o}{10}, \quad v_2 = 0 \text{ or } v_1 = -2v_o \quad (2)$$

$$\text{From (1) and (2), } 40 = -14v_o - 2v_o \rightarrow v_o = -2.5V$$

**Chapter 5, Solution 20.**

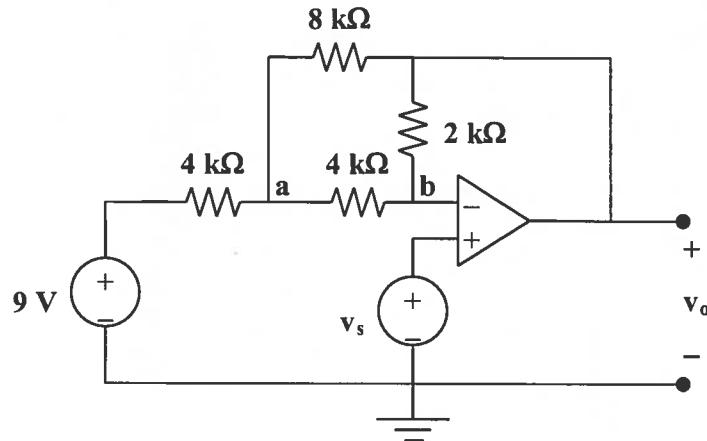

At node a,

$$\frac{9 - v_a}{4} = \frac{v_a - v_o}{8} + \frac{v_a - v_b}{4} \longrightarrow 18 = 5v_a - v_o - 2v_b \quad (1)$$


At node b,

$$\frac{v_a - v_b}{4} = \frac{v_b - v_o}{2} \longrightarrow v_a = 3v_b - 2v_o \quad (2)$$

But  $v_b = v_s = 2$  V; (2) becomes  $v_a = 6 - 2v_o$  and (1) becomes

$$-18 = 30 - 10v_o - v_o - 4 \quad v_o = -44/(-11) = 4 \text{ V.}$$

**Chapter 5, Solution 28.**

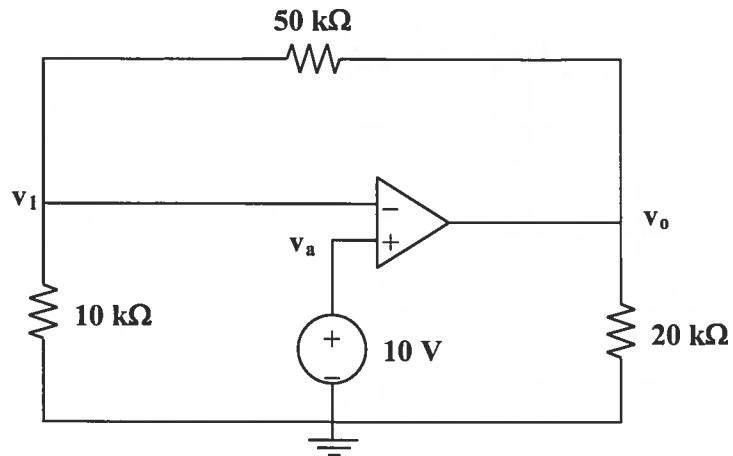

$$\text{At node 1, } \frac{0 - v_1}{10k} = \frac{v_1 - v_o}{50k}$$

But  $v_1 = 10V$ ,

$$-5v_1 = v_1 - v_o, \text{ leads to } v_o = 6v_1 = 60V$$

Alternatively, viewed as a noninverting amplifier,

$$v_o = (1 + (50/10)) (10V) = 60V$$

$$i_o = v_o/(20k) = 60/(20k) = 3 \text{ mA.}$$

### Chapter 5, Solution 30.

The output of the voltage becomes

$$v_o = v_i = 1.2 \text{ V}$$
$$(30k\parallel 20k) = 12k\Omega$$

By voltage division,

$$v_x = \frac{12}{12+60} (1.2) = 0.2 \text{ V}$$

$$i_x = \frac{v_x}{20k} = \frac{0.2}{20k} = \frac{20}{2 \times 10^6} = 10 \mu\text{A}$$

$$p = \frac{v_x^2}{R} = \frac{0.04}{20k} = 2 \mu\text{W.}$$