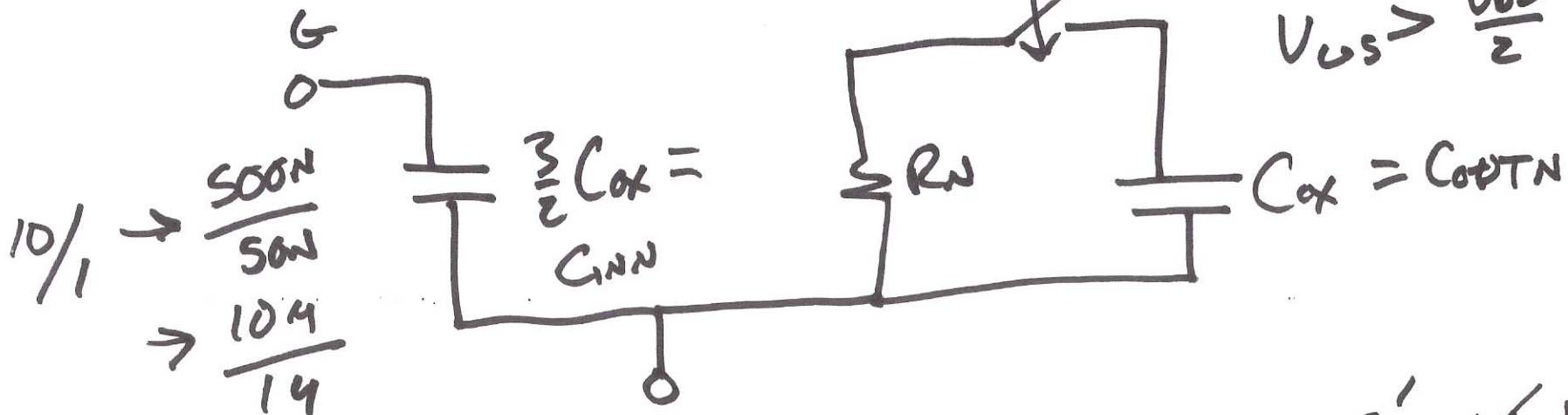


Process characteristic time constant.

Switch closes when $V_{GS} > \frac{V_{DD}}{2}$



10/1 → $\frac{500n}{50n}$
 → $\frac{10\mu}{1\mu}$

$$\tau_N = R_N \cdot C_{ox} = \frac{V_{DD}}{\frac{\mu_n C_{ox} W}{2L} (V_{DD} - V_{THN})^2} \cdot C_{ox} \cdot W \cdot L$$

$\tau_P = 3\tau_N$

$\tau_N \propto L^2$

(L-scale)

true for long channel

1 · 1μm = 1μm
 1 · 50nm = 50nm
 Scale



Short-channel Processes

$$\tau_n = R_n \cdot C_{ox} = \frac{U_{DD}}{I_{on} \cdot W} \cdot C_{ox} \cdot L \cdot W$$

$$\tau_n \propto L$$

Short-channel

$$\tau_p = 2 \cdot \tau_n$$

Long channel

$$\tau_n = 25 \text{ ps}, \tau_p = 75 \text{ ps}$$

Short channel

$$\tau_n = 2.1 \text{ ps}, \tau_p = 4.2 \text{ ps}$$


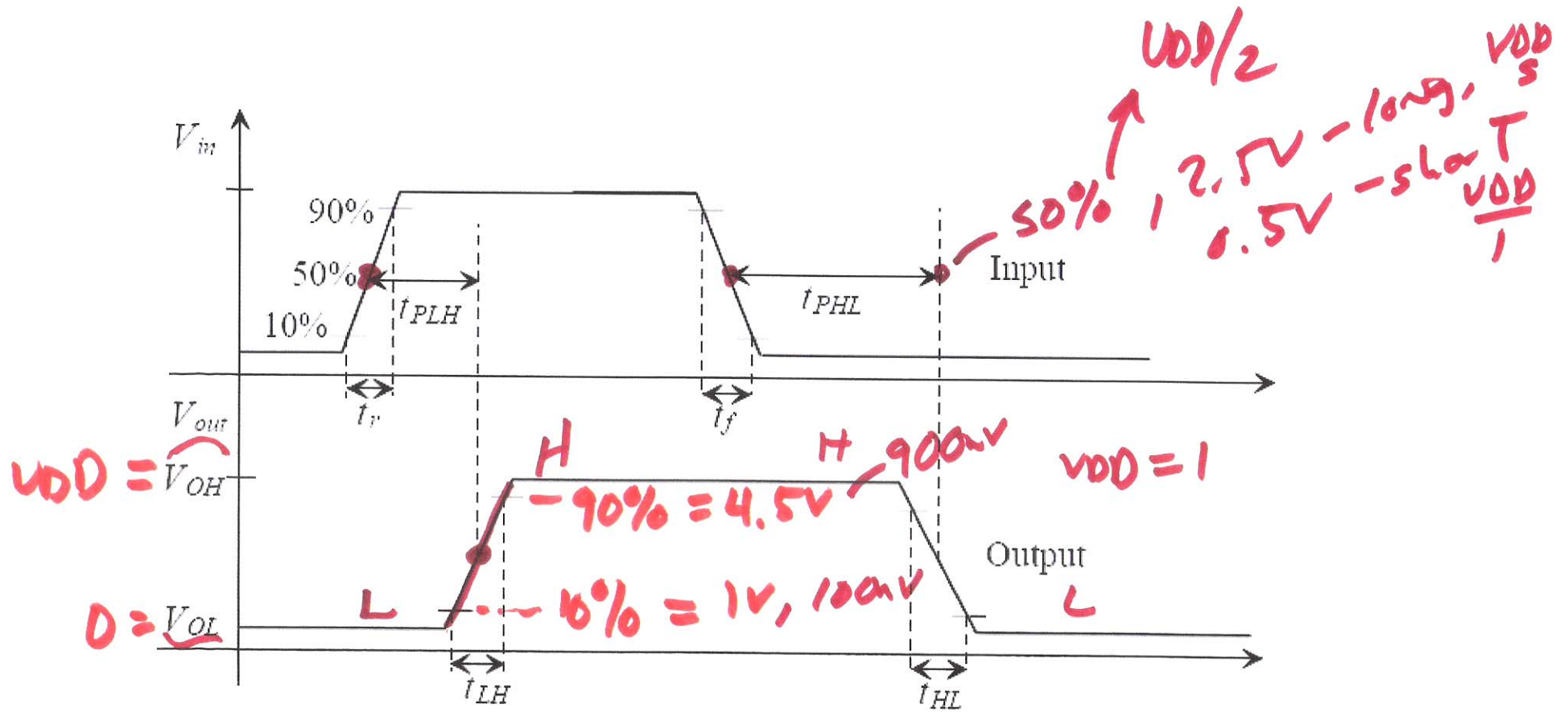


Figure 10.9 Definition of delays and transition times.

TTL \rightarrow 0.6 - 2.6V
 $V_{DD} = 5V$
 0

3)

@ VDD = 5V

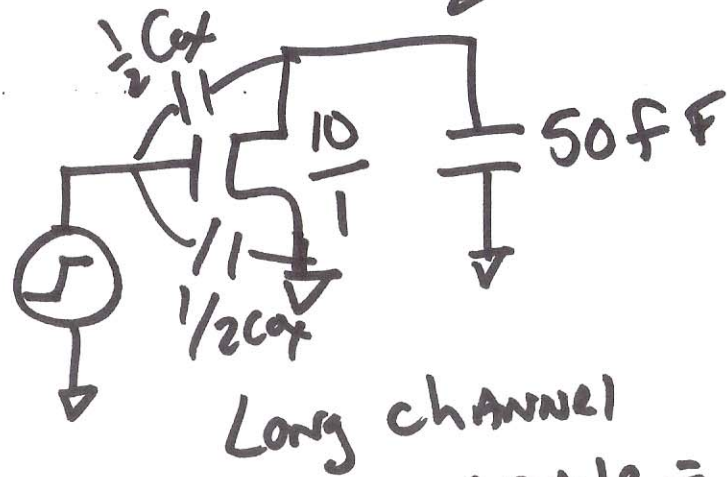

$$R_N = 15K \cdot \frac{1}{10} = 1.5K$$


$$C_{ox}' = 1.75 \frac{fF}{\mu m^2}$$

Long channel
SCALE = 1 μm

$$C_{ox} = 10 \cdot 1 \cdot (\text{scale})^2 \cdot 1.75 fF = 17.5 fF$$

$$\frac{W}{L} = \frac{10}{1} = \frac{10 \mu m}{1 \mu m}$$

$$RC = 1.5K \cdot 67.5 fF$$

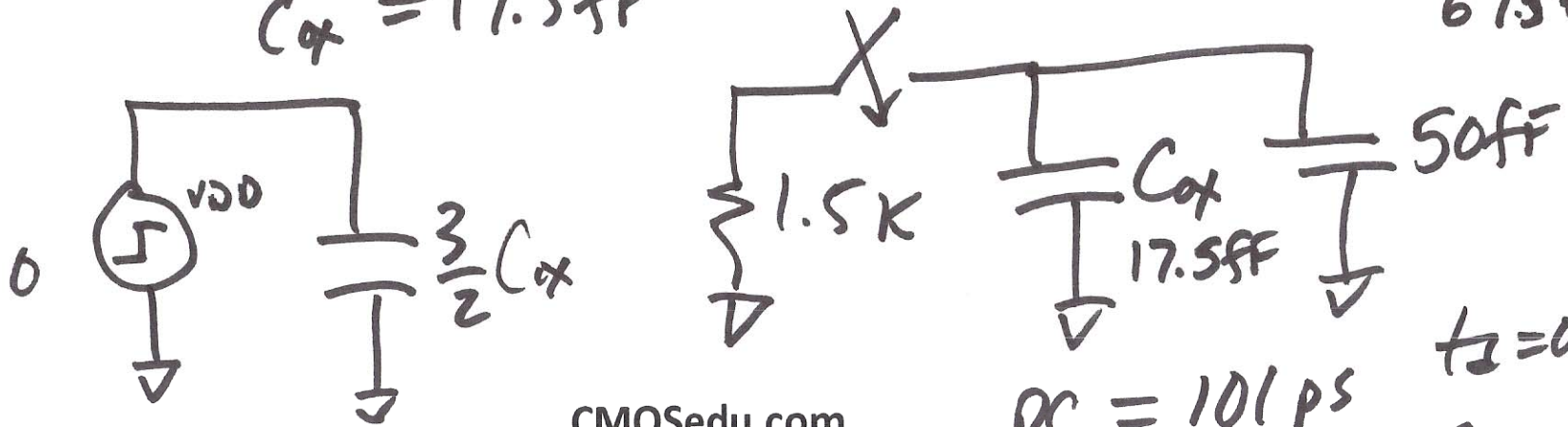


$$RC = 101 ps$$


$$t_d = 70 ps$$

$$t_2 = 0.7 \tau$$

4)

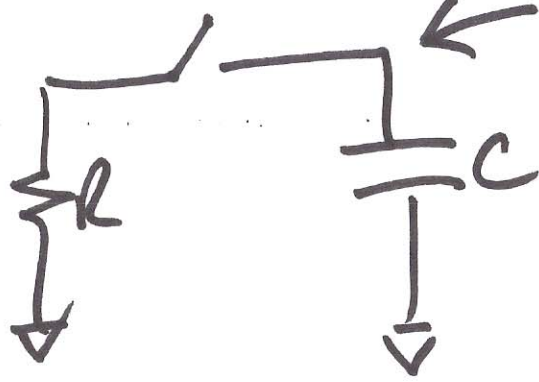

$$V_{out}(t) = V_{DD} e^{-t/RC}$$

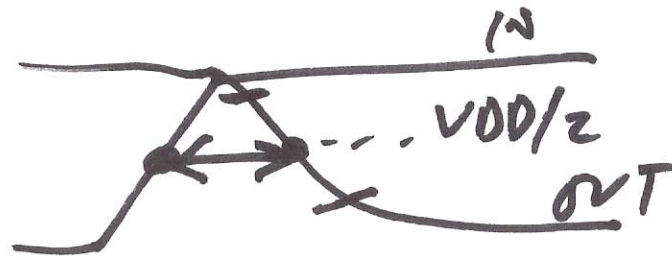

$$t_d = 0.7 RC$$

t_{delay} measured at
50% points



$$t_d = 70 \text{ ps}$$

$$\frac{V_{DD}}{2} = V_{DD} e^{-t_d/RC}$$

$$\ln \frac{1}{2} = \ln e^{-t_d/RC}$$

$$-0.7 = -t_d/RC$$

5)

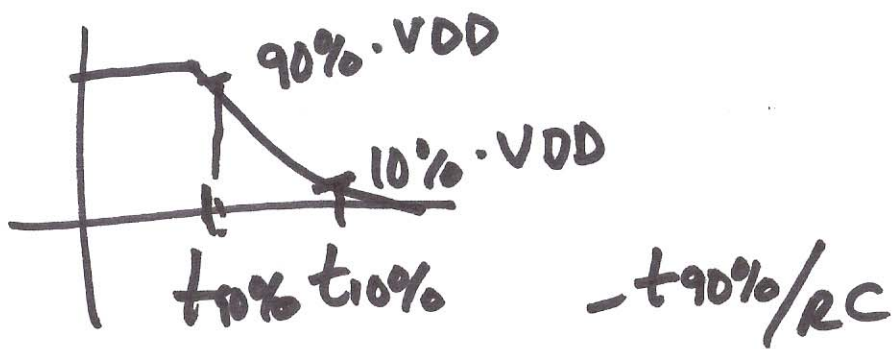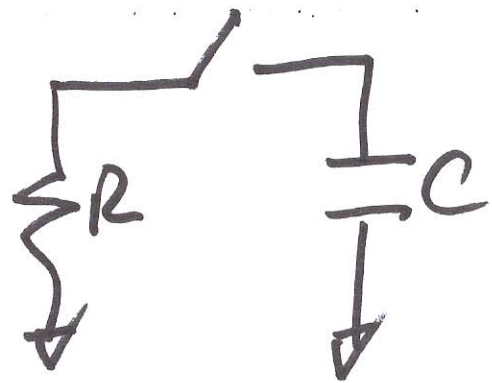

$$.9VDD = VDD e^{-t_{90\%}/RC}$$

$$.1VDD = VDD e^{-t_{10\%}/RC}$$

$$\ln a - \ln b = \ln \frac{a}{b}$$

$$t_{90\%} = -RC \ln .9$$

$$t_{10\%} = -RC \ln .1$$

$$t_d = 70ps$$

$$t_f = 220ps$$

$$t_f = t_{10\%} - t_{90\%} = -RC (\ln .1 - \ln .9)$$

$$= -RC \ln \frac{1}{9}$$

$$= RC \ln 9$$

$$t_f = 2.2RC$$

b)

$$t_f = 220ps$$