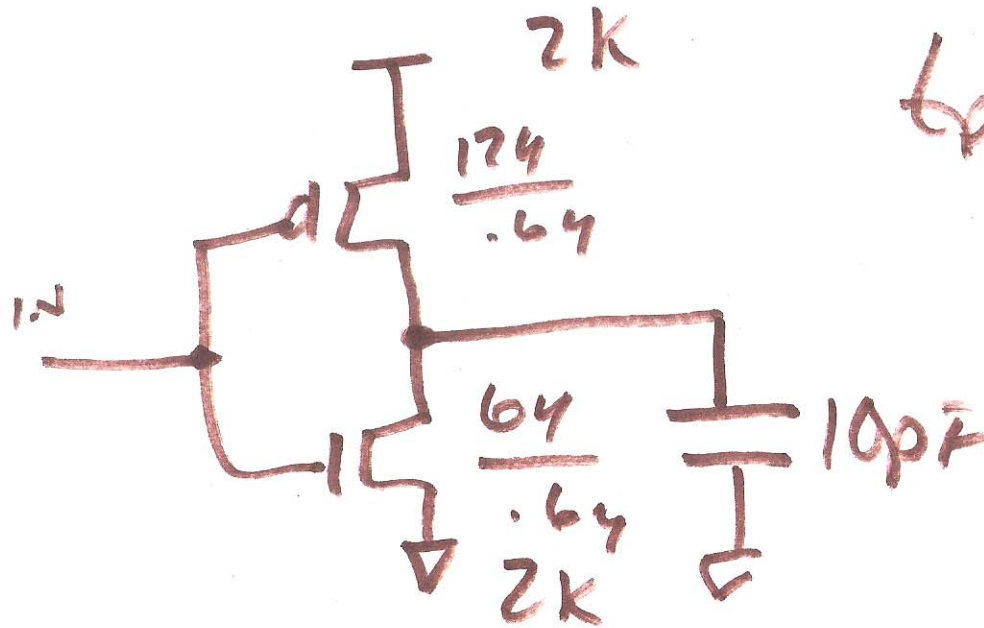


11.4 Sizing for Large capacitive loads

11/14/14




$$t_{PHL} = t_{PLH} =$$

$$\approx 0.7 \cdot 2K \cdot 10pF$$

$$= \underline{\underline{14ns}}$$

17

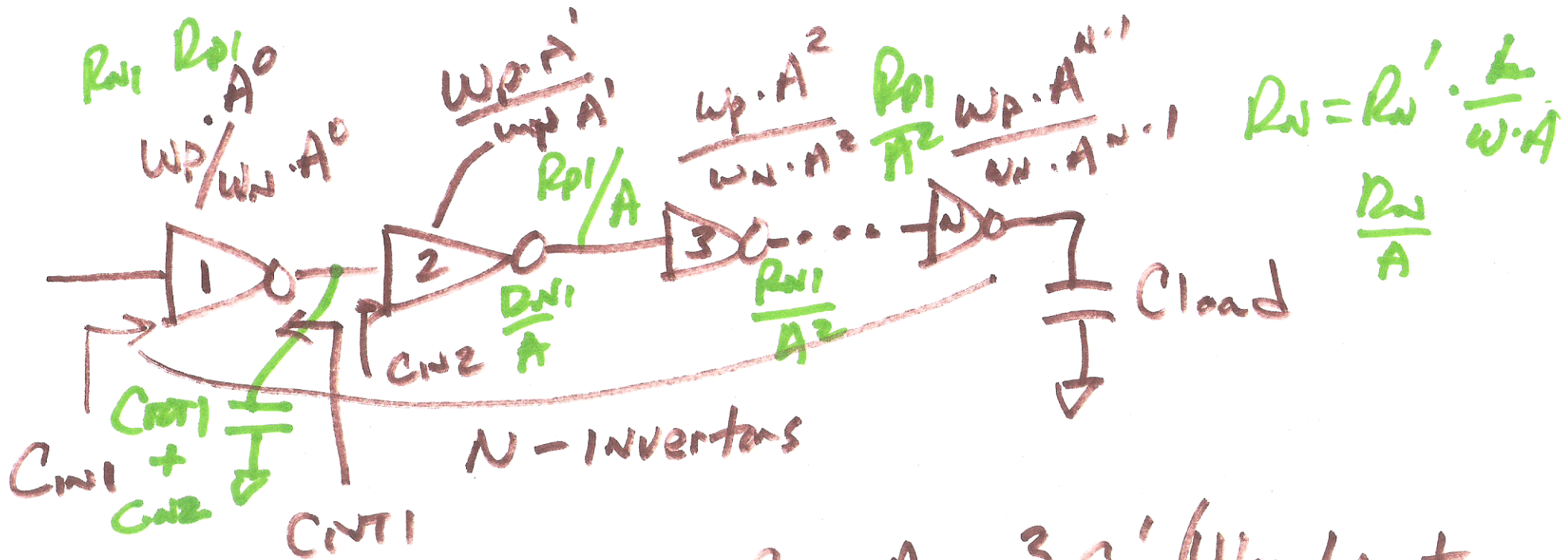

$$C_{in3} = C_{in1} \cdot A^2 = C_{in2} \cdot A$$

$$C_{load} = C_{in1} \cdot A^N$$

$$A = \left(\frac{C_{load}}{C_{in1}} \right)^{\frac{1}{N}}$$

$$C_{in2} = C_{in1} \cdot A = \frac{3}{2} C_{ox}' (W_{p1} \cdot L_{p1} + W_{n1} \cdot L_{n1}) \cdot A$$

$$C_{out2} = C_{out1} \cdot A = C_{ox}' (W_{p1} L_{p1} + W_{n1} L_{n1}) \cdot A$$

$$C_{out1} \cdot \frac{3}{2} = C_{in1}$$

$$R_w = R_w' \cdot \frac{L}{W \cdot A} = \frac{R_w}{A}$$

2)

$$t_{pHL} + t_{pLH} = 0.7 (R_{o1} + R_{p1}) \left(\underbrace{C_{in2}}_{A \cdot C_{in1}} + \underbrace{C_{out1}}_{\frac{2}{3} C_{in1}} \right) +$$

$$0.7 \left(\frac{R_{o1}}{A} + \frac{R_{p1}}{A} \right) \cdot \left(\underbrace{C_{in3}}_{A^2 \cdot C_{in1}} + \underbrace{C_{out2}}_{\frac{2}{3} C_{in1} \cdot A} \right) +$$

$$0.7 \left(\frac{R_{o1}}{A^2} + \frac{R_{p1}}{A^2} \right) \left(A^3 \cdot C_{in1} + \frac{2}{3} C_{in1} \cdot A^2 \right)$$

$$t_{oHL} + t_{oLH} = 0.7 (R_{o1} + R_{p1}) \cdot \sum_{k=1}^N (C_{outk} + A \cdot C_{in})$$

$$\frac{t_{oHL} + t_{oLH}}{\Delta V} = 0$$

$$\begin{aligned} \text{NB } C_{load} \\ = C_o \cdot A^N \end{aligned}$$

3)

$$D = 0.7 \cancel{(R_{n1} + R_{p1}) C_{load}} + (R_{n1} + R_{p1}) 0.7 \cdot C_{in1}$$

$$\left(\frac{\ln \frac{C_{load}}{C_{in1}}}{-N^2} \right) N \left(\frac{C_{load}}{C_{in1}} \right)^{1/2} = \left(\frac{C_{load}}{C_{in1}} \right)^{1/2}$$

$$\left(\left(\frac{C_{load}}{C_{in1}} \right)^{1/2} + N \left(\frac{C_{load}}{C_{in1}} \right)^{1/2} \right)$$

$$\frac{\ln \frac{C_{load}}{C_{in1}}}{-N^2}$$

↙ ?

$$N = \ln \frac{C_{load}}{C_{in1}} \approx 3 \quad \frac{\ln A}{-N} = \ln \left(\frac{C_{load}}{C_{in1}} \right)^{1/2}$$


$$A = \left(\frac{C_{load}}{C_{in1}} \right)^{1/2} = 2.92$$

$$C_{load} = 10pF$$

$$C_{in1} = \frac{3}{2} \cdot 2.5fF (12 \cdot 6 + 6 \cdot 6)$$

$$\text{ideal } A = e = 2.71 = 40fF$$

4)

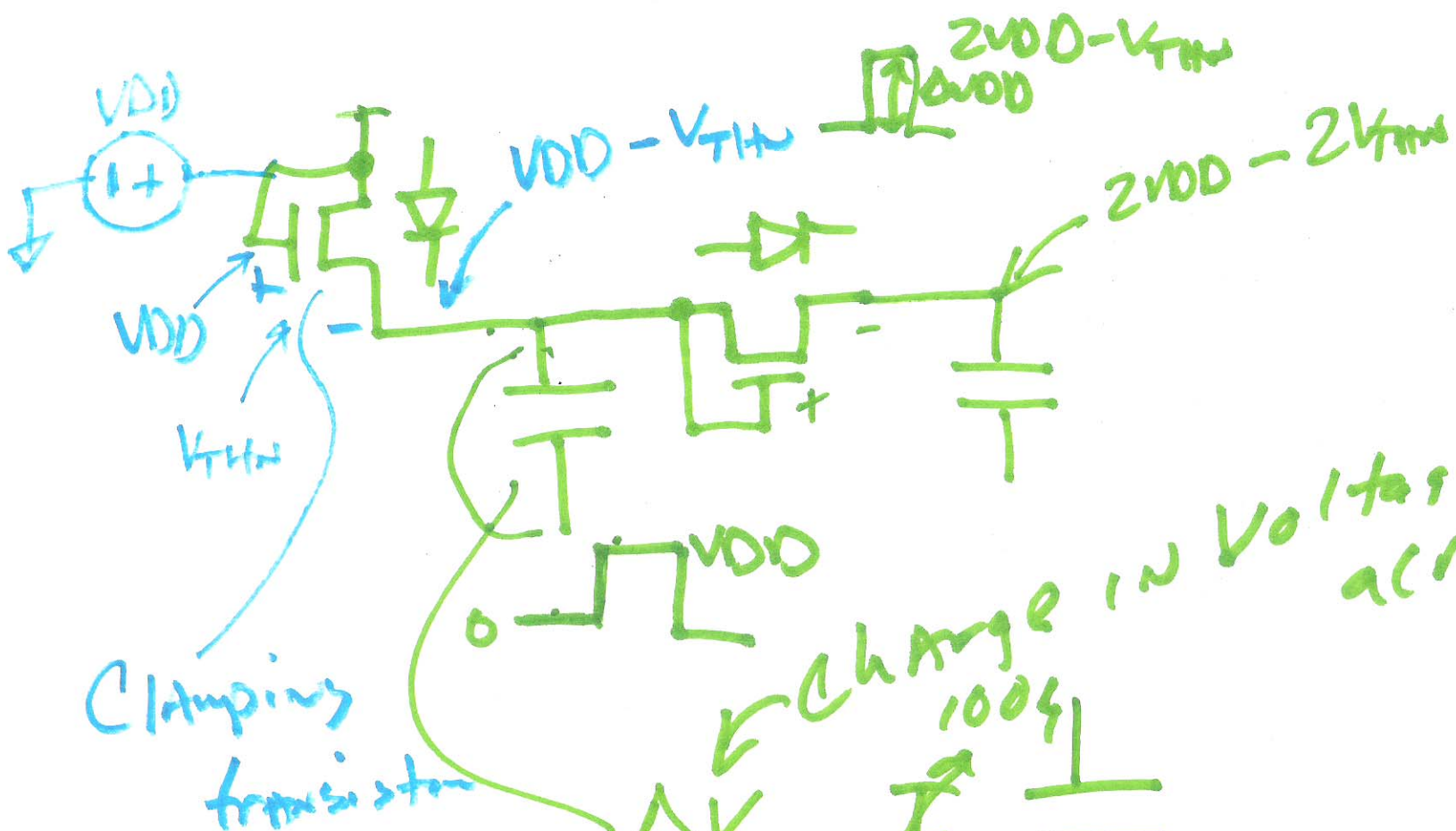

Clamping transistor

$$\frac{\Delta V}{\Delta t} = \frac{I}{C} \frac{1}{\text{period}}$$

$$I = C \frac{dV}{dt}$$

change in voltage across AP caps
e.g. 200mV

$$\frac{200\text{mV}}{10\text{ns}} = \frac{100\mu\text{A}}{C}$$

$$C = \frac{10^{-4} \cdot 10^{-8}}{0.2 \cdot 10^{-8}} \text{ S.p.F.}$$

5)