
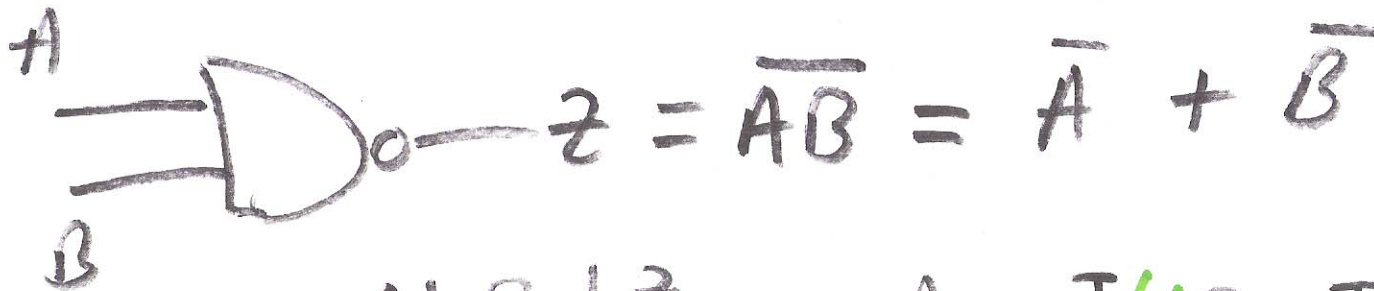



# Lecture 24

11/21/14

## Static logic gates

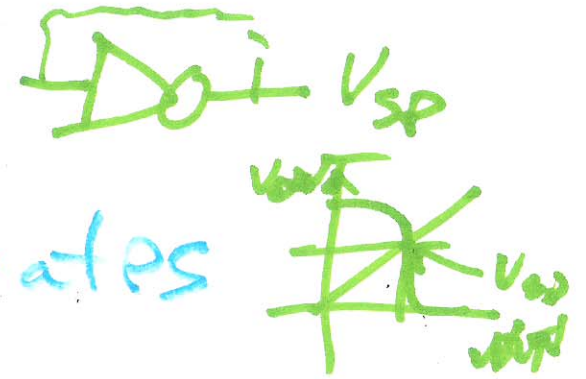

A	B	Z
0	0	1
0	1	1
1	0	1
1	1	0


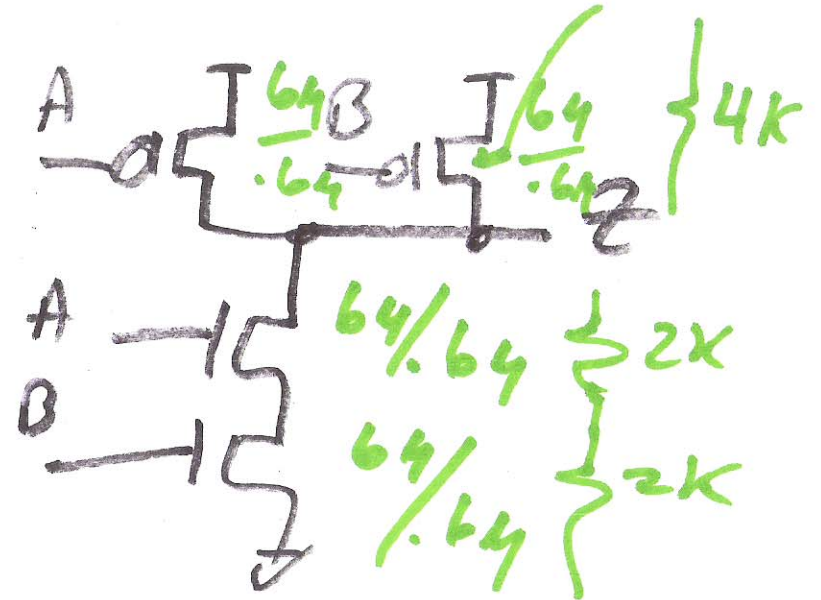


UNLV

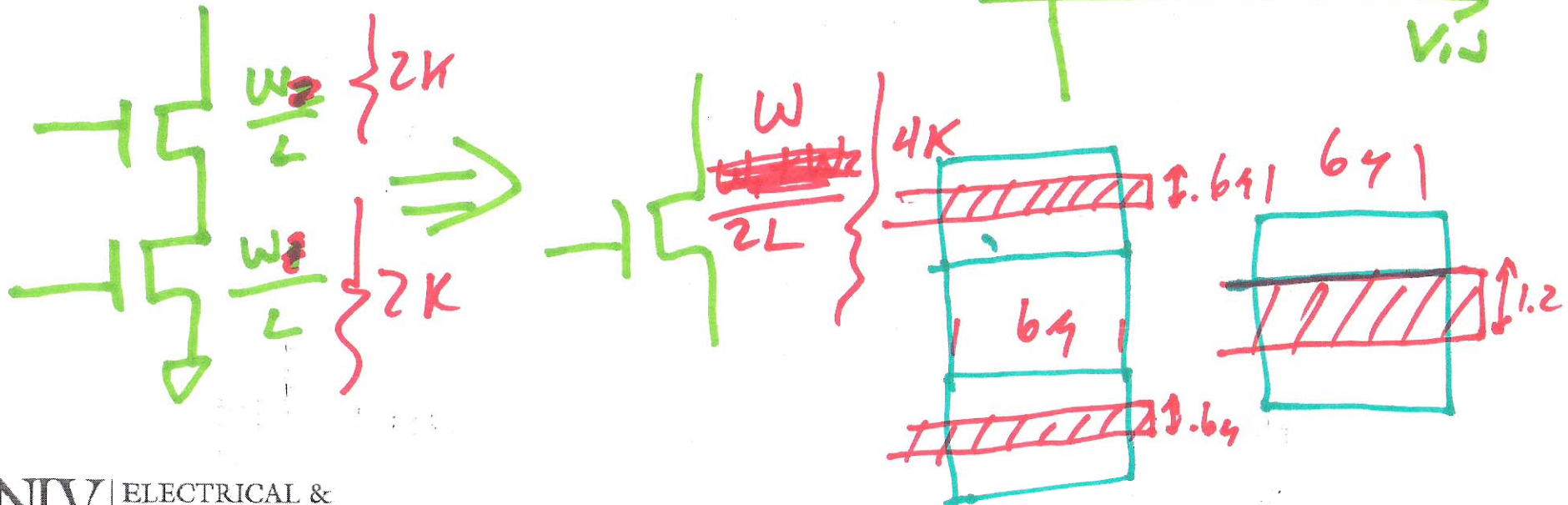
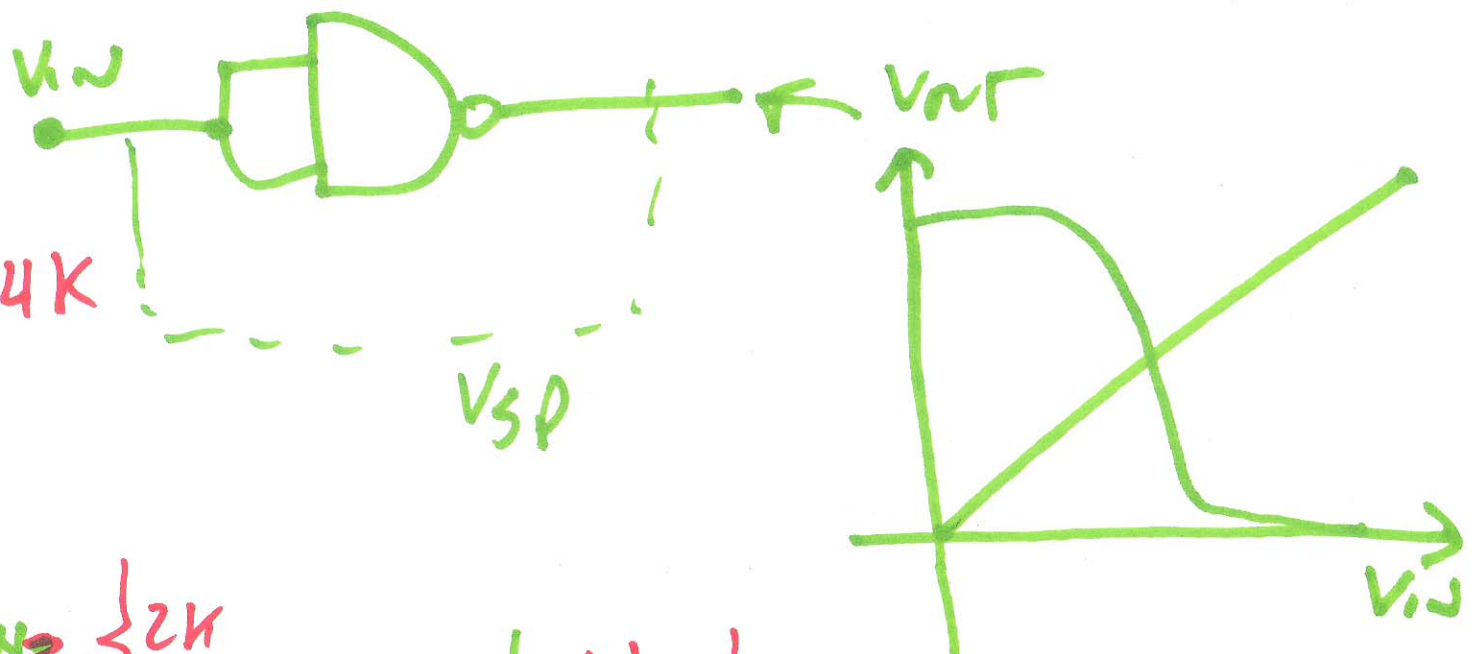
# Switching point voltage

$$\frac{L}{W_1 + W_2} \cdot \rho_1$$

$$\frac{1.2}{64} \cdot 20K \cdot \frac{1}{2} = 4K$$



2)

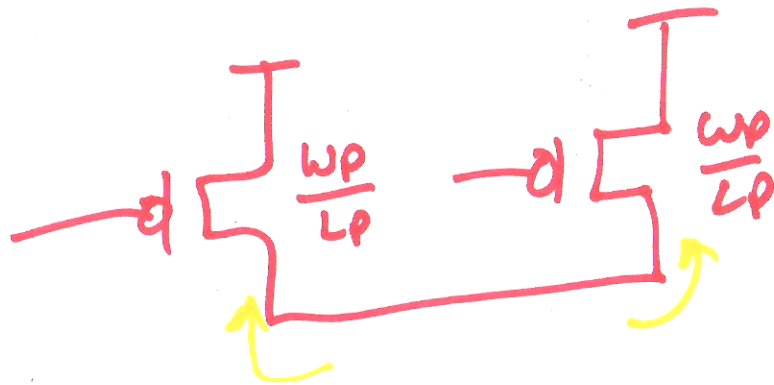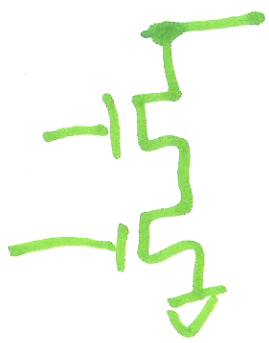


$$\beta = K_P \cdot \frac{W}{L} \cdot \frac{10}{.6}$$

$$\beta_P \cdot 2 = \beta_N$$

$$K_{Pp} = \mu_p \cdot C_{ox}$$

$$K_{Pn} = \mu_n \cdot C_{ox}$$

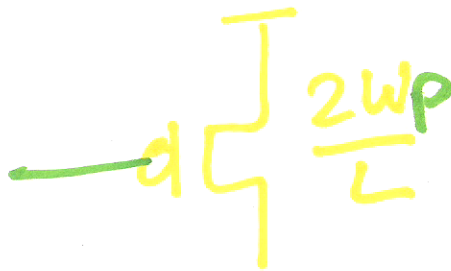

$$R_p' \cdot \frac{L}{2W} = 40k \cdot \frac{.6}{124} = 2k$$

$$K_{Pp} \cdot 2 = K_{Pn}$$

$$V_{sp} = \frac{\sqrt{\frac{\beta_N}{N^2 \cdot \beta_P}} \cdot V_{TN} + (V_{DD} - V_{THp})}{1 + \sqrt{\frac{\beta_N}{N^2 \cdot \beta_P}}}$$

$$2\beta_{P1}$$

$$\frac{\beta_N}{2}$$



$$V_{DD} - V_{so} - V_{os} = 0$$

CMOSedu.com

$$\begin{array}{l} \rightarrow \text{---} \left[ \begin{array}{l} \beta_n = K_{PN} \cdot \frac{W_n}{L_n} \\ \beta_n = K_{PN} \cdot \frac{W_n}{L_n} \end{array} \right. \\ \downarrow \end{array}$$


 $\Rightarrow$ 

$$\left[ \begin{array}{l} K_{PN} \cdot \frac{W_n}{2L_n} \end{array} \right]$$

$$\frac{\beta_n}{2}$$

$$\begin{array}{l} \rightarrow \text{---} \left[ \begin{array}{l} \uparrow \\ \uparrow \end{array} \right] \quad \uparrow N \\ K_{PP} = 2 \frac{W_p}{L_p} \end{array}$$

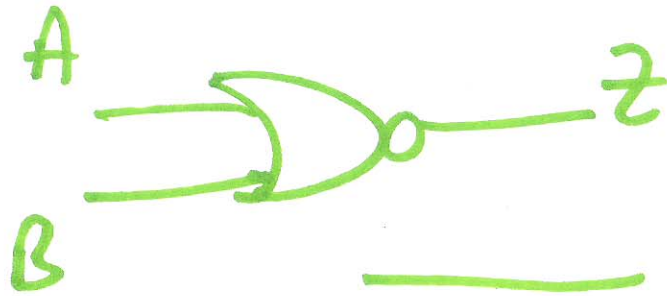
$$I_0 = \frac{\beta}{2} (V_{GS} - V_{THN})^2 \Rightarrow V_{GS} = \sqrt{\frac{2I_0}{\beta}} + V_{THN}$$




$$z = A + B$$

$$= \overline{\overline{A} \overline{B}}$$

A	B	z
0	0	<del>0</del> 1 ←
0	1	0
1	0	0
1	1	0

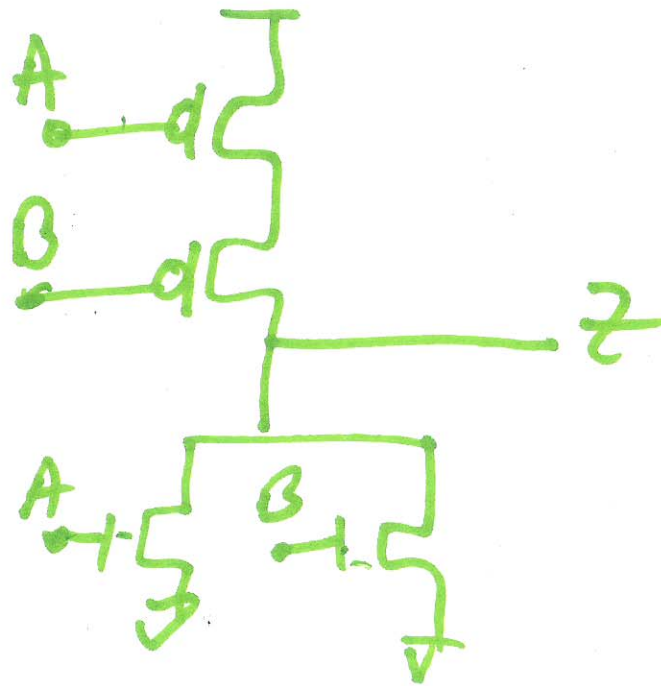




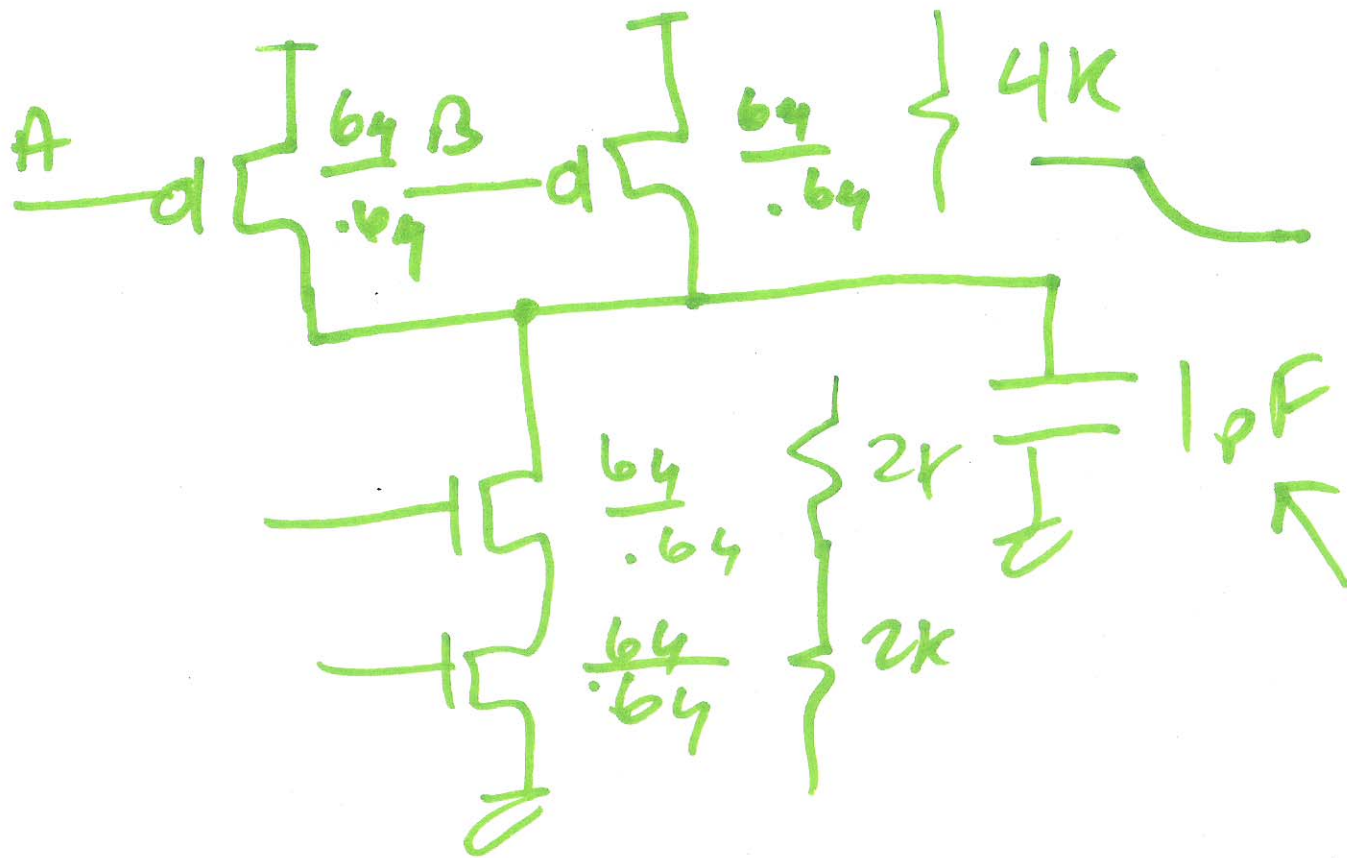


$$t_{pHL} = 0.7(4k) 1pF = \underline{\underline{2.8ns}}$$

$$t_{pLH} = 0.7(4k) 1pF = \underline{\underline{2.8ns}}$$

6)

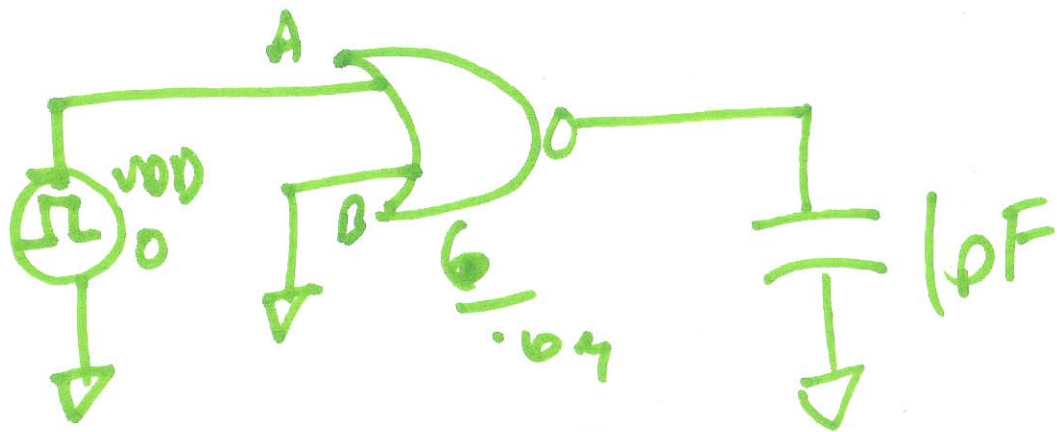


$$t_{pHL} \approx t_{pLH}$$

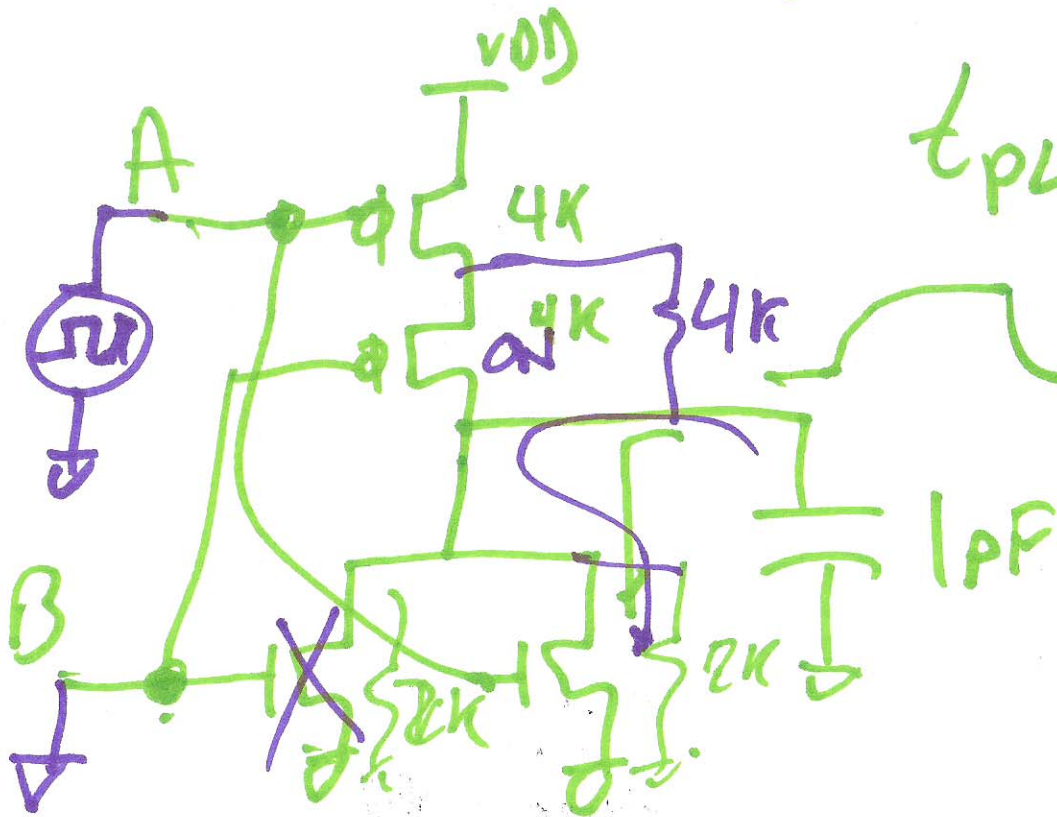

$$t_{pLH} = 0.7 \cdot 2 \cdot 4k \cdot 1pF$$

$$t_{pHL} = 0.7 \cdot 2k \cdot 1pF$$

7)

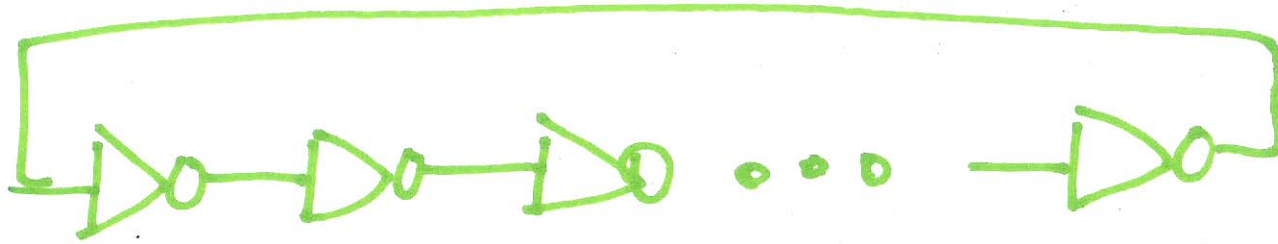

N-Stage Ring Oscillator

$$NMOS \rightarrow \frac{124}{.64} \quad PMOS \rightarrow \frac{214}{.64}$$

If  $N = 51$  what is  $f_{osc}$ ?

What is the delay of an inverter?

$t_{PHL}$     $t_{PLH}$



