
 


**Figure 15.1** Defect density effects on yield.


22.23

 


**Figure 15.2** Floor plan for an adder.



**Figure 15.3** Standard cell layout of an inverter.

 

Figures from CMOS Circuit Design, Layout, and Simulation, Copyright Wiley-IEEE, CMOSedu.com

 

**Figure 15.4** Connection of two inverter standard cells to a bus.

 
 


Figure 15.5 (a) Double inverter; (b) two-input NAND; (c) two-input NOR and transmission gate.

 
 


Figure 15.6 SR latch using NAND gates.



 
 



Figure 15.7 Section of the layout shown in Fig. 15.6.

 


**Figure 15.8** SR latch using NOR gates.

 

(a)

 


(b)

 

(c)

Figure 16.9 Connection of power and ground to standard cells.

 

**Figure 15.10** Decoupling capacitor.



 
 


Figure 15.11 Busing structure used to decrease signal coupling.

 

 

**Figure 15.12** Schematic and layout of a latch.


 


Figure 15.13 Layout of an AOI static adder.

 

**Figure 15.14** Layout of the complete adder.

