

NOVEMBER 2, 2015

Lecture 19

~~EE~~ 721

memory

circuit

Design

19.4 System  
Considerations

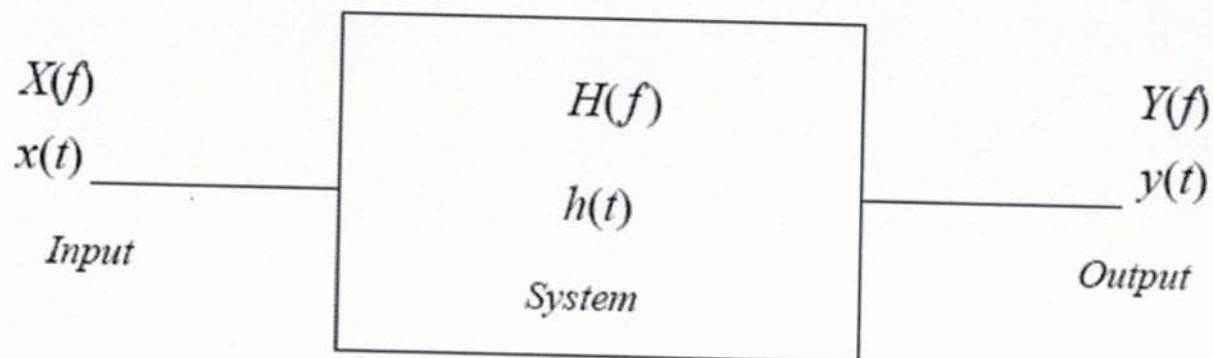


Figure 19.40 Representation of a system with input and output.

distortionless transmission

$$y(t) = x(t - t_d) \cdot K$$



↑  
output  
spectrum

↑  
delay through system  
 $-t_d \cdot 2\pi f$


$$Y(f) = K \cdot X(f) \cdot e$$



$$\left\{ \begin{aligned} Y(f) &= \\ -2\pi f \cdot t_d \end{aligned} \right.$$

$$|Y(f)| = K \cdot |X(f)|$$

  

**Figure 19.41** Magnitude and phase response of a distortionless system.

 

 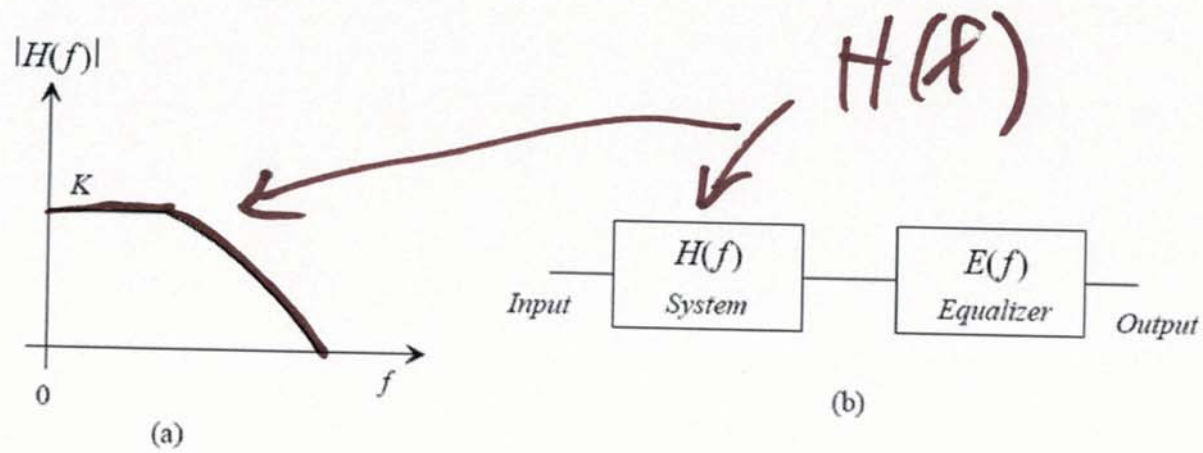

**Figure 19.42** Using an equalizer to lower distortion in a system.






 
 


Figure 19.43 Bi-phase data encoding.

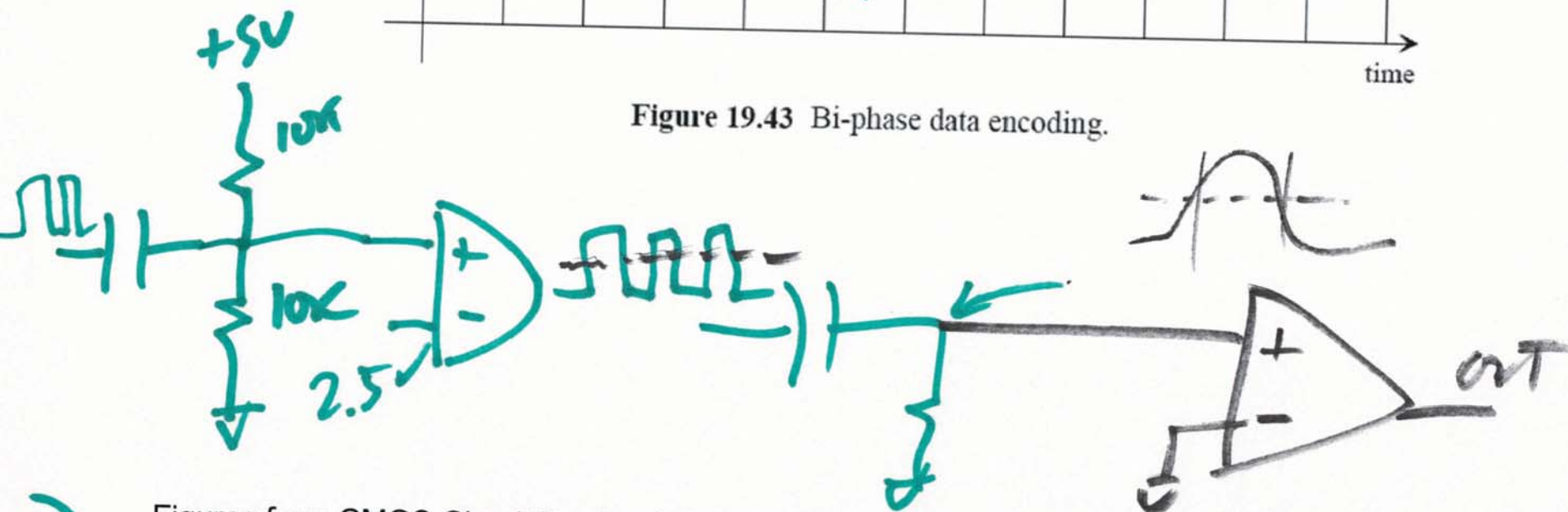



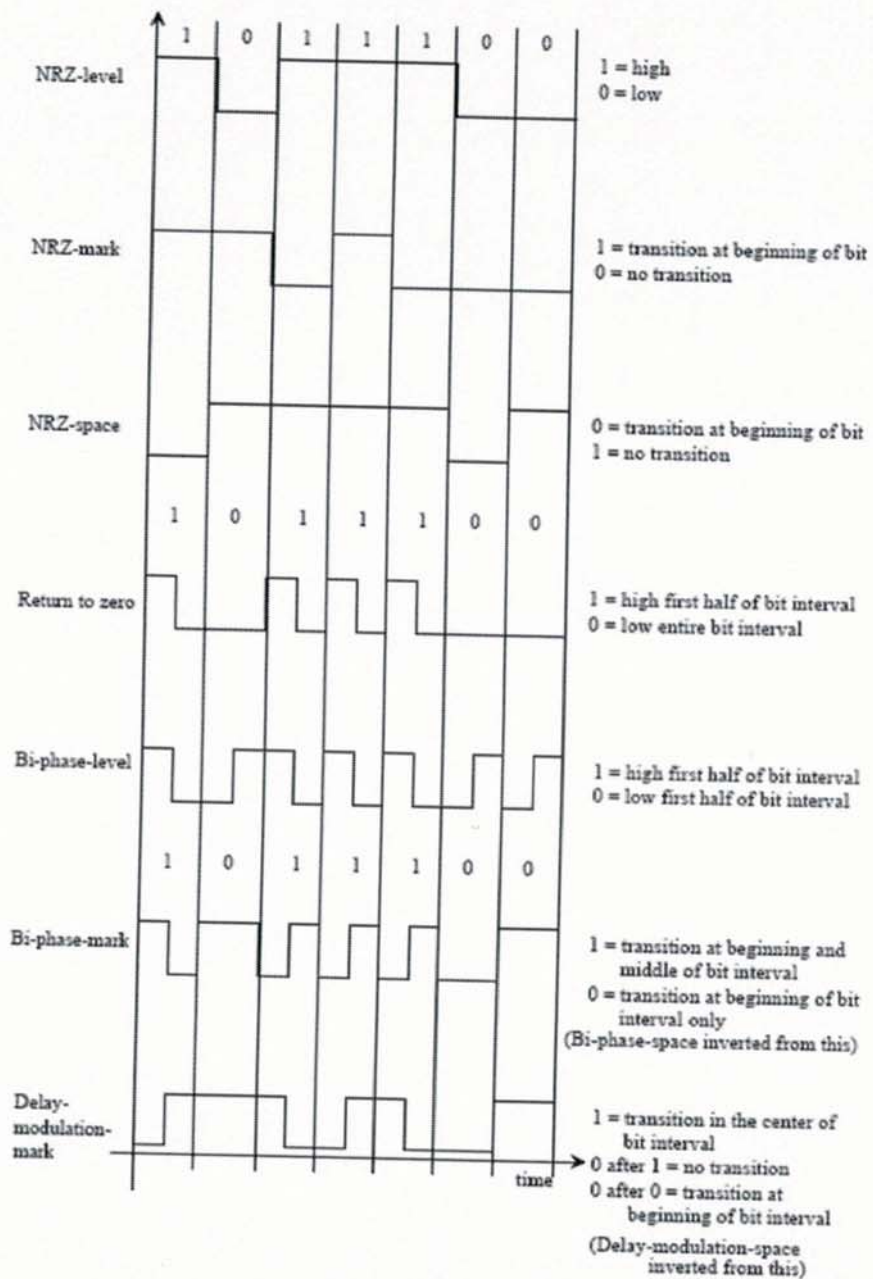


Figure 19.44 Data transmission formats.

 

**Figure 19.45** The problems of using clock without the divide by 2 to lock on data.

 

**Figure 19.46** Problems trying to lock on a data stream that is one-half the dclock frequency.





 


Figure 19.47 Detecting the edges in NRZ data.

Using an edge detector.

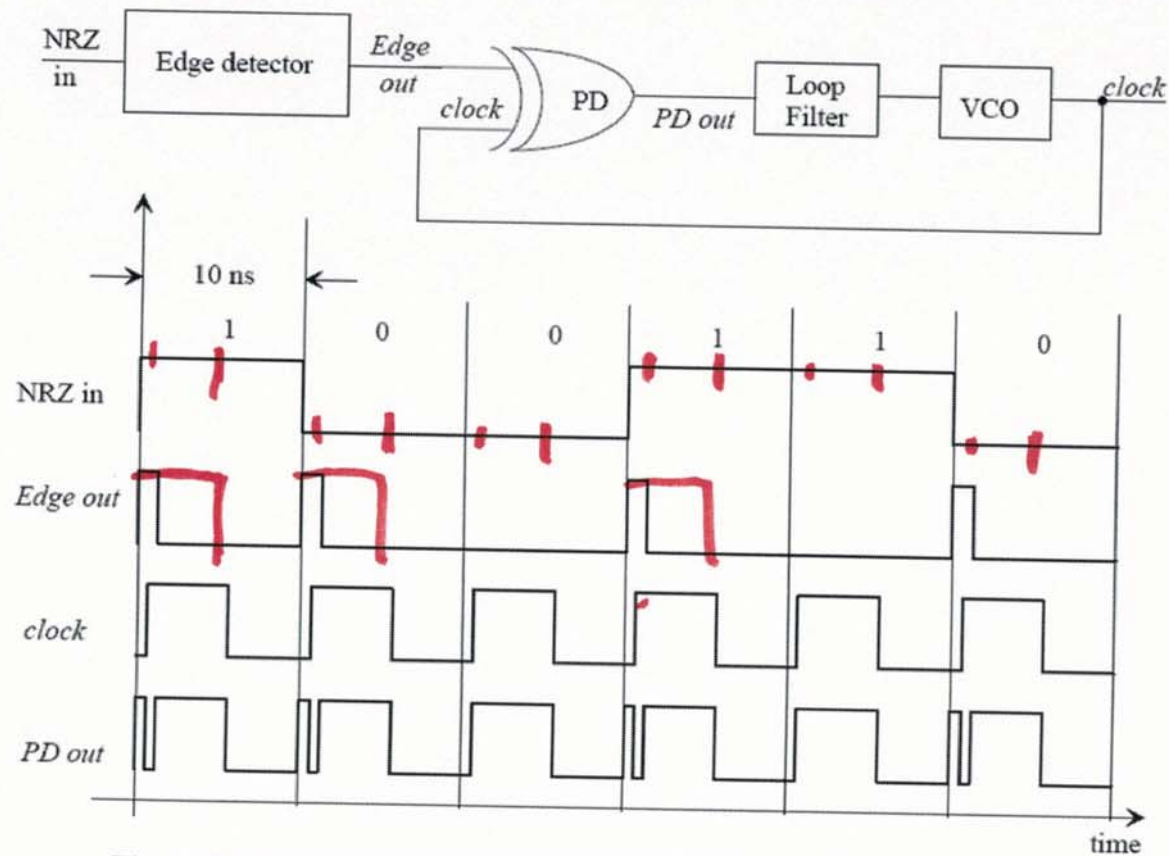

**Figure 19.48** Clock-recovery circuit for NRZ using an edge detector. Note that the DPLL is in lock, when the rising edge of clock is centered on the edge output pulse.

 

self-correcting  
COR

 


Figure 19.49 The PD (Hogge) portion of a self-correcting, clock-recovery circuit in lock.


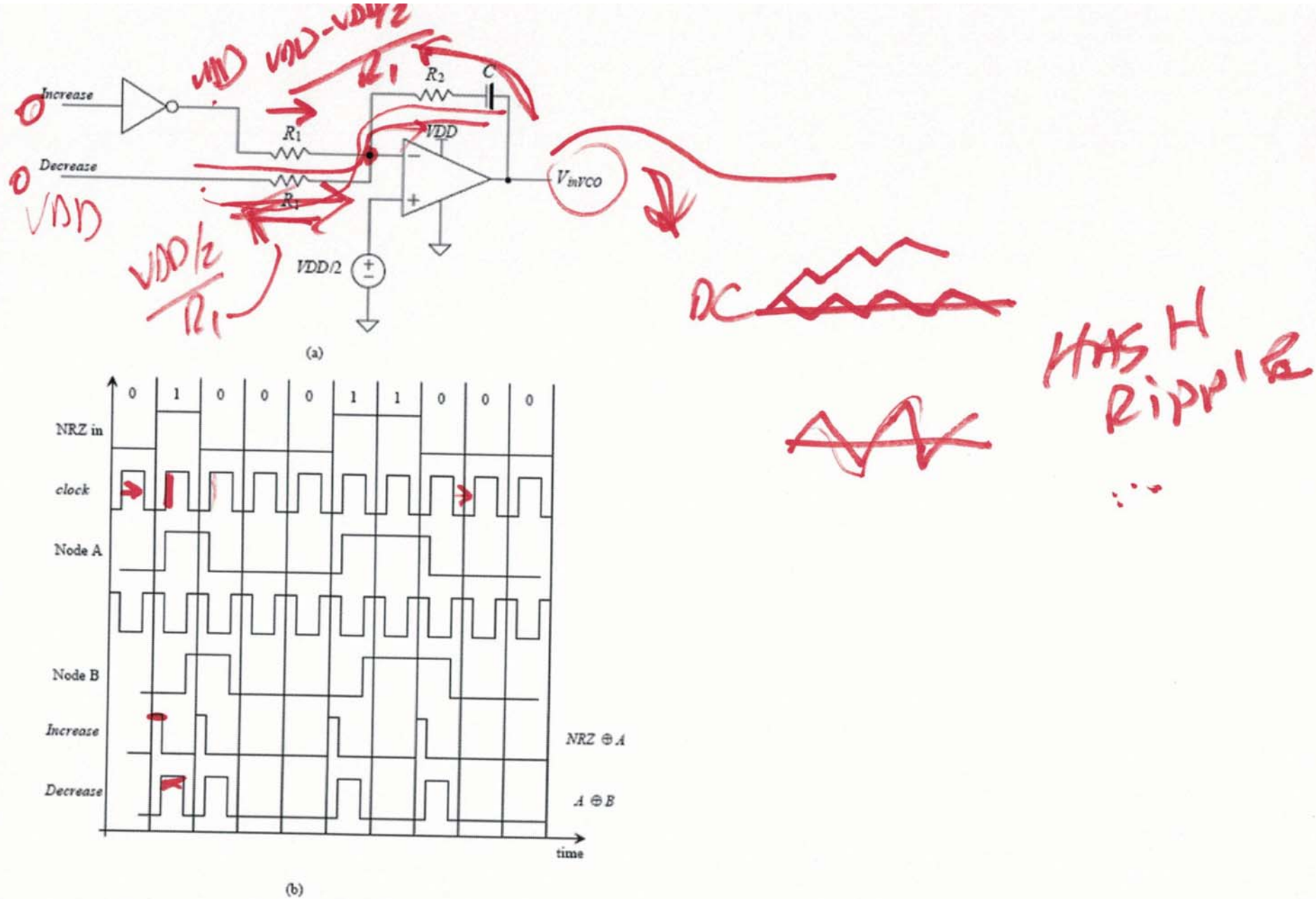



Figure 19.50 (a) Possible loop filter used in a self-correcting (Hogge) DPLL and (b) waveforms when the loop is not in lock and the clock leads the center of the data.

 



**Figure 19.51** (a) Idealized view of clock and data without jitter and (b) with jitter.



 

**Figure 19.52** Self-correcting PD with charge pump output.