
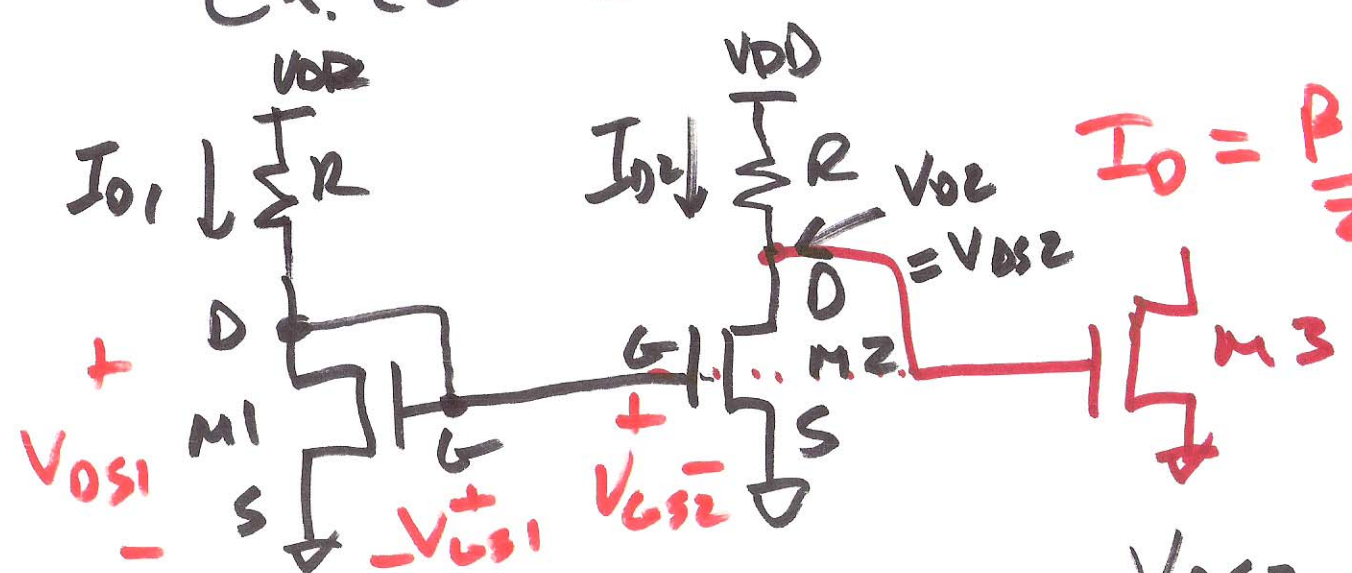


# CH. 20 CURRENT MIRRORS


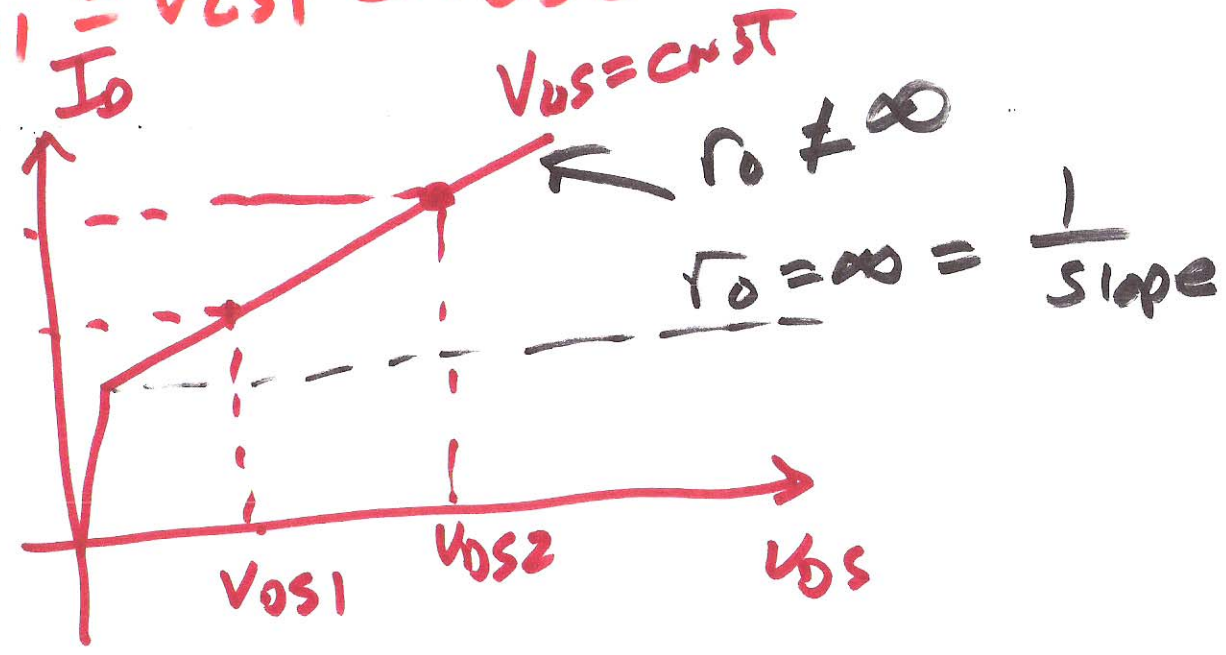


$$I_D = \frac{\beta_n}{2} (V_{GS} - V_{THN})^2$$

$$V_{GS1} = V_{GS2} = V_{GS3} = V_{GS2}$$



17

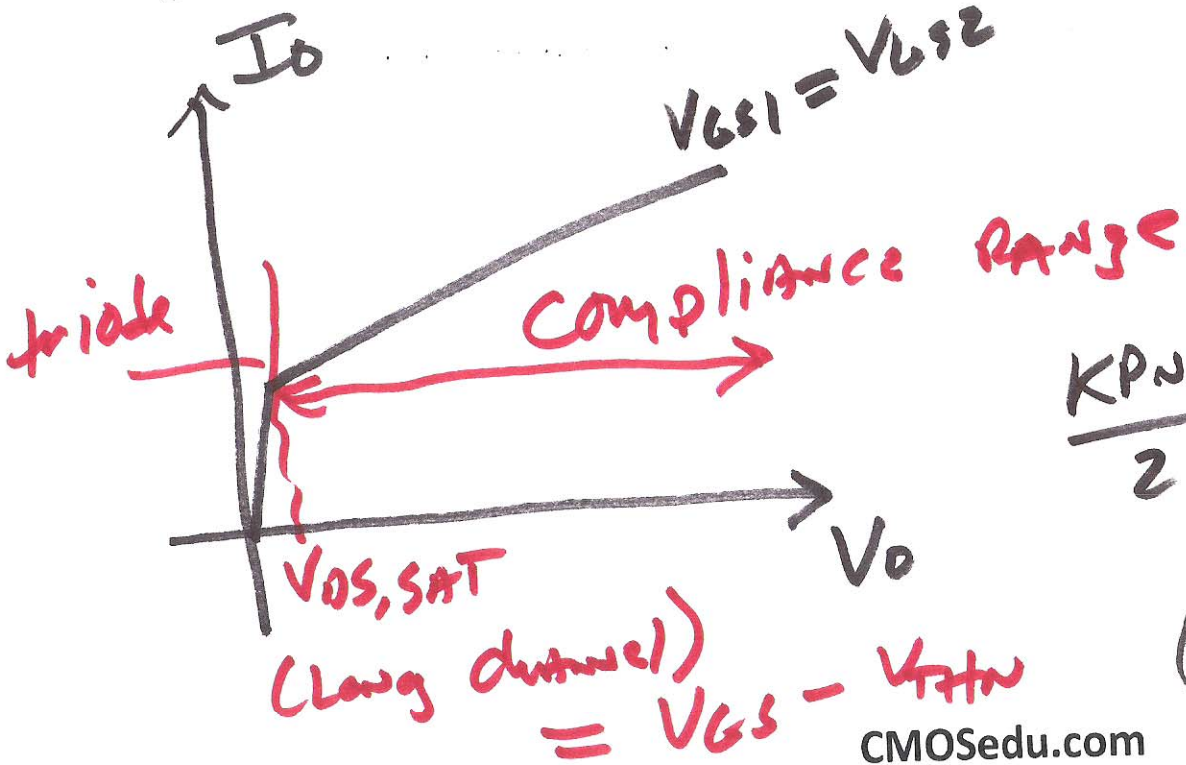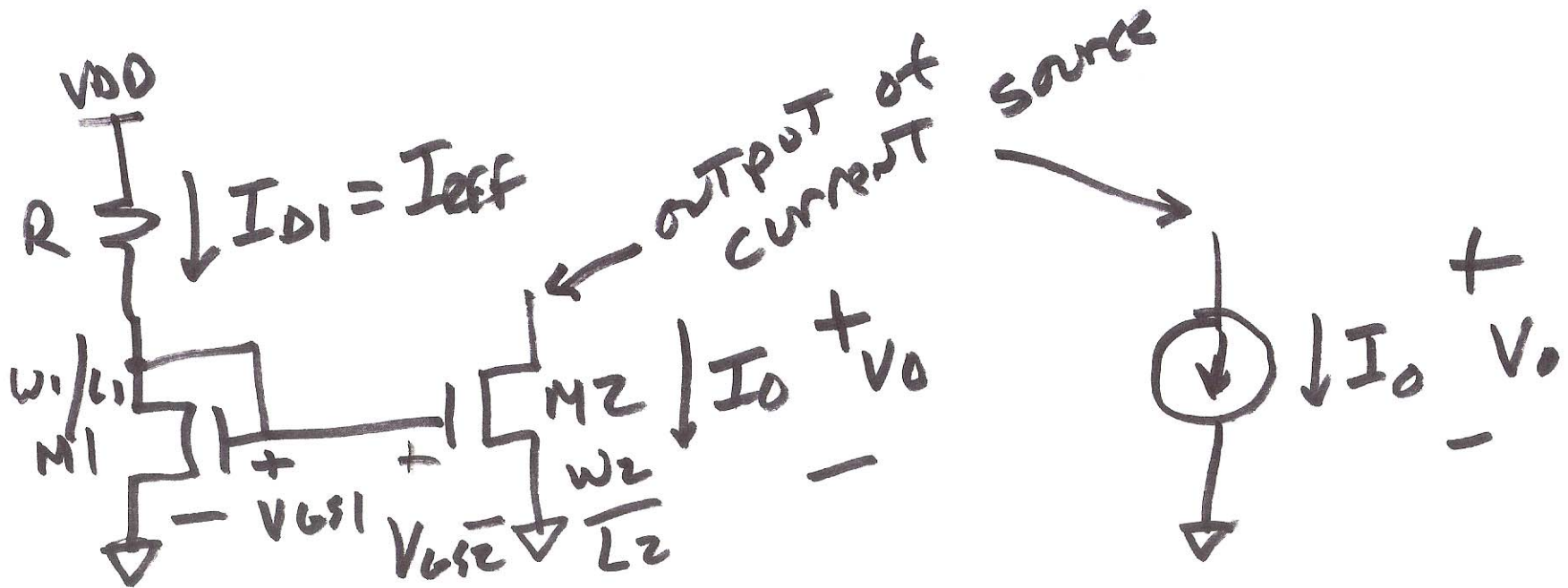

source

$I_{REF} =$

$I_{D1} =$

$$\frac{K_{PN}}{2} \cdot \frac{W_1}{L_1} (V_{GS} - V_{THN})^2 \cdot (1 + \lambda(V_{DS} - V_{DS,SAT}))$$

2)

$$I_{O2} \rightarrow \frac{I_O}{I_{REF}} = \frac{\frac{K_{PN}}{2} \frac{W_2}{L_2} (V_{GS1} - V_{THN})^2 \cdot (1 + \lambda (V_O - V_{DS1, SAT}))}{\frac{K_{PN}}{2} \frac{W_1}{L_1} (V_{GS1} - V_{THN})^2 \cdot (1 + \lambda (V_{GS1} - V_{DS1, SAT}))}$$

$I_{O1}$  ↗



Generally you set  $L_1 = L_2$

$$\frac{I_O}{I_{REF}} = \frac{W_2}{W_1} \cdot \frac{1 + \lambda (V_O - V_{DS1, SAT})}{1 + \lambda (V_{GS1} - V_{DS1, SAT})}$$

Approximate

$$\frac{I_O}{I_{REF}} \approx \frac{W_2}{W_1}$$


operating in saturation

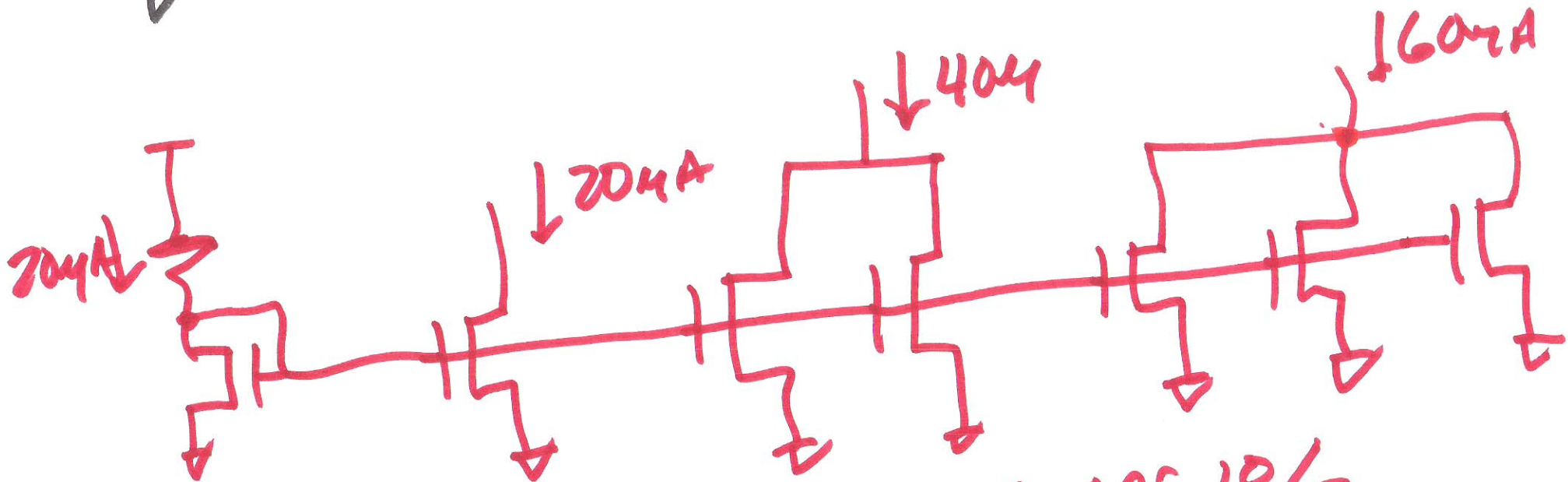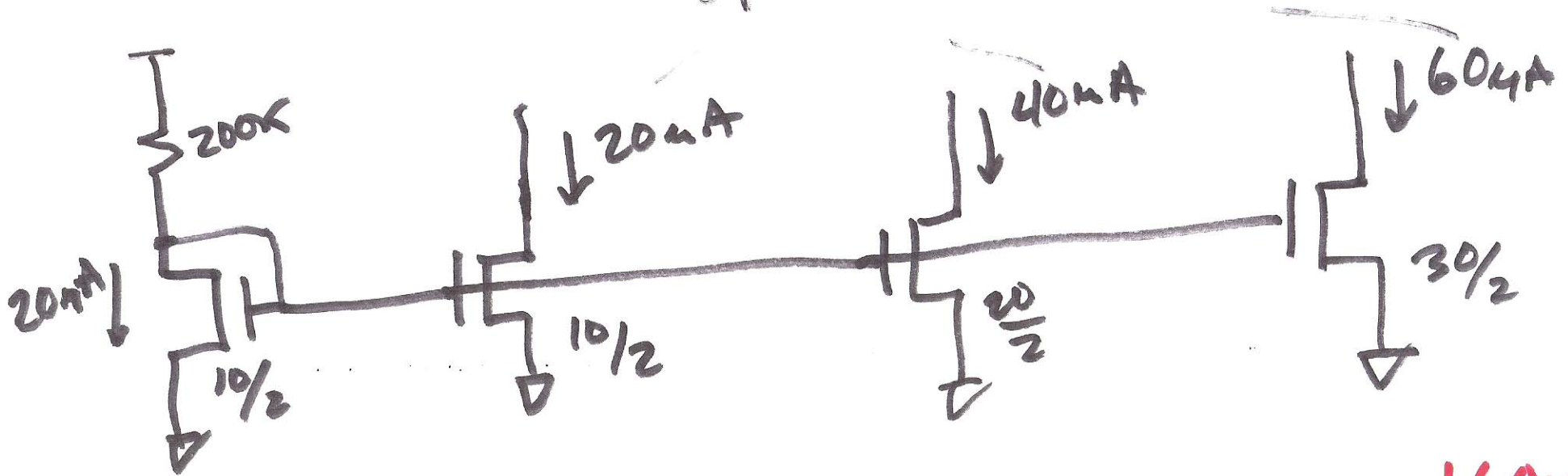

All MOS ARE 10/2

$M = \# \text{ devices in parallel}$

EX. 20.1

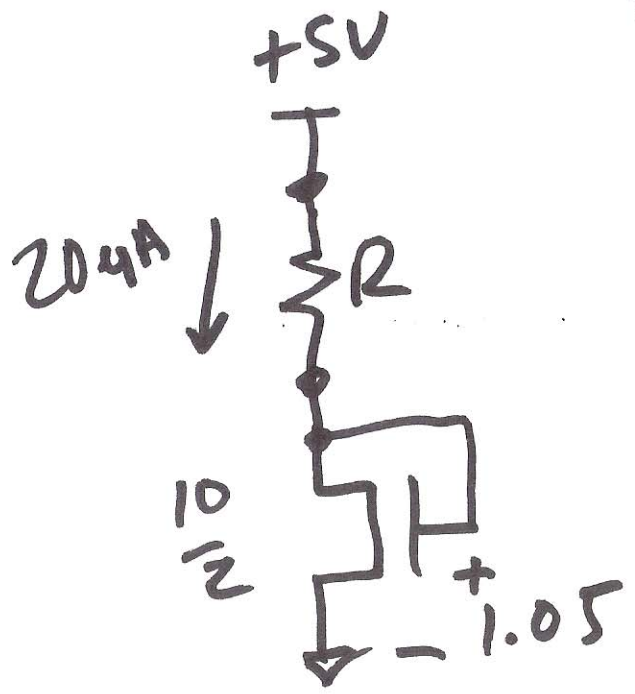

$$204\mu\text{A} = \frac{5 - 1.05}{R}$$

$$R = 200\text{k}$$

5)




# MATCHING

perfect

matching

then

$$I_{O1} = I_{O2}$$

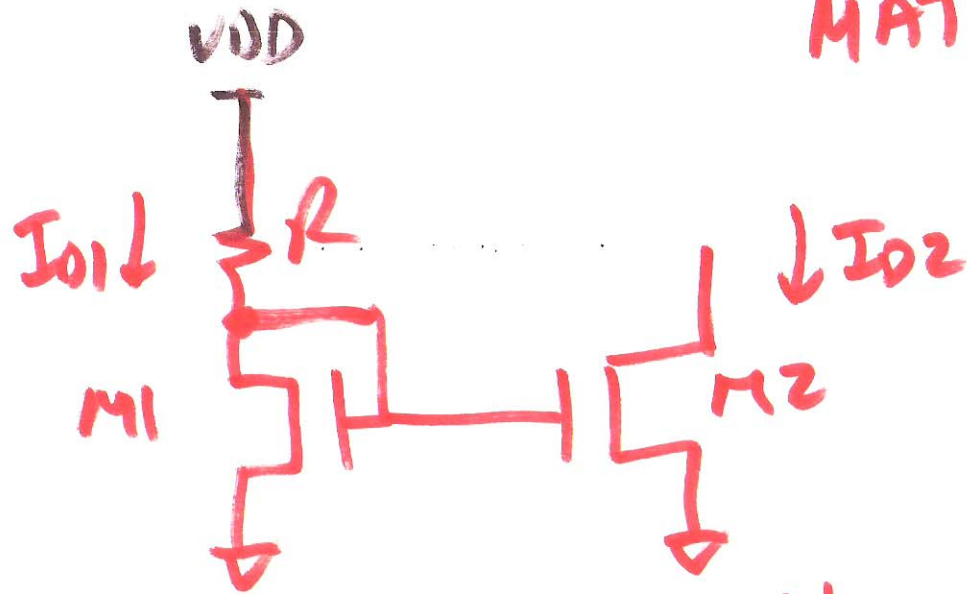

Threshold voltage matching

$$V_{THN1} \neq V_{THN2}$$

$$V_{THN1} = V_{THN} - \frac{\Delta V_{THN}}{2}$$

$$V_{THN2} = V_{THN} + \frac{\Delta V_{THN}}{2}$$

$$\frac{\Delta I_{DQ}}{\Delta V_{THN}}$$

$$\frac{I_0}{I_{REF}} = \frac{\frac{K_{PN}}{2} \frac{W}{L} (V_{GS} - V_{THN} - \frac{\Delta V_{THN}}{2})^2}{\frac{K_{PN}}{2} \frac{W}{L} (V_{GS} - V_{THN} + \frac{\Delta V_{THN}}{2})^2}$$

$$= \frac{\left(1 - \frac{\Delta V_{THN}}{2(V_{GS} - V_{THN})}\right)^2}{\left(1 + \frac{\Delta V_{THN}}{2(V_{GS} - V_{THN})}\right)^2}$$

$$\frac{I_0}{I_{REF}} \approx 1 - \frac{2\Delta V_{THN}}{V_{GS} - V_{THN}} = 1 - \frac{2\Delta V_{THN}}{V_{DS,SAT}}$$


reduce the effects of threshold voltage mismatch use large,

CMOSedu.com

$V_{GS} \gg V_{DS,SAT}!$

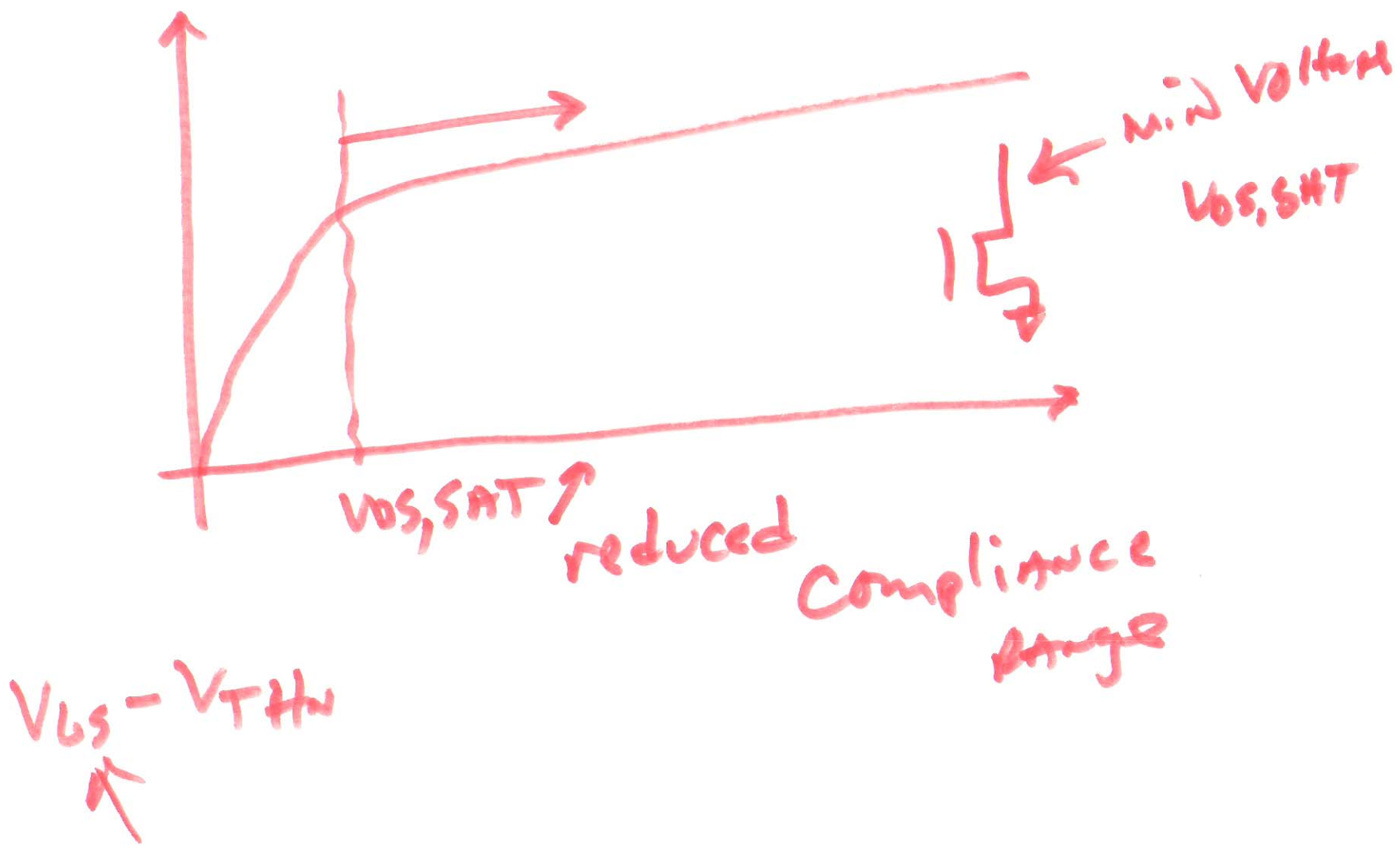1)

$f_T \uparrow$  with  $V_{DS} \uparrow$  &  $V_{DS,SAT} \uparrow$



8)




for  $C_{ox}$  or  $\mu$  mismatch  
 i.e.  $KP$

$$\frac{I_0}{I_{REF}} \approx 1 + \frac{\Delta KP_n}{KP_n}$$

depends  
 process

MOST important for good matching  
 $V_{OS}$
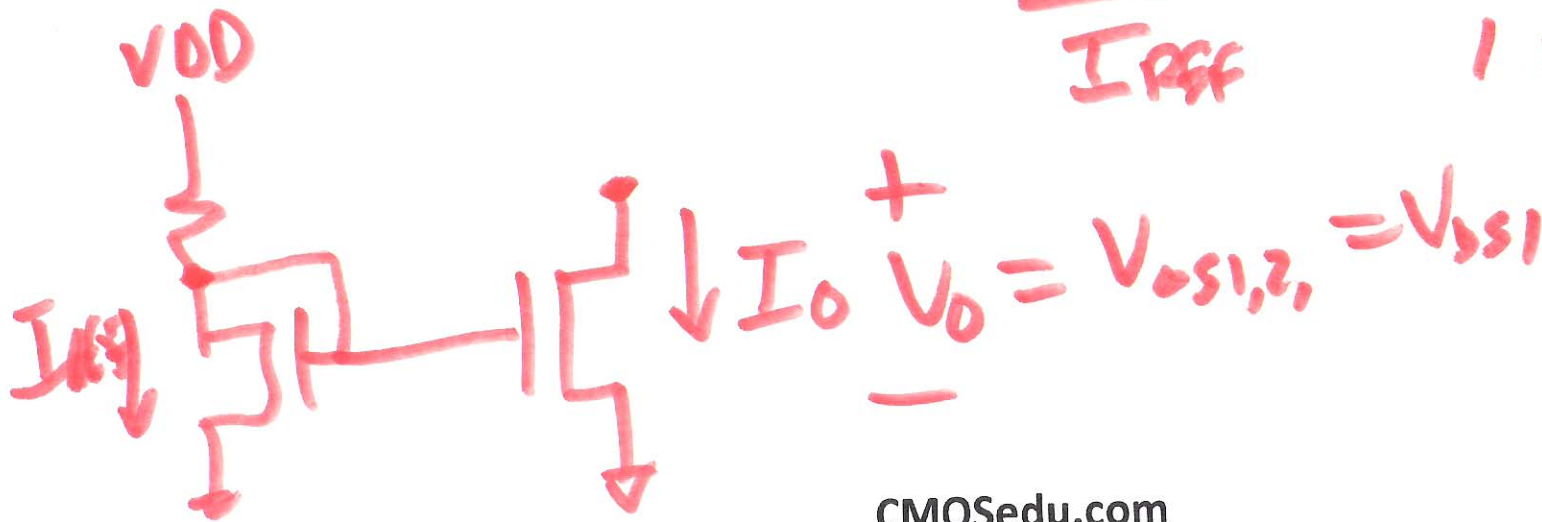
$$\frac{I_0}{I_{REF}} \approx \frac{1 + \lambda_2 \cdot V_0}{1 + \lambda_1 \cdot V_{DS1}}$$



45:28

a)