
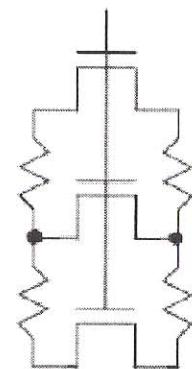


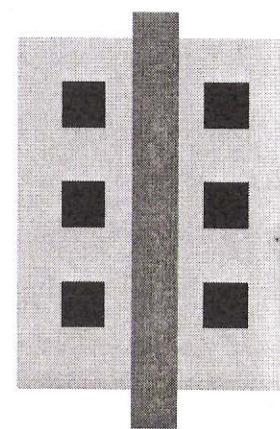

(a)



(b)



(c)

Figure 20.5 (a) Large device with a single contact and (b) its equivalent circuit.
(c) Adding more contacts to reduce parasitic resistance.

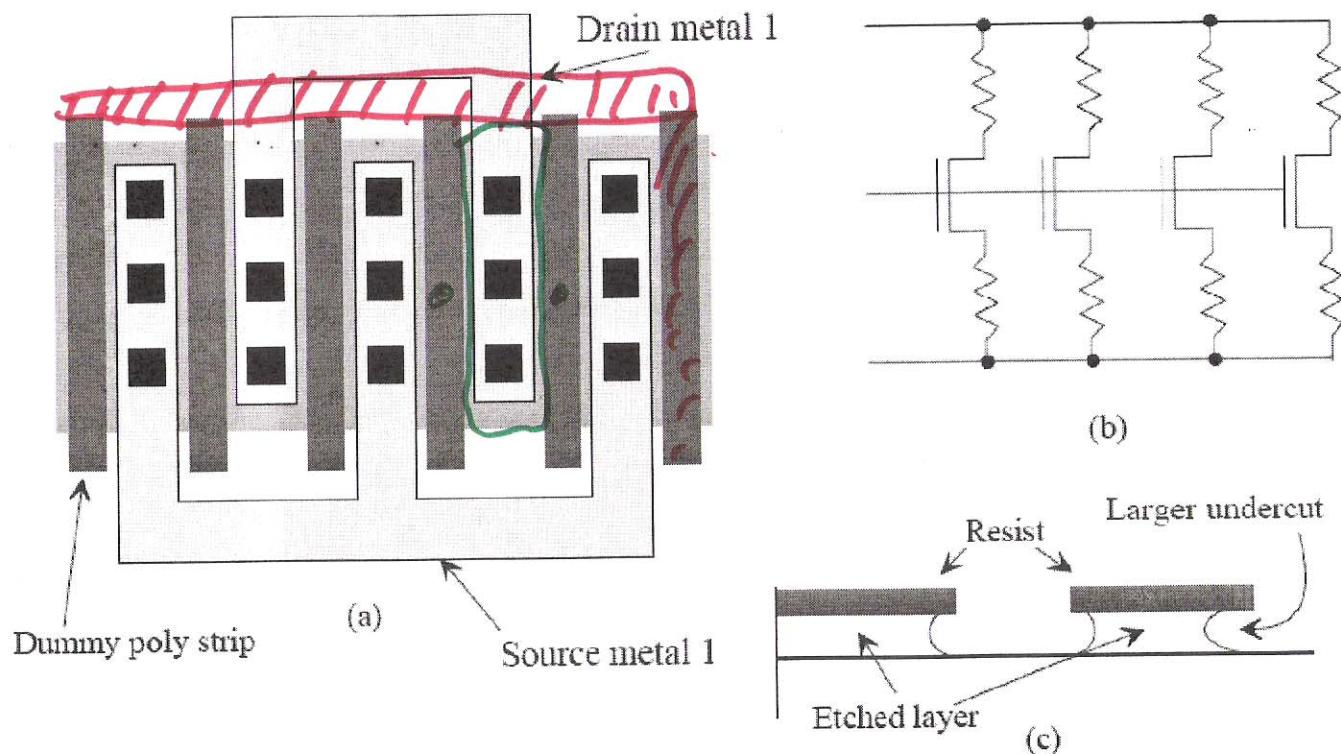


Figure 20.6 (a) A parallel device with dummy strips, (b) the equivalent circuit, and (c) undercutting.




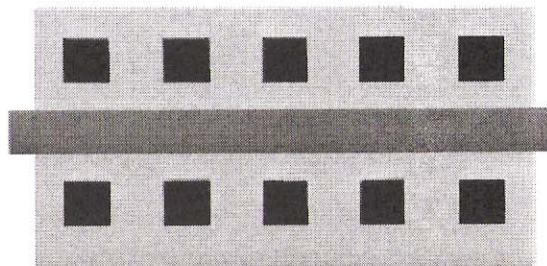
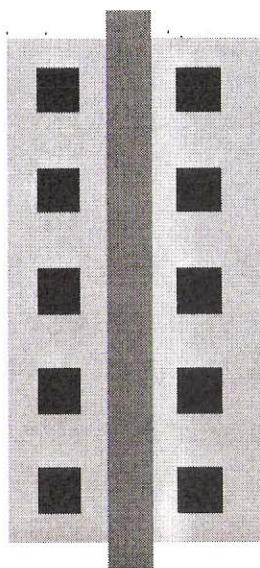
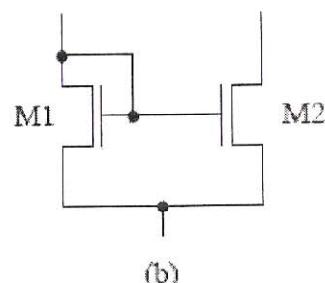


Figure 20.7 Devices with differing orientation (bad).

want, for good matching, devices
to have same orientation.
you also want devices
to be close

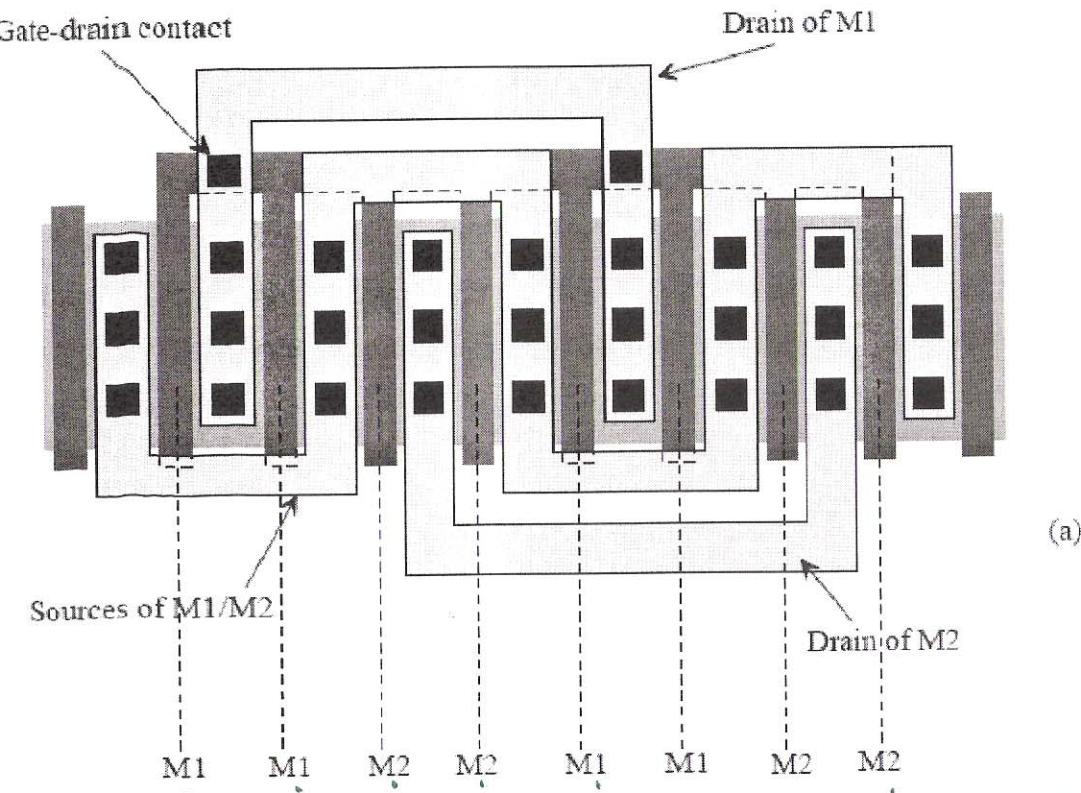

Ch. 5
Common -Centroid
Layout

Figure 20.8 (a) Layout of a simple current mirror using interdigititation and (b) equivalent circuit.

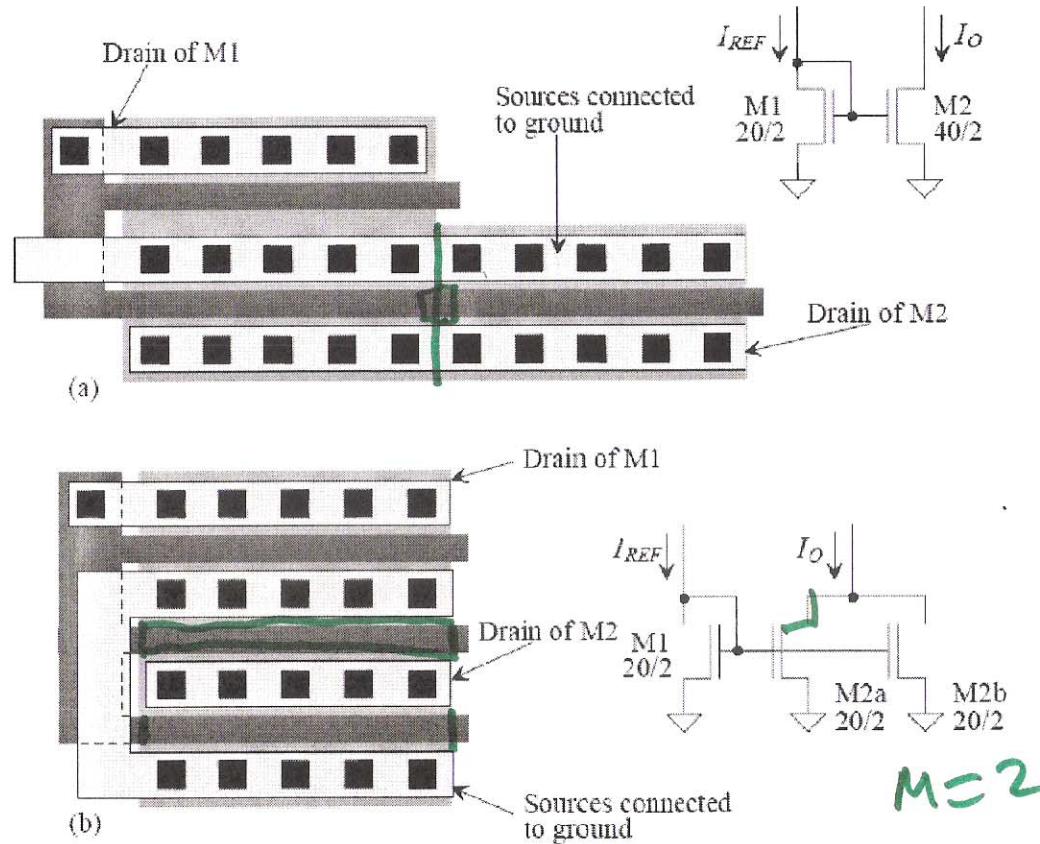


Figure 20.9 Layout of a current mirror (a) without width correction and (b) with width correction.




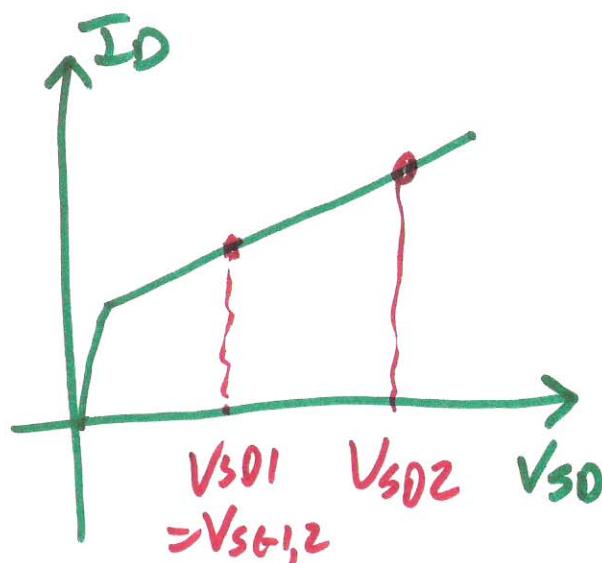
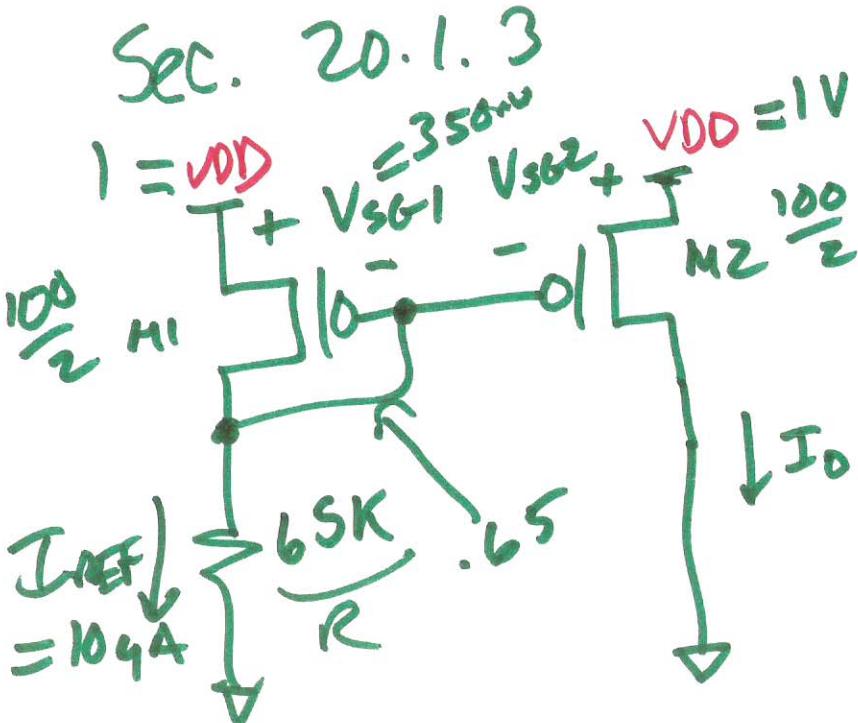


TABLE 9.2
SCALE = 50m
 $S4/100\text{nm}$

$$\frac{1 - .35}{65K} = 104A$$

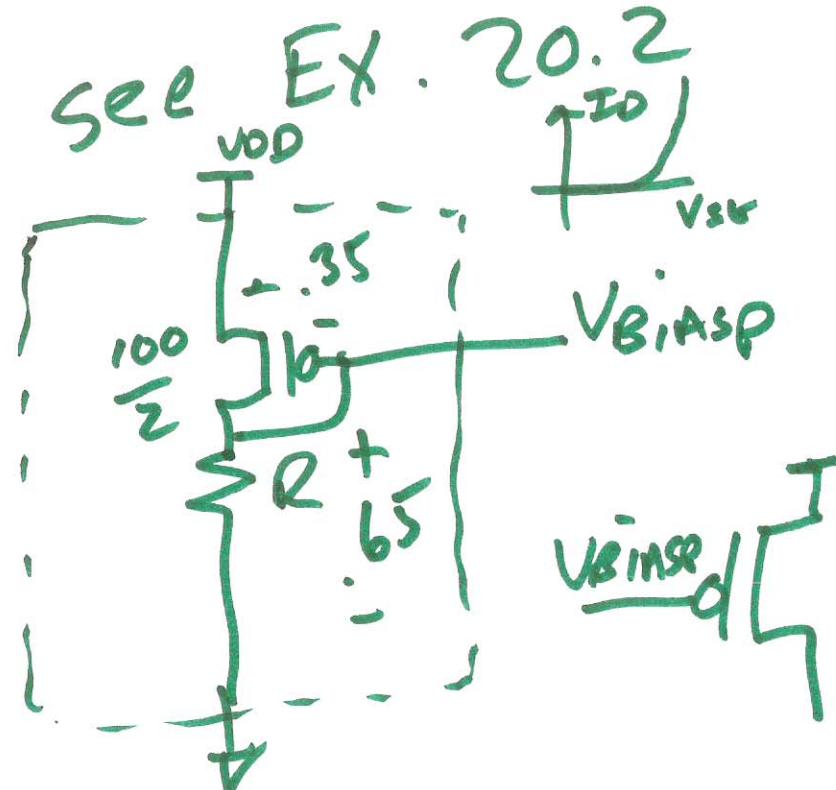

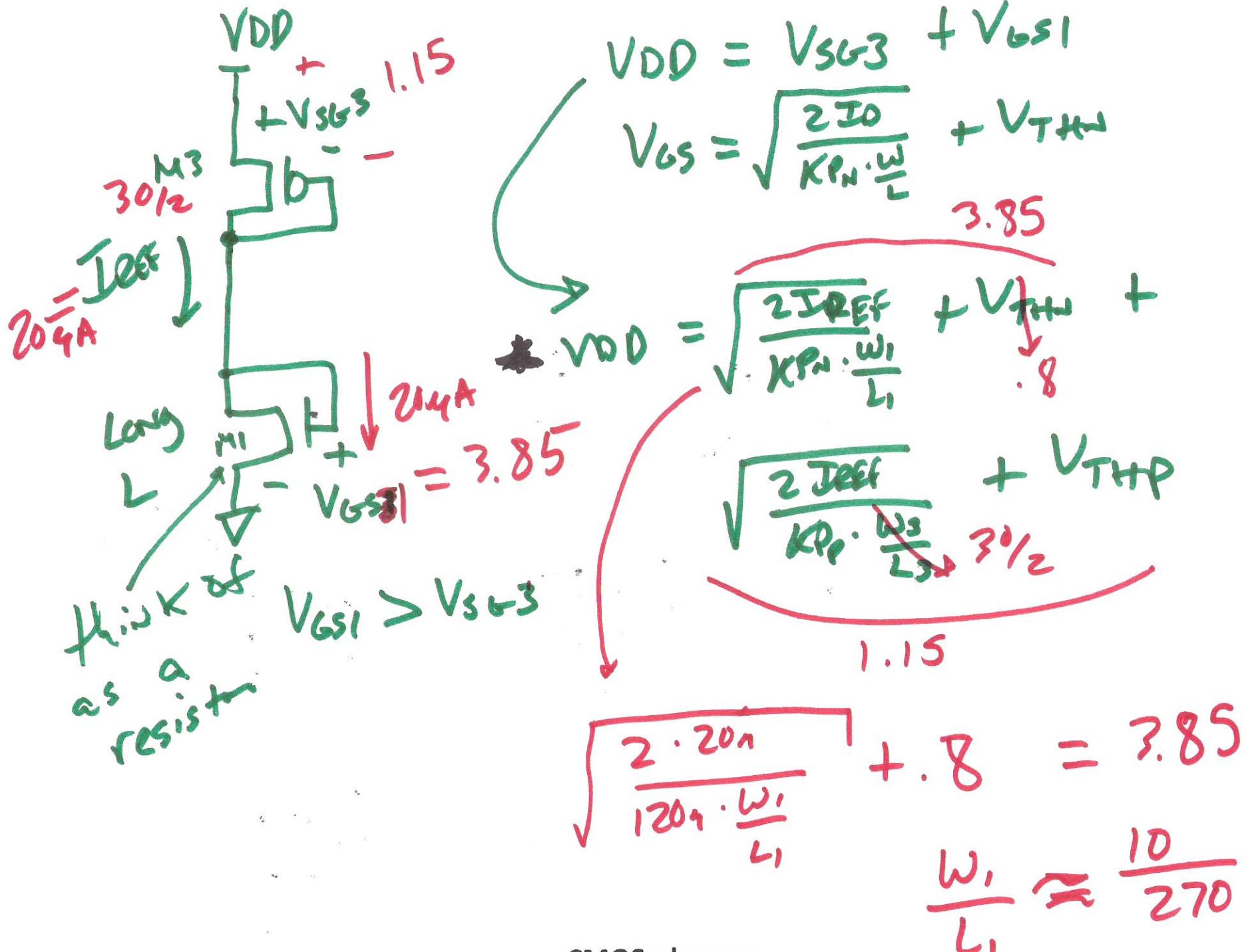

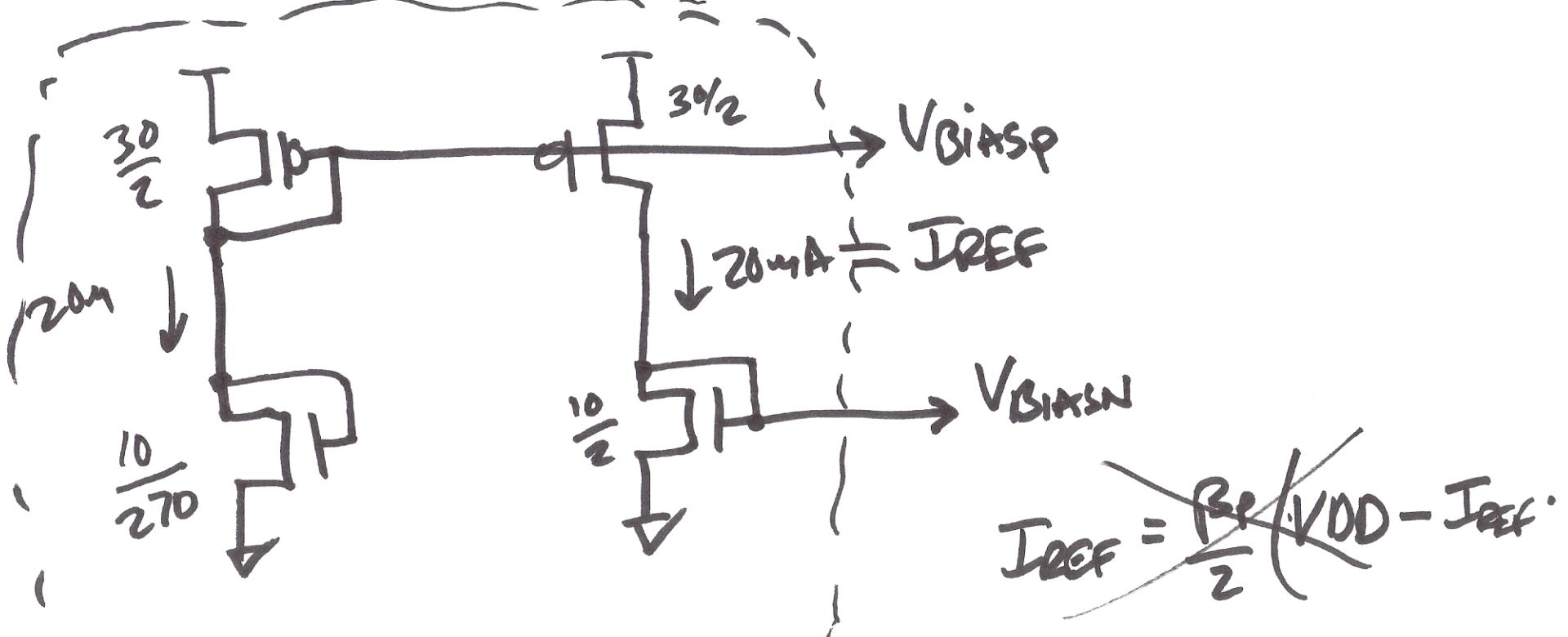


How sensitive is I_{2EF}

to changes in VOD?

to changes in VDD!


$$\frac{\delta I_{REF}}{\delta VDD} = \frac{\delta +}{VDD} = \frac{2VDD}{K} - \frac{2(V_{THn} + V_{THp})}{K}$$
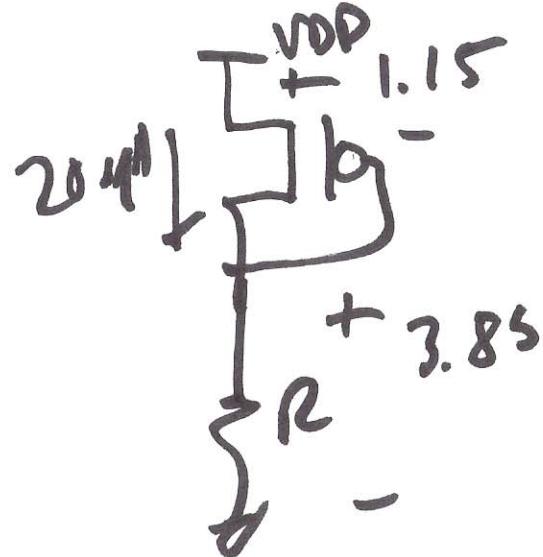
$$\frac{\delta I_{REF}}{\delta VDD} = \frac{12NA}{\mu V}$$



long channel

$$R = \frac{3.85}{204} \approx 192K$$

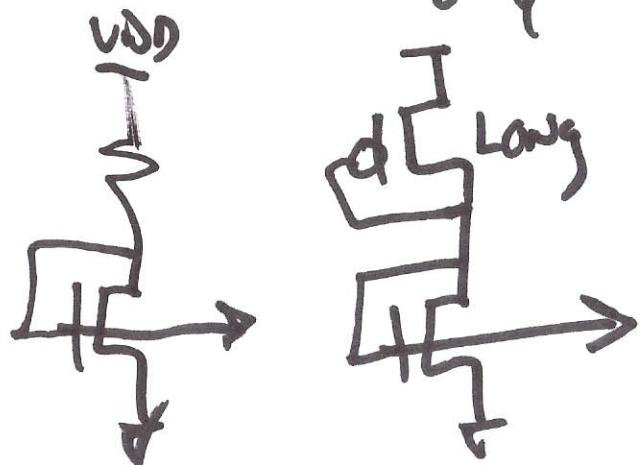

$$I_{REF} = \frac{V_{DD} - V_{BE(VRR)/V_{SG}}}{R}$$

~~$$I_{REF} = \frac{V_{DD}}{R}$$~~

~~$$I_{REF} = \frac{V_{DD}}{2R}$$~~


$$I_{REF} \approx \frac{V_{DD}}{R}$$

$$\frac{\delta I_{REF}}{\delta V_{DD}} = \frac{1}{R}$$

$$5 \text{ nA}/\text{mV}$$

Beta - Multiplier, self-biased reference

Start - SP
CKT Not Shown

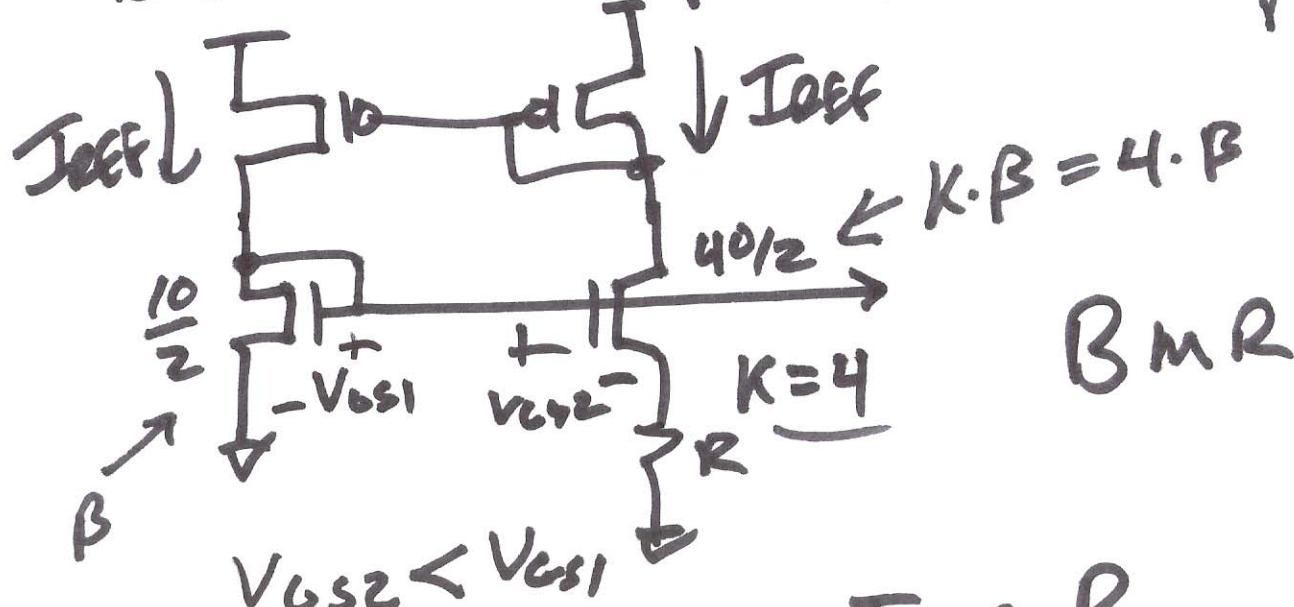

$$V_{GS1} = V_{GS2} + I_{REF} \cdot R$$

$$V_{GS} = \sqrt{\frac{2I_0}{\beta}} + V_{THN}$$

$$\sqrt{\frac{2I_{REF}}{\beta}} + V_{THN} = \sqrt{\frac{2I_{REF}}{K \cdot \beta}} + V_{THN} + I_{REF} \cdot R$$

$$I_{REF} \cdot R = \sqrt{\frac{IDBF \cdot 2}{B}} \left(1 - \frac{1}{\sqrt{K}} \right)$$

$$I_{REF} \cdot R^2 = \frac{2}{KP \cdot \frac{W_1}{L_1}} \cdot \left(1 - \frac{1}{\sqrt{K}} \right)^2$$

$$I_{REF} = \frac{2}{KP \cdot \frac{W_1}{L_1} \cdot R^2} \left(1 - \frac{1}{\sqrt{K}} \right)^2$$


independent of VDD!

$$\text{If } K=4 \quad I_{REF} = \frac{1}{2KP \cdot \frac{W_1}{L_1} \cdot R^2}$$

$$g_m = \sqrt{2 \cdot KP \cdot \frac{W_1}{L} \cdot I_{REF}} = \frac{1}{R} \quad (K=4)$$

$$.8PA/nV$$

11)

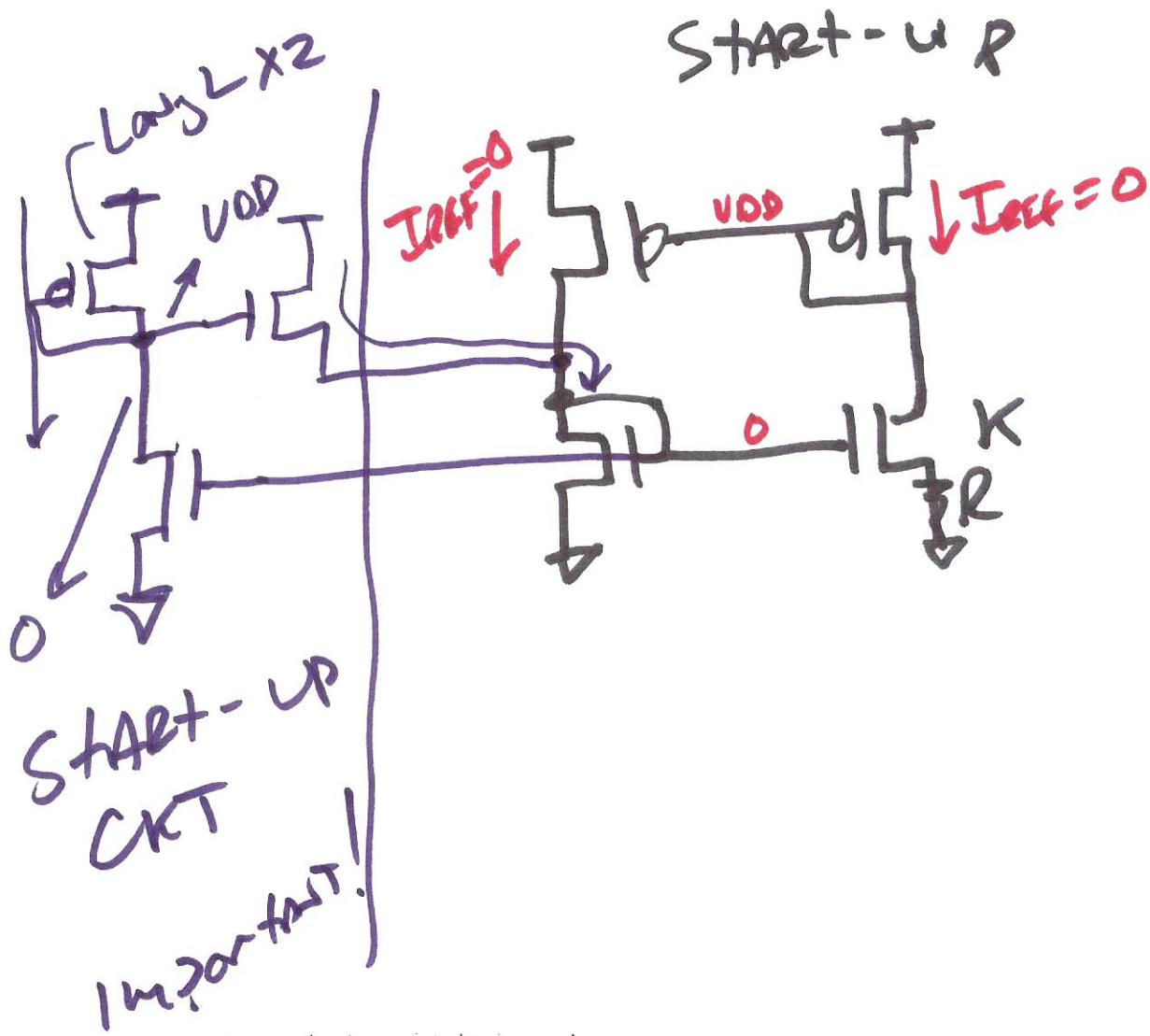

(2)