
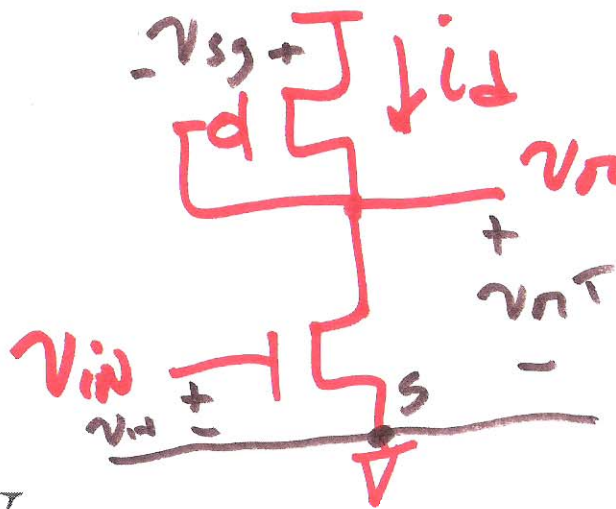


# Sec. 21.1

## Gate-drain connected loads

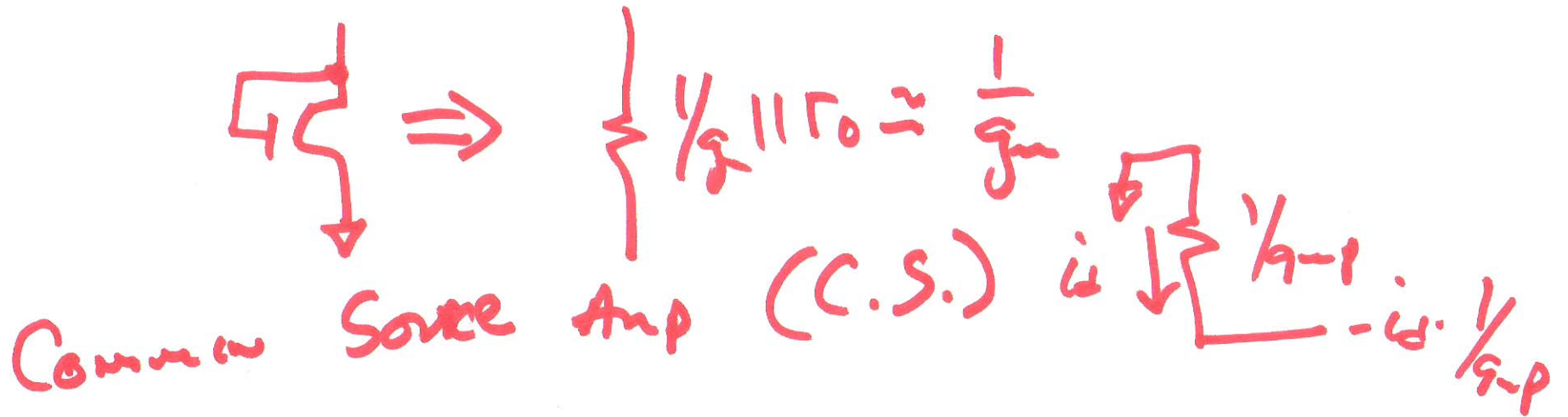


$$v_{out} = -i_d \cdot \frac{1}{g_{m,p}}$$

$$i_d = g_{m,n} \cdot v_{in}$$

$$\frac{v_{out}}{v_{in}} = - \frac{\frac{1}{g_{m,p}}}{\frac{1}{g_{m,n}}} = - \frac{R_{eq, load}}{R_{eq, source}}$$




11

C.S.

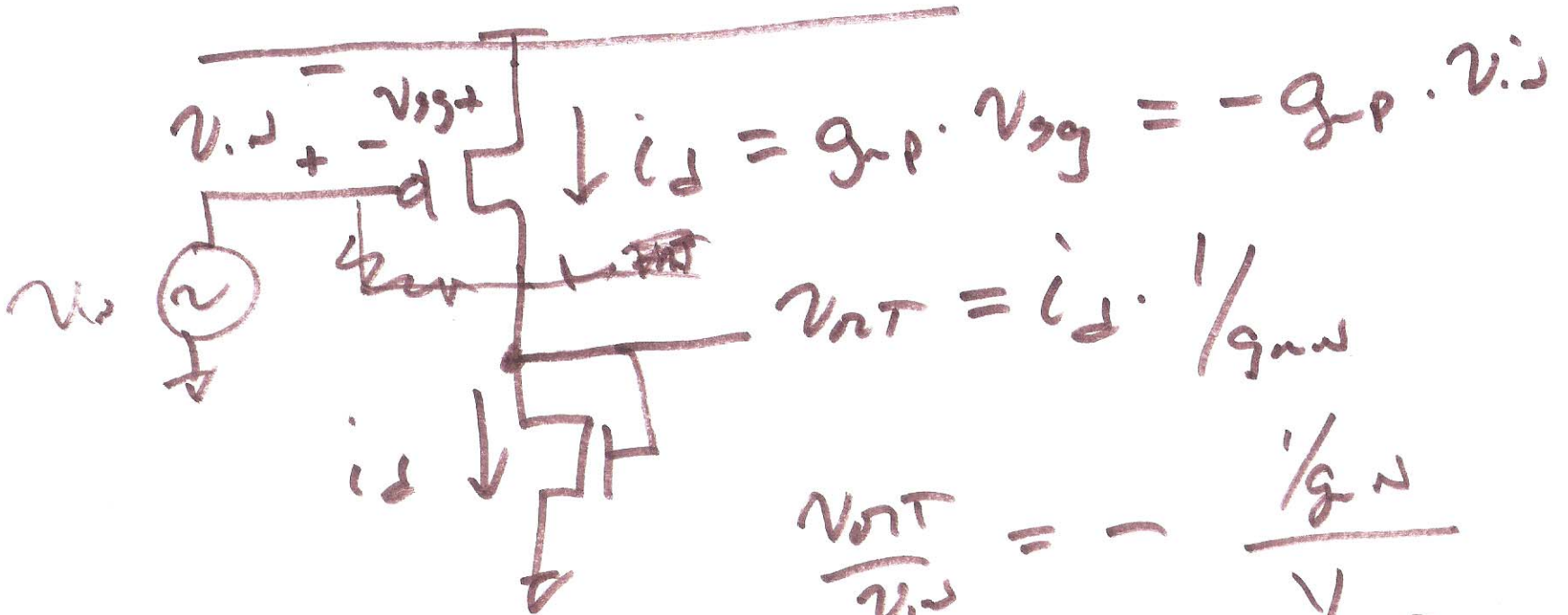


$$\frac{v_{out}}{v_i} = - \frac{g_{mN}}{g_{mP}}$$


Let's not neglect  $r_{o'}$ .

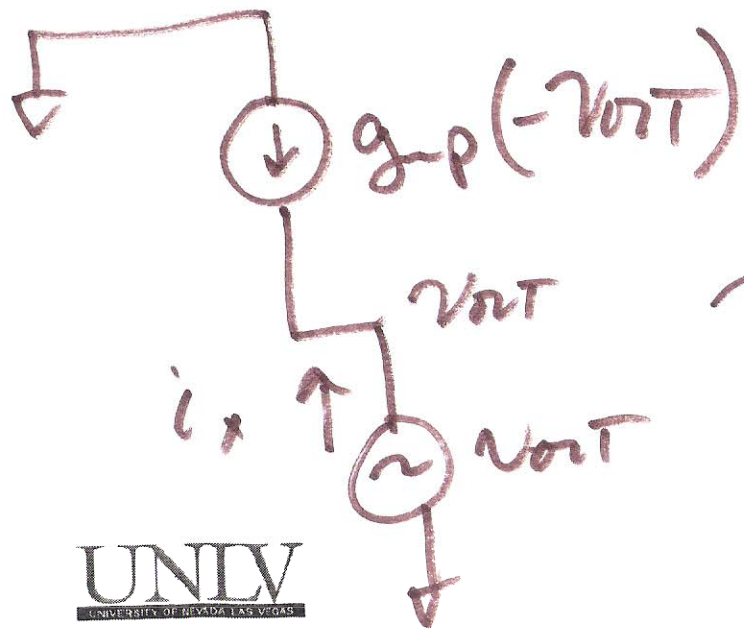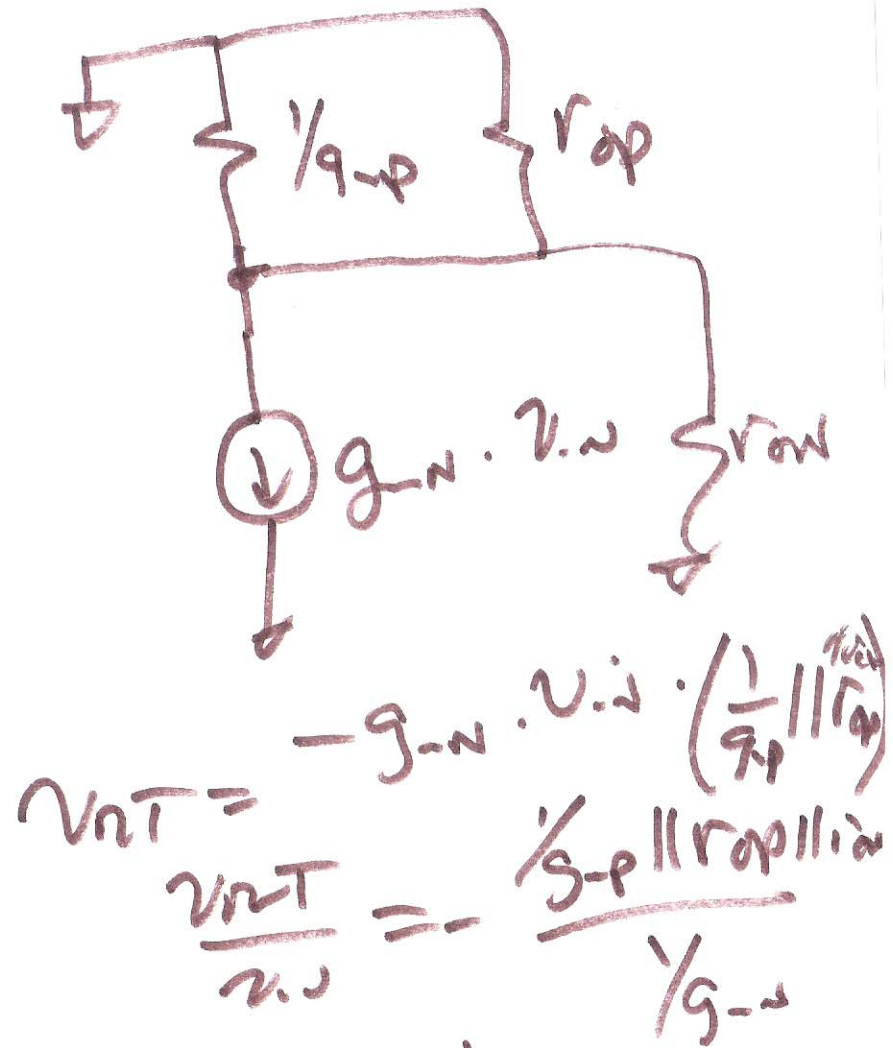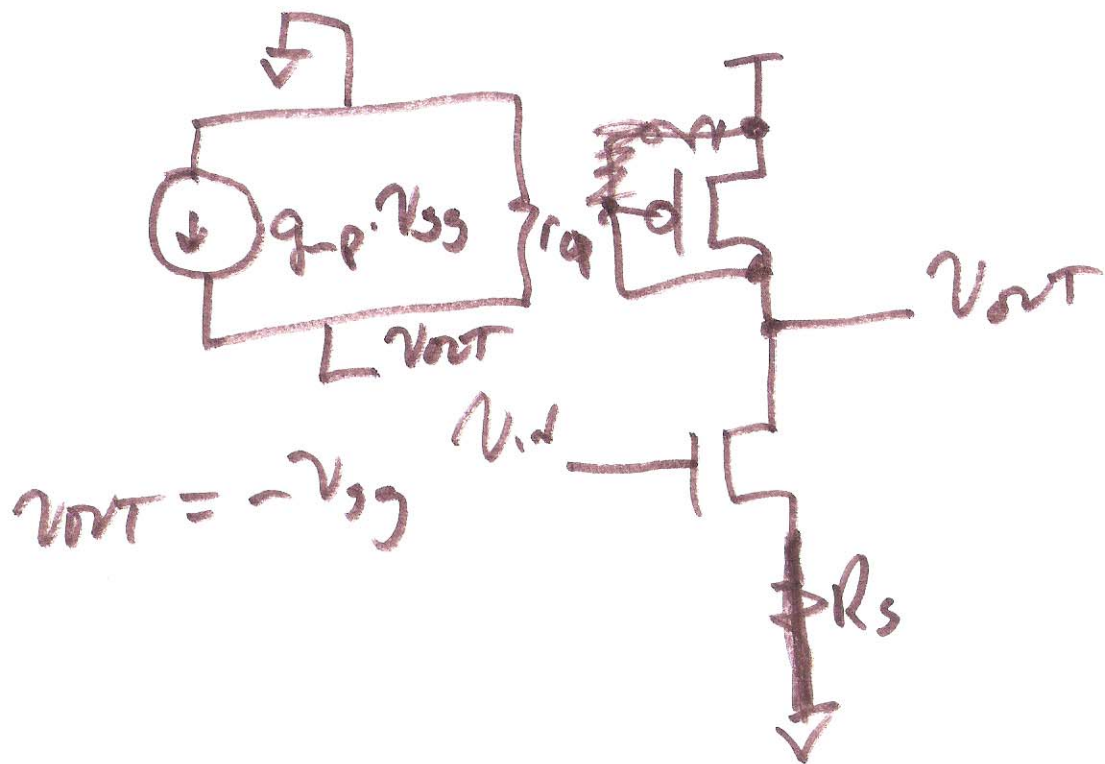
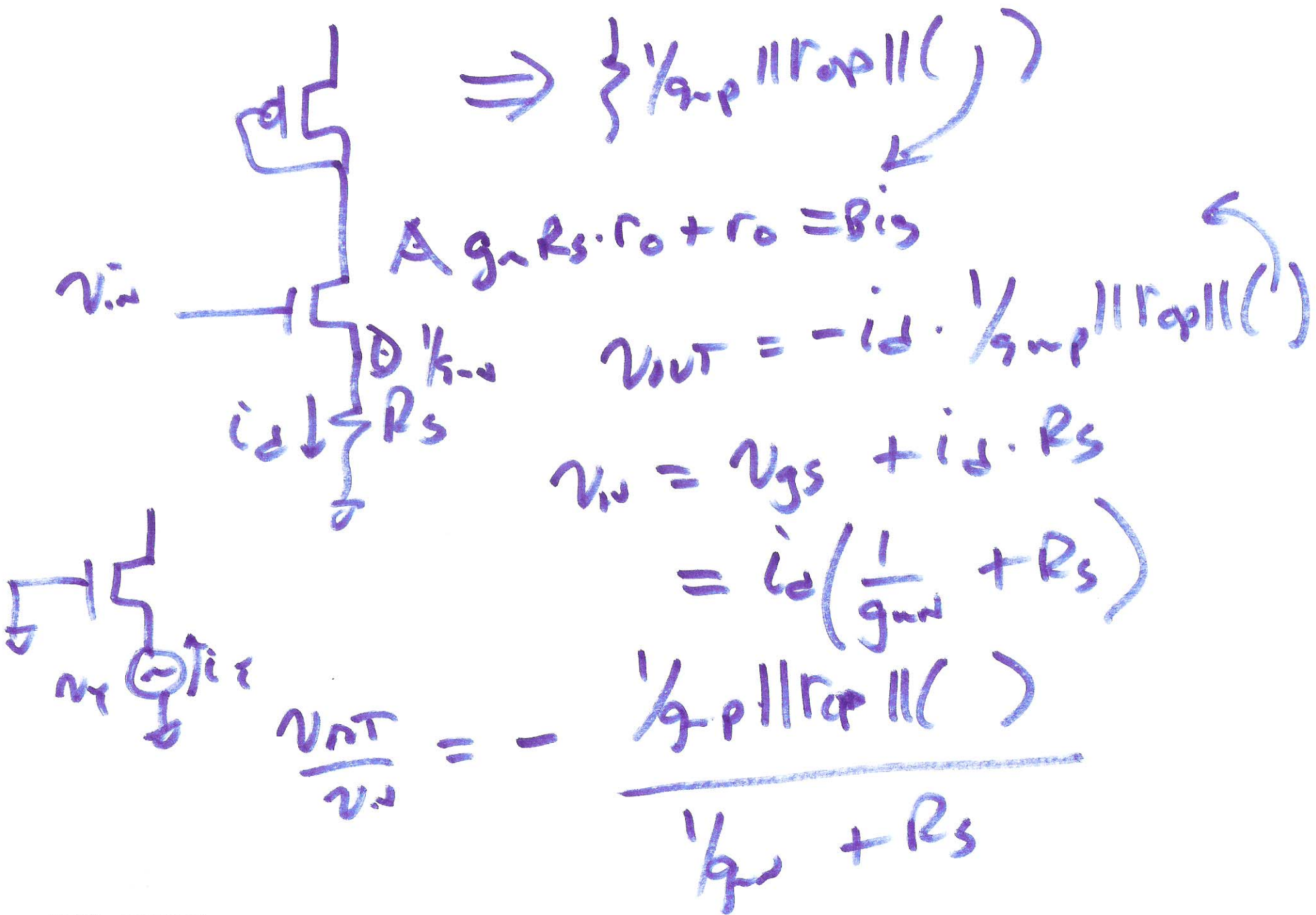
$$\frac{v_{out}}{i_x} = \frac{v_{out}}{-g_{-p}(-v_{out})} = \frac{1}{g_{-p}}$$



4)

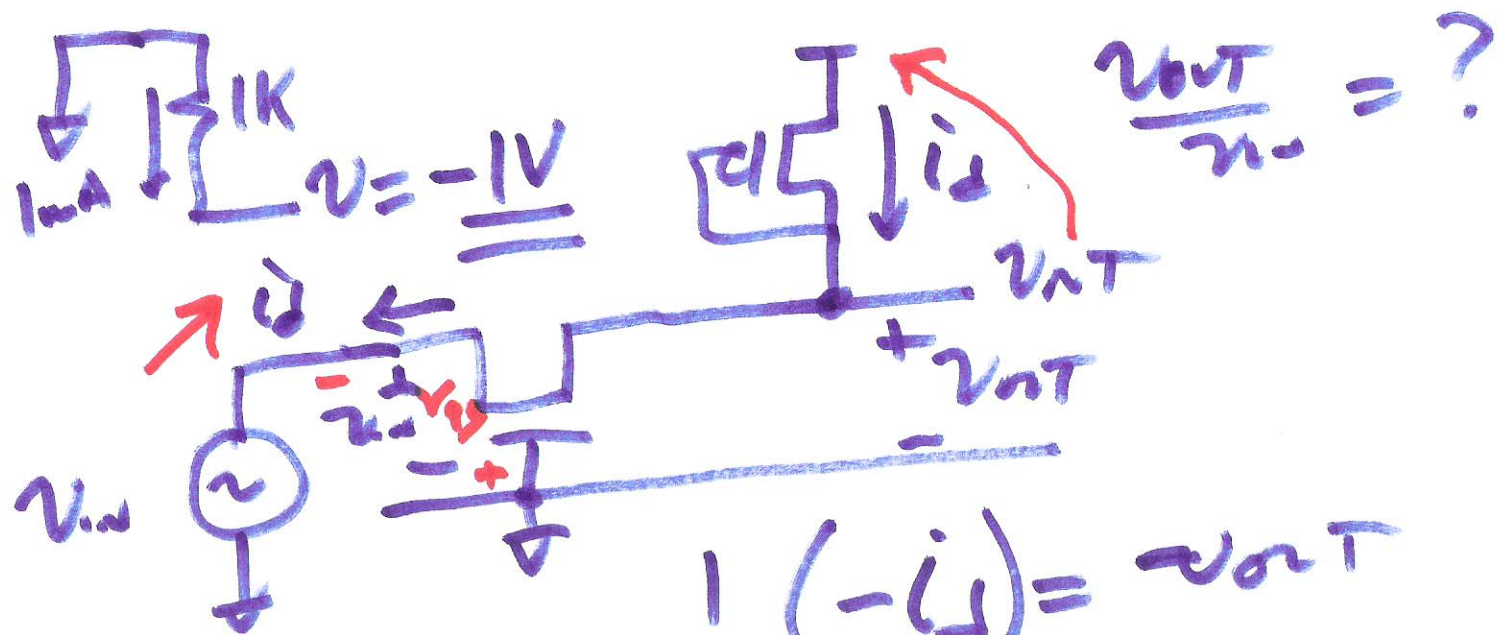

C.G.  
Amp


$$\frac{1}{g_{sp}} (-i_d) = v_{out}$$

$$v_{in} = -v_{gs} = -\frac{i_d}{g_{ms}}$$

$$-i_d = v_{in} \cdot g_{ms}$$

$$\frac{v_{out}}{v_{in}} = \frac{g_{ms}}{g_{sp}} = \frac{1}{1/g_{ms}}$$

# C.D. (source follower)

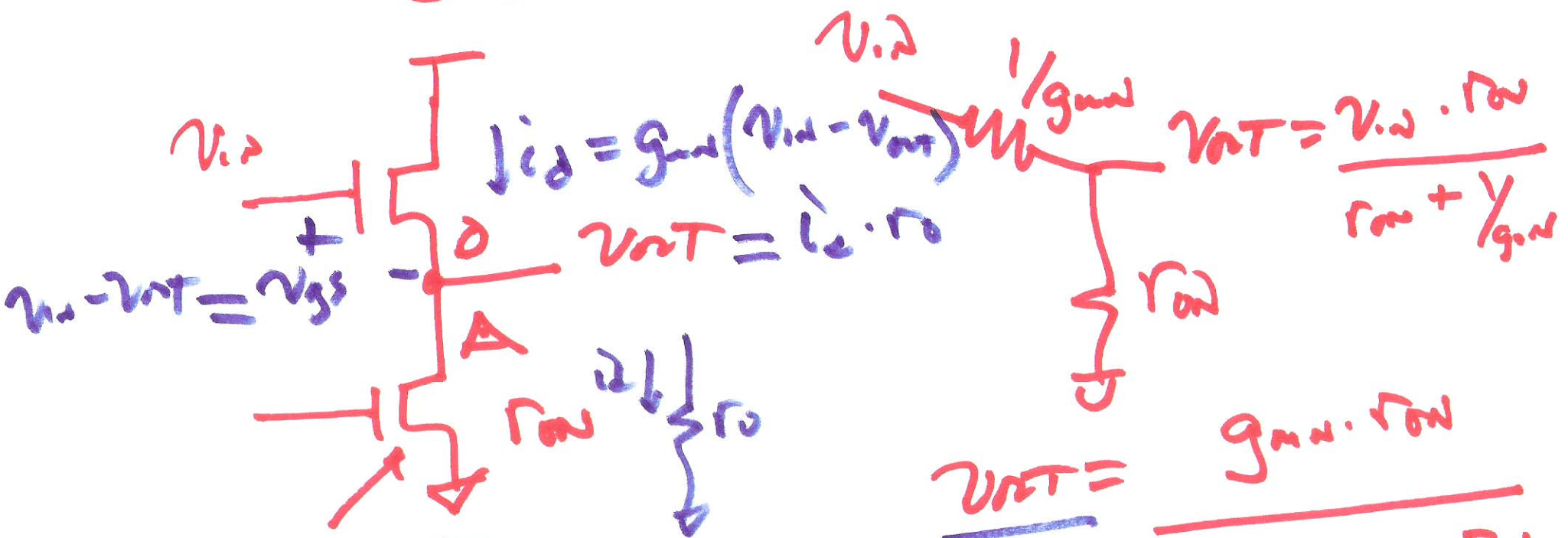

Current mirror

$$\frac{v_{out}}{v_{in}} = \frac{g_m \cdot r_{oN}}{1 + g_m \cdot r_{oN}}$$

$$\frac{v_{out}}{v_{in}} = \frac{i_d \cdot r_o}{i_d} = \frac{g_m \cdot (v_{in} - v_{out}) r_o}{g_m \cdot (v_{in} - v_{out}) r_o}$$


b)

$$v_{out} = g_{mN}(v_{in} - v_{out}) r_o$$

$$v_{out} = g_{mN} r_o v_{in} - g_{mN} r_o v_{out}$$


$$v_{out} \cdot (1 + g_{mN} r_o) = g_{mN} r_o v_{in}$$
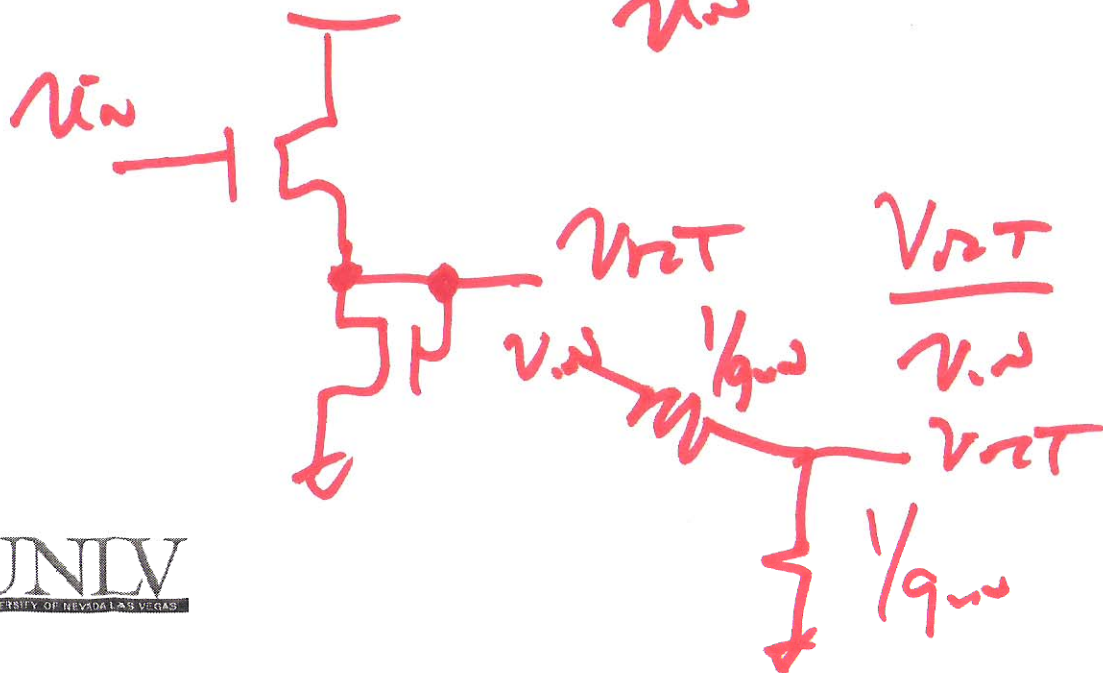
$$\frac{v_{out}}{v_{in}} = \frac{g_{mN} r_o}{1 + g_{mN} r_o}$$



$$\frac{v_{out}}{v_{in}} = \frac{1/g_{mN}}{1/g_{mN} + 1/g_{mN}} = \frac{1}{2}$$

→

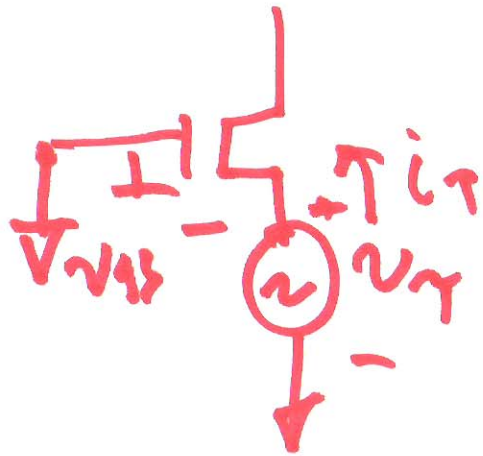


$$\text{Photosource} = \frac{v_T}{i_T} = \frac{-v_{gs}}{-g_m v_{gs}}$$

$$v_T = -v_{gs} \qquad = \frac{1}{g_m}$$

$$i_T = -i_d$$

$$i_d = g_m v_{gs}$$




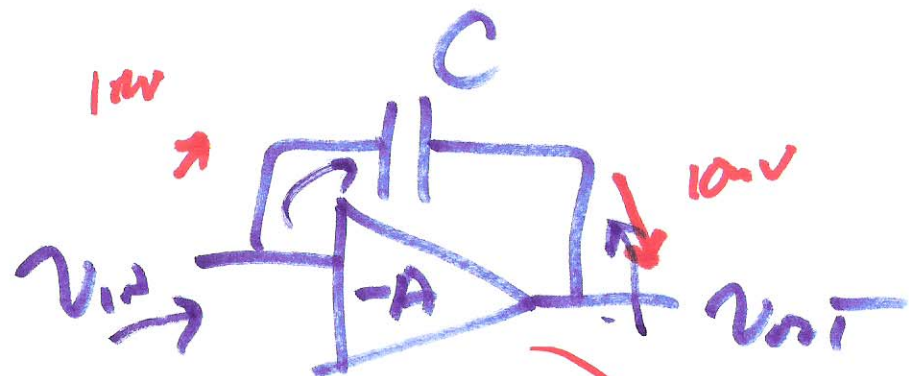


$$i = C \frac{dv}{dt}$$

$$(v_{in} + |v_{out}|) \cdot C$$

$$|| \cdot C$$

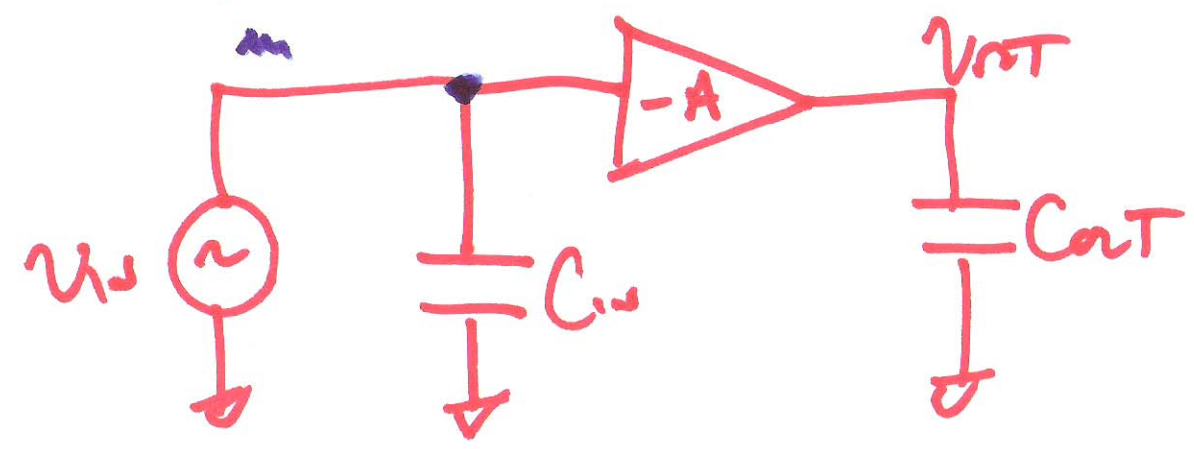


9

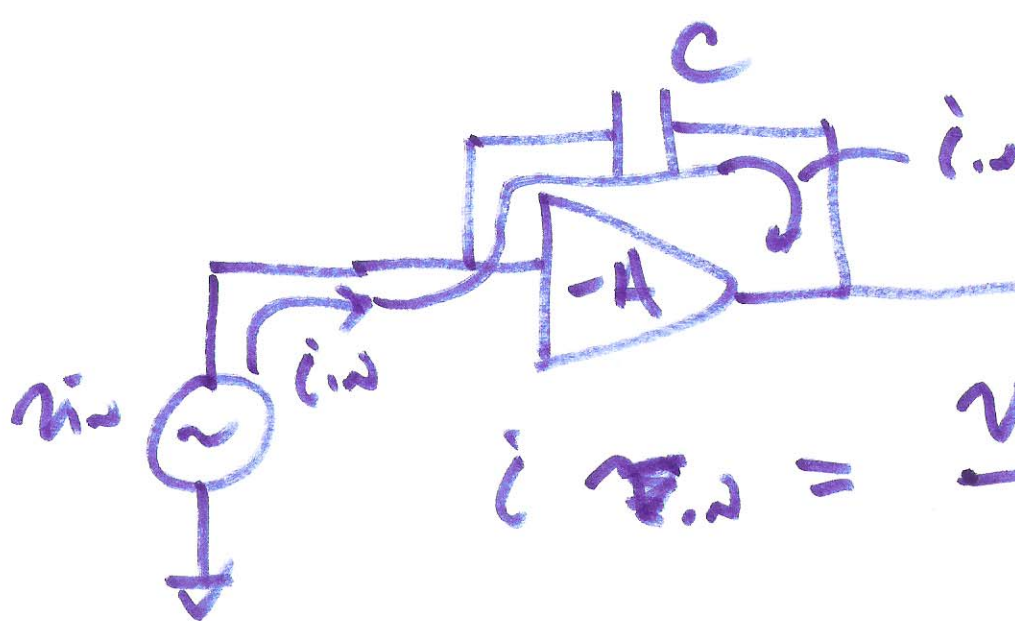

$$v_{in} = -\frac{v_{out}}{A}$$


$$v_{out} = -A \cdot v_{in} \left(\frac{1}{A} + 1\right)$$
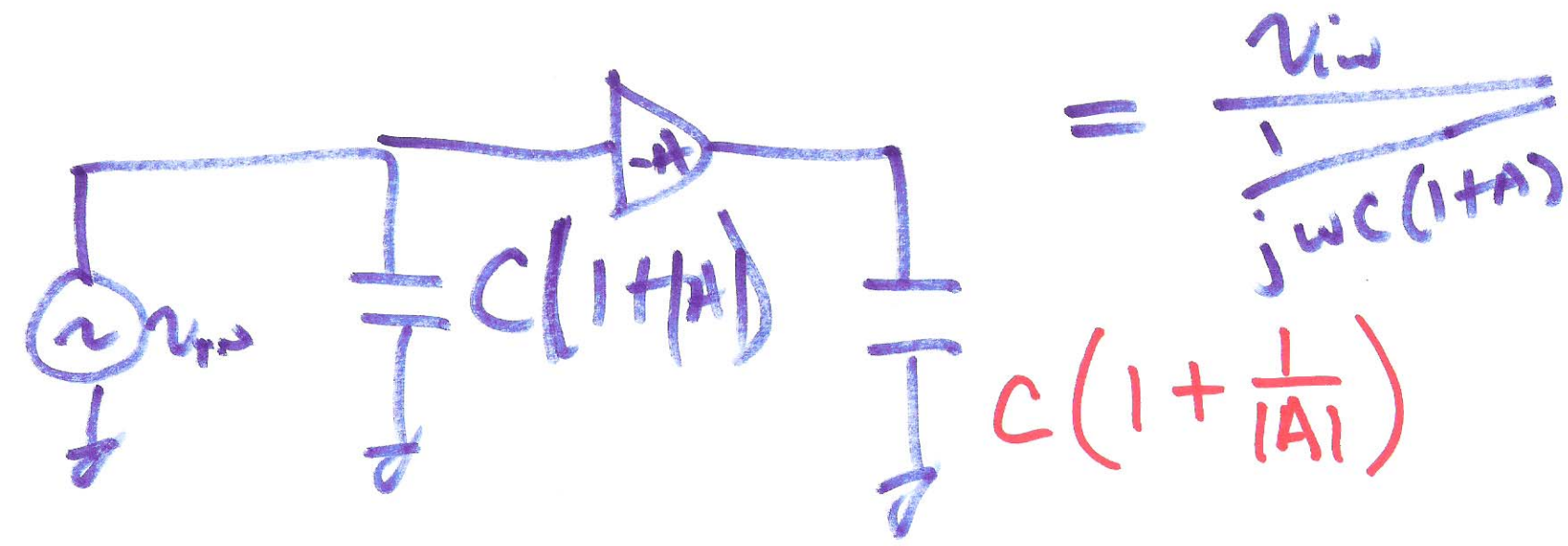
$$i_{in} = \frac{v_{in} - v_{out}}{1/j\omega C} = \frac{v_{in}(1+A)}{1/j\omega C}$$




$$= \frac{v_{in}}{j\omega C(1+A)}$$


$$C\left(1 + \frac{1}{|A|}\right)$$

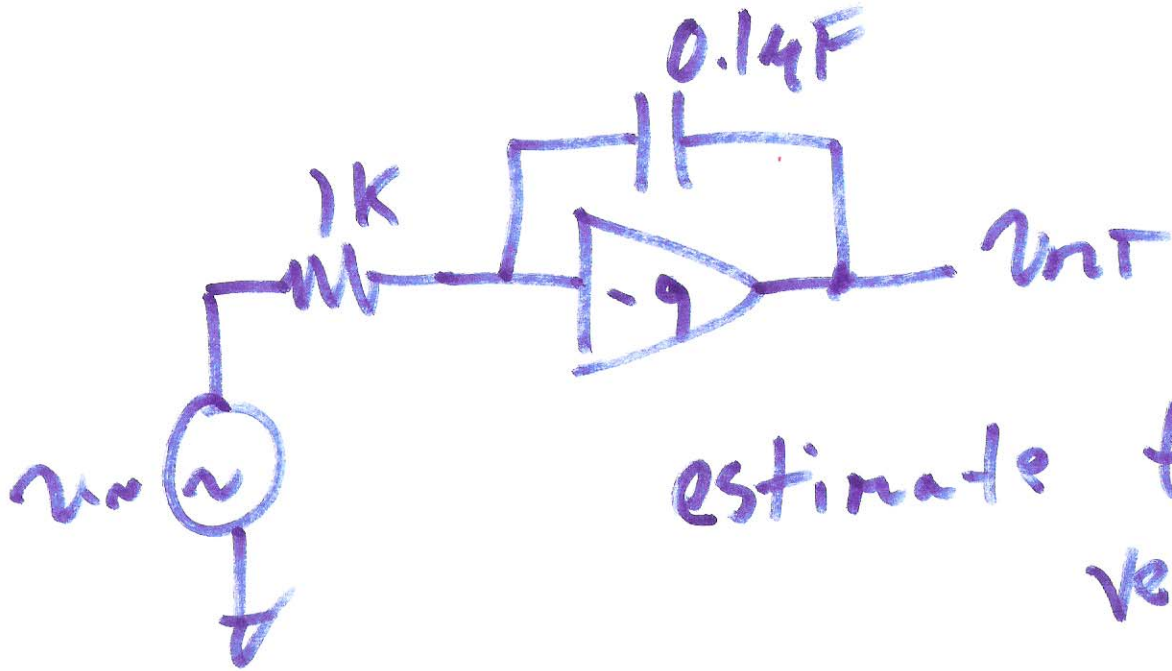

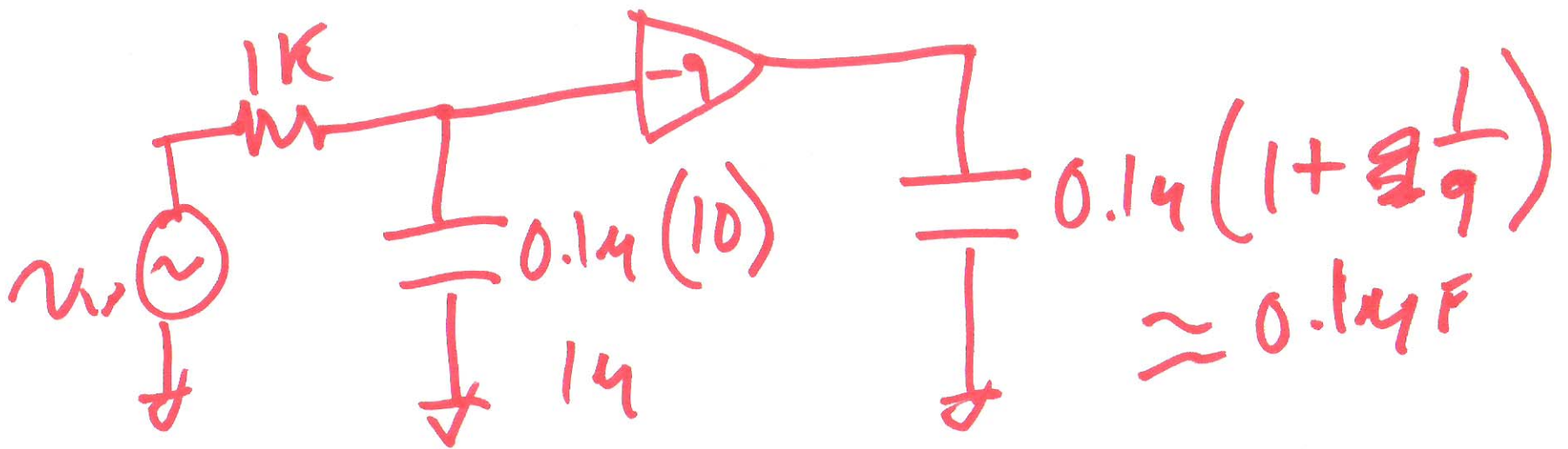estimate the 3dB freq.  
verify with SPICE


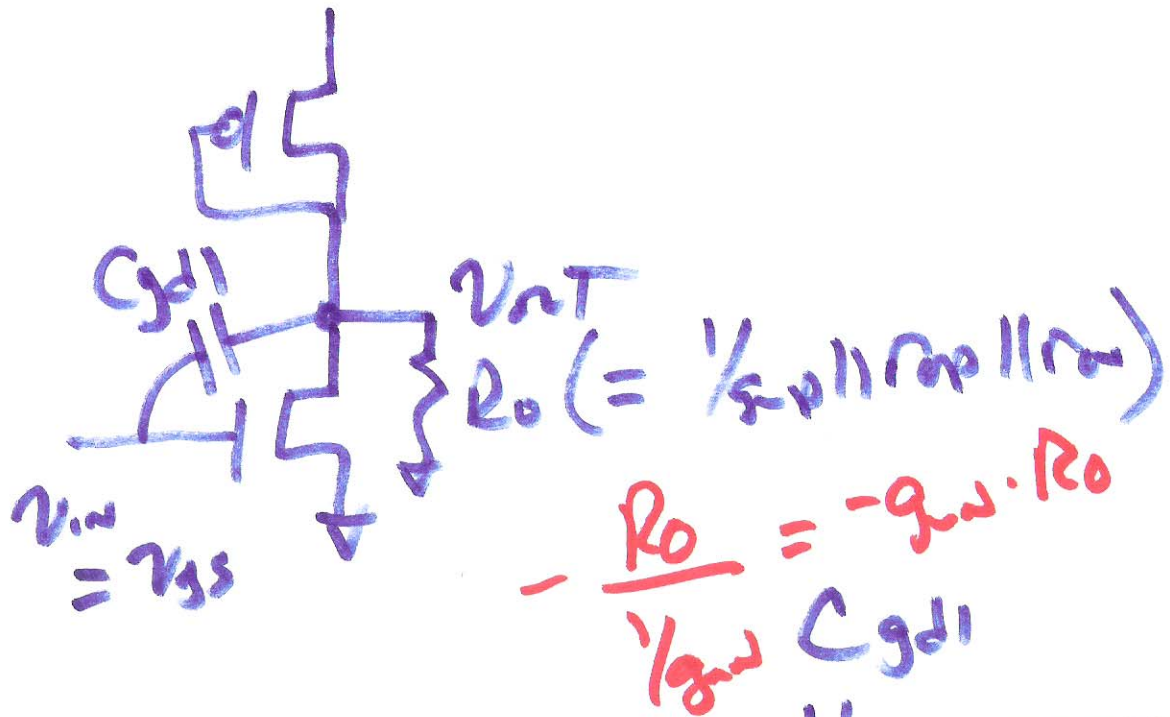
$$f_{3dB} = 159 \text{ Hz} = \frac{1}{2\pi \cdot 1\text{K} \cdot 14\text{F}}$$




$$Roll \frac{1}{j\omega C_o} =$$

$$R_o \cdot \frac{1}{j\omega C_o}$$

$$R_o + \frac{1}{j\omega C_o}$$

$v_{out}$

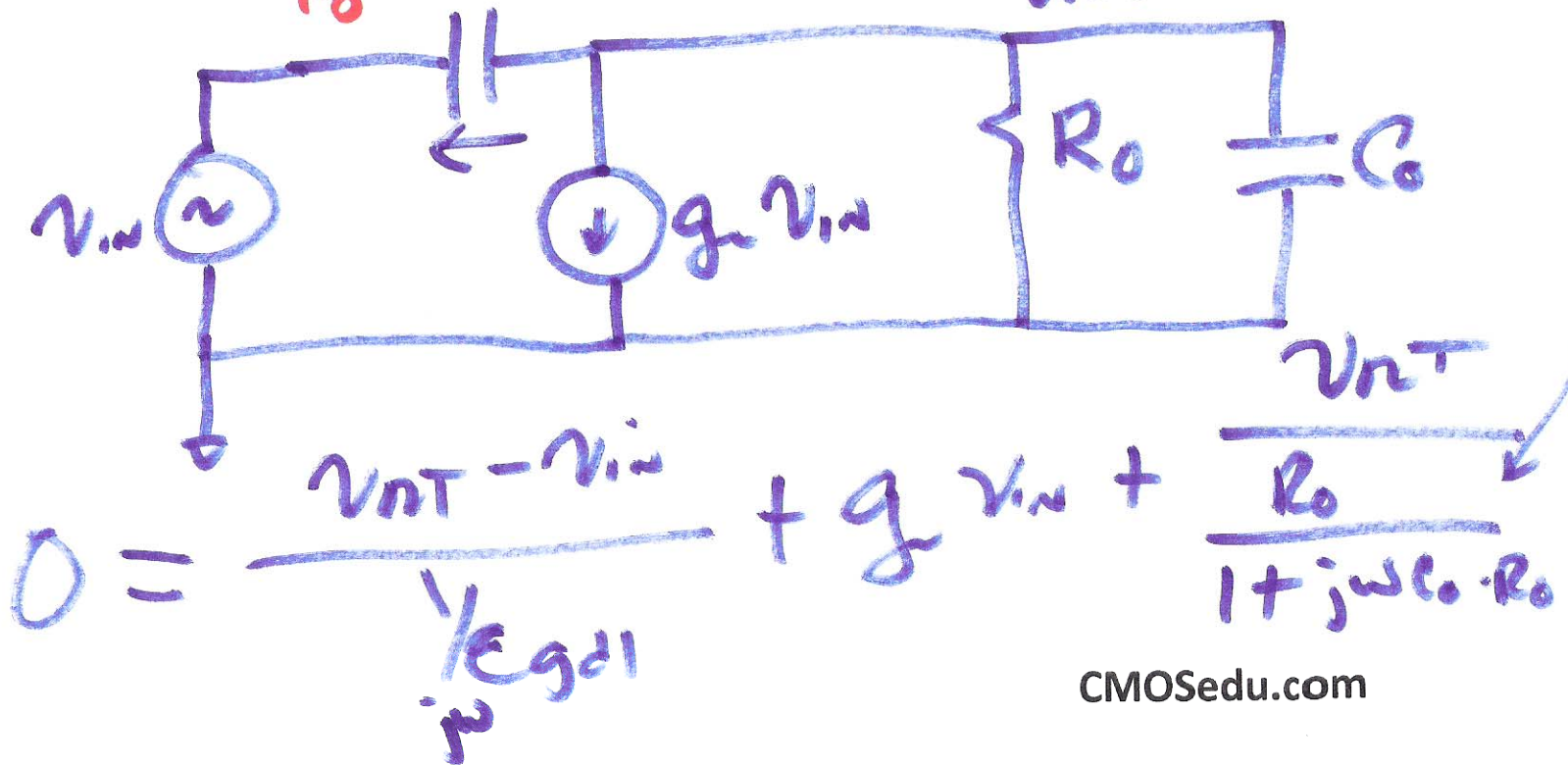

$$0 = V_{out} \cdot j\omega C_{gd1} - v_{in} \cdot j\omega C_{gd1} + v_{in} \cdot g_m + V_{out} \cdot \frac{1}{R_o} + V_{out} \cdot j\omega C_o$$

$$0 = V_{out} \left( j\omega (C_o + C_{gd1}) + \frac{1}{R_o} \right) + v_{in} \left( g_m - j\omega C_{gd1} \right)$$

$$\frac{V_{out}}{v_{in}} = \frac{-(g_m - j\omega C_{gd1})}{\frac{1}{R_o} + j\omega (C_o + C_{gd1})}$$

$$= \frac{-g_m R_o \left( 1 - \frac{j\omega C_{gd1}}{g_m} \right)}{1 + j\omega (C_o + C_{gd1}) R_o}$$