
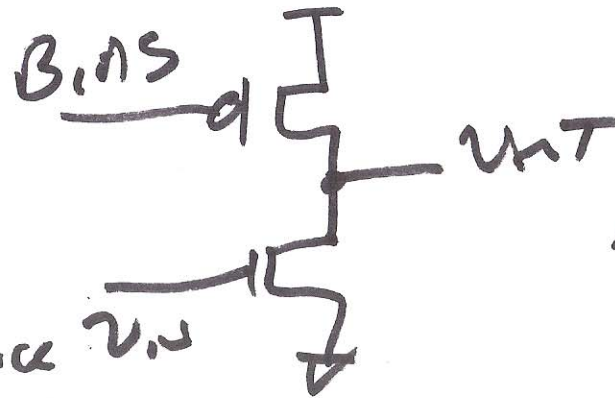



21.2 CURRENT SOURCE LOADS

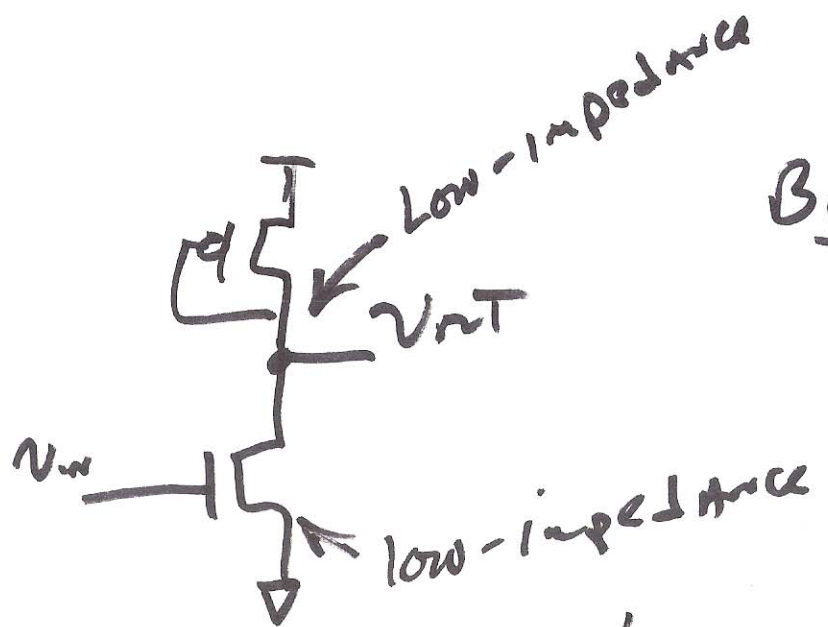

$$\frac{v_{out}}{v_{in}} = \frac{-r_{o,n} \parallel r_{o,p}}{1/g_{m,n}}$$

$$= -g_{m,n} r_{o,n} \parallel r_{o,p}$$
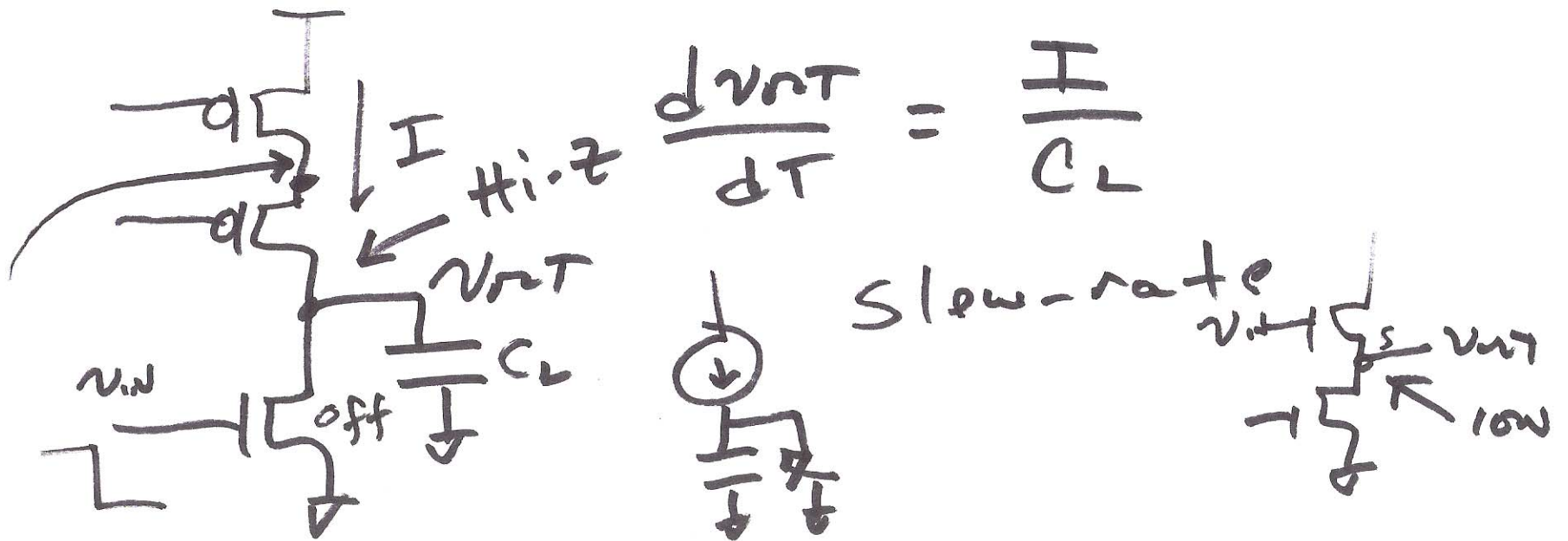
$$\frac{v_{out}}{v_{in}} = - \frac{1/g_{m,p}}{1/g_{m,n}} = - \frac{g_{m,n}}{g_{m,p}}$$




$$\frac{v_{out}}{v_{in}} = - \frac{R_{out} \parallel r_{out}}{1/g_{m,n}} \approx -g_{m,n} r_{out}$$

open CKT gain!

$$\frac{dv}{dt} = \frac{20 \mu A}{1 pF} \left(\frac{V}{s} \right) = \frac{20V}{14s} = \frac{2V}{100ns}$$

2)

C.S. Amp with current source load

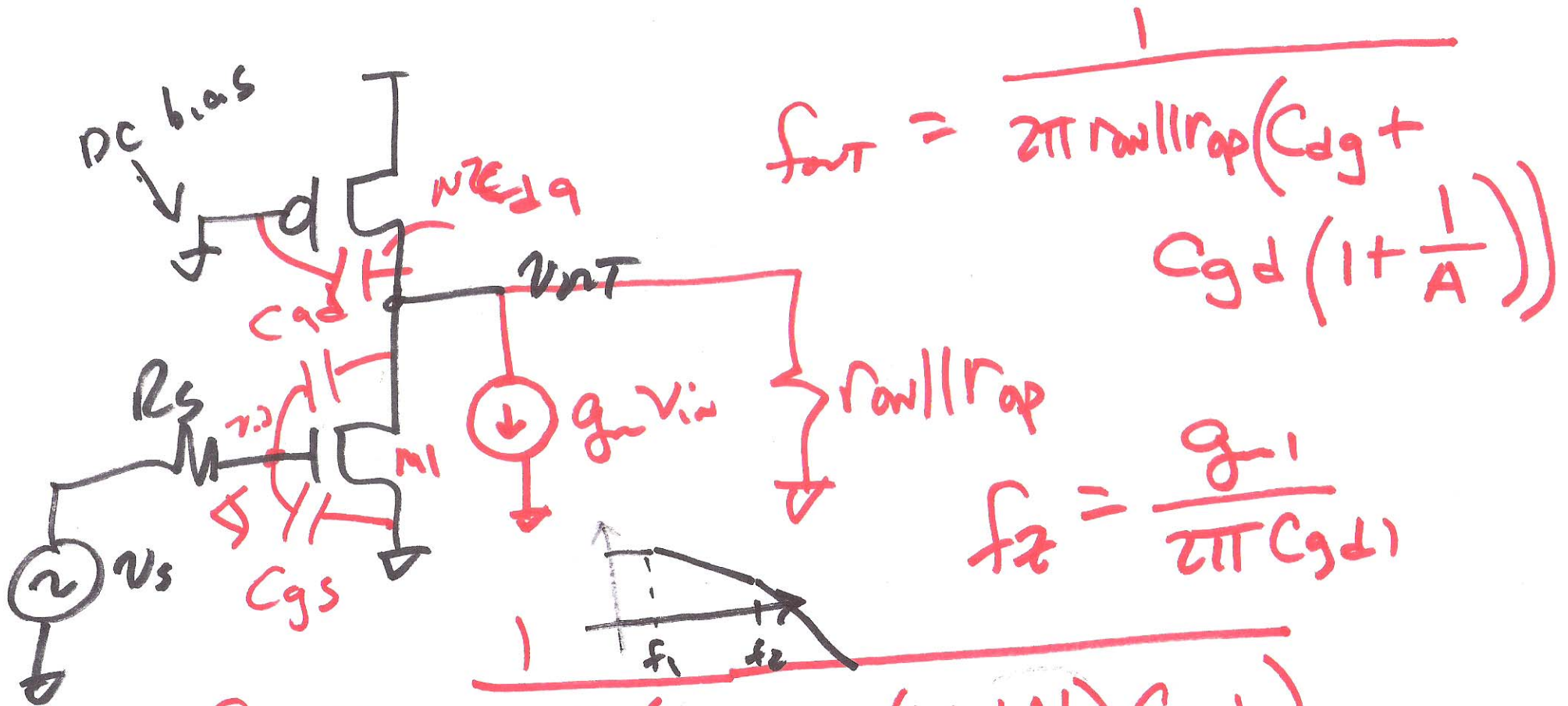

$$f_{out} = \frac{1}{2\pi r_o || r_{op} (C_{dg} + C_{gd} (1 + \frac{1}{A}))}$$



$$f_z = \frac{g_m}{2\pi C_{gd}}$$

$$f_{in} = 2\pi R_s (C_{gs} + (1 + |A|) C_{gd})$$

$$g_m \cdot r_o || r_{op}$$

3)

AC CKT

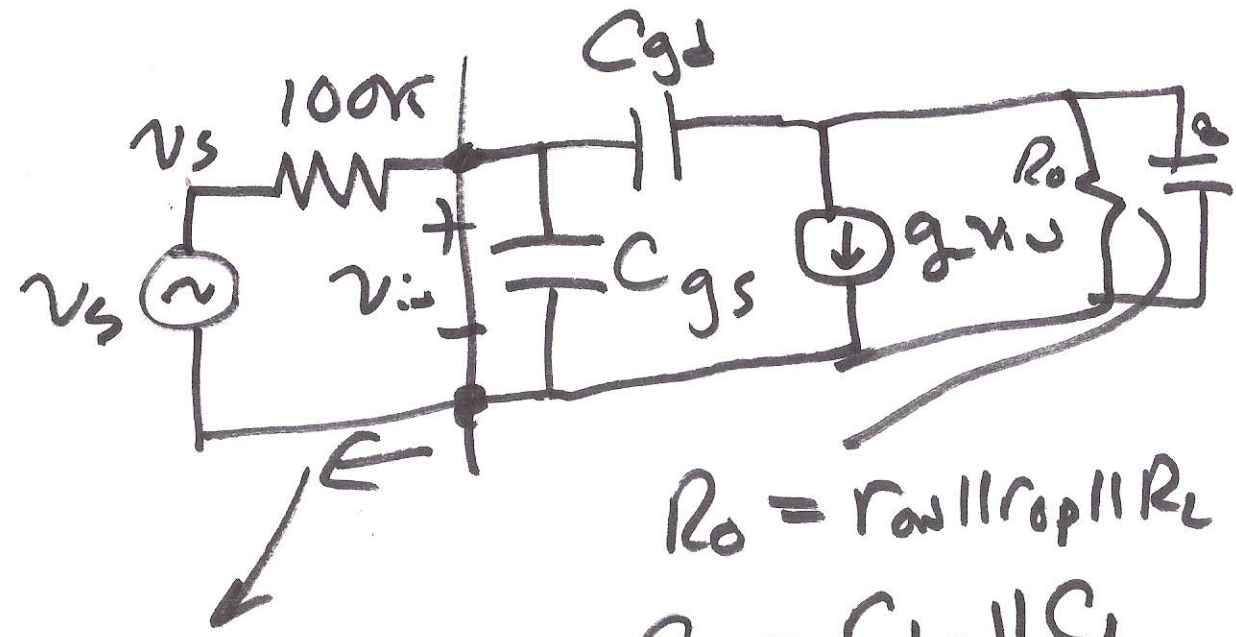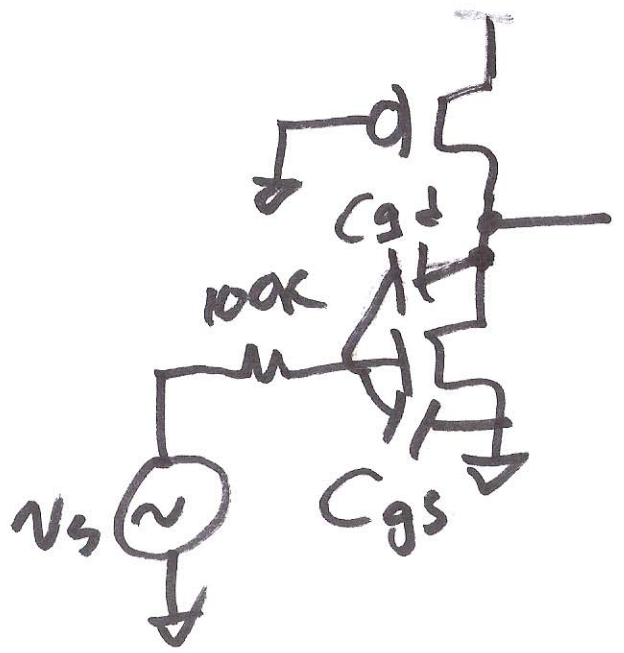


$$R_o = r_{o1} \parallel r_{o2} \parallel R_L$$

$$C_o = C_{gd} \parallel C_L$$

$$f_{un} = \frac{g_{m1}}{2\pi C_c} = \frac{1}{2\pi (\frac{1}{g_m}) C_c}$$

$$= \frac{1504}{2\pi \text{ 1PF}}$$

$$= 25 \text{ MHz} \approx$$

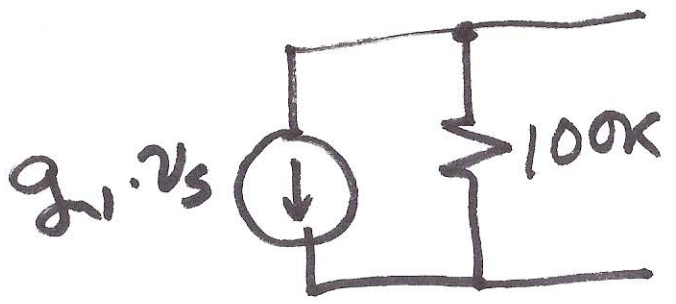

$$g_{m1} = \frac{1}{100k}$$

4)

$$1 - s \frac{C_c}{g_{m2}}$$


$$\left| s \frac{C_c}{g_{m2}} \right| = 1$$

Ans.

$$\frac{2\pi f \cdot C_c}{g_{m2}} = 1$$

$$f_z = \frac{g_{m2}}{2\pi C_c}$$
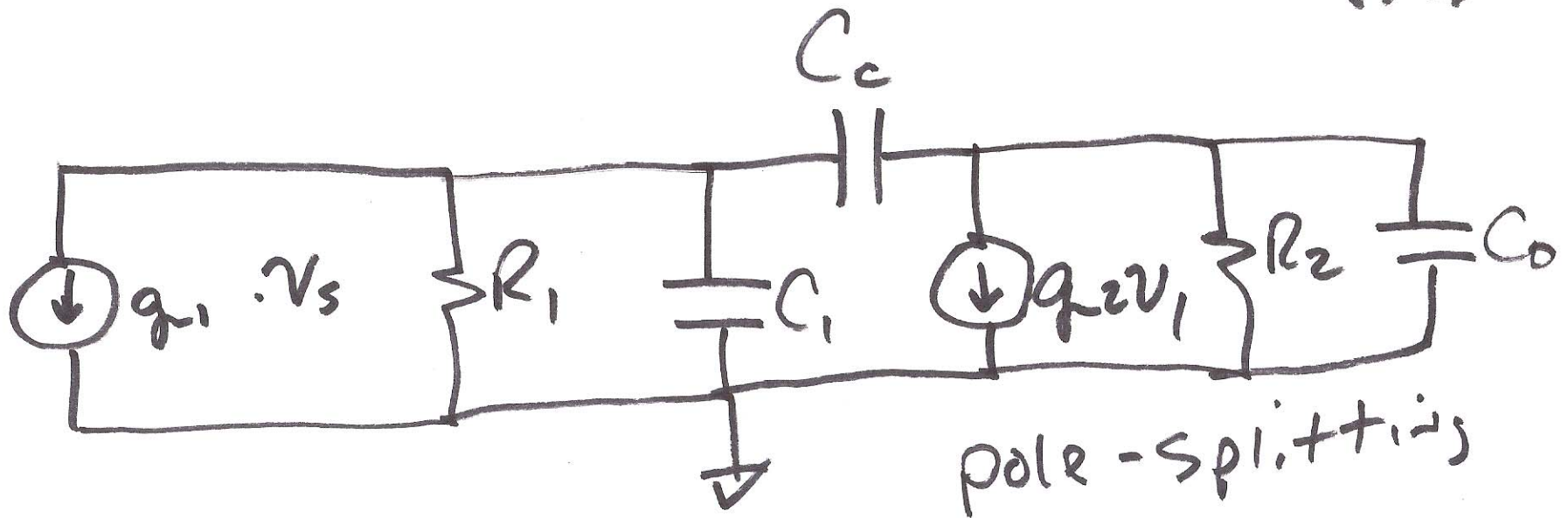
$$= \frac{1}{2\pi \left(\frac{1}{g_{m2}}\right) C_c}$$



5)

$$A_v(f) = \frac{v_{out}(f)}{v_{in}} = \frac{-g_m \cdot r_{out} || r_{op} \rightarrow 330}{1 + j \frac{f}{f_{3dB}} \rightarrow 4.8 \text{ kHz}}$$

$$f_{3dB} = f_1 = \frac{1}{2\pi \cdot R_s \cdot g_m \cdot r_{out} || r_{op} \cdot C_c}$$

$$\left| \frac{v_{out}}{v_{in}} \right| = 1 = \frac{330}{\sqrt{1 + \left(\frac{f_{cut}}{4.8 \text{ kHz}} \right)^2}} \cdot \frac{g_m \cdot r_{out} || r_{op}}{2\pi R_s \cdot C_c}$$

$$1 + \left(\frac{f_{cut}}{4.8 \text{ kHz}} \right)^2 = \left(\frac{1}{330^2} \right)^{-1}$$

$$f_{cut} \approx 330 \cdot 4.8 \text{ kHz} = 1.584 \text{ MHz}$$

6)