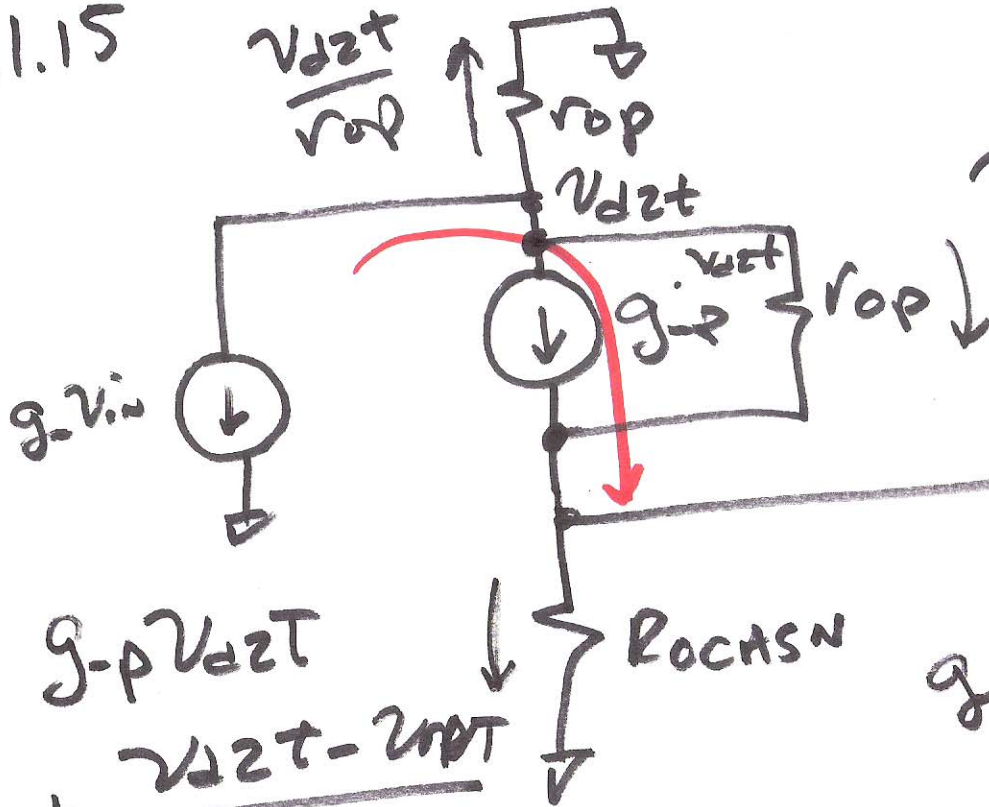


Ch 21 Sec. 21.3

Push-Pull amplifier

A 21.15



$$\frac{v_{out}}{v_{in}} = -g_m R_{OCASN} = 1504 \cdot 3756$$

$$\frac{v_{dzt} - v_{out}}{r_{op}} \cdot \frac{v_{out}}{g_m v_{in}} = R_{OCASN} = 3.756$$

$$v_{out} \approx -g_m v_{in} R_{OCASN}$$

$$\frac{v_{out}}{R_{OCASN}} = g_{m-p} v_{dzt} + \frac{v_{dzt} - v_{out}}{r_{op}}$$



$$g_m v_{in} + \frac{v_{dzt}}{r_{op}} + g_{m-p} v_{dzt} + \frac{v_{dzt} - v_{out}}{r_{op}} = 0$$

$$g_m v_{in} + \frac{v_{dzt}}{r_{op}} + \frac{v_{out}}{R_{OCASN}} = 0$$


1)

Push-pull Amplifiers

Class AB

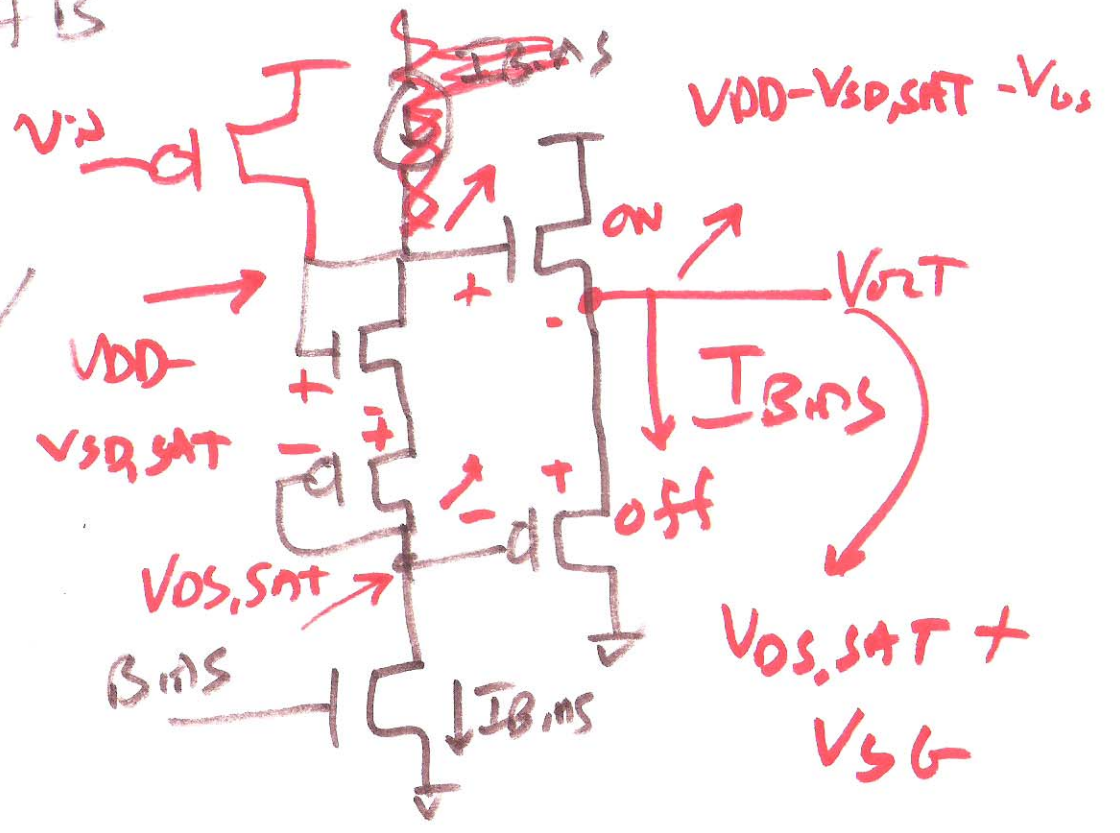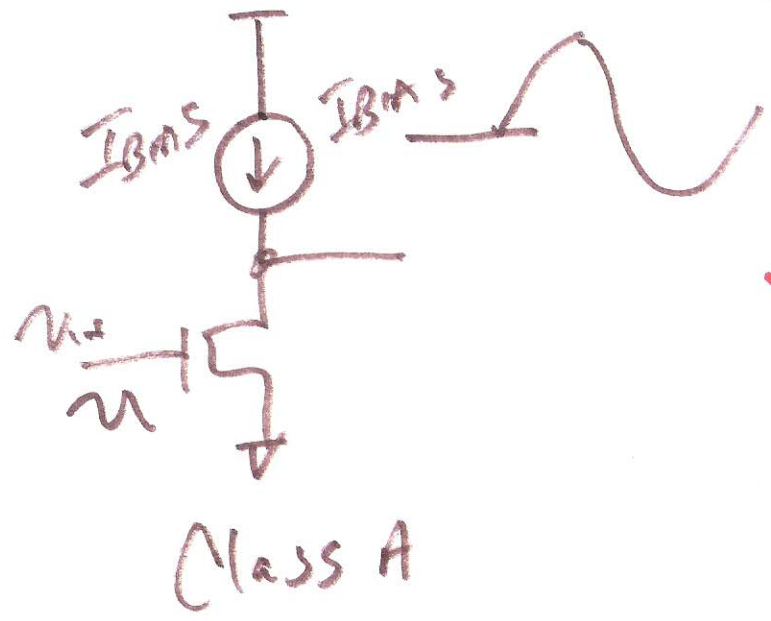

2)


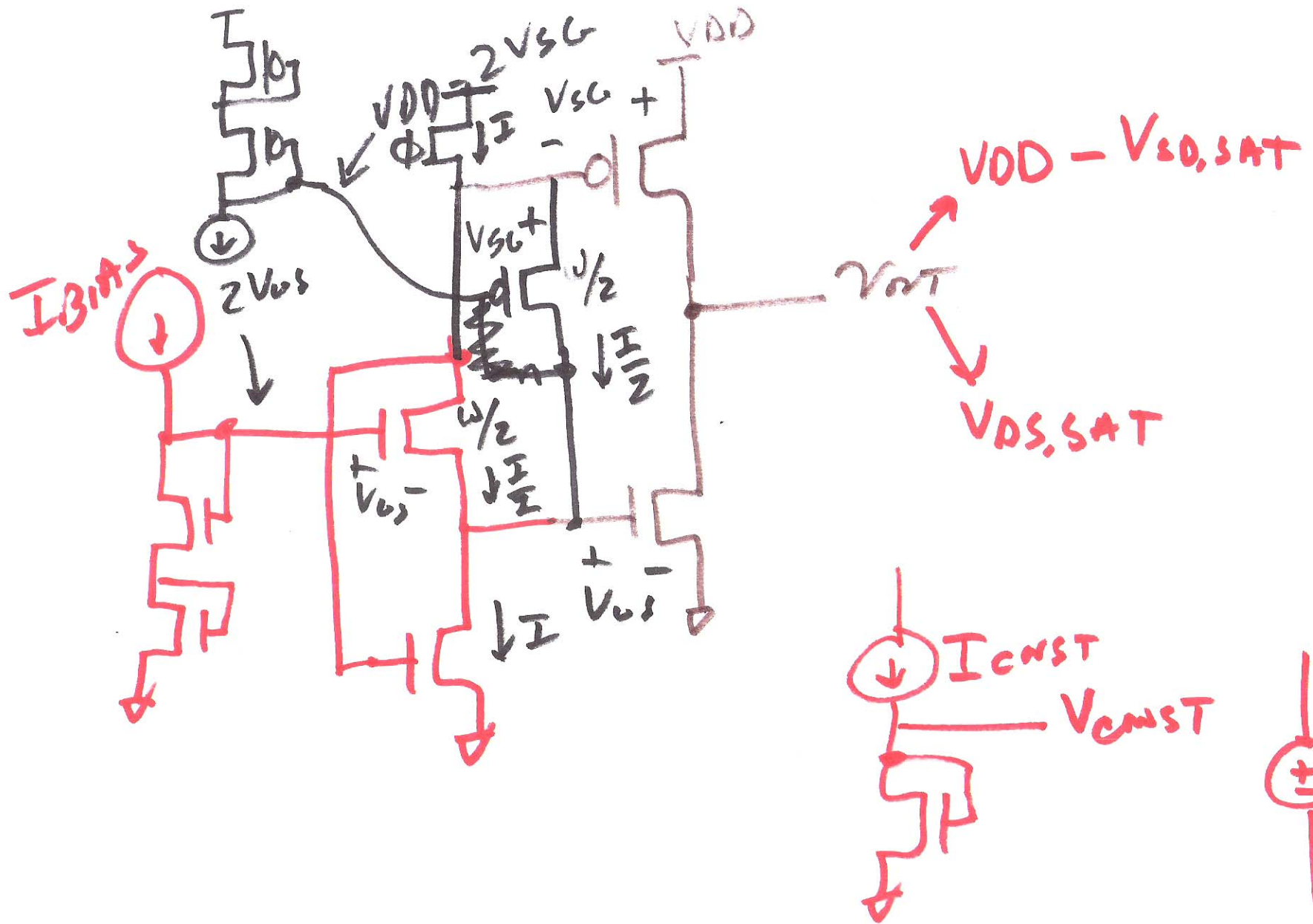


3)

$$\frac{1}{g_n} \parallel \frac{1}{g_p}$$



$$\frac{1}{g_n} + \frac{1}{g_p}$$

$$\frac{1}{g_n + g_p}$$

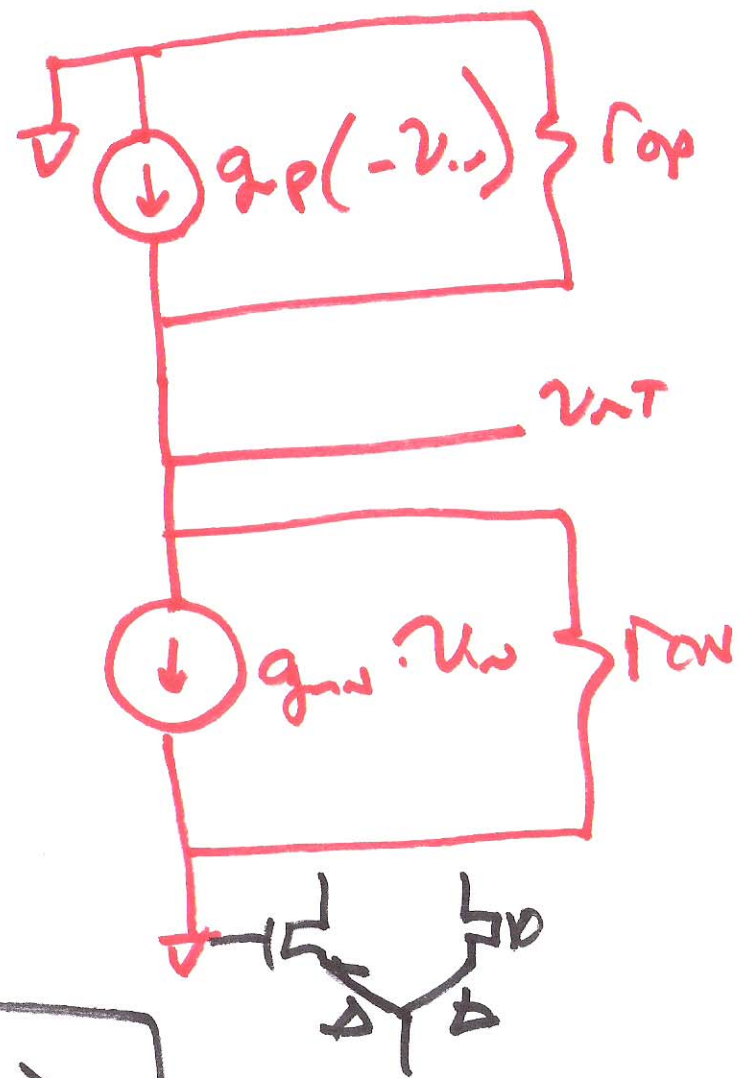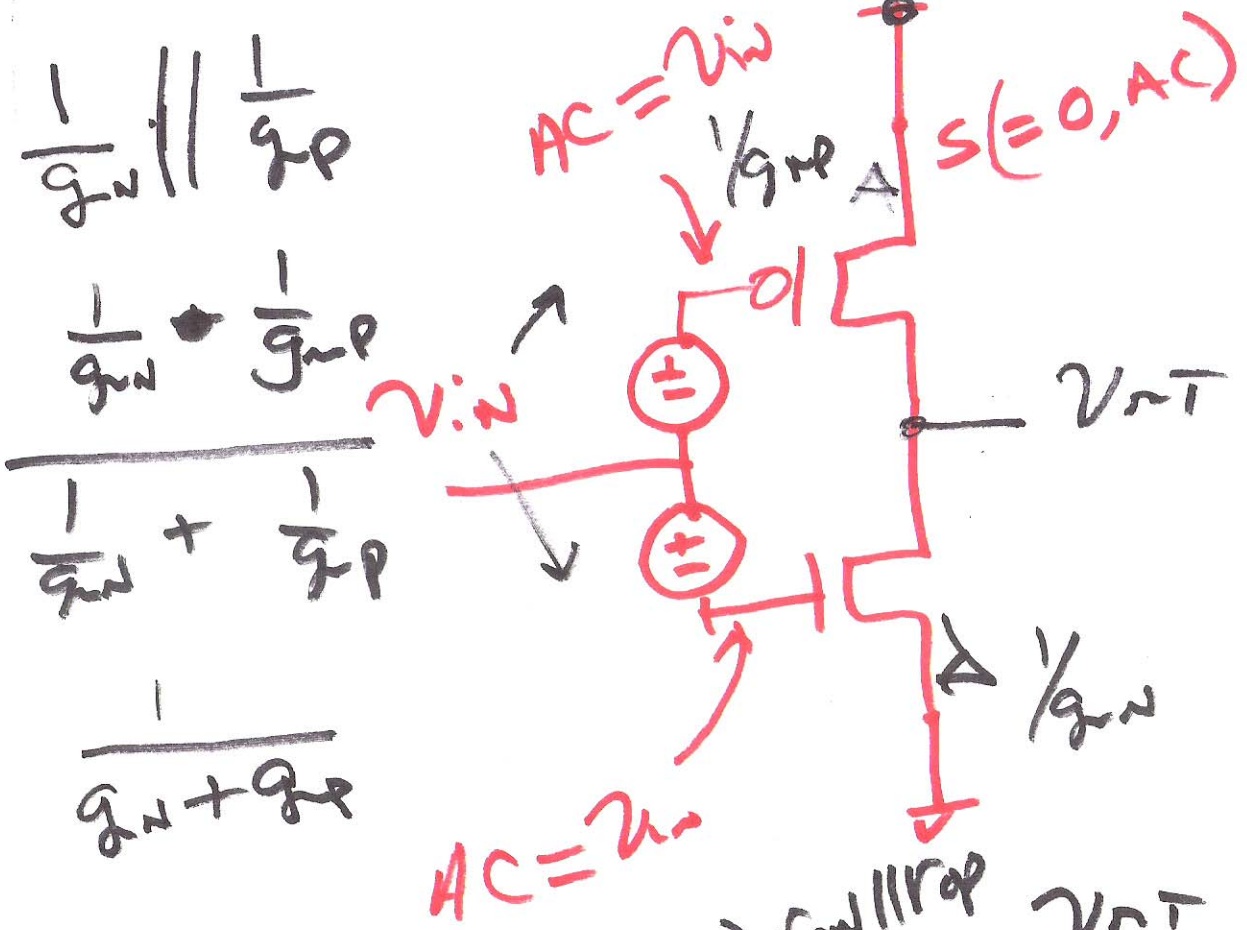

$$v_{out} = -v_{in} (g_p + g_n) r_{on} \parallel r_{op}$$

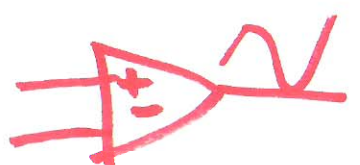
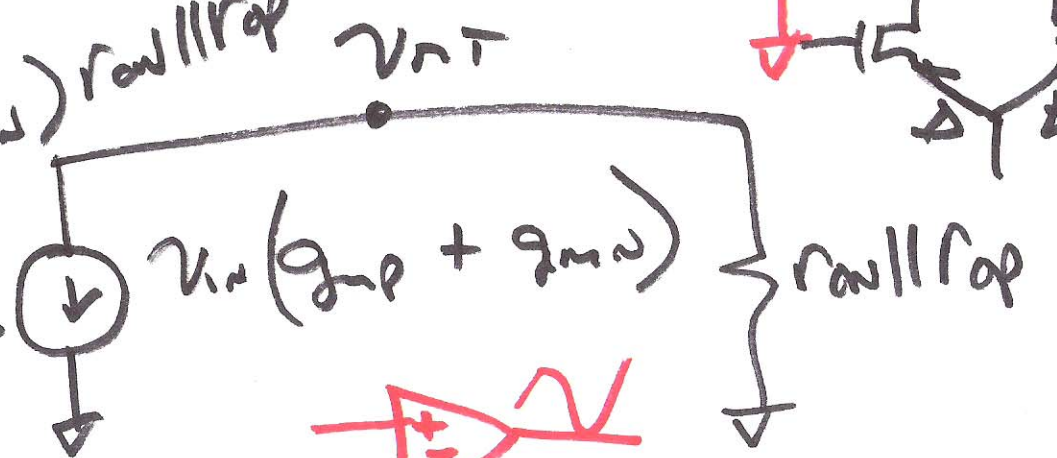
$$\frac{v_{out}}{v_{in}} = - \frac{r_{on} \parallel r_{op}}{g_p + g_n}$$



4)

$$\frac{v_{out}}{v_{in}} = - (g_p + g_n) (r_{on} || r_{op})$$

$$= - \left(\sqrt{\beta_p \cdot 2(I_D + i_d)} + \sqrt{\beta_n \cdot 2(I_D + i_d)} \right) \cdot \left(\frac{1}{\lambda_n (I_D + i_d)} || \frac{1}{\lambda_p (I_D + i_d)} \right)$$

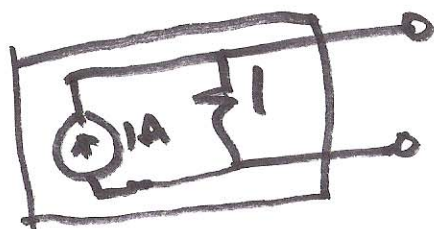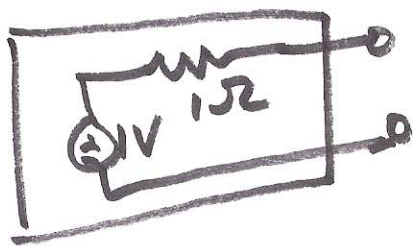

Normally we assume $i_d \ll I_D$
 $i_d + I_D \approx I_D$
 $R_{in} = \frac{v_{DD}/2}{\sqrt{2}}$

5)