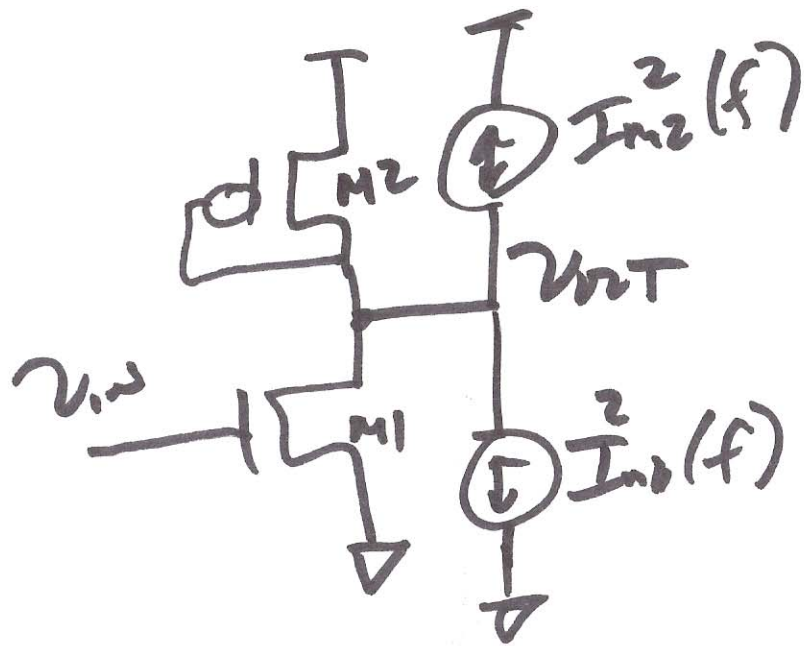


$$I_{n1}^2(f) = \frac{KF \cdot I_D^{AF}}{f \cdot C_{ox} \cdot L \cdot W} + \frac{8KT}{3} \cdot g_m \cdot \frac{A^2}{Hz}$$

Flicker noise

Thermal noise

Fig. 21.14 CS with gate-drain connected load



$$V_{noise}^2(f) = \left(\frac{1}{g_m} \right)^2 \cdot \left(I_{n1}^2(f) + I_{n2}^2(f) \right)$$

$$G_{AIN} = \frac{1/g_{m2}}{1/g_{m1}} = \frac{g_{m1}}{g_{m2}}$$

Input referred noise

$$V_{\text{noise}}^2(f) = \frac{(I_{n1}(f) + I_{n2}(f))^2}{\left(\frac{g_{m1}}{g_{m2}}\right)^2} \left(\frac{1}{g_{m2}}\right)^2$$

Low noise


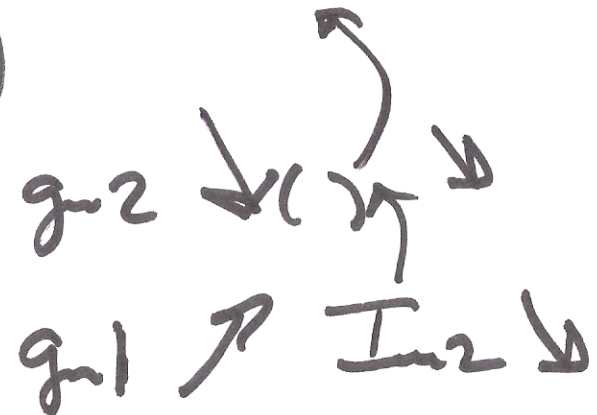


Fig. 21.17

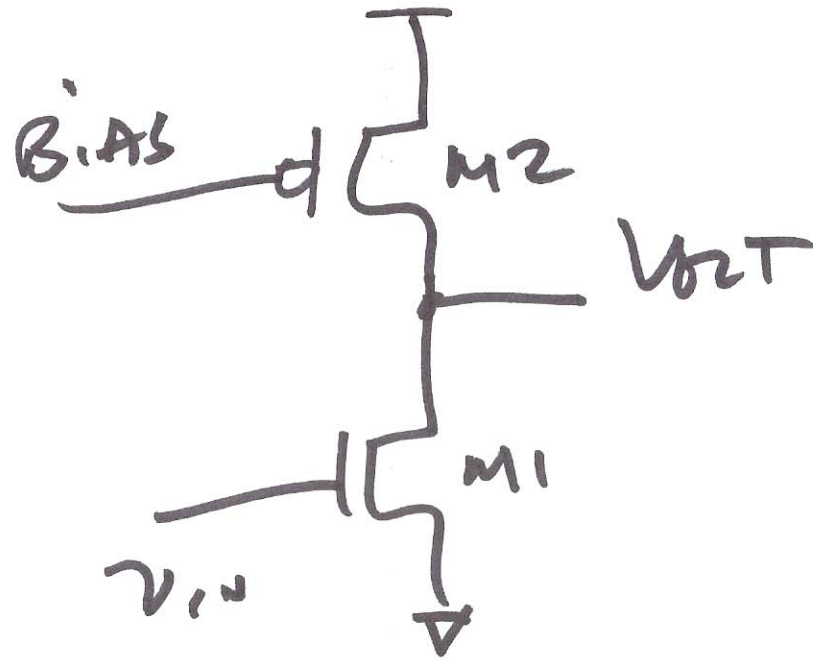

Eq. 21.74

$$V_{NOISE}^2(f) =$$

$$(I_{n1}^2 + I_{n2}^2) (r_{o1} || r_{o2})^2$$


$$A^2 = g_{m1}^2 \cdot (r_{o1} || r_{o2})^2$$

$$V_{NOISE}^2(f) = \frac{I_{n1}^2 + I_{n2}^2}{g_{m1}^2}$$

$g_{m2} \downarrow$ $I_{n2} \downarrow$ $V_{NOISE} \downarrow$
 $g_{m1} \uparrow$ $V_{NOISE} \downarrow$

$134 \mu V$
 $84 \mu V$
 $83 \mu V$
 $g_{m2} \downarrow$
 $g_{m1} \uparrow$

3)

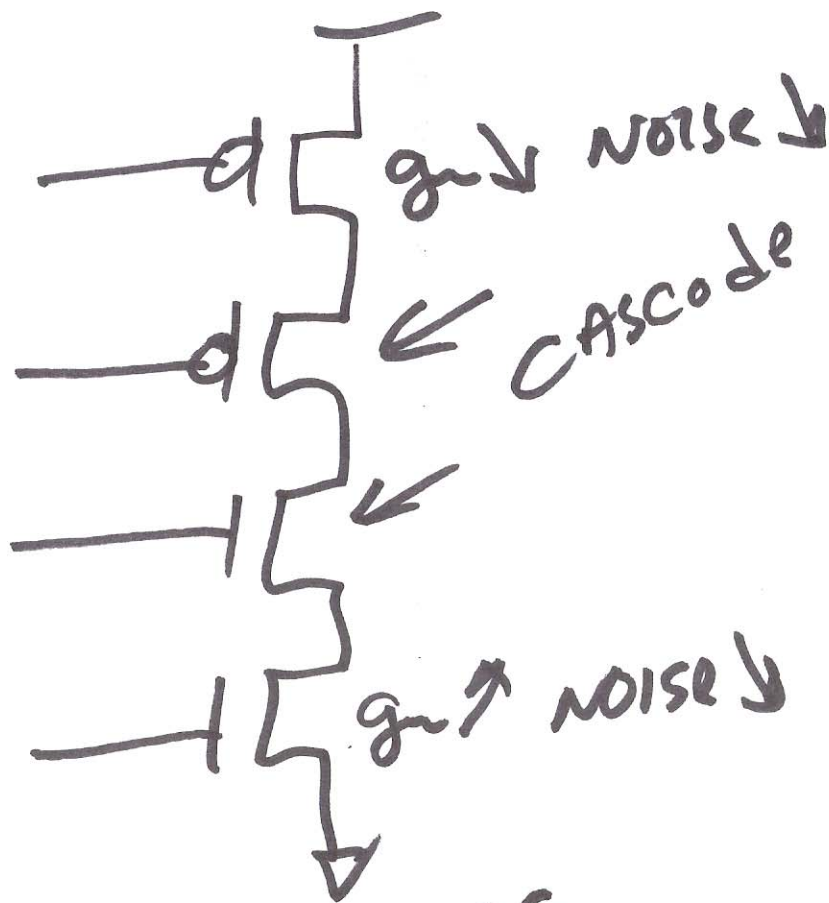


don't contribute much to output noise

same noise performance as CS with current mirror load

Fig. 21.35

$g_{m2} \rightarrow 46 \mu\text{V}$
 $g_{m1} \rightarrow 36 \mu\text{V}$
 $40 \mu\text{V}$
 \uparrow load

Fig 2.44

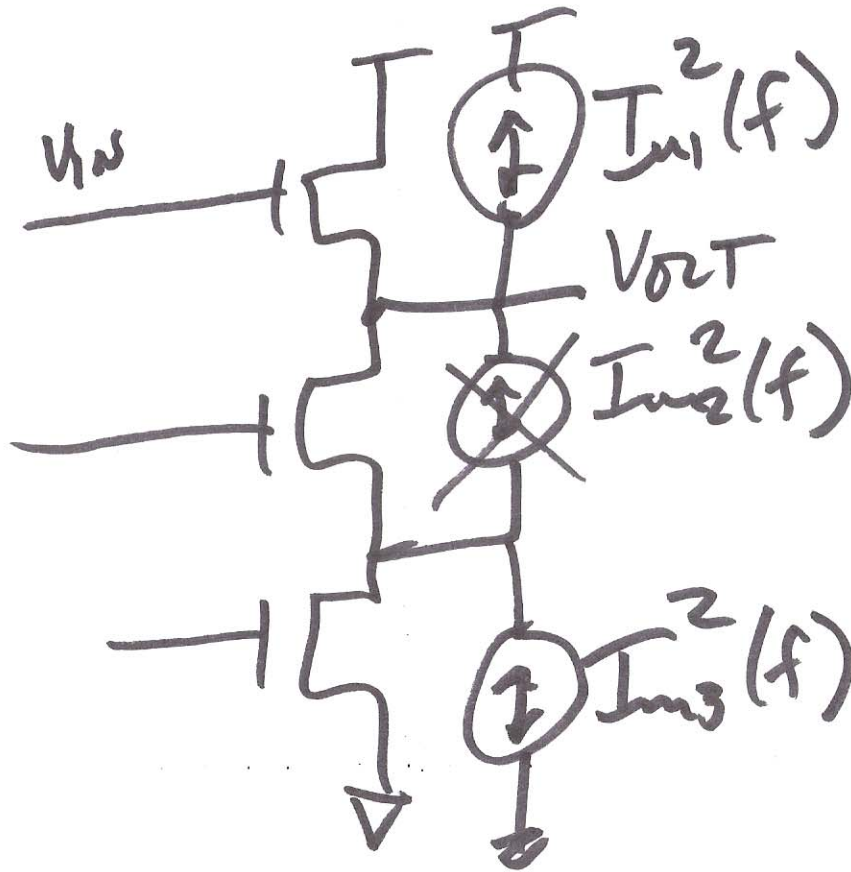

$$V_{out\ noise}^2(f) = \left(I_{n1}^2(f) + I_{n2}^2(f) \right) \cdot \left(\frac{1}{g_{m1}} \parallel R_{out} \right)^2$$

Use large g_{m1}
to reduce
OUTPUT NOISE

5)