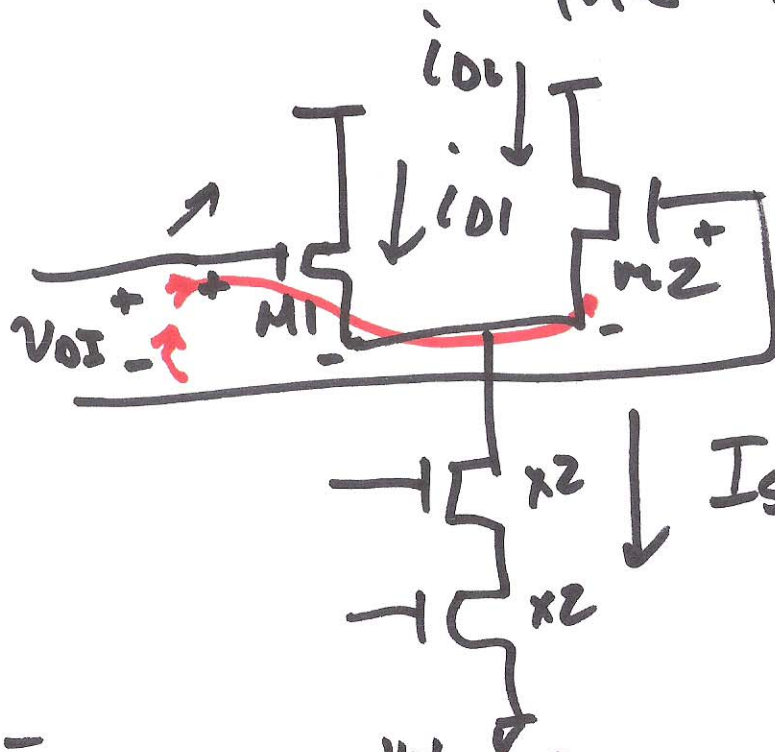


Sec. 22.1

Diff. Amps

the

Source-coupled pair



$$v_{O2} = v_{GS1} - v_{GS2}$$

$$= \sqrt{\frac{2i_{O1}}{\beta_N}} + V_{TN} - \sqrt{\frac{2i_{O2}}{\beta_N}}$$

$$- V_{TN}$$

$$I_{SS} = i_{O1} + i_{O2}$$


$$I_{O1} + i_{d1}$$

$$\sqrt{i_{d1}} = \sqrt{\frac{\beta_N}{2}} \left(\frac{V_{GS} + V_{GS1}}{v_{GS}} - V_{TN} \right)$$

$$v_{OI} = \sqrt{\frac{2}{\beta_N}} \left(\sqrt{i_{d1}} - \sqrt{i_{d2}} \right)$$

$$v_{OI,MAX} = ? \sqrt{\frac{2I_{SS}}{\beta_N}} \text{ MOSedu.com}$$

MAX cur

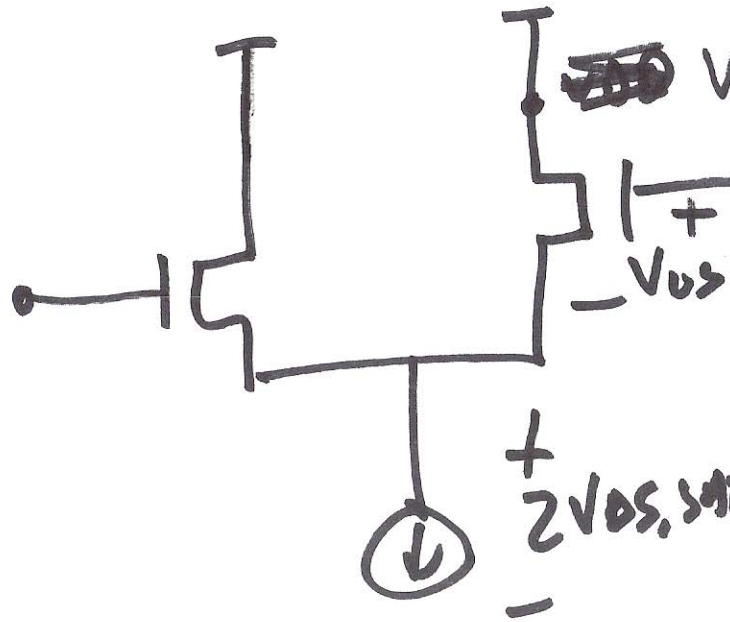

$$V_{DS} \geq V_{GS} - V_{THN}$$


$$V_D \geq V_G - V_{THN}$$

$$V_{DD} \geq V_{cm, I_{MAX}} - V_{THN}$$

$$V_{cm, I_{MAX}} \leq V_{DD} + V_{THN}$$

$$V_{cm, I_{MAX}} \leq V_{DD} - V_{SD, SAT} + V_{THN}$$

2)

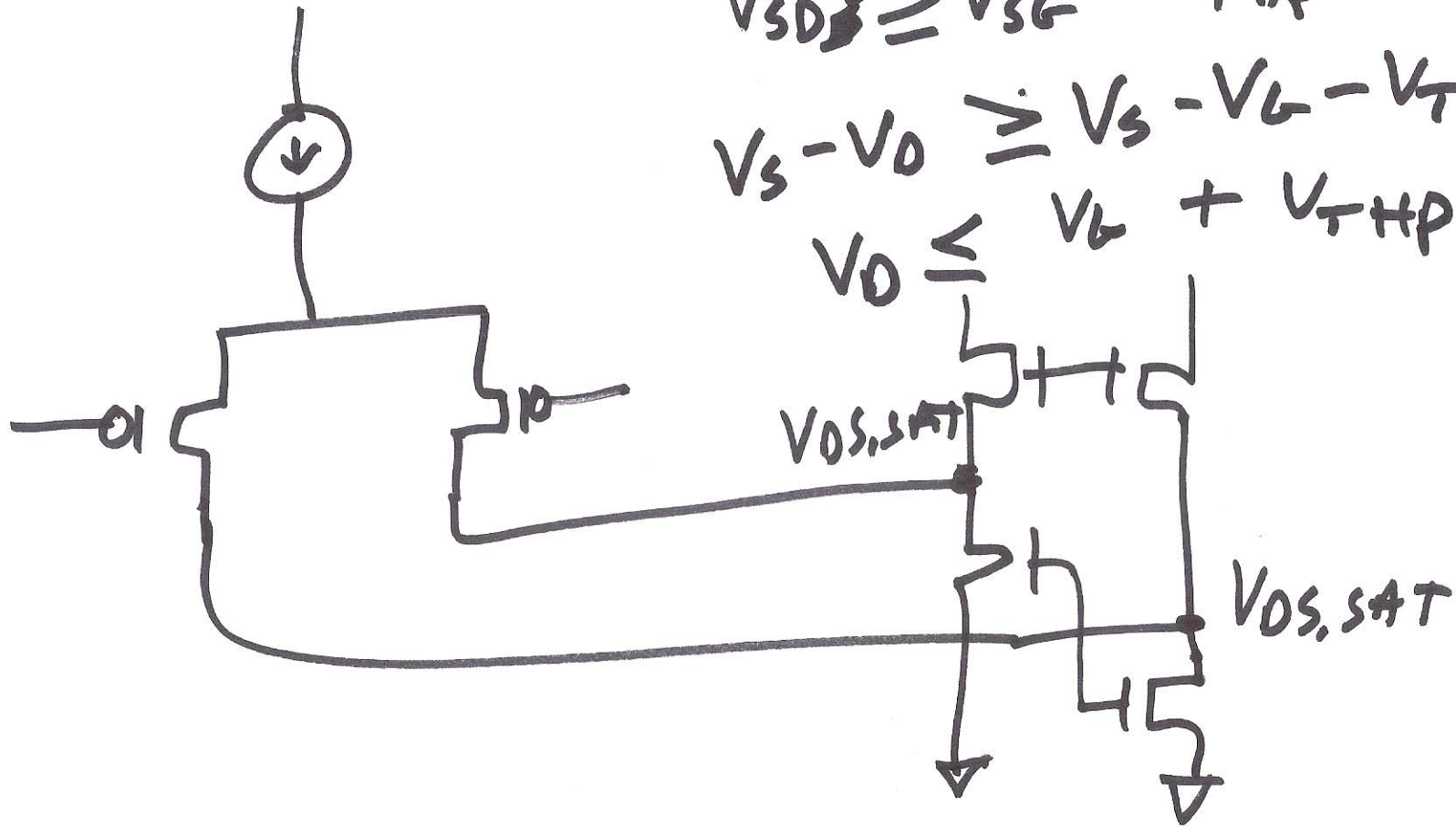


$$V_{SDS} \geq V_{SG} - V_{THP}$$

$$V_S - V_D \geq V_S - V_G - V_{THP}$$

$$V_D \leq V_G + V_{THP}$$

$$V_{DS,SAT} \leq V_{ICM, \min} + V_{THP}$$
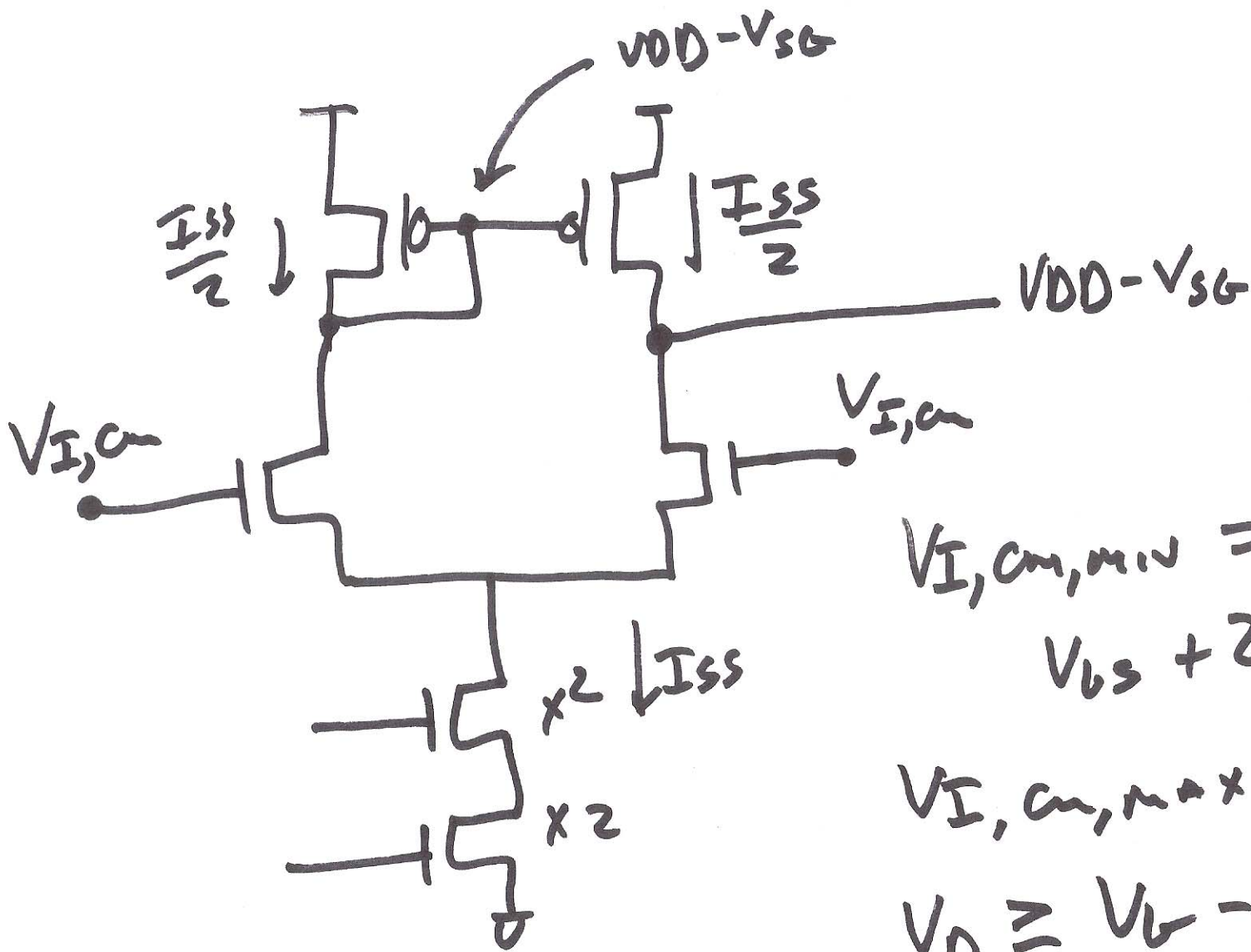
$$V_{ICM, \min} \geq V_{DS,SAT} - V_{THP}$$



$$V_{I,cm,min} = V_{GS} + 2V_{DS,sat}$$

$$V_{I,cm,max} \rightarrow$$

$$V_D \geq V_G - V_{THN}$$


$$V_{I,cm,max} \leq V_{DD} - V_{SG} + V_{THP}$$

$$V_{DD} - V_{SG} \geq V_{I,cm,max} - V_{THN}$$

$$= V_{DD} - V_{DS,sat} - V_{THN} + V_{THP}$$

4)

MIN supply voltage

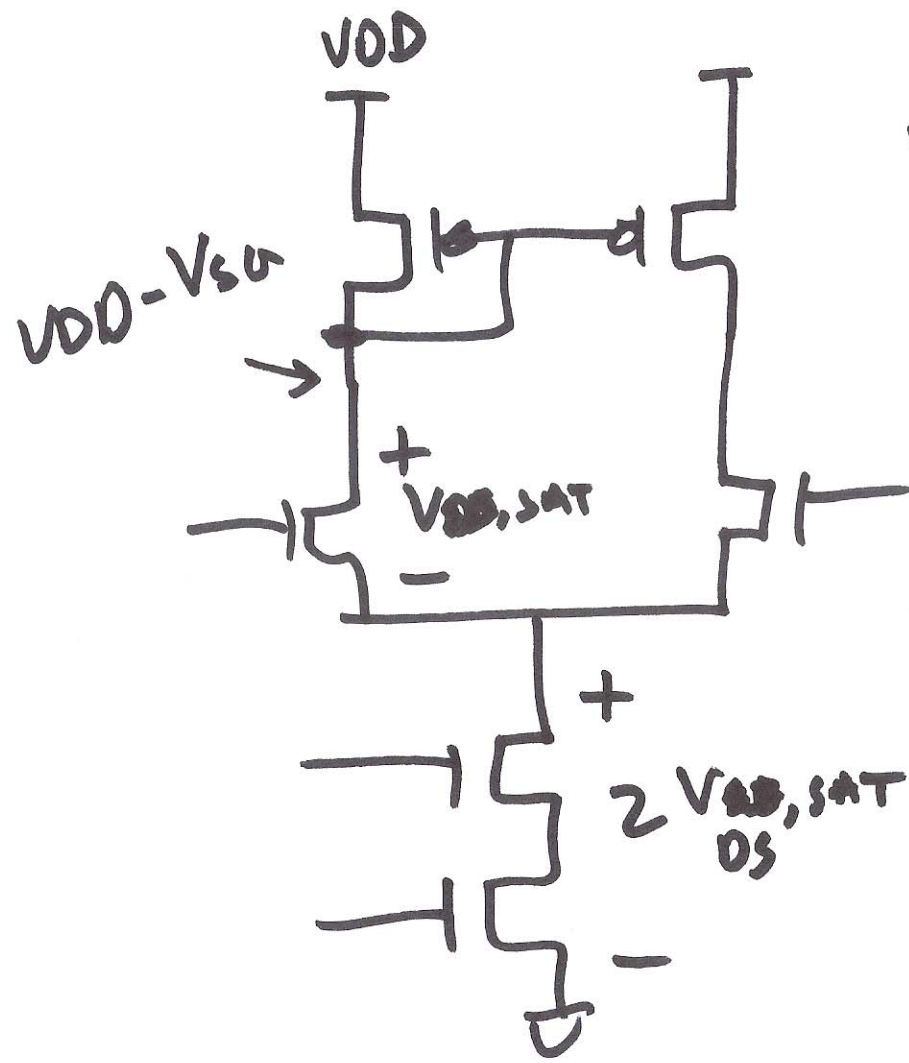


$$VDD_{min} = \cancel{VDD} V_{SG} + 3 V_{DS,SAT}$$

$$1.15 + .75$$

$$\underline{\underline{1.9V}}$$



5)

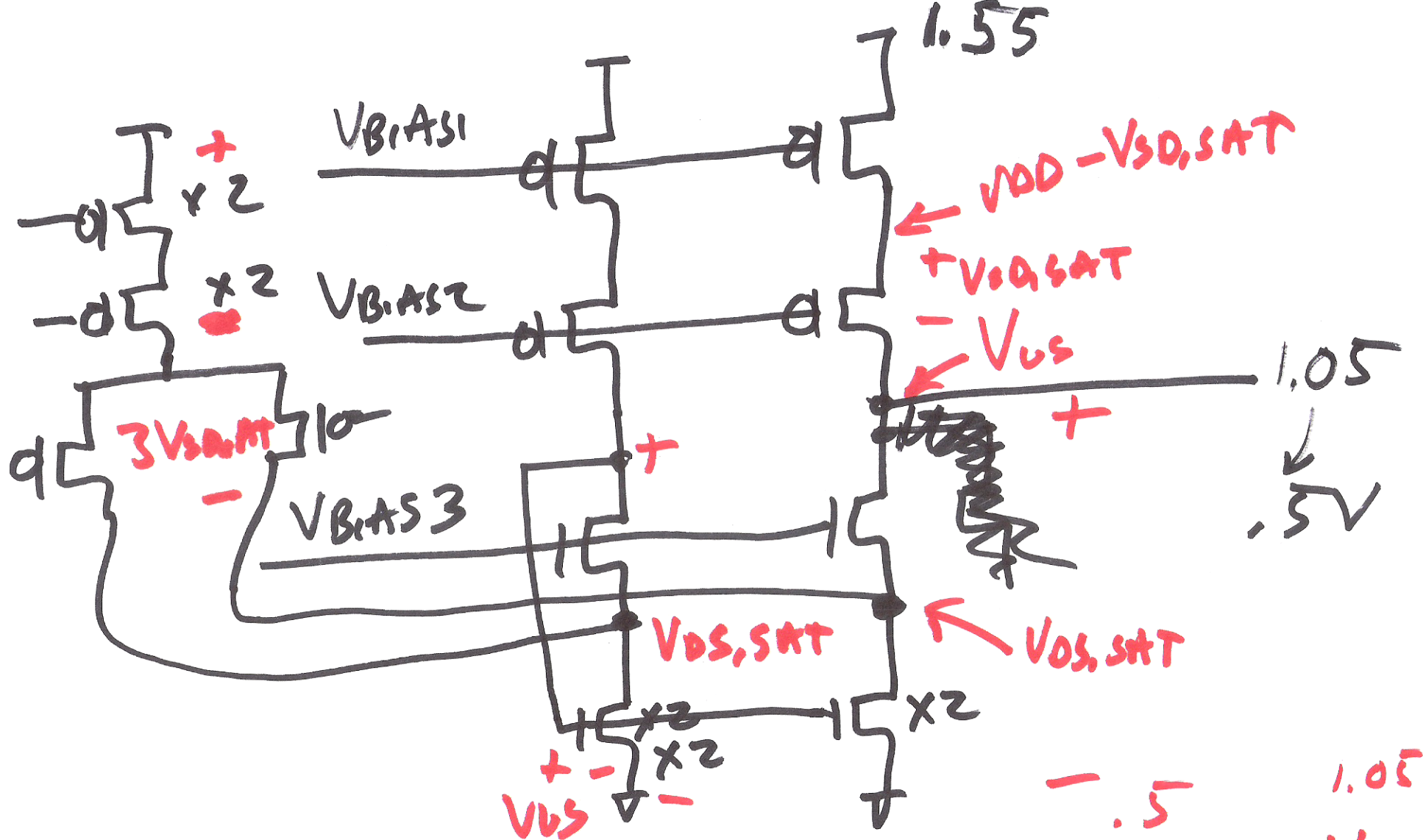

$$\begin{aligned}
 \rightarrow V_{DD_{min}} &= 2V_{SD,SAT} + V_{GS} \\
 &= 1.55
 \end{aligned}$$

6)

AC CKT

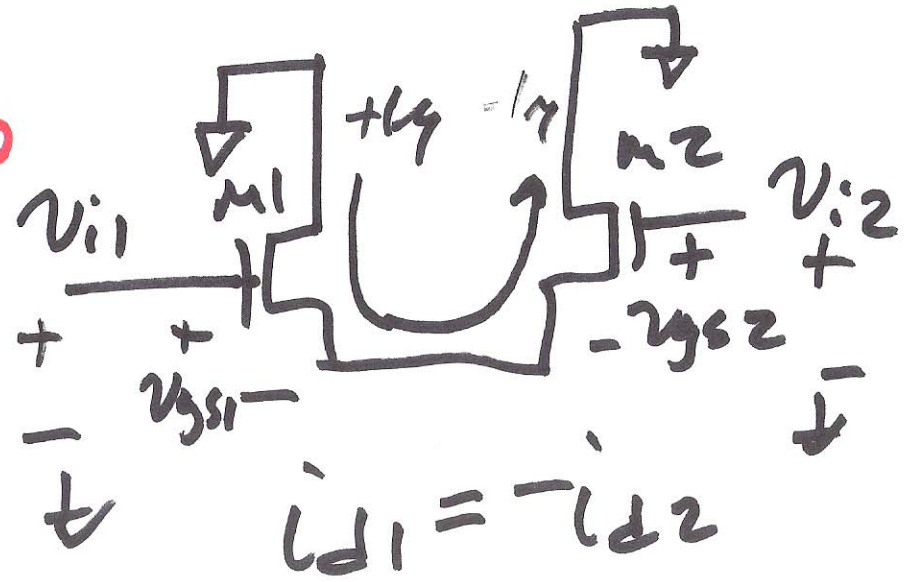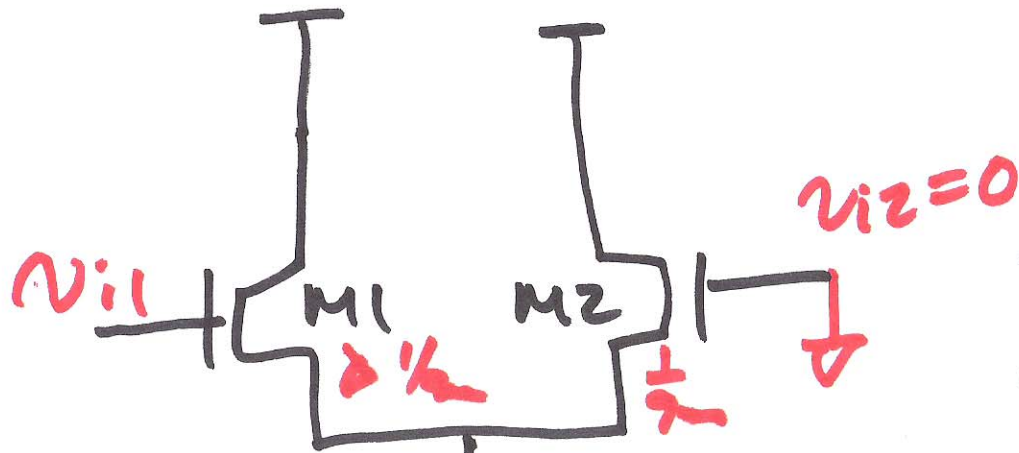


$$v_{i1} - v_{gs1} + v_{gs2} - v_{i2} = 0$$

$$v_{di} = v_{i1} - v_{i2} = v_{gs1} - v_{gs2}$$

$$i_{d1} = \frac{g_m}{2} \cdot v_{di} = \left(\frac{i_{d1}}{g_m} - \frac{i_{d2}}{g_m} \right)$$

$$i_{d1} = \frac{g_m}{2} \cdot v_{i1}$$

TABLE 9.1

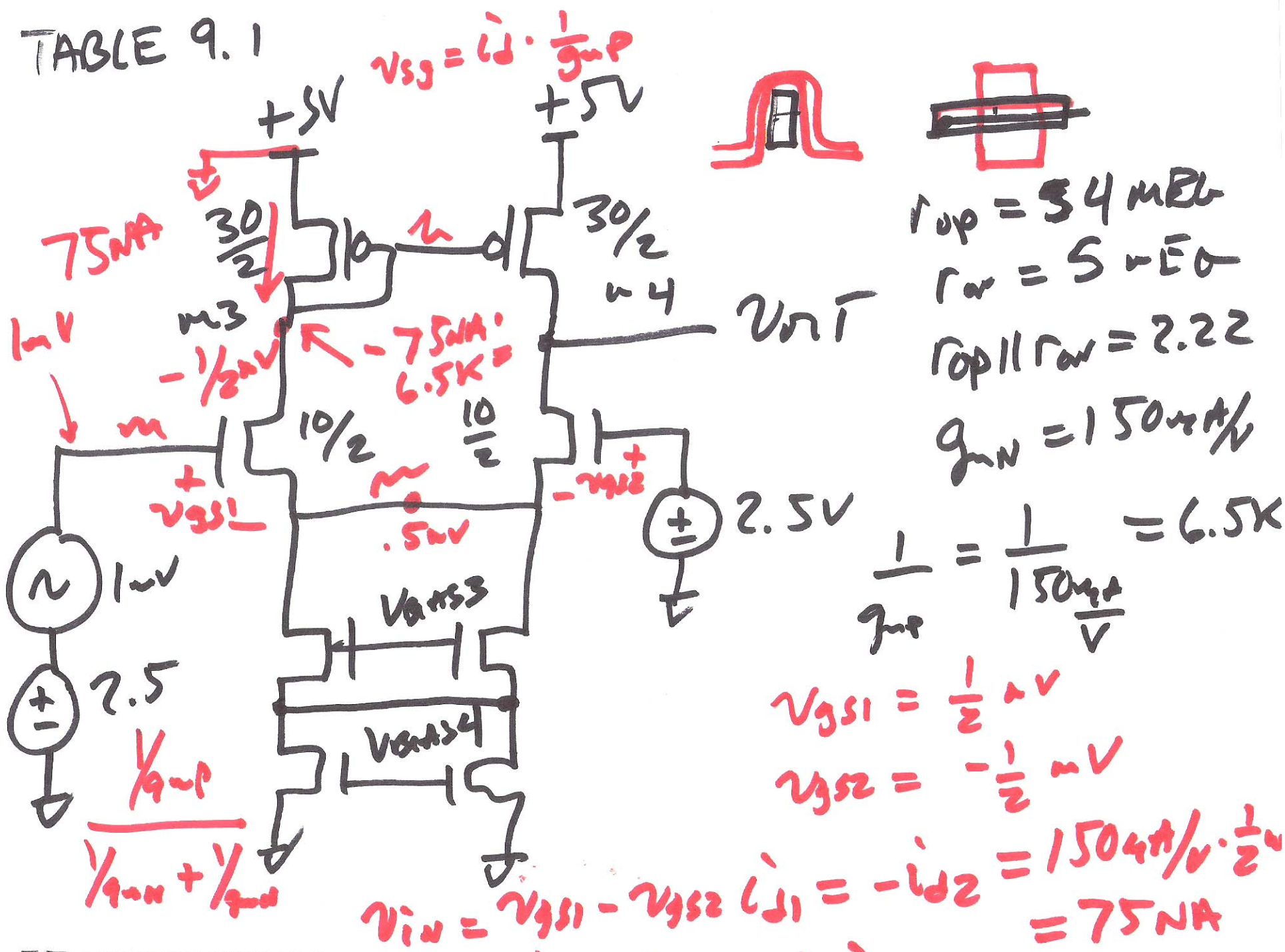


8)

$$\frac{v_{out}}{v_{in}} = \frac{r_{op} || r_{on} \cdot Z_{i2}}{\frac{Z_{i1}}{g_{m2}} \cdot \beta} = \frac{r_{op} || r_{on}}{\beta g_{m2}}$$

$$g_{m2} r_{op} || r_{on}$$

$$v_{out} = Z_{i2} \cdot r_{op} || r_{on}$$

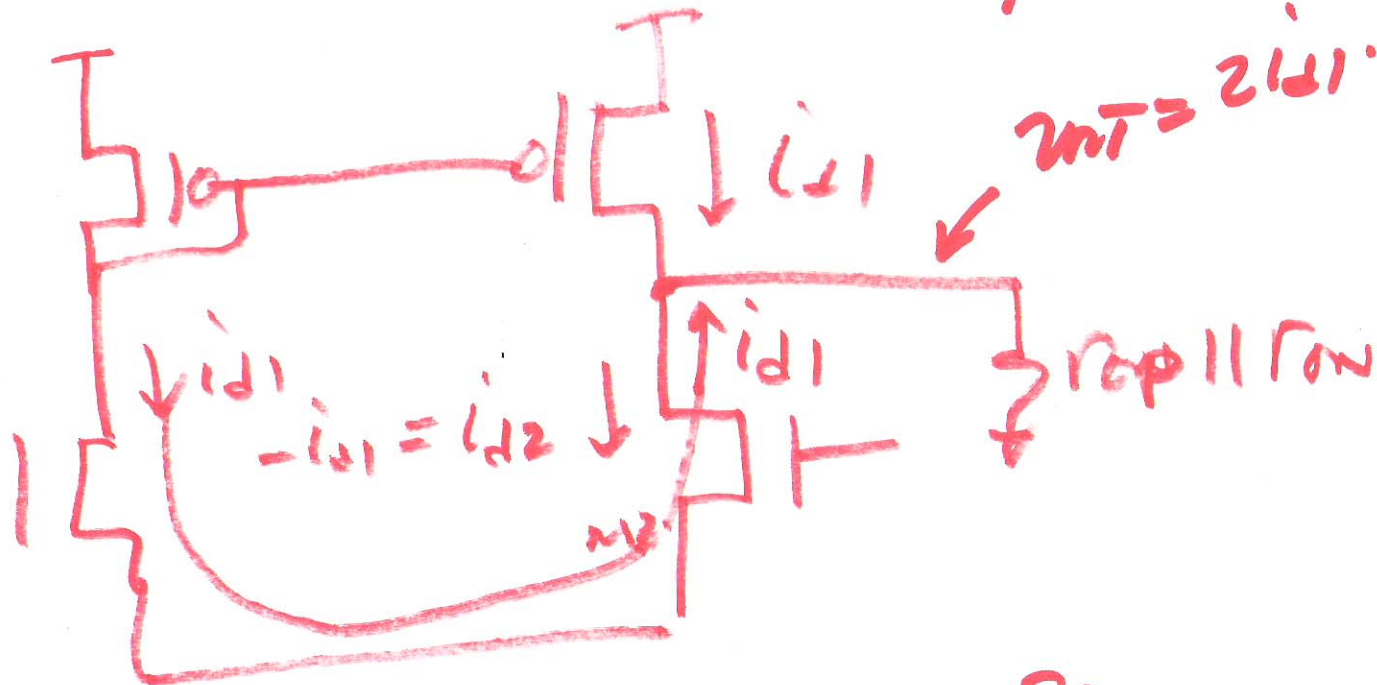

$$150\mu \cdot 2.22 \text{ mS}$$

$$\frac{v_{out}}{v_{in}} = 330$$

$$1 \text{ mV} \quad v_{out} = 330 \text{ mV}$$

a)