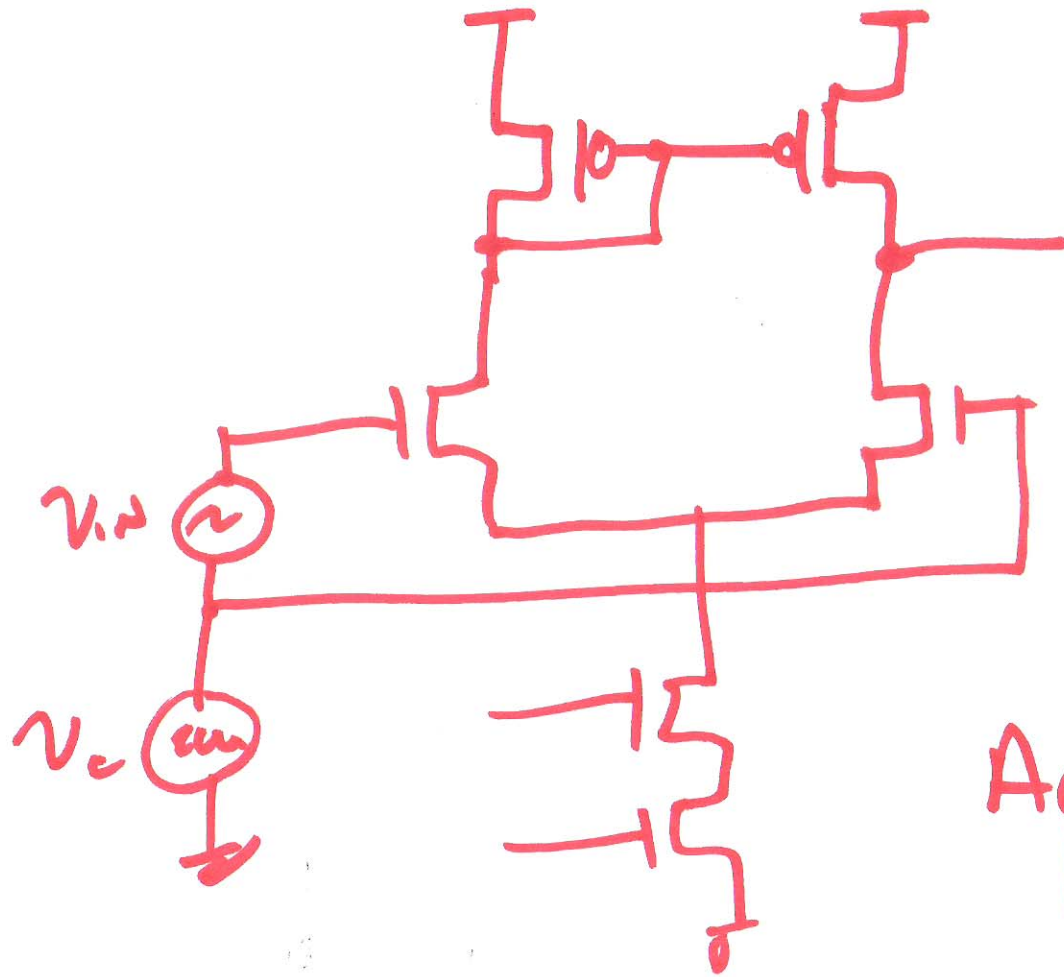


# SEC. 22.1.3 CMRR



$$v_{out} = A_d v_{dm}$$


$$\frac{v_{out}}{v_{dm}} = g_m r_{out} r_{op}$$

ideally

$$A_c = \frac{v_{out}}{v_c} = 0$$

Common-mode gain

1)

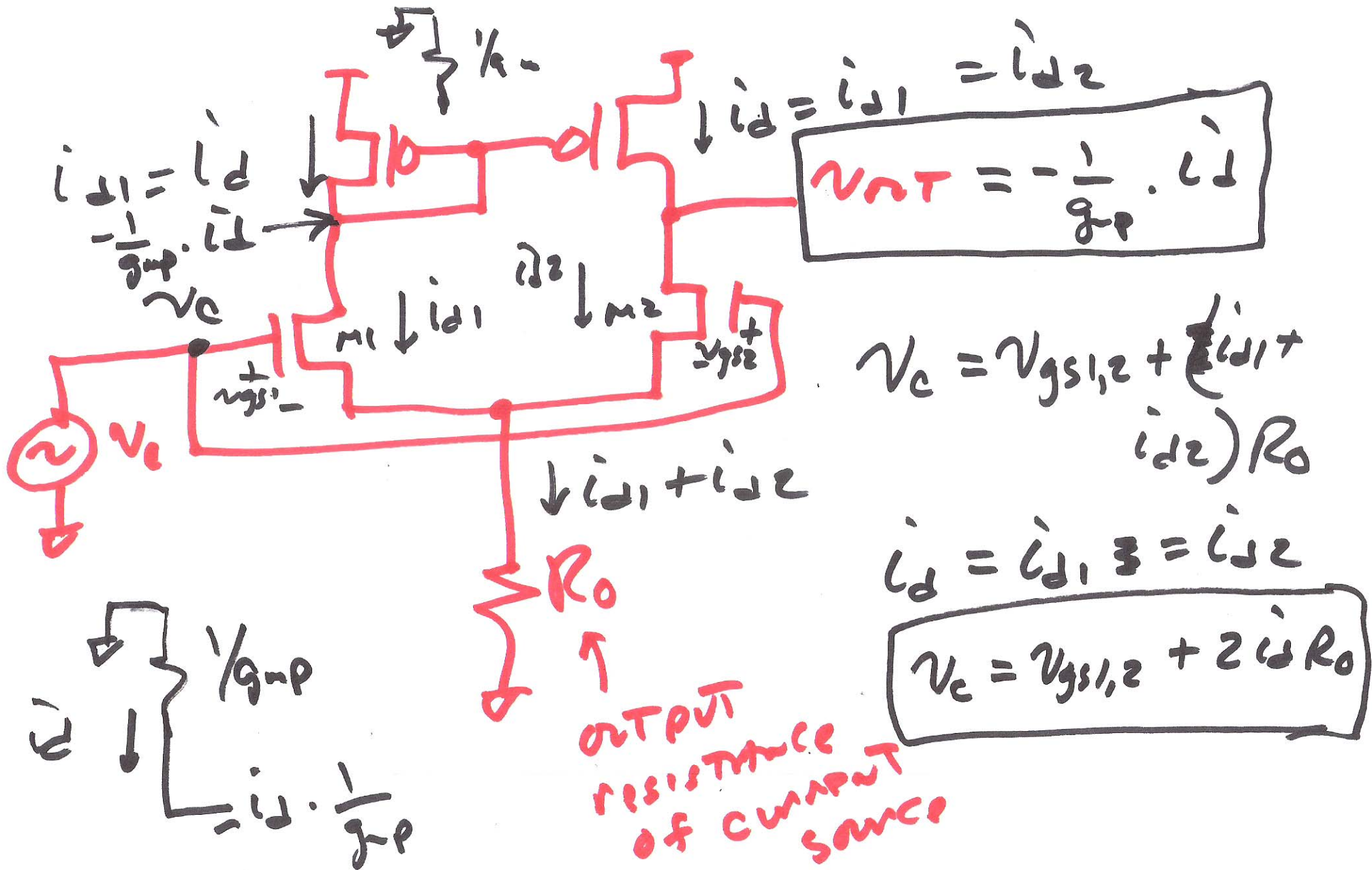

$$v_{NT} = -\frac{1}{g_p} \cdot i_d$$

$$v_c = v_{gs1,2} + (i_{d1} + i_{d2})R_o$$

$$i_d = i_{d1} = i_{d2}$$

$$v_c = v_{gs1,2} + 2i_d R_o$$


OUTPUT RESISTANCE OF CURRENT SOURCE

$$v = IR \Rightarrow v = IR$$

2)

$$|A_c| = \left| \frac{v_{out}}{v_c} \right| = \frac{\frac{1}{g_p} \cdot i_d}{v_{gs1,2} + 2\omega R_o}$$

$$v_{gs} = \frac{i_c}{g_{mN}}$$

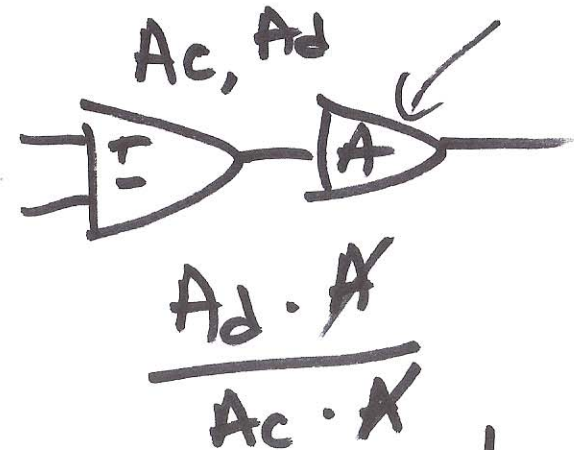


$$|A_c| = \frac{\frac{1}{g_p}}{\frac{1}{g_n} + 2R_o} \approx \frac{1}{2g_p \cdot R_o}$$


$$CMRR = 20 \log \frac{A_d}{A_c}$$

$$= 20 \log \frac{g_{mN} r_{oN} || R_{op}}{\frac{1}{2g_p R_o}}$$

3)

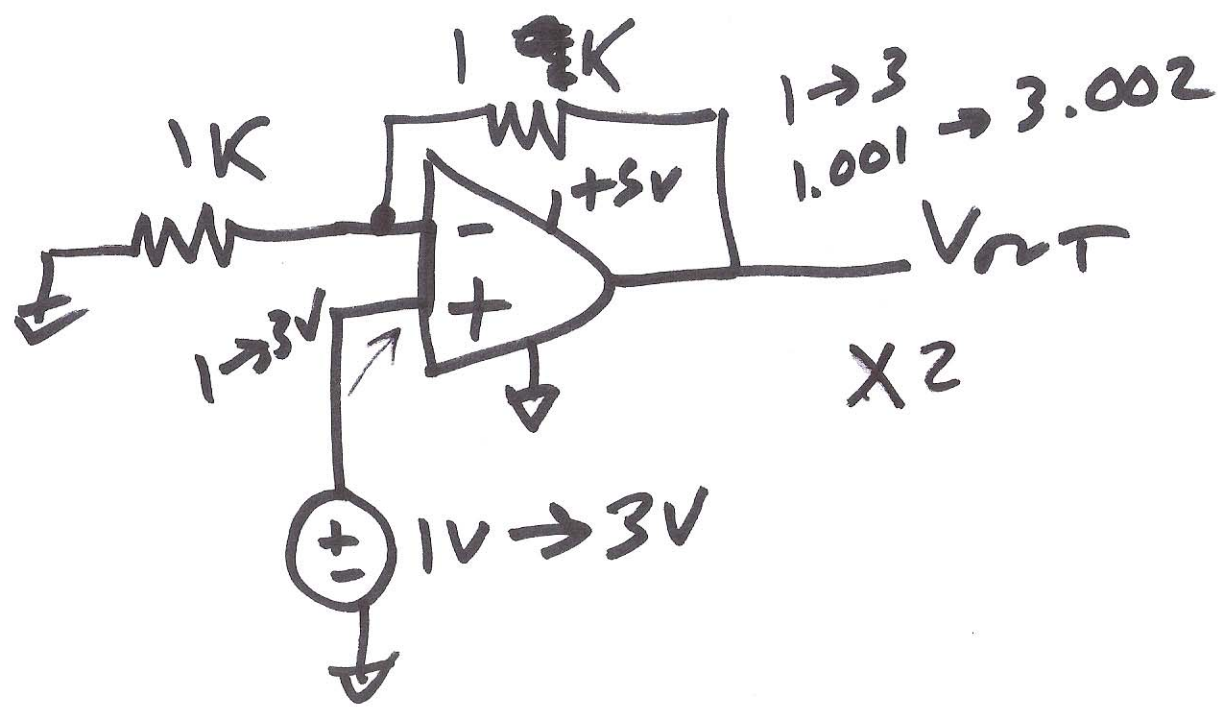

4)

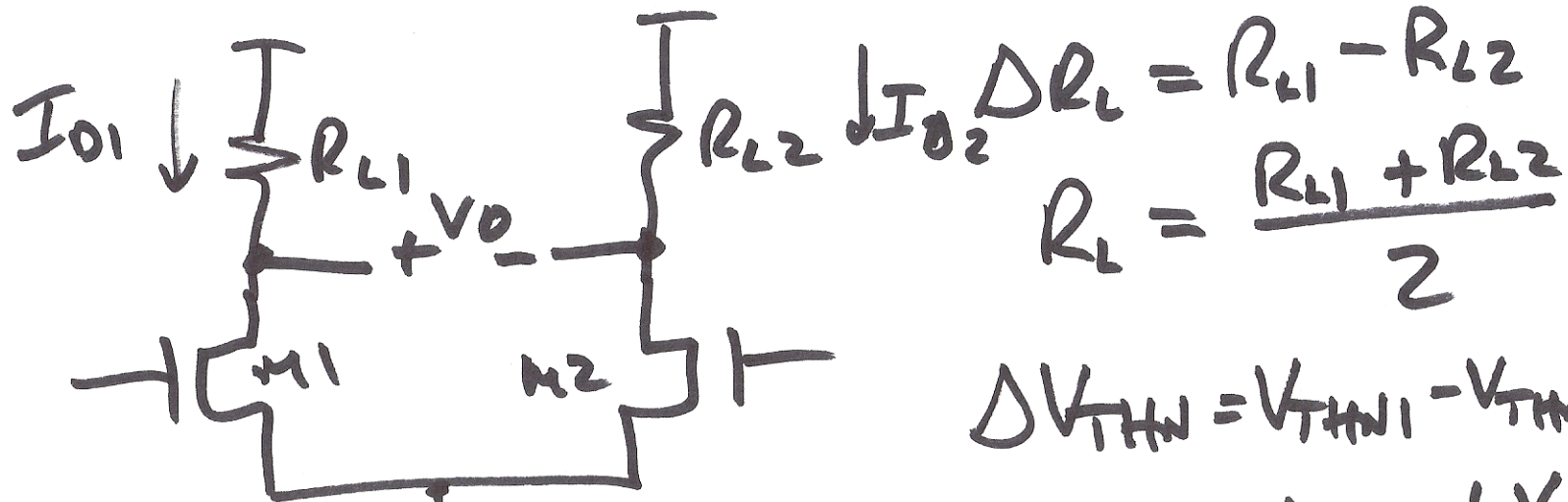

$$\Delta R_L = R_{L1} - R_{L2}$$

$$R_L = \frac{R_{L1} + R_{L2}}{2}$$

$$\Delta V_{THN} = V_{THN1} - V_{THN2}$$

$$V_{THN} = \frac{V_{THN1} + V_{THN2}}{2}$$

$$\Delta \frac{W}{L} = \frac{W}{L}_1 - \frac{W}{L}_2$$

$$\frac{W}{L} = \frac{\frac{W}{L}_1 + \frac{W}{L}_2}{2}$$

$$V_{OS} = V_{GS1} - V_{GS2}$$


GET EQ. (28.29)

$$V_O = V_{DD} - I_{O1} \cdot R_{L1} - (V_{DD} - I_{O2} R_{L2}) \frac{W}{L} = \frac{\frac{W}{L}_1 + \frac{W}{L}_2}{2}$$


$$I_{O1} = \frac{K_{PN}}{2} \frac{W}{L}_1 (V_{GS1} - V_{THN1})^2$$

$$I_{O2} = \frac{K_{PN}}{2} \frac{W}{L}_2 (V_{GS2} - V_{THN2})^2$$

5)

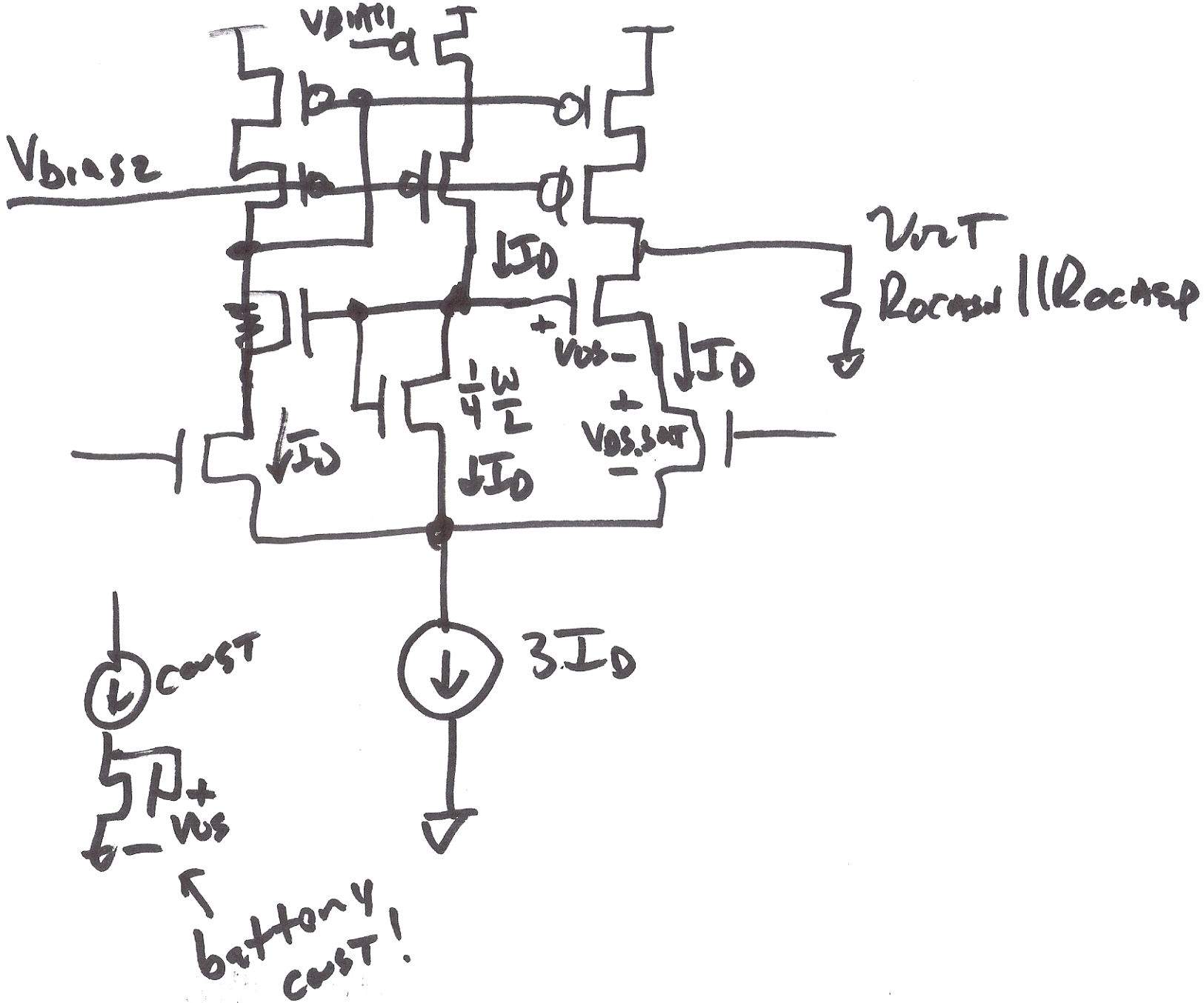


6)

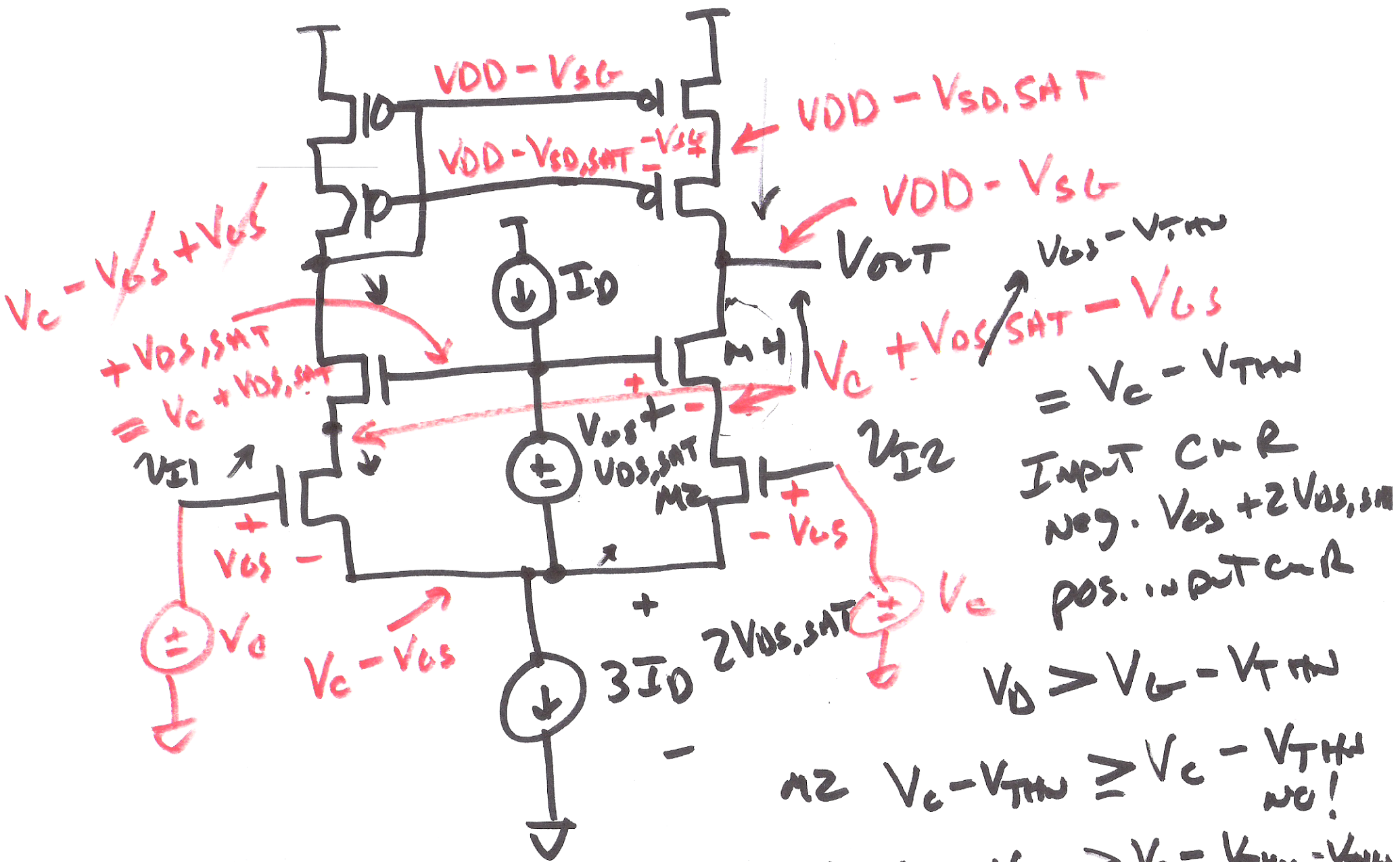

$V_{GS} - V_{THN}$   
 $= V_c - V_{THN}$   
 Input current  
 neg.  $V_{OS} + 2V_{OS,SAT}$   
 pos. input current

$V_D \geq V_G - V_{THN}$   
 $M2 \quad V_c - V_{THN} \geq V_c - V_{THN}$   
 no!  
 $M4 \quad V_{DD} - V_{SG} > V_c - V_{THN} - V_{THN}$   
 $V_c < V_{DD} - V_{SG} + 2V_{THN}$   
 $V_c < 4.65$

7)

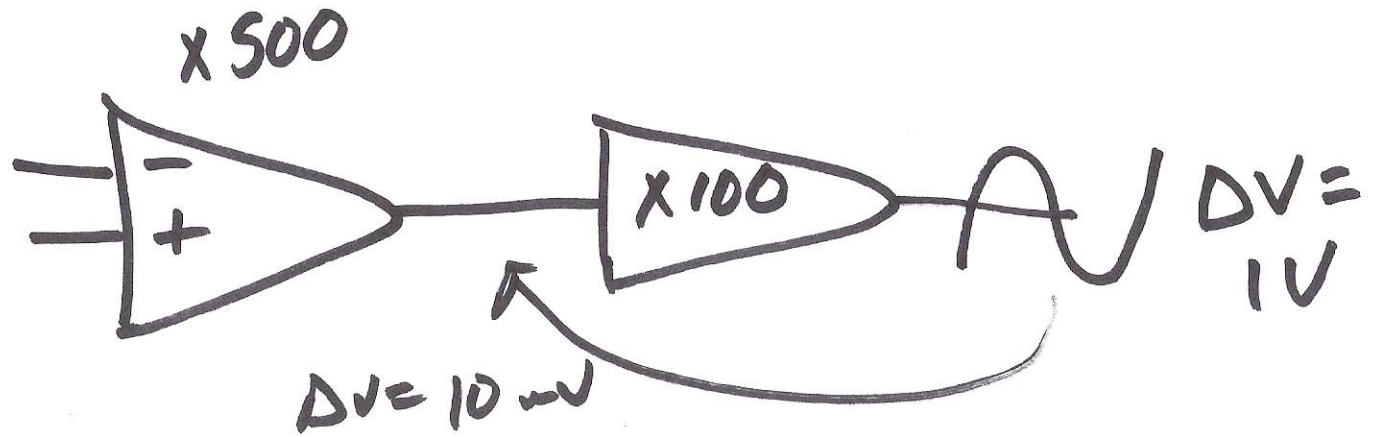


OUTPUT max

$$V_{DD} - 2V_{SD, SAT}$$

OUTPUT min

$$V_C - V_{THN} + V_{DS, SAT}$$



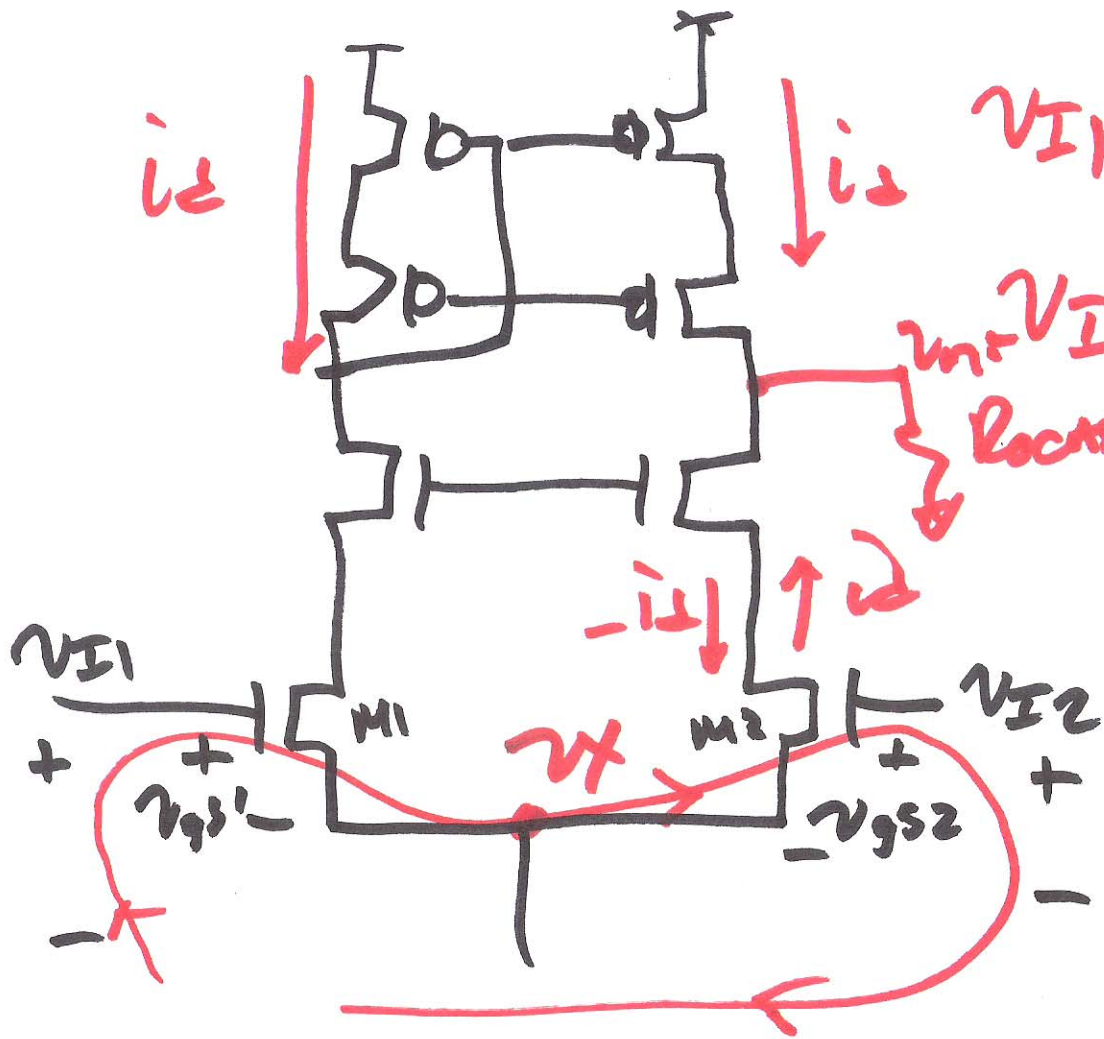

$$v_{I1} - v_{gs1} + v_{gs2} - v_{I2} = 0$$

$$v_{I1} - v_{I2} = v_{gs1} - v_{gs2}$$

$$R_{ocsn} || R_{ocsp} = \frac{i_{D1}}{g_m} - \frac{i_{D2}}{g_m}$$

$$i_{D1} = -i_{D2} = i_D$$

$$v_{I1} - v_{I2} = \frac{2}{g_m} \cdot i_D$$

$$i_D = \frac{g_m}{2} (v_{I1} - v_{I2})$$

$$v_{IT} = 2i_D \cdot R_{ocsn} || R_{ocsp}$$

$$\frac{v_{IT}}{v_{ID}} = g_m R_{ocsn} || R_{ocsp} \quad v_{I1} = 1 \mu V \quad v_{I2} = 0$$

$$v_x = \frac{1}{2} \mu V$$

$$v_{gs1} = \frac{1}{2} \mu V$$

$$v_{gs2} = -\frac{1}{2} \mu V$$

9)