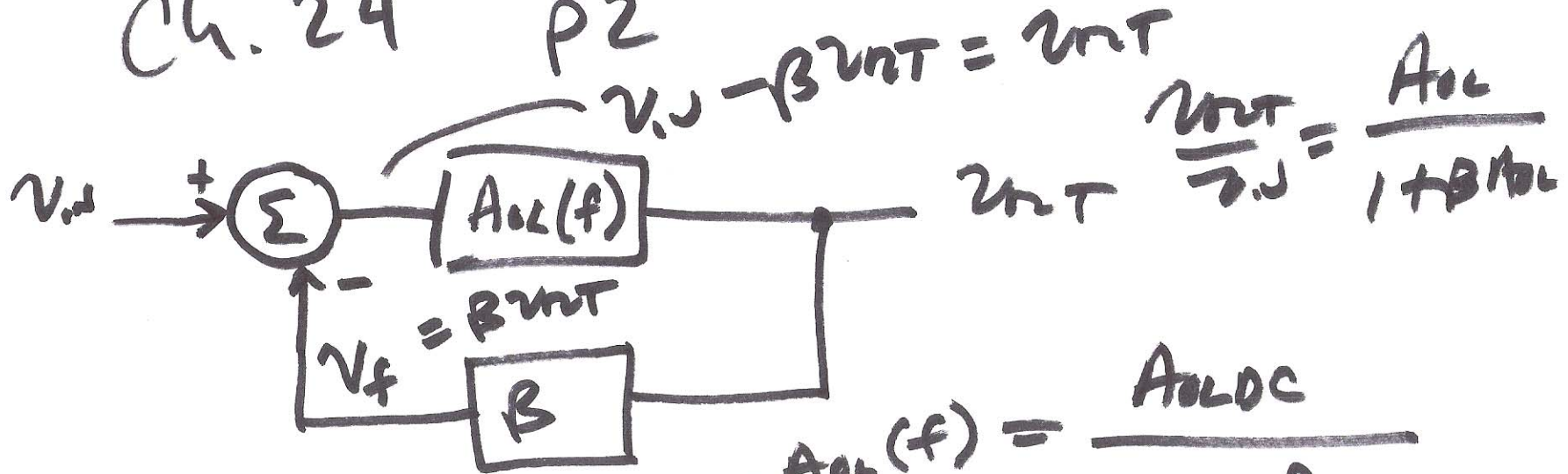



Ch. 24

P2



$$A_{OL}(f) = \frac{A_{OLDC}}{1 + j \frac{f}{f_{3dB}}}$$

$R_1 = 1k$
 $R_2 = 9k$
 $\beta = 0.1$

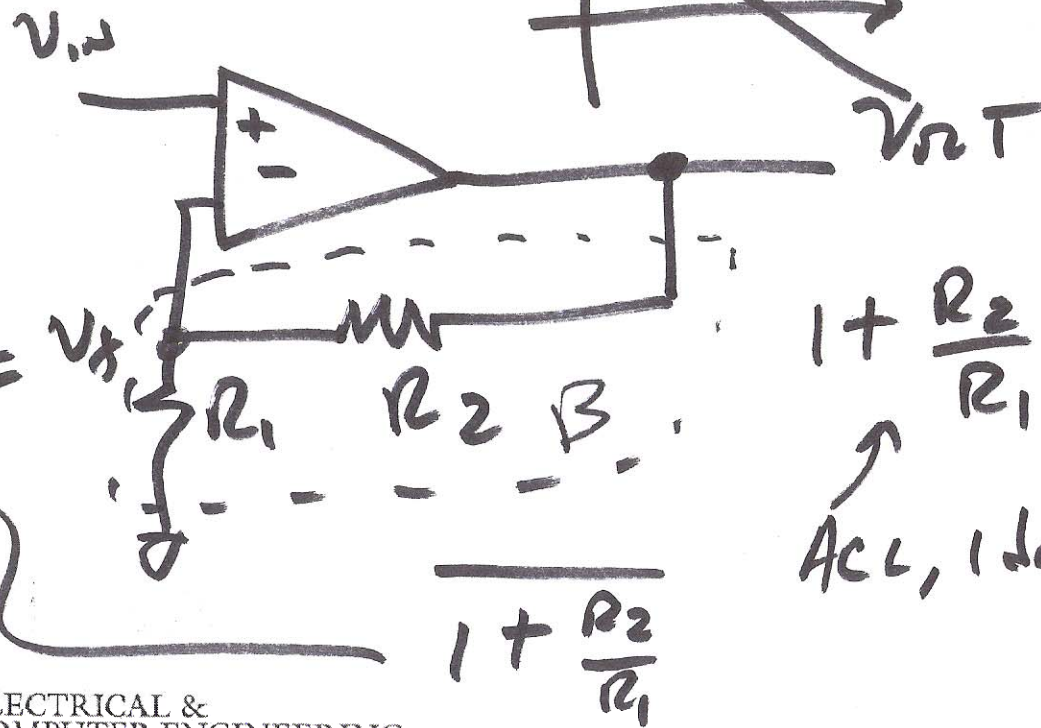

$$\beta = \frac{R_1}{R_1 + R_2}$$

$1 + \frac{R_2}{R_1}$
 $A_{CL, ideal}$

tvp.
 $A_{OLDC} = 10^3$
 $f_{3dB} = 1kHz$

1)

$$A_{CL}(f) = \frac{A_{OL}(f)}{1 + \beta A_{OL}(f)}$$

β becomes unstable when

$$\beta = 0.1 \rightarrow A_{CL}|_{ideal} = 10 \quad \beta A_{OL}(f) = -1$$

$$A_{CL} = \frac{1}{\frac{1}{A_{OL}} + \beta}$$

$A_{OL} \rightarrow \infty$ (ideal)

$$A_{CL} = \frac{1}{\beta}$$

$$|\beta A_{OL}(f)| = 1$$



$\beta = 1$
 $|A_{OL}| = 1$
 $\beta = 0.1, A_{CL} = 10$
 $|A_{OL}| = 10$

$$\angle \beta A_{OL}(f) = 180^\circ$$

$\beta = 1$ (worst case)

$$|A_{OL}(f)| = 1$$

$$\angle A_{OL}(f) = 180^\circ$$

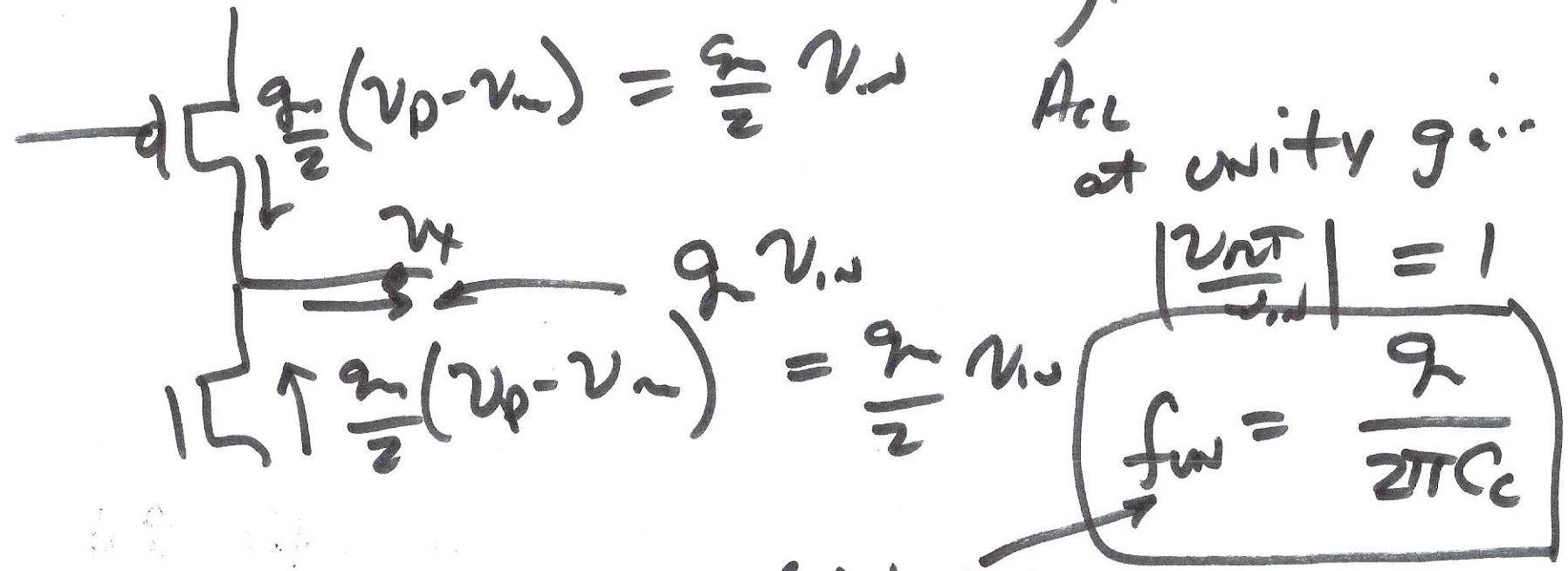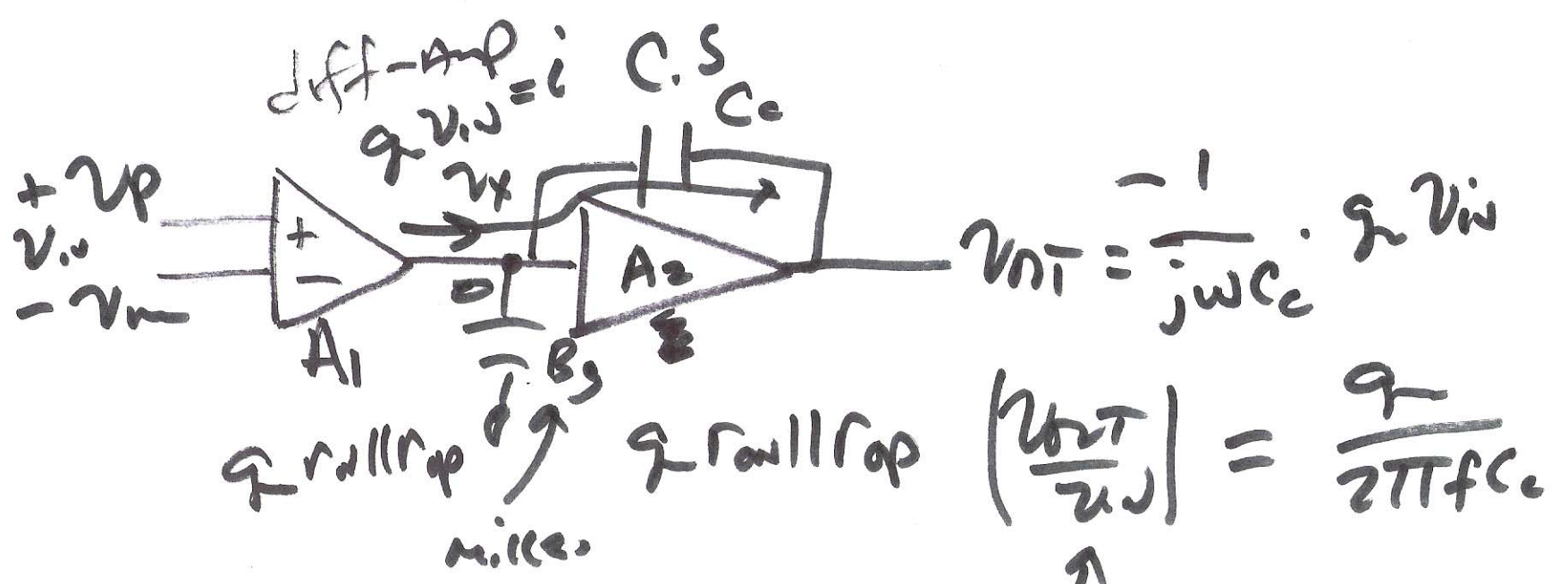

3)

$$A_{OLDC} = 1,000$$

$$f_{BW} = 10^7 \text{ Hz} = A_{CL} \cdot BW$$

$$A_{CL} = 1, \quad BW = 10 \text{ MHz}$$

$$A_{CL} = 10, \quad BW = 1 \text{ MHz}$$

$$A_{CL} = 100, \quad BW = 100 \text{ kHz}$$

$$A_{CL} = 1 \text{ K}, \quad BW = 10 \text{ K}$$

$$A_{CL} = 10 \text{ K}, \quad BW = 1 \text{ K}$$

$$A_{CL}(f) = \frac{1,000}{1 + j \frac{f}{10 \text{ K}}}$$

4)

$$A_{CL} = 10, \beta = 0.1$$


$$A_{CL} = \frac{A_{OL}}{1 + \beta A_{OL}}, \quad A_{OL} = \frac{10^3}{1 + j \frac{f}{10^4}}$$

$$= \frac{10^3}{1 + j \frac{f}{10^4} + \frac{1}{10} \cdot 10^3}$$

$$= \frac{10^3}{101 + j \frac{f}{10^4}} \cdot \frac{1}{100}$$


$$A_{CL} = \frac{10}{1 + j \frac{f}{10^6}}$$

5)

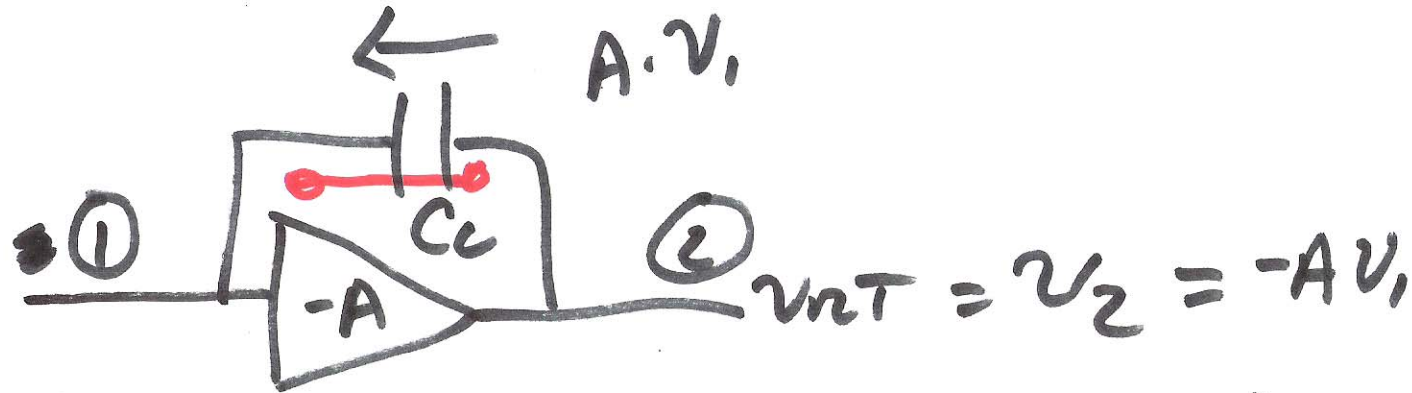


$$\frac{v_2 - v_1}{1/j\omega C_c} = \frac{-v_1 (A+1)}{1/j\omega C_c}$$

$$= \frac{-v_1}{j\omega C_c (1+A)}$$

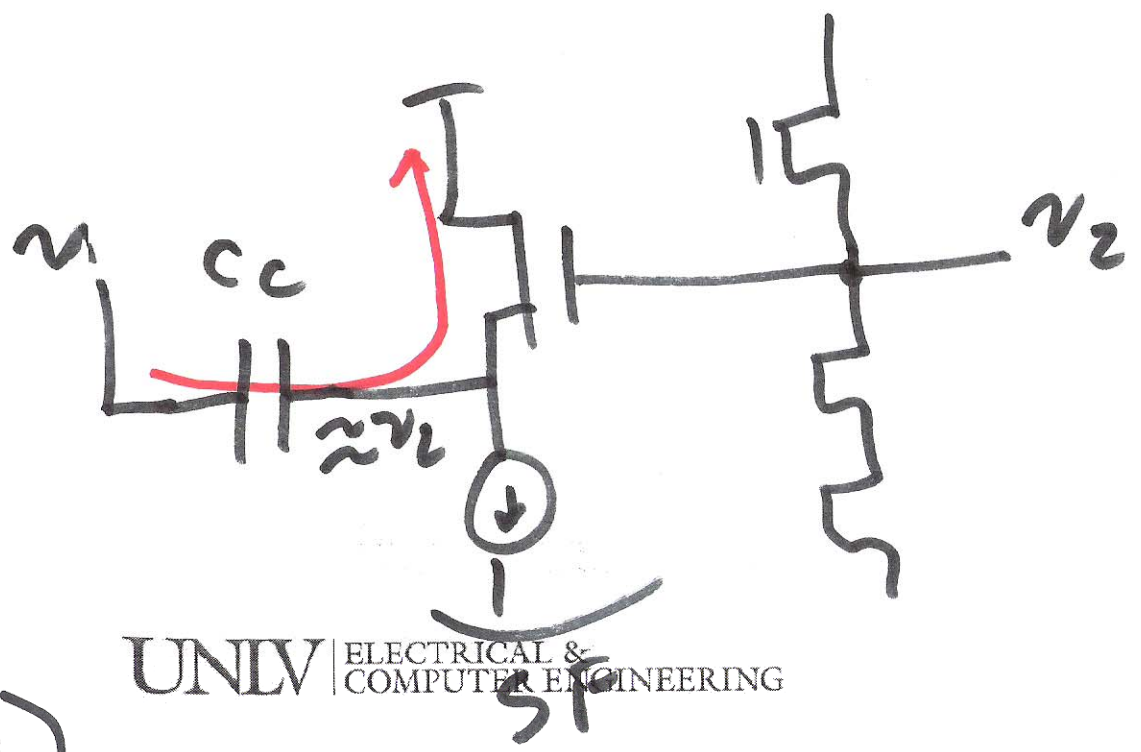

6)

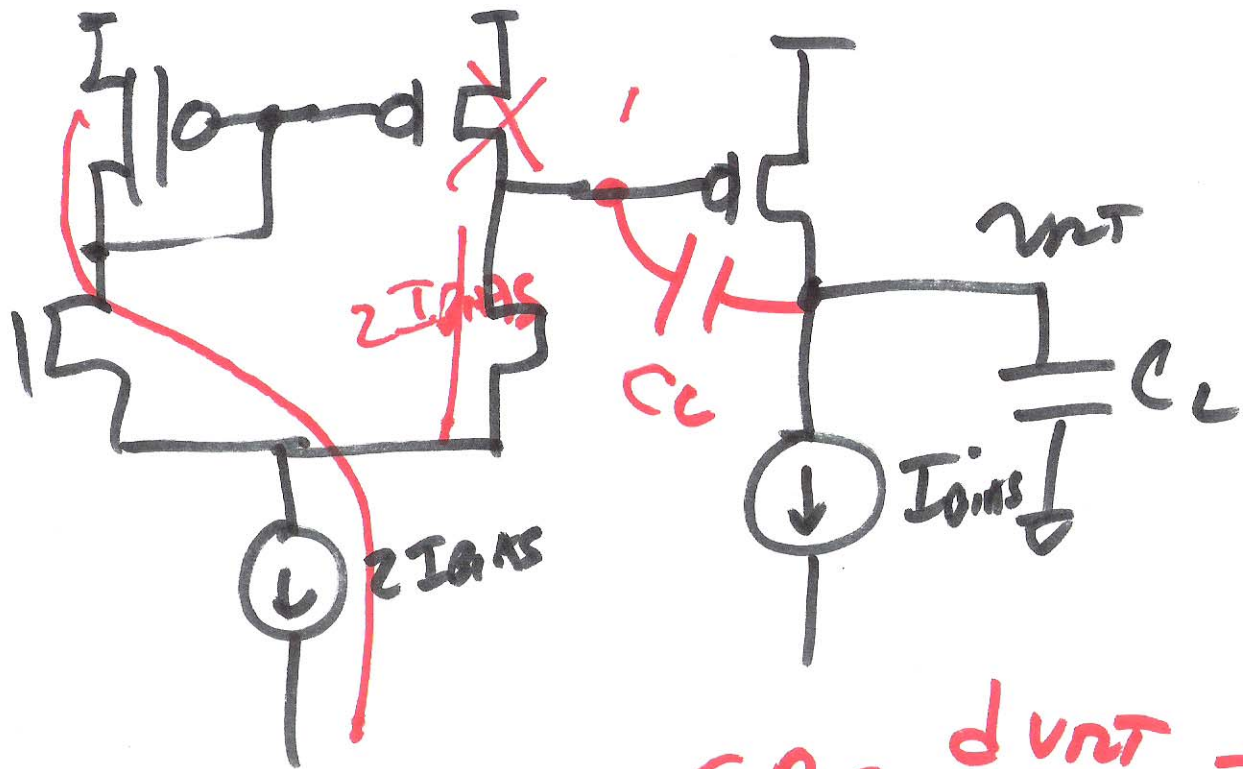

$$\frac{dV_{NT}}{dt} = \frac{I_{bias}}{C_L}$$

$$SR = \frac{dV_{NT}}{dt} = \frac{2I_{bias}}{C_c}$$

$$\frac{dV_{NT}}{dt} = \frac{20\mu A}{2.4pF} = 8.33 \frac{V}{\mu s}$$

$$t_1 = \frac{1}{2} / 8.33 V / \mu s$$

to half a volt

$$= 60ns$$

7)