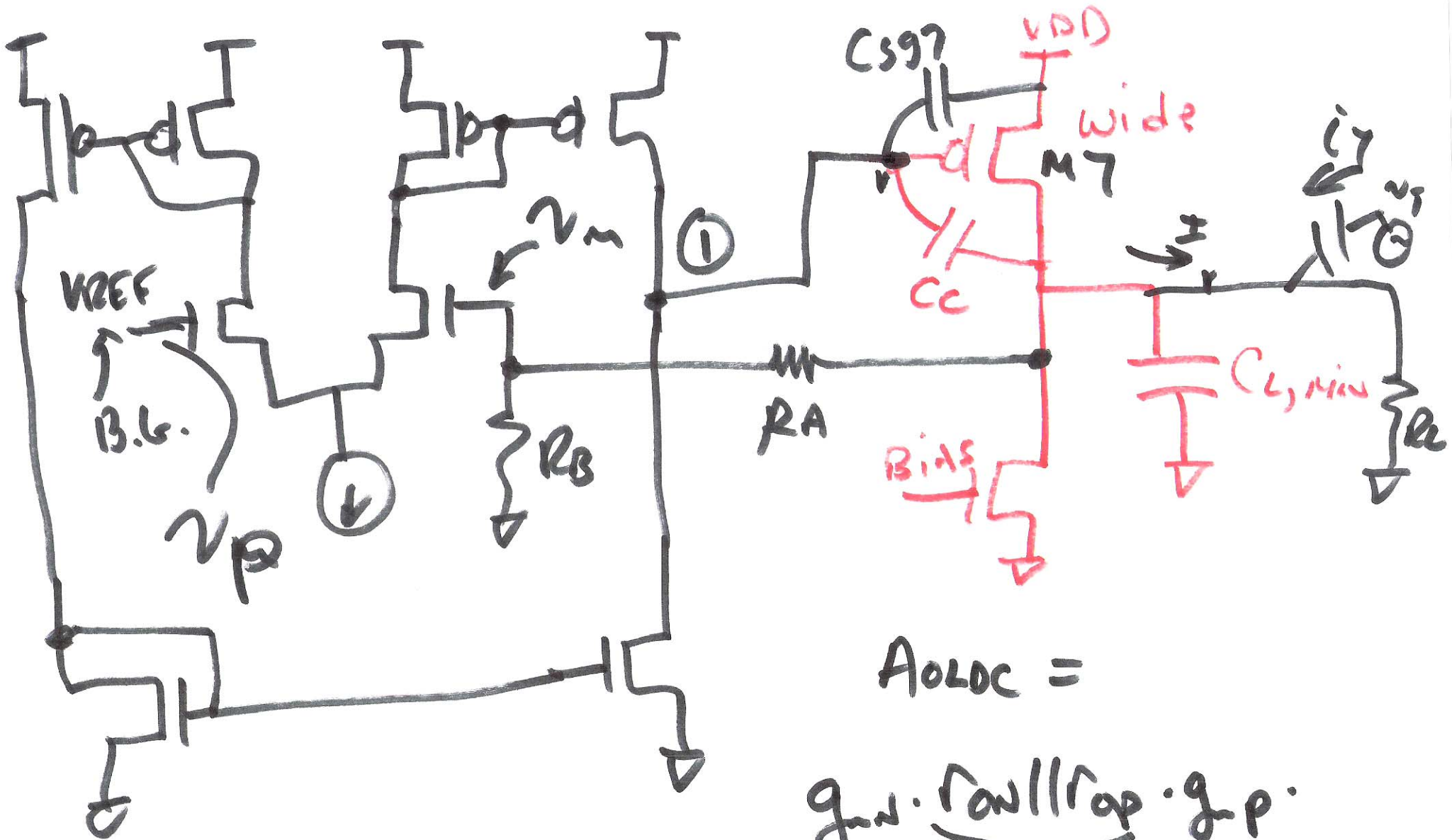



2)



$A_{OLDC} =$

$$g_{m1} \cdot (r_{o1} \parallel r_{op}) \cdot g_{m2}$$
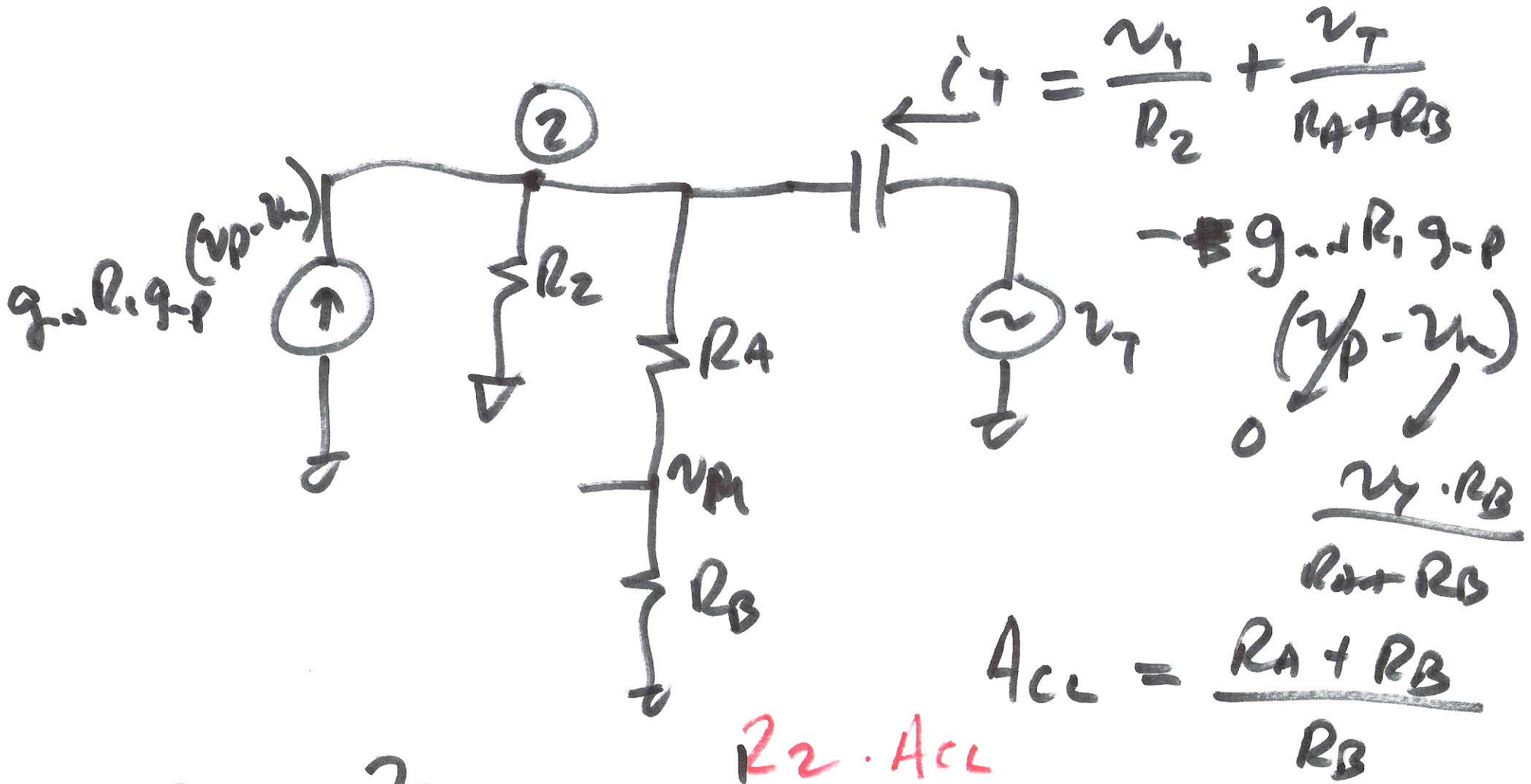
$$A_{OLDC} = g_{m1} \cdot R_1 \cdot g_{m2} \cdot R_2 \cdot \frac{r_{o1} \parallel r_{op} \parallel R_L}{R_2}$$




$$R_{CL} = \frac{v_T}{i_T} = \frac{R_2 \cdot A_{CL}}{\frac{A_{CL}}{R_2} + g_{mN} g_{mP} R_2} \approx \frac{R_2 \cdot A_{CL}}{g_{mN} g_{mP} R_2} = \frac{R_2 \cdot A_{CL}}{A_{OLDC}}$$

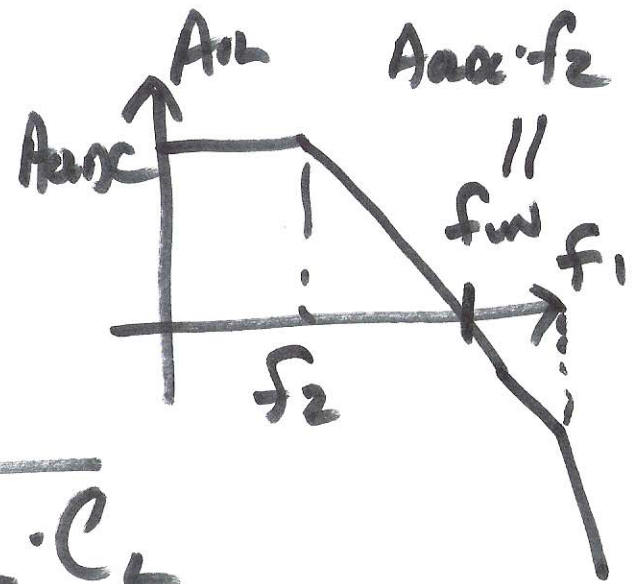4)

$\beta < 1, A_{CL} > 1$
 $A_{CL, ideal} = \frac{1}{\beta}$

$$f_2 = \frac{1}{2\pi R_{CL} \cdot C_L}$$



$$f_1 = \frac{1}{2\pi R_1 \cdot C_{SS7}} = 1.7 \text{ MHz}$$

$$= \frac{A_{OLDC}}{2\pi R_2 \cdot A_{CL} \cdot C_L}$$

key points

$$f_2 = \frac{A_{OLDC}}{2\pi R_2 C_L \cdot A_{CL}}$$

$$= \frac{277}{2\pi (111 \text{ k}) \cdot C_L}$$

$$f_w = 1 \text{ MHz}$$

USE small A_{OLDC}
 LARGE C_L
 Problem with A_{OLDC} is control

5)

$$f_{un} = A_{OLDC} \cdot f_2 = \frac{A_{OLDC}^2}{2\pi R_2 C_{L,min} A_{CL}}$$

$$= 1 \text{ MHz} \quad A_{OLDC} = g_{mN} R_1 \cdot g_{mP} R_2$$

$$C_{L,min} = \frac{g_{mN}^2 R_1^2 g_{mP}^2 R_2}{2\pi f_{un} \cdot A_{CL}}$$

//
1,000 pF

$$R_2 \approx R_{L,max} = 1 \text{ k}$$

6)