
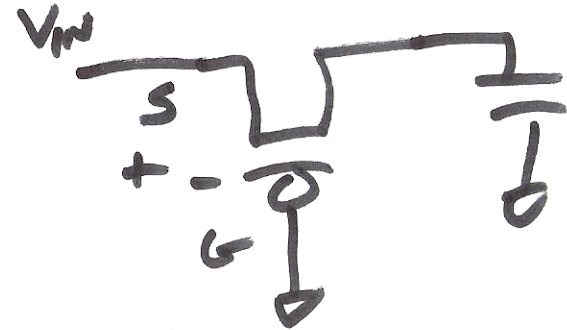


DYNAMIC Analog Circuits

25.1/25.2


PASS gate



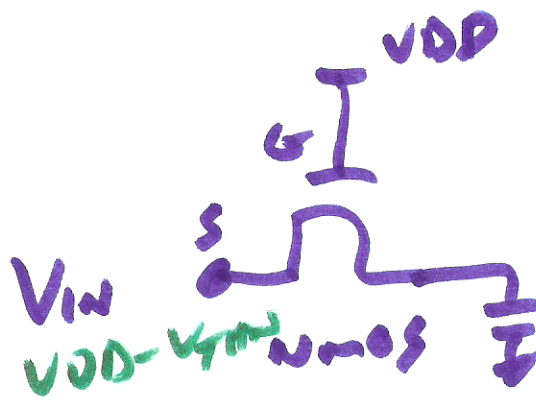


$V_{SG} = V_{THP}$
shuts OFF

$$V_{GS} = V_{DD} - (V_{DD} - V_{THP})$$


$$V_{GS} = V_{THP}$$

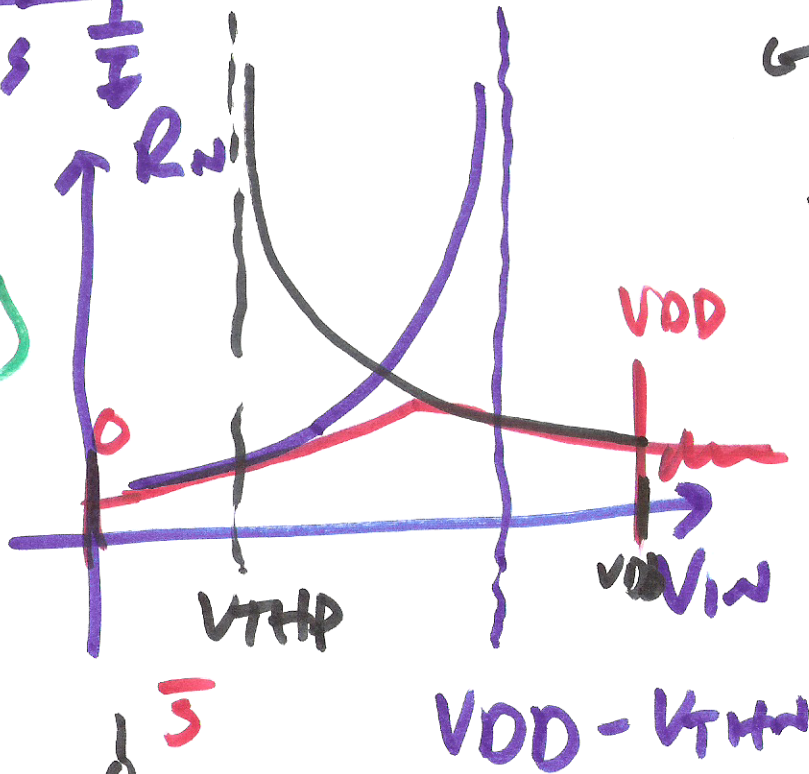

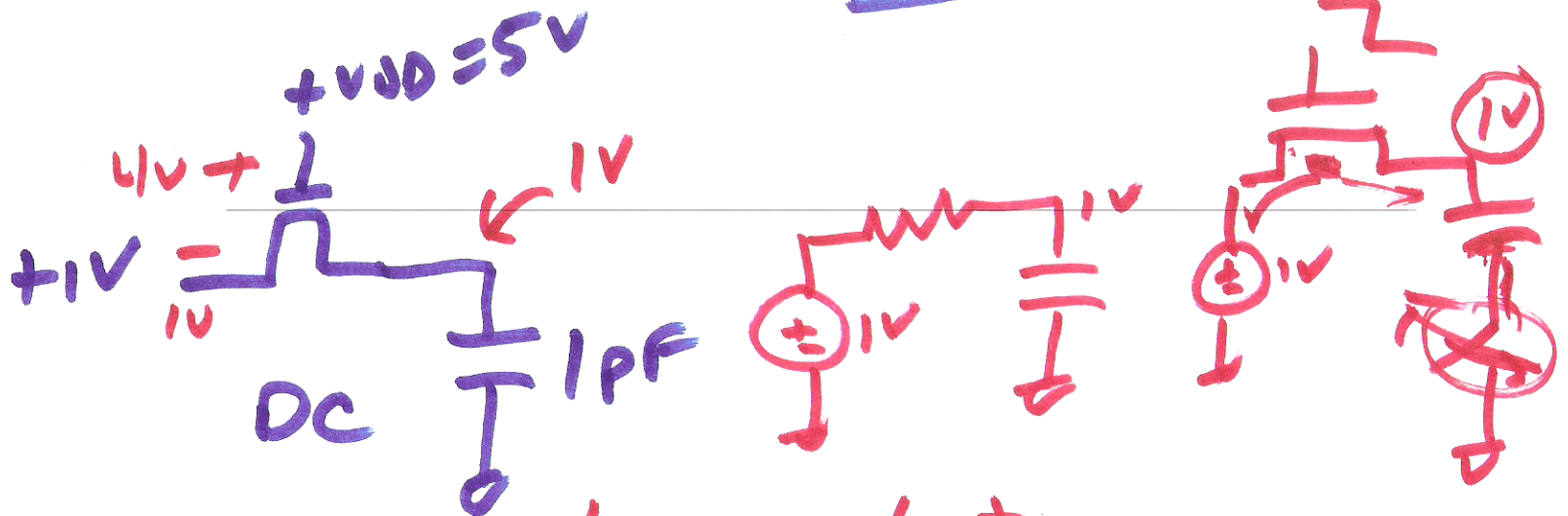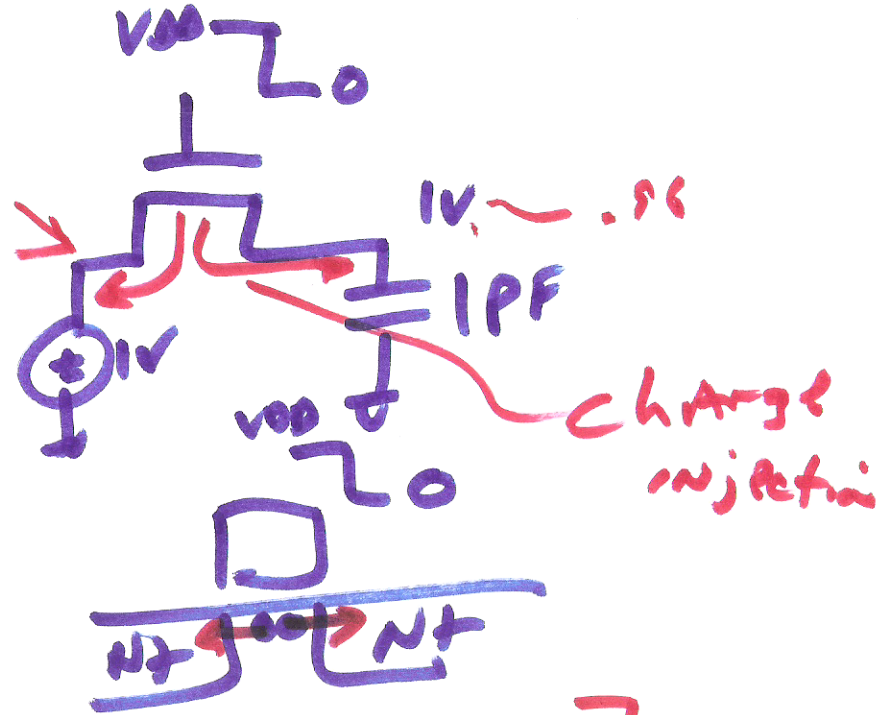
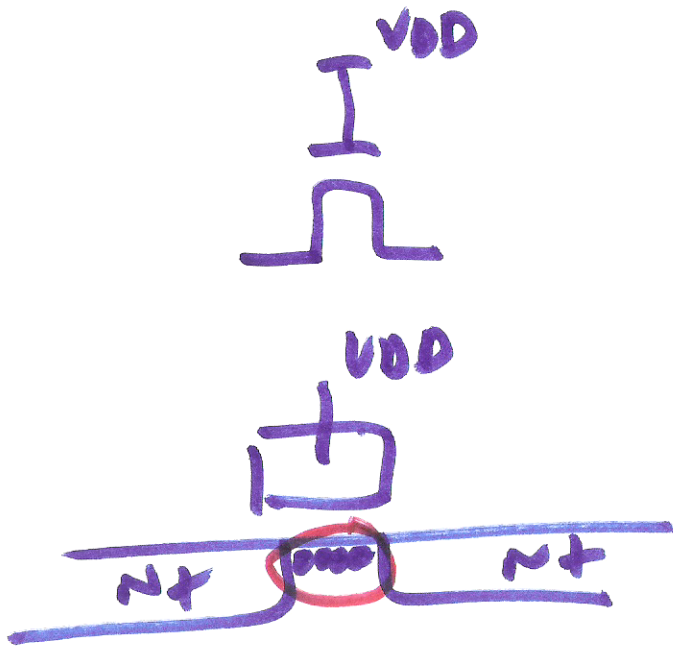


TURN isn't important
(not talking about RC delay)

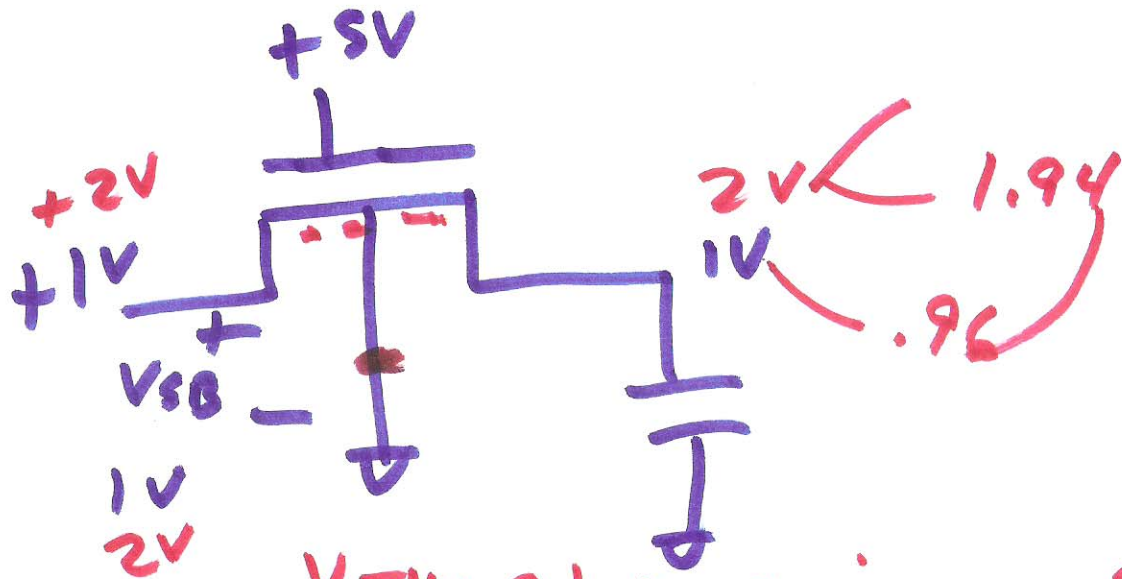
Charge Injection causes Non-linearity (distortion)




V_{TH} change is nonlinearity

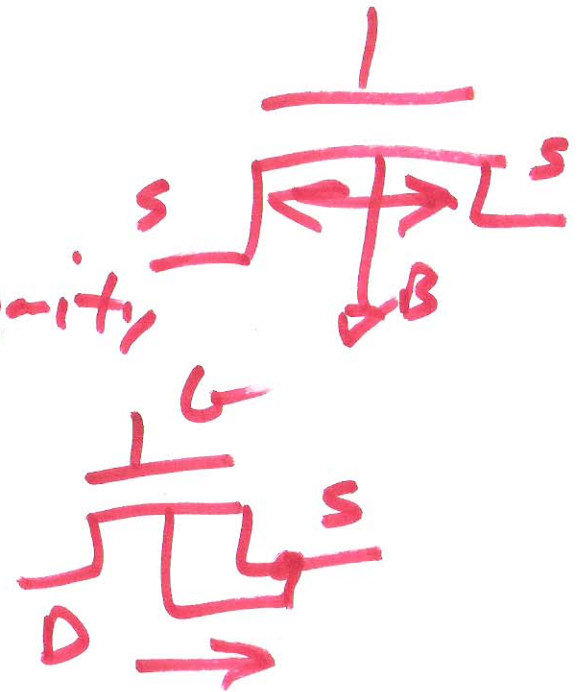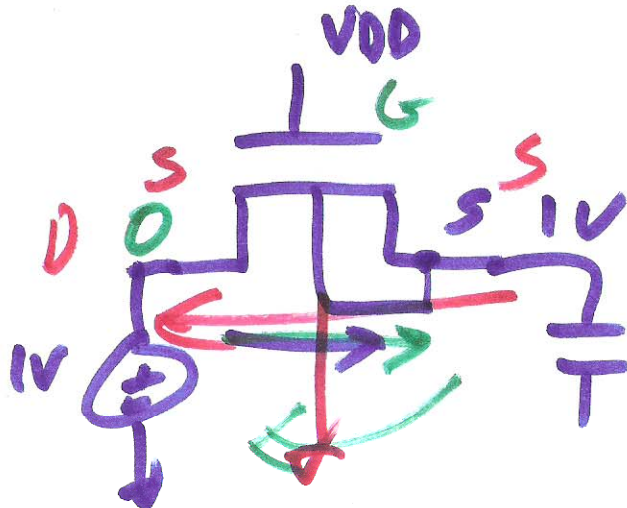

CAPACITIVE feed through

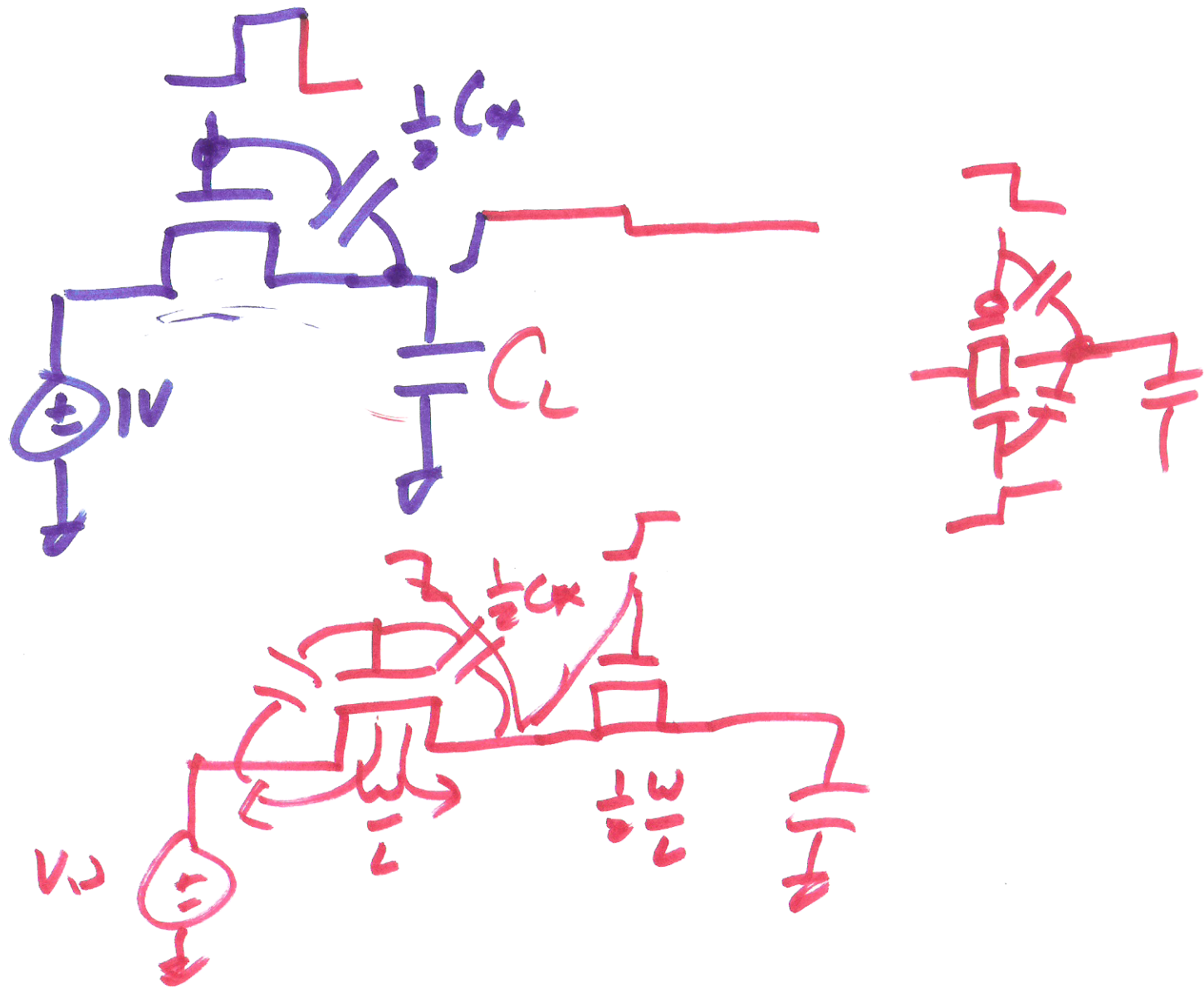

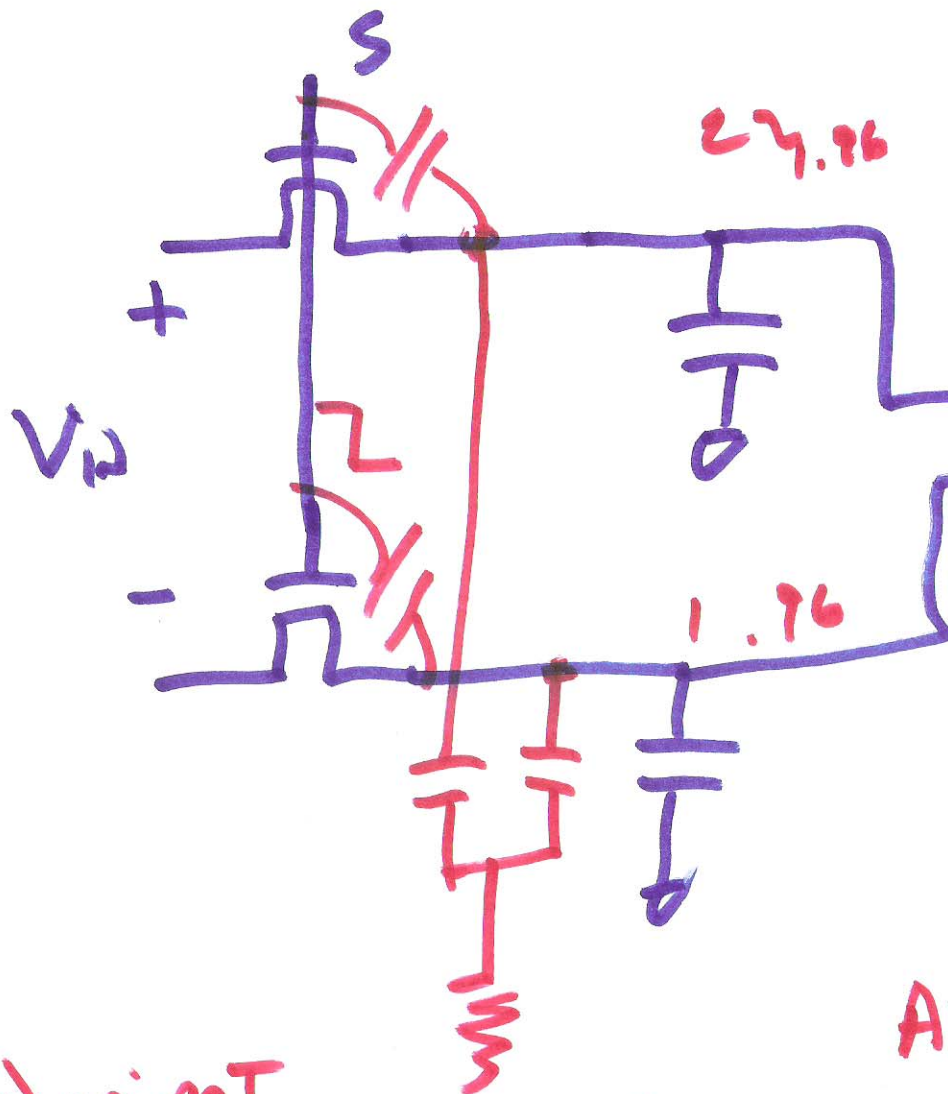

f.i.d. design

1) Reduction in the effects of coupled noise

$$Ax + Bx^2 + Cx^3 + Dx^4$$

2) even-order distortion harmonics cancel out

$$A(-x) + B(-x)^2 + C(-x)^3$$

$$Ax - (-Ax) = 2Ax$$

$$Bx^2 - Bx^2 = 0$$

$$Cx^3 - (-Cx^3) = 2Cx^3$$

3) reject charge injection and cap. feed through

5)

10-bit ADC

$$1\text{LSB} = \frac{2^{10}}{1.024} = 1\text{mV}$$


$$V_{\text{AFT}} - V_{\text{REF-}} = 1.024\text{V}$$



0000000000 $\rightarrow 0$
1111111111 $\rightarrow 1.023\text{V}$

Neglect $\frac{1}{2}\text{LSB}$

Estimate size of hold capacitors required
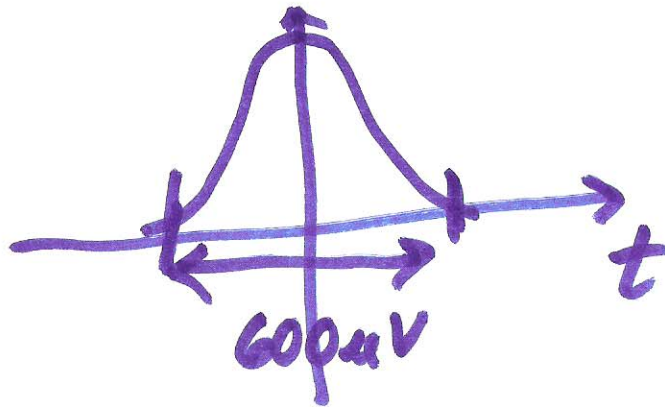
$$V_{\text{noise}} = 100\text{mV voltage}$$



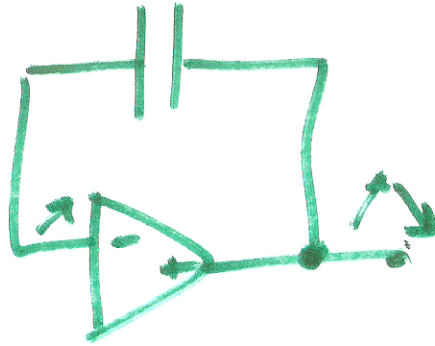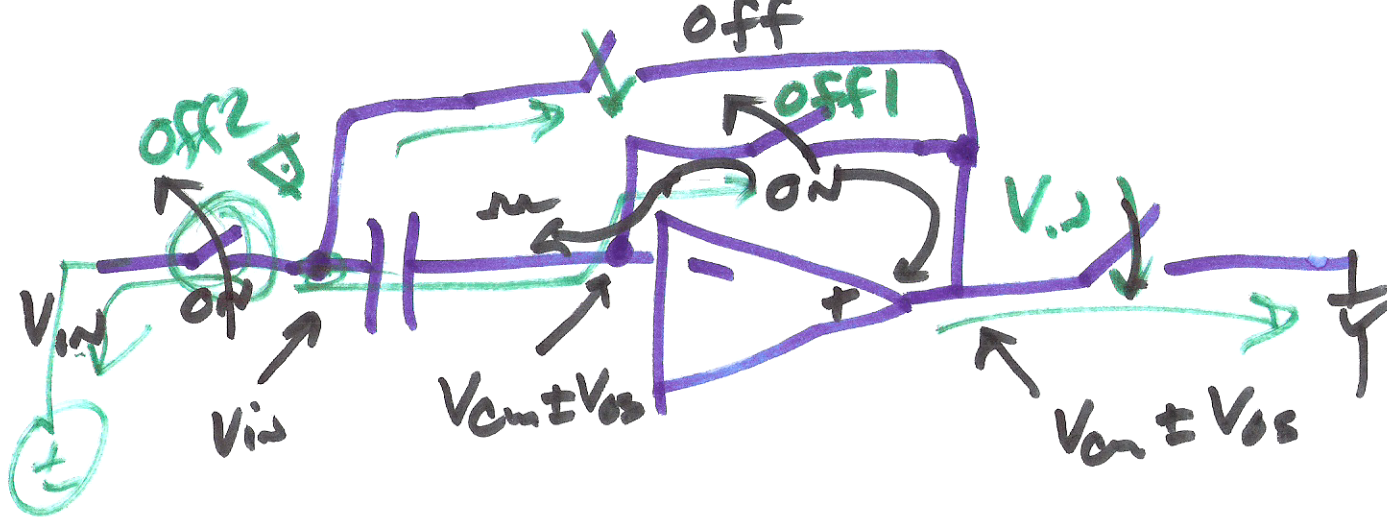

8)