
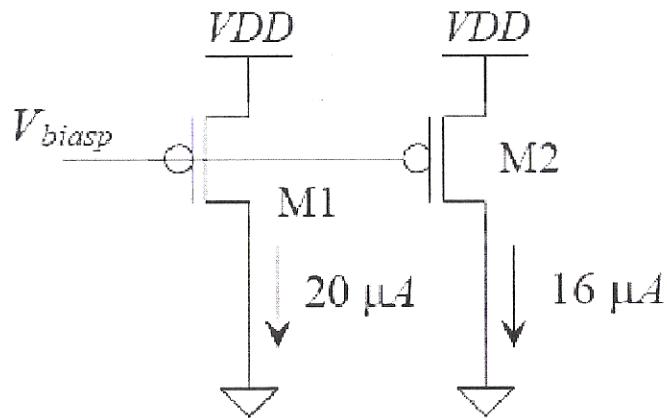


26.2

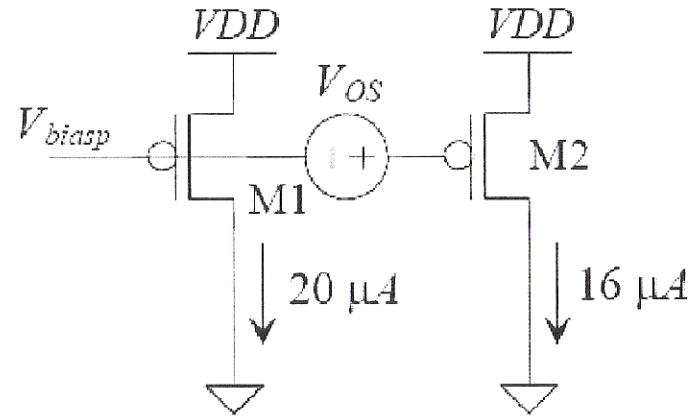



(a) M1 and M2 are mismatched.



(b) M1 and M2 are perfectly matched
(as in a SPICE simulation).

Figure 26.5 How we add an offset into the circuit to model mismatch.

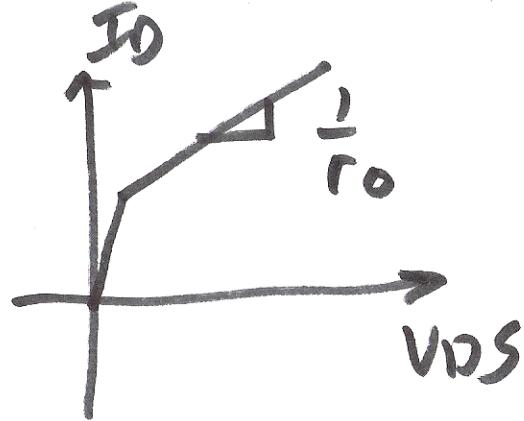

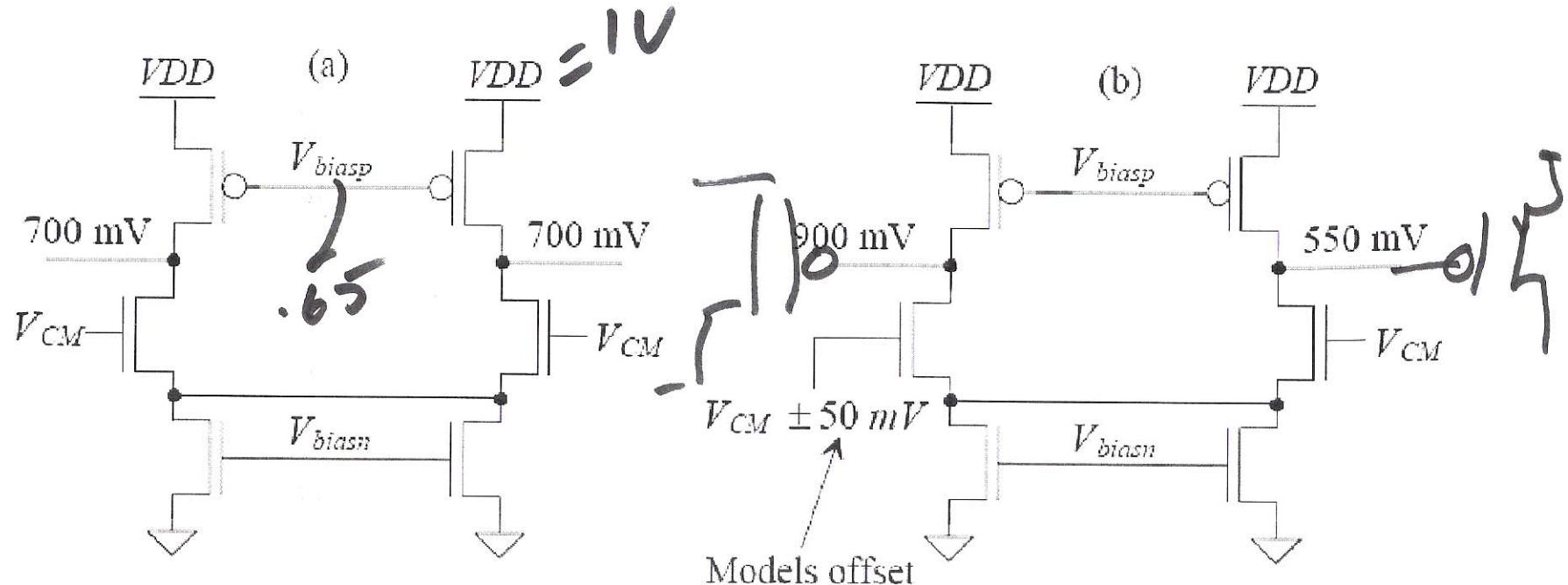

NMOS are 10/1

PMOS are 20/1

Bias circuit seen in Fig. 26.3

$$V_{CM} = VDD/2 = 500 \text{ mV}$$

Figure 26.6 Comparing the diff-amp's output voltages with and without an offset.

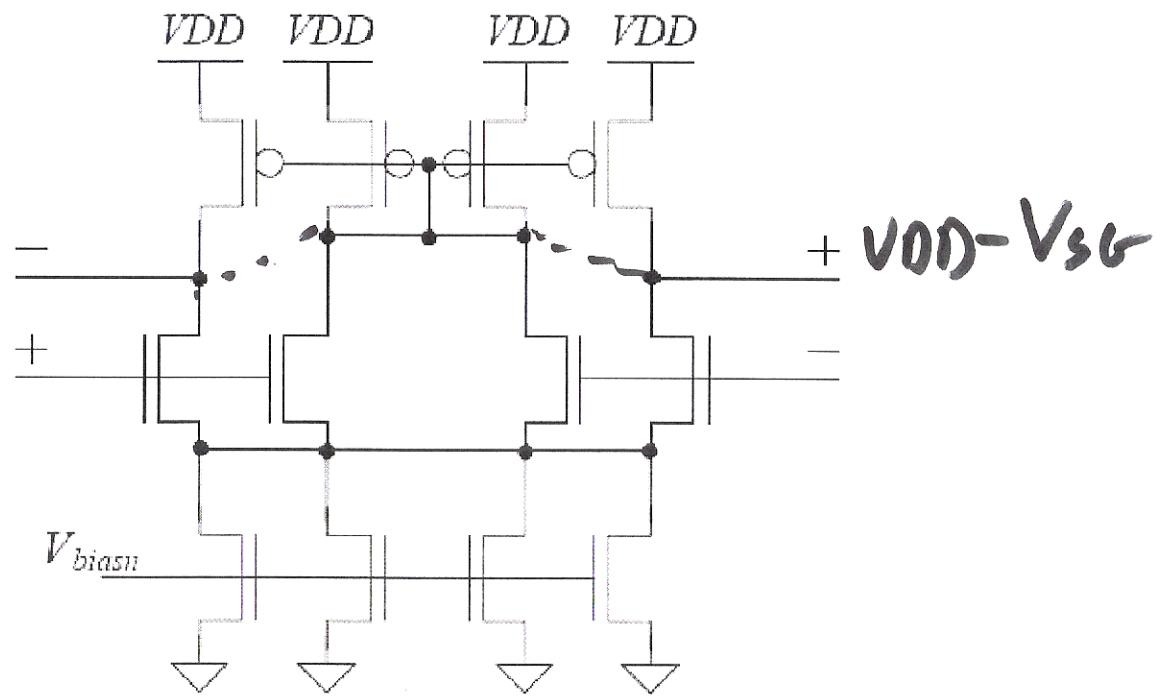


Figure 26.7 A fully-differential diff-amp that generates its own bias for the PMOS.

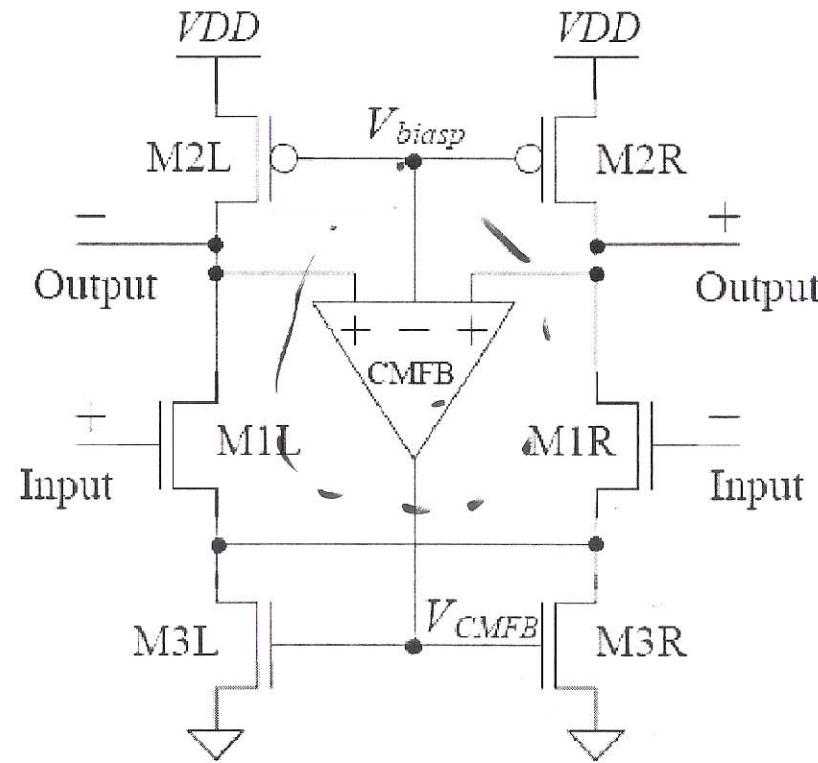


Figure 26.8 Using a common-mode feedback (CMFB) amplifier to set the output voltages.



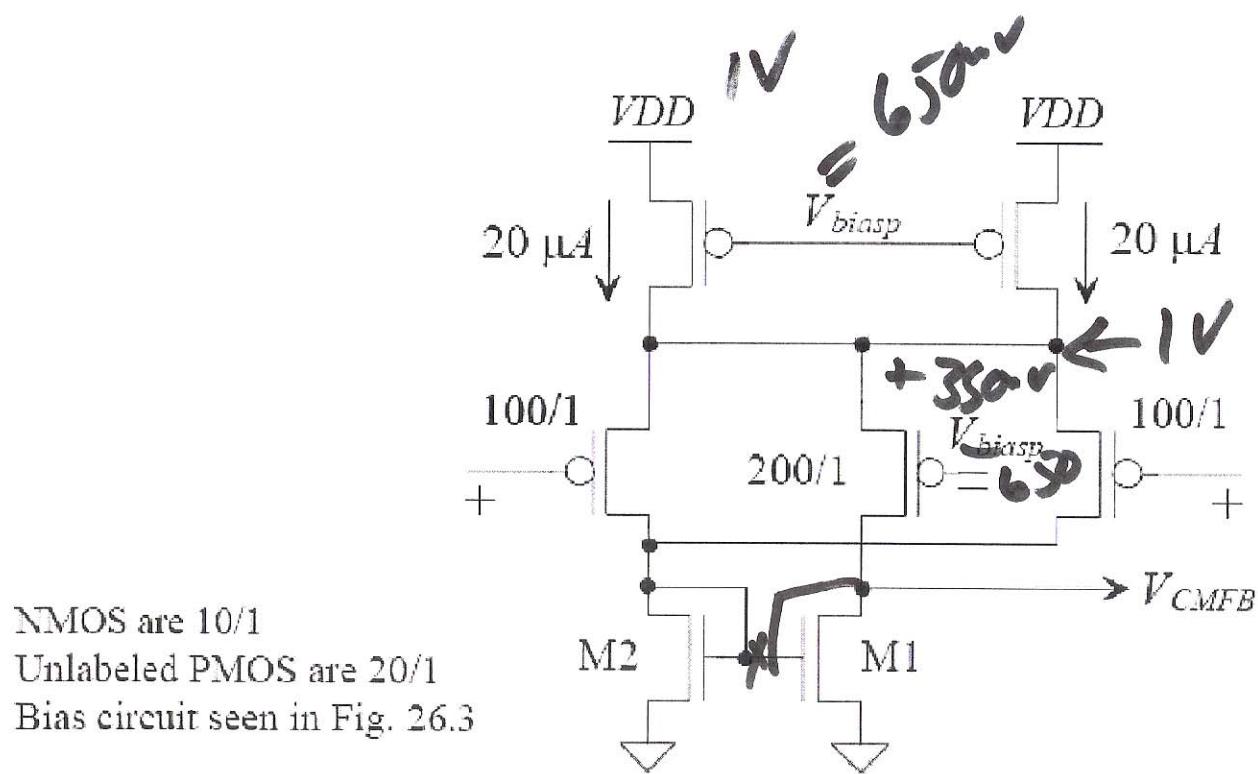


Figure 26.9 Implementation of the CMFB amplifier in Fig. 26.8.

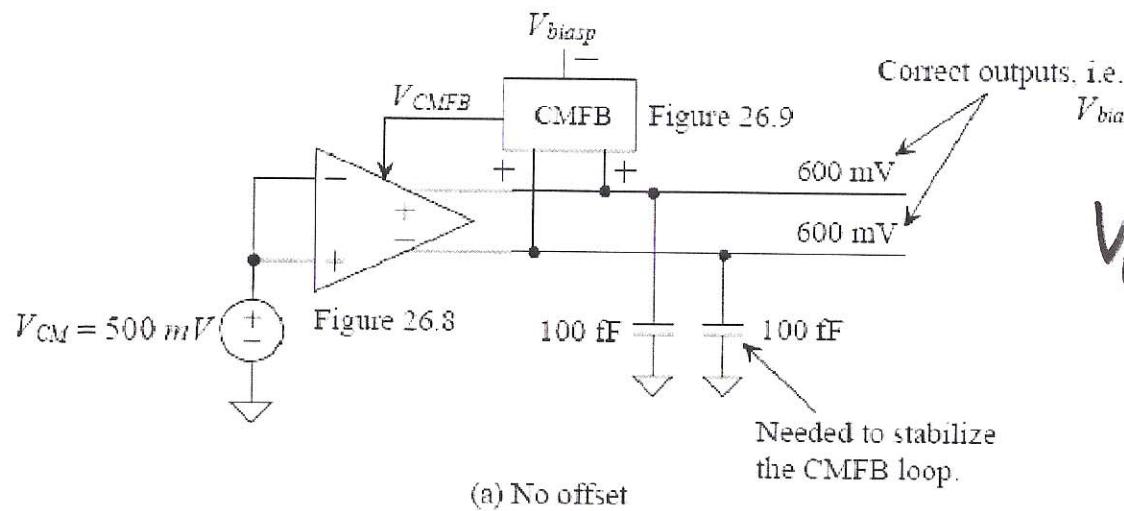

$$V_{S0} = 400 \text{ mV}$$

$$V_{biasp} = 600 \text{ mV}$$

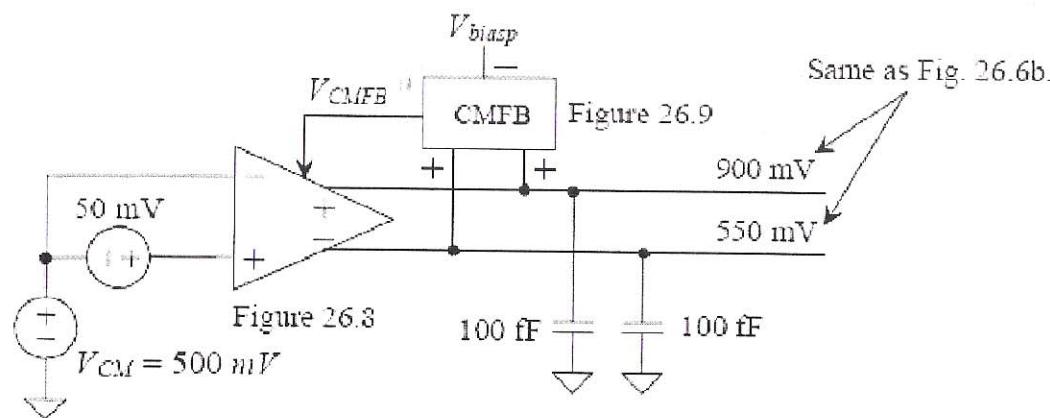

(b) With a 50 mV offset. Note how the CMFB isn't doing anything.

Figure 26.10 Simulating the operation of the CMFB circuit in Fig. 26.9.

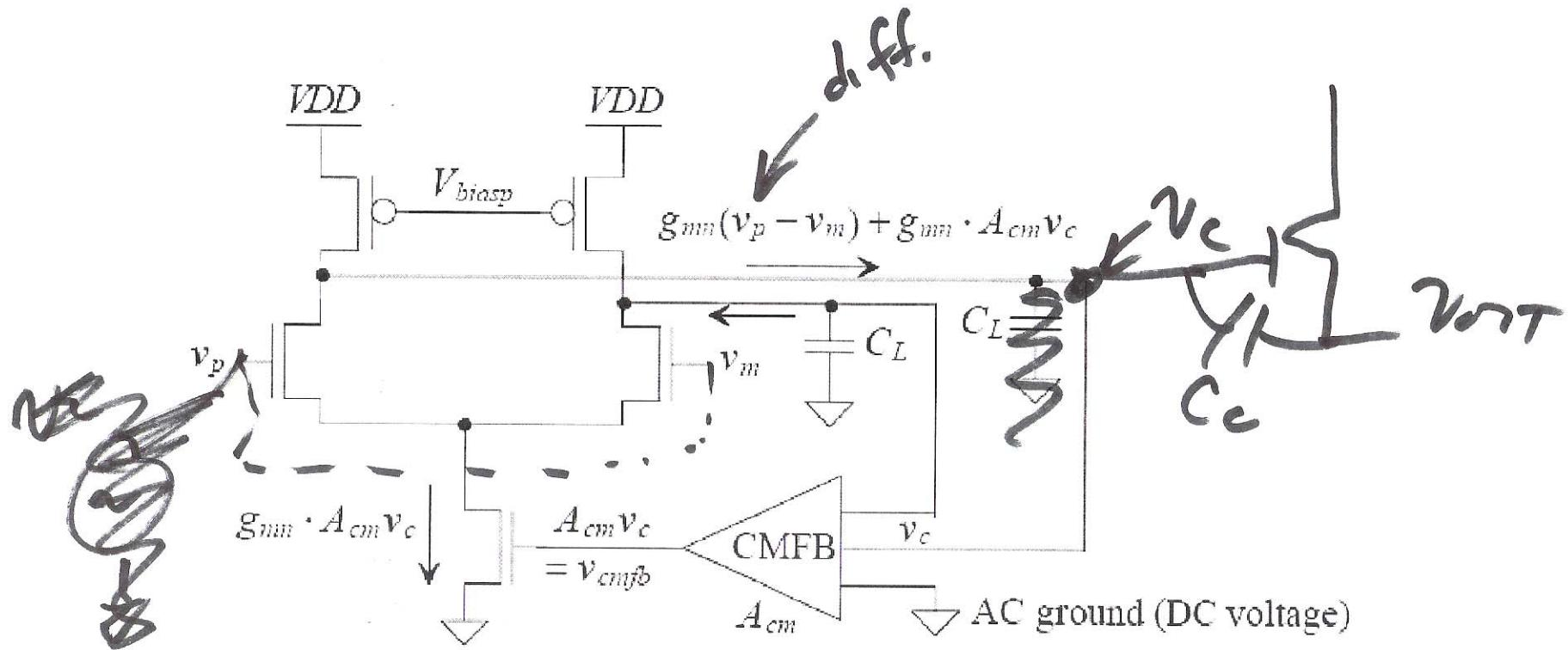


Figure 26.11 Schematic view of differential and CM feedback.

$$\frac{v_c}{v_{ci}} = \left| g_m \cdot A_{cm} \cdot \frac{1}{j\omega C_L} \right| = 1 < 1 \quad (26.2)$$

$$f_{m,ci} = \frac{g_m A_{cm}}{2\pi \cdot C_L}$$

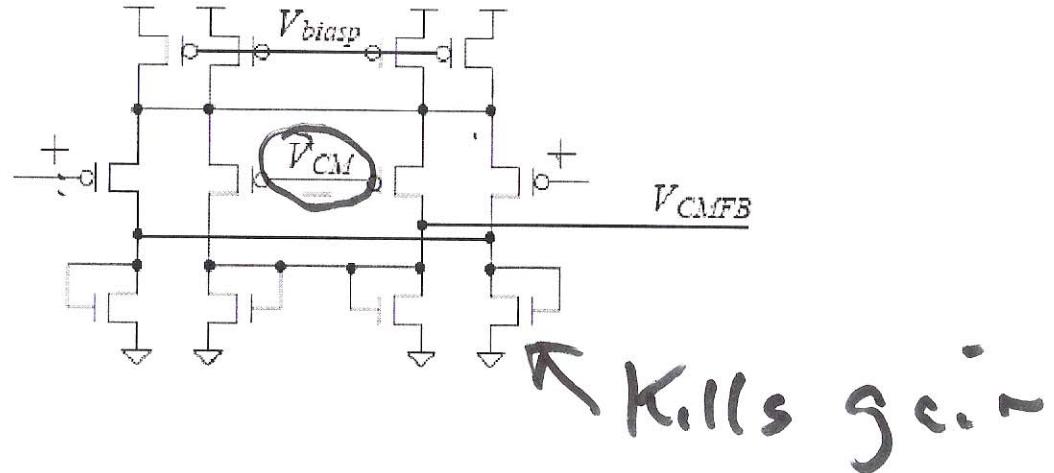


Figure 26.12 A CMFB amplifier with a gain of nominally unity.


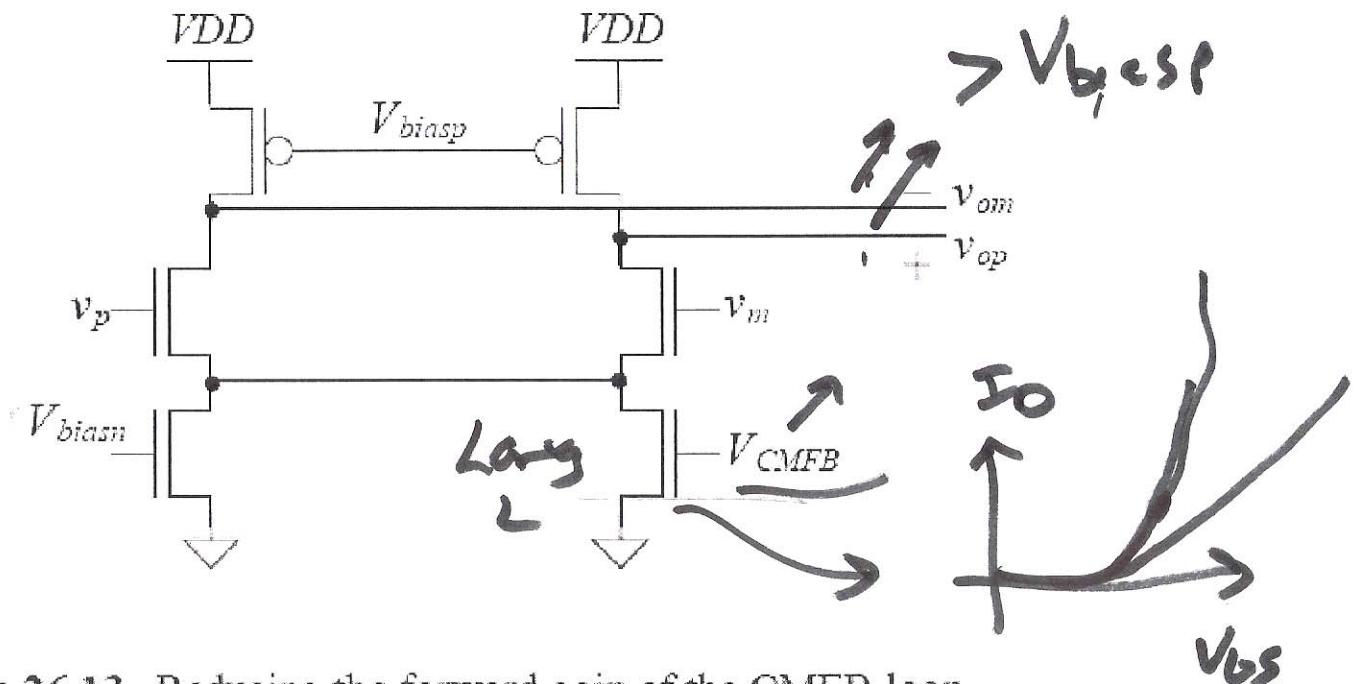



Figure 26.13 Reducing the forward gain of the CMFB loop.

NMOS - diff-Amp

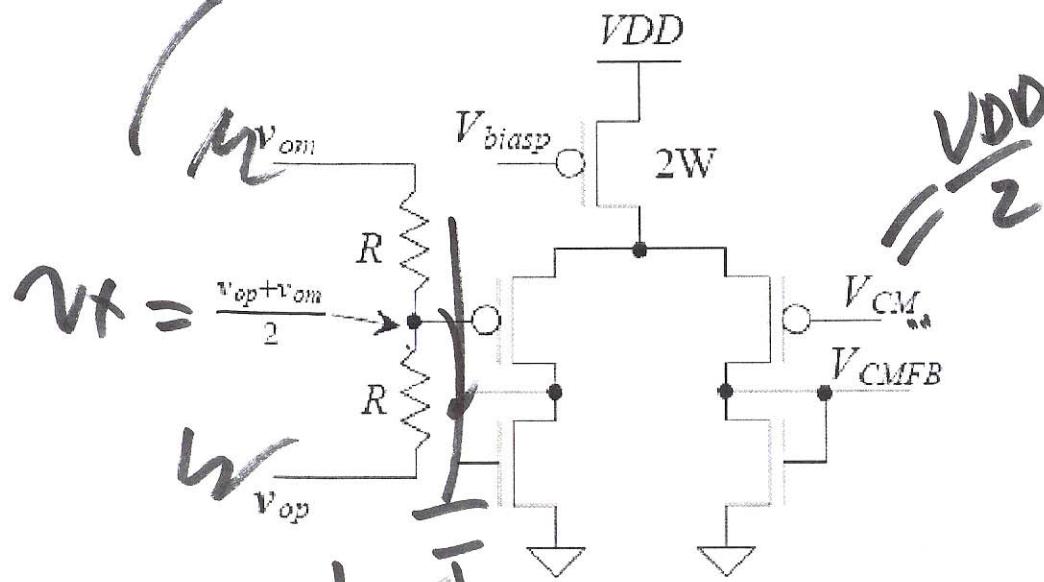



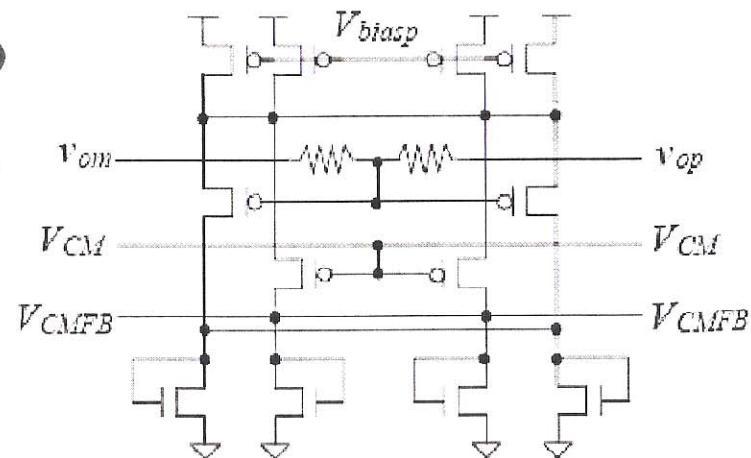(a) Using resistors to average differential output signals.



(b) Symmetrical implementation of the CMFB circuit in (a).

Figure 26.14 Increasing CMFB amplifier input range.

$$\frac{v_{op} + v_{om}}{2} = \left(\frac{v_{om} - v_{op}}{2R} \right) R + \frac{2V_{DP}}{2} = v_x$$

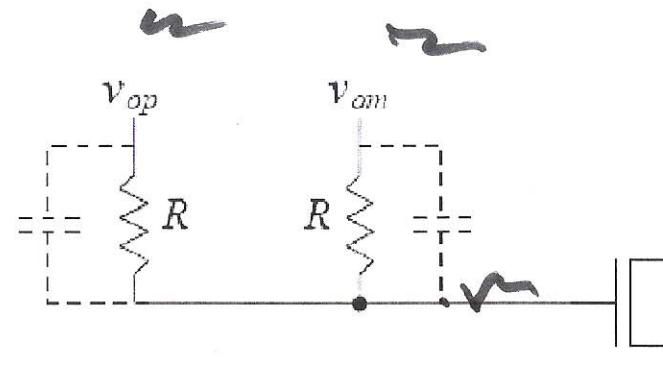


Figure 26.15 Adding parasitic capacitances across the resistors to compensate for the input capacitance of the MOSFET.

ideal output of diff-pair

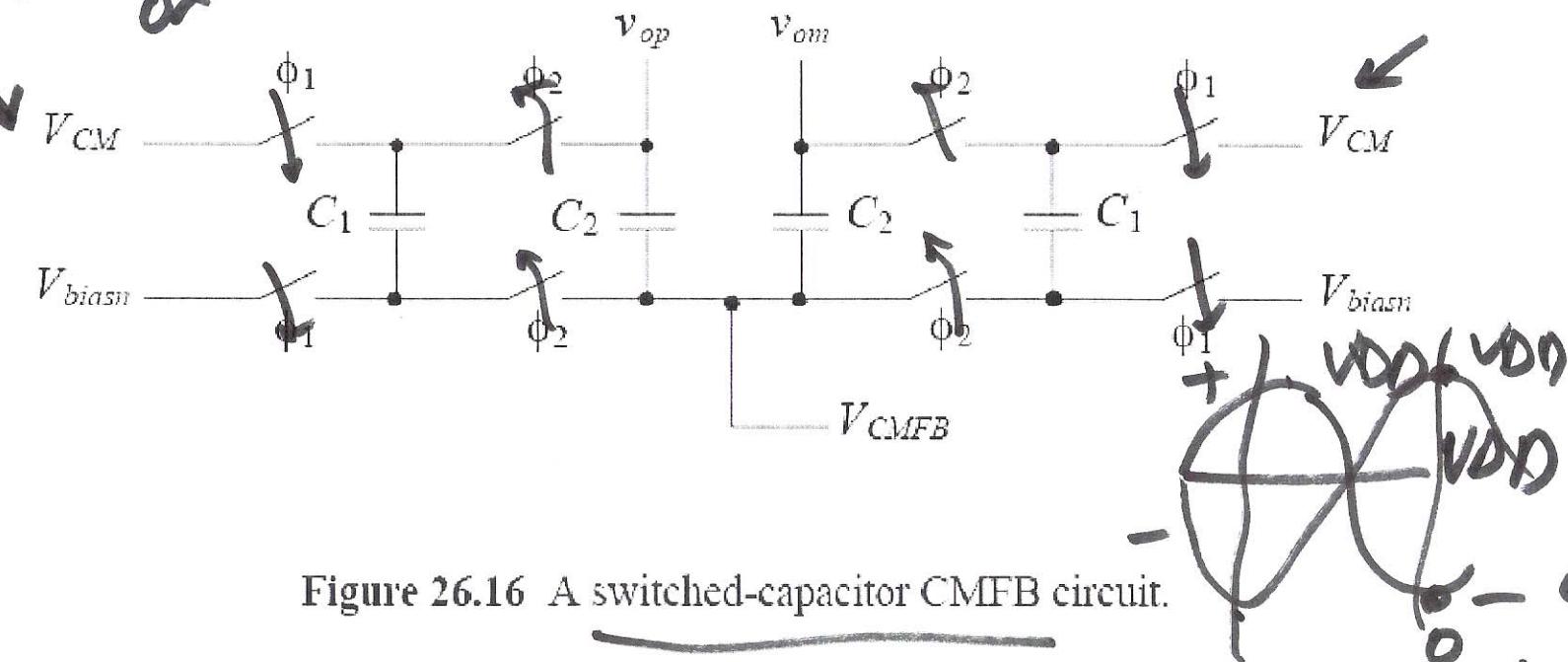


Figure 26.16 A switched-capacitor CMFB circuit.

$V_+ - V_- = V_{DD}$
 $V_+ - V_- = 0 - V_{DD}$
 $= -V_{DD}$

NMOS 10/1

PMOS 20/1

Bias circuit from Fig. 26.3

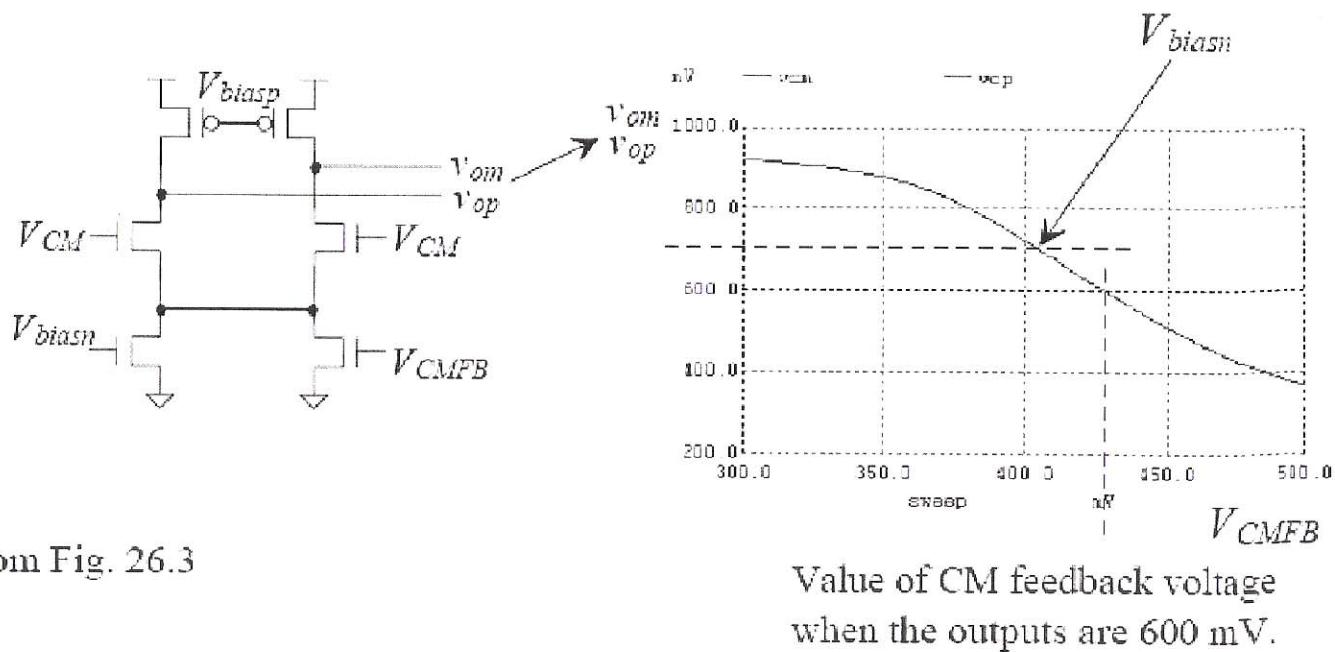


Figure 26.17 Plotting the output voltages as a function of the CM feedback voltage.