
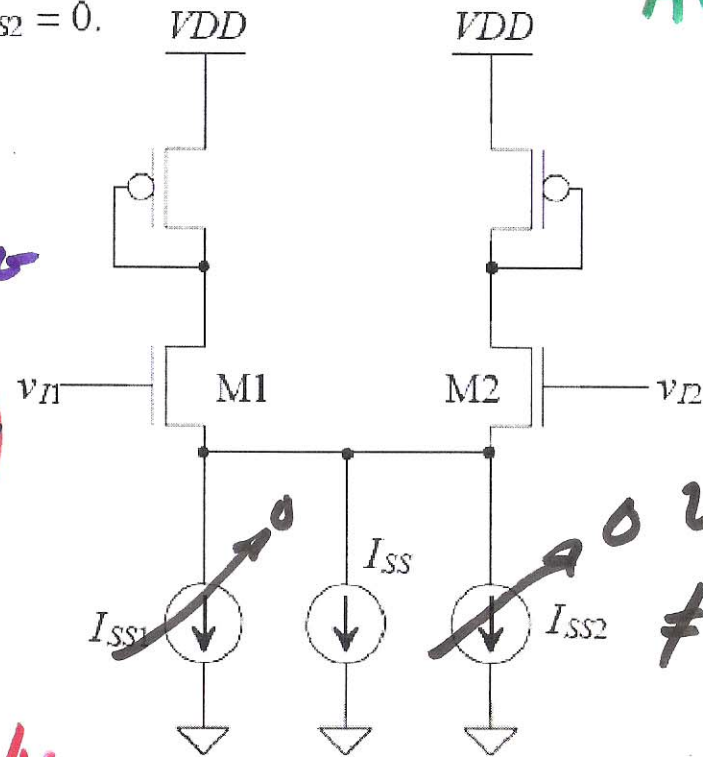


27.2

If $v_{I1} = v_{I2}$ then $I_{SS1} = I_{SS2} = 0$.

Adaptive biasing

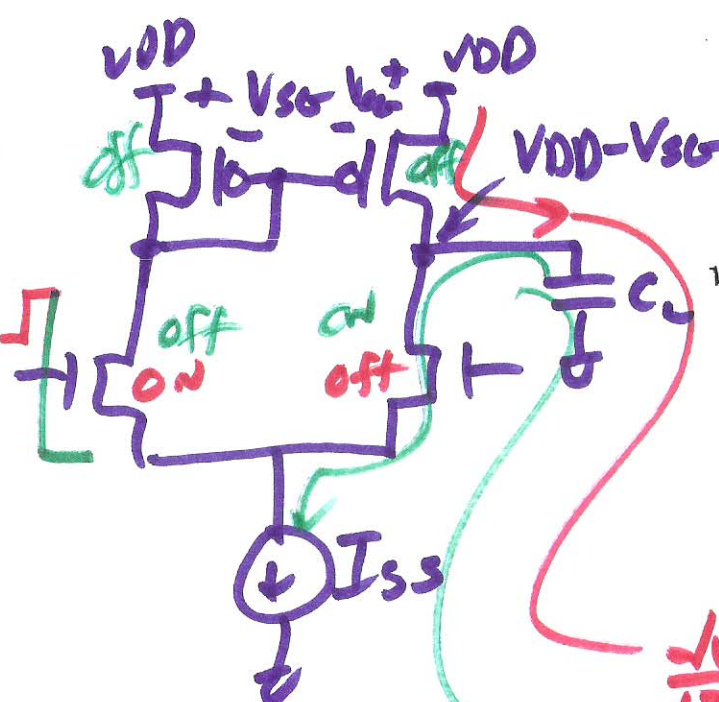

$0 \quad v_{I1} = v_{I2}$
 $\neq 0 \quad v_{I1} \neq v_{I2}$

$$\frac{dv}{dT} = \frac{I_{SS}}{C}$$

$$\frac{dv}{dT} = \frac{I_{SS}}{C}$$

Figure 27.18 Adaptively biased diff-amp.

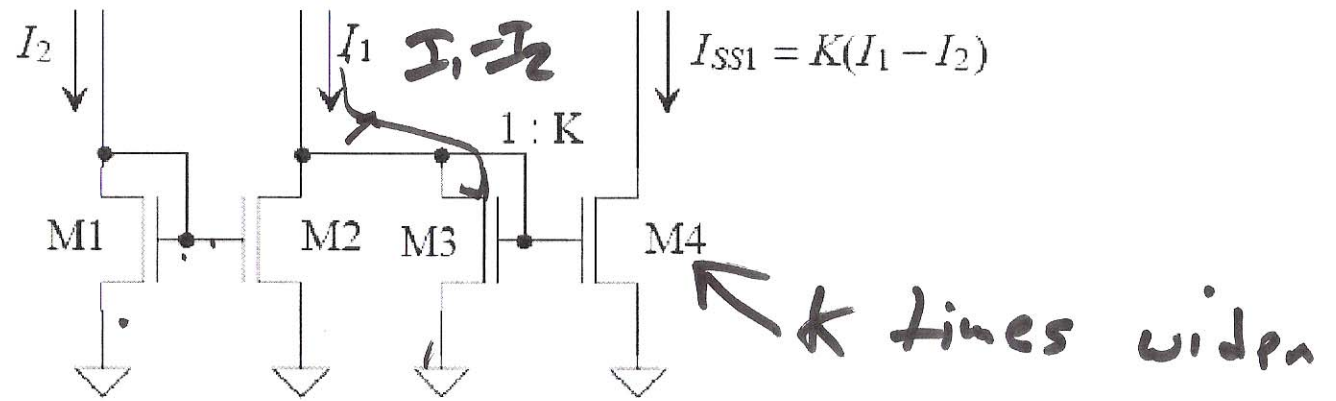


Figure 27.19 Current diff-amp used in adaptive biasing.

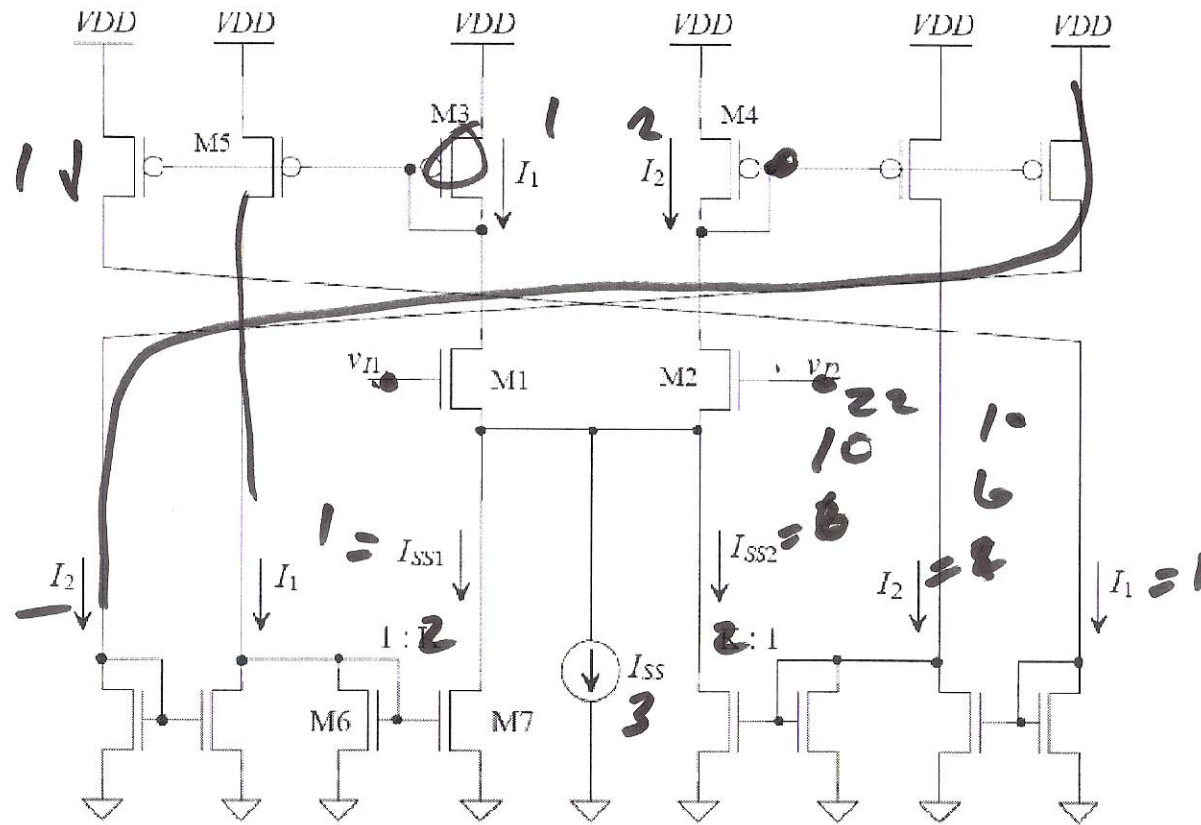


Figure 27.20 Adaptively biased diff-amp.

$k > 1$ we positive f.b.

$$I_{SS2} = I_{SS} (1 + k + k^2 + k^3 \dots)$$

$k < 1$

3)

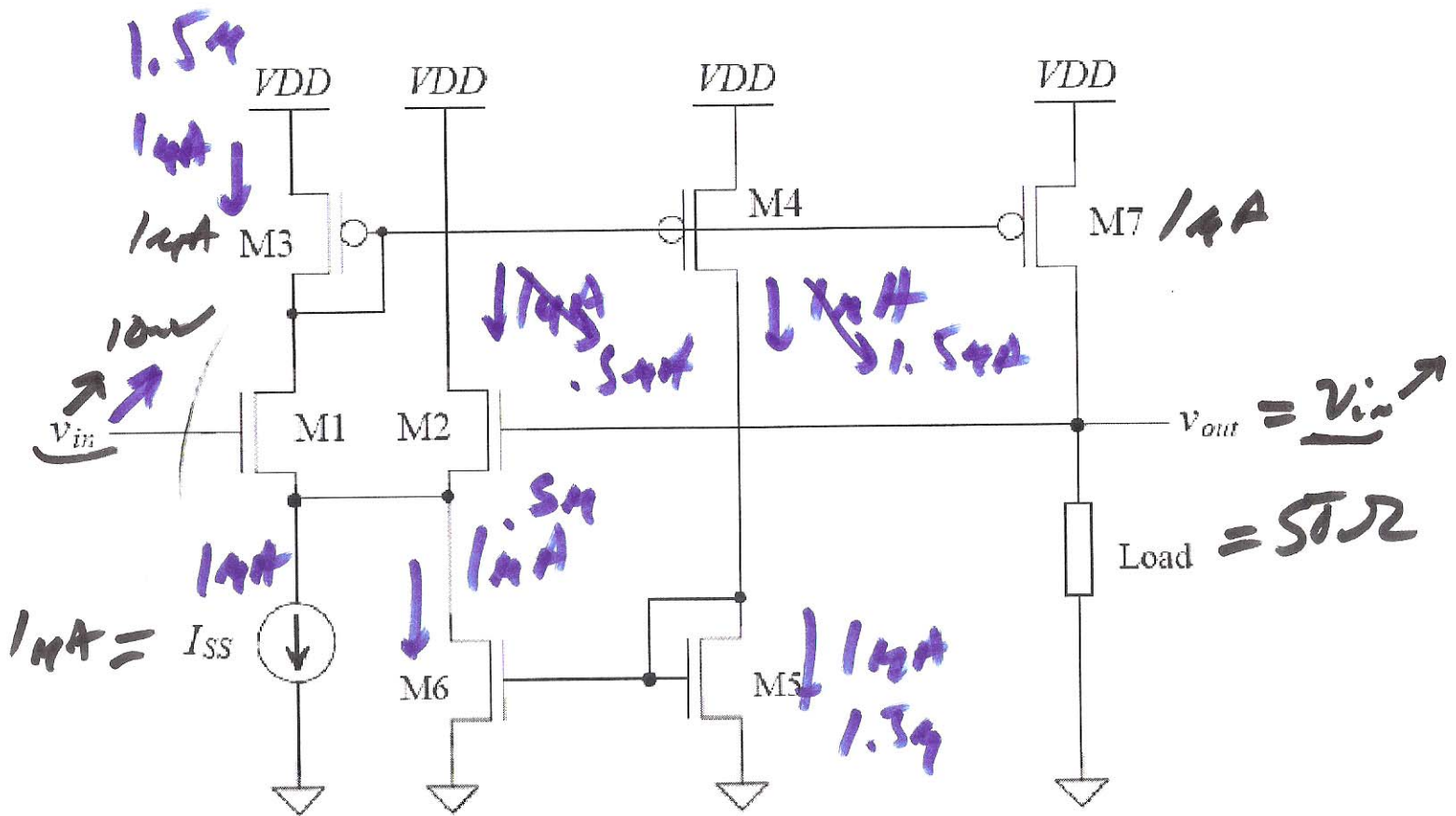


Figure 27.21 Adaptive voltage follower.

4)


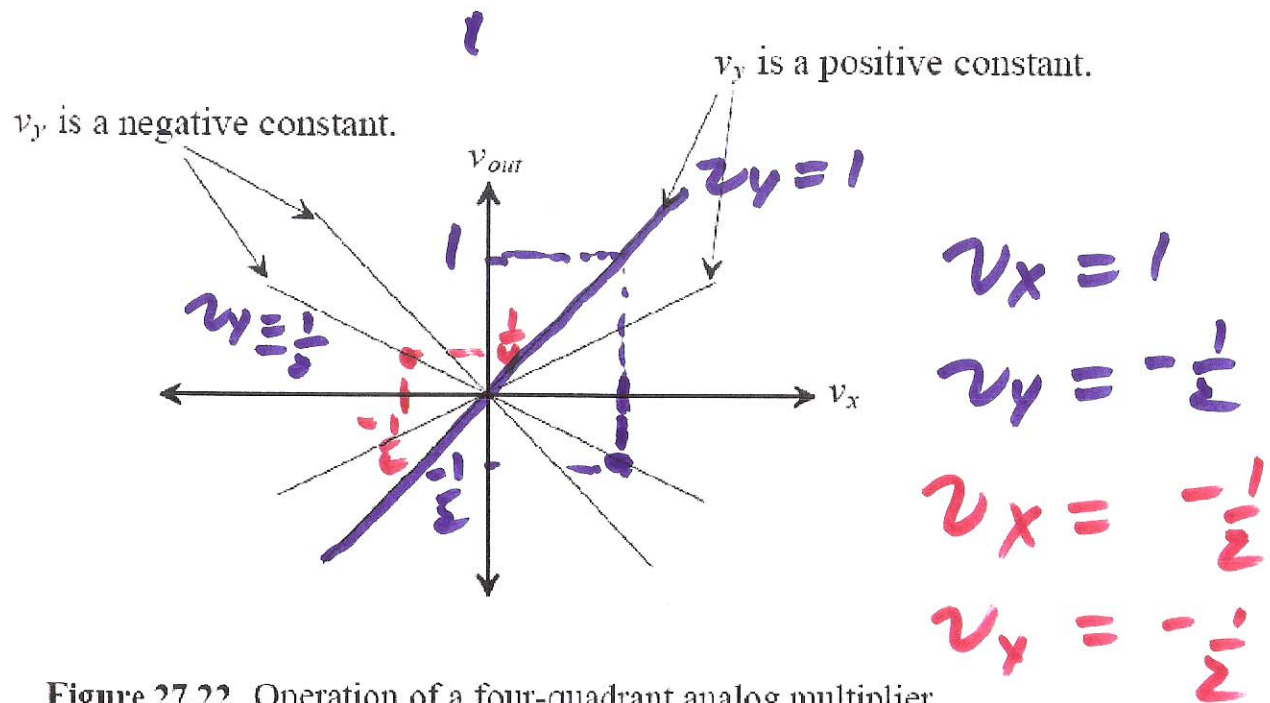
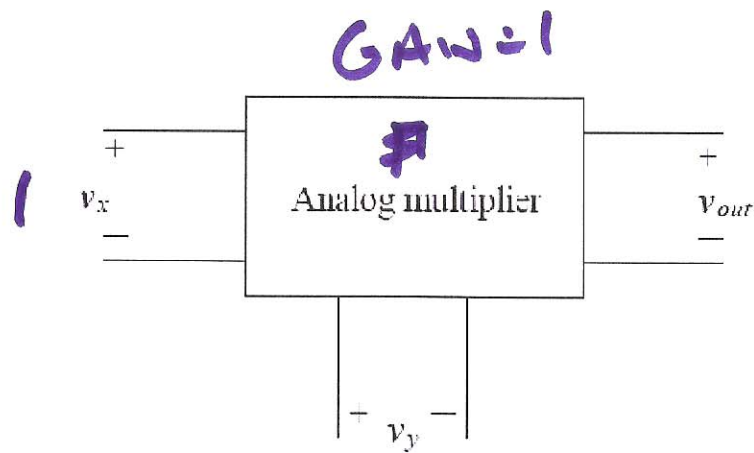


Figure 27.22 Operation of a four-quadrant analog multiplier.

5)

operate in triode

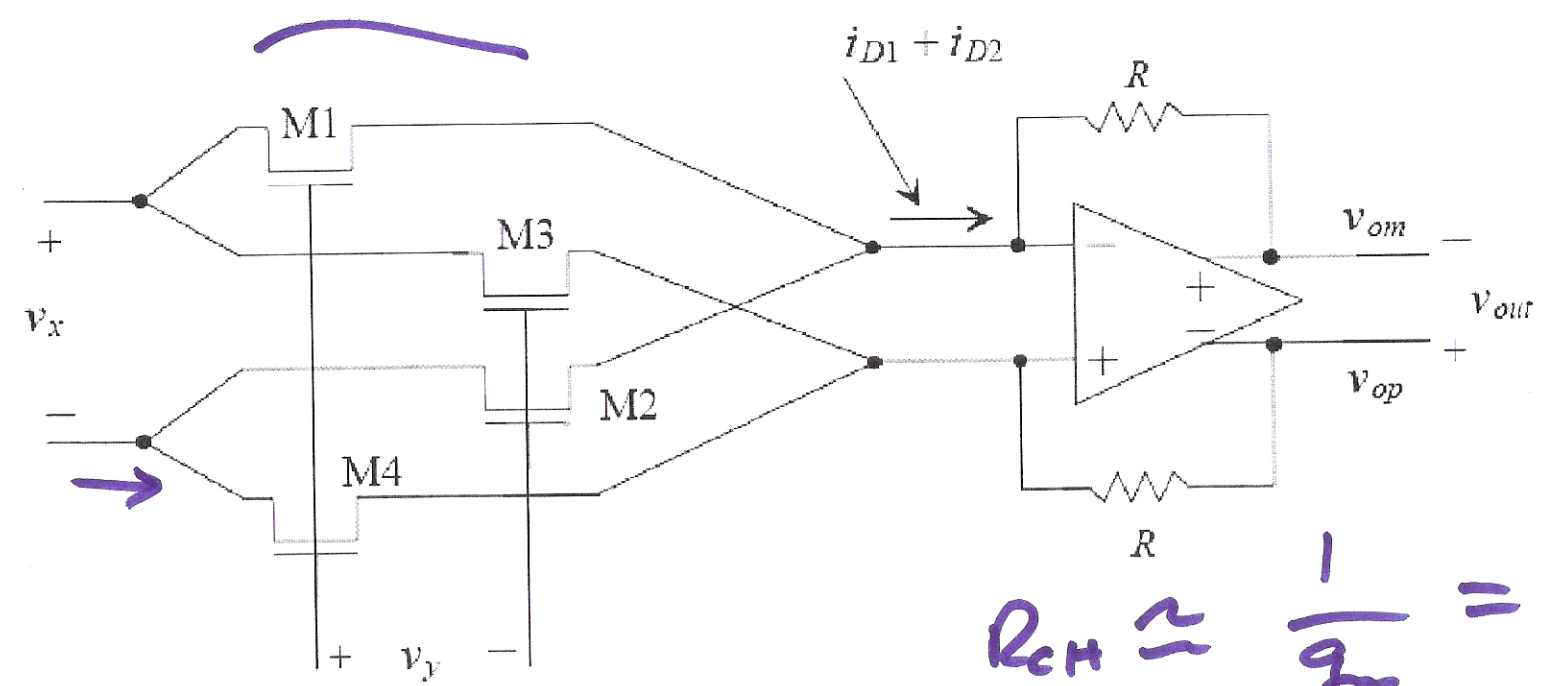

$$R_{eff} \approx \frac{1}{g_m} = \frac{1}{\frac{K_p \mu C}{2} (V_{GS} - V_{TH})^2}$$

Figure 27.23 CMOS analog multiplier.

$$v_x = i \cdot R_{eff} = \frac{i}{\frac{K_p \mu C}{2} (V_{GS} - V_{TH})^2}$$

6

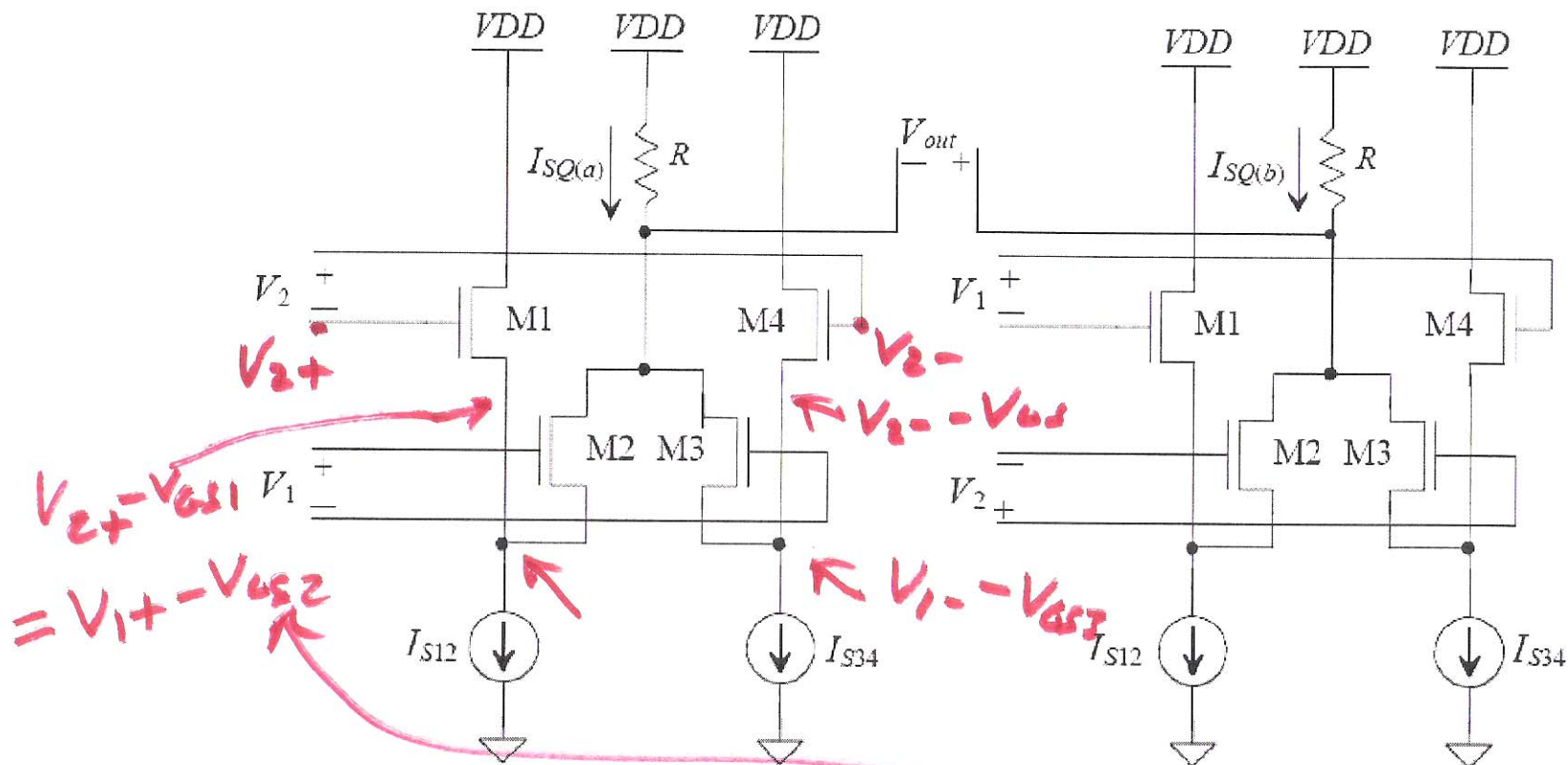


Figure 27.28 (a) Sum-squaring circuit and (b) difference squaring circuit.

$$I_{D1} + I_{D2} = I_{S12}$$

$$I_D = \frac{\beta}{2} (V_{GS} - V_{THN})^2 \rightarrow V_{GS} = \sqrt{\frac{2I_D}{\beta}} + V_{THN}$$