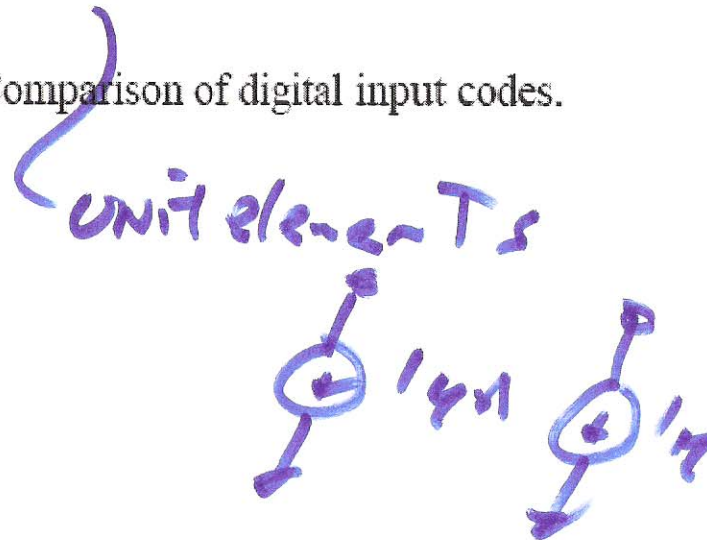


# Sec. 29.1

Decimal	Binary	Thermometer	Gray	Two's Complement
0	000	0000000	000	000
1	001	0000001	001	111
2	010	0000011	011	110
3	011	0000111	010	101
4	100	0001111	110	100
5	101	0011111	111	011
6	110	0111111	101	010
7	111	1111111	100	001

Figure 29.1 Comparison of digital input codes.




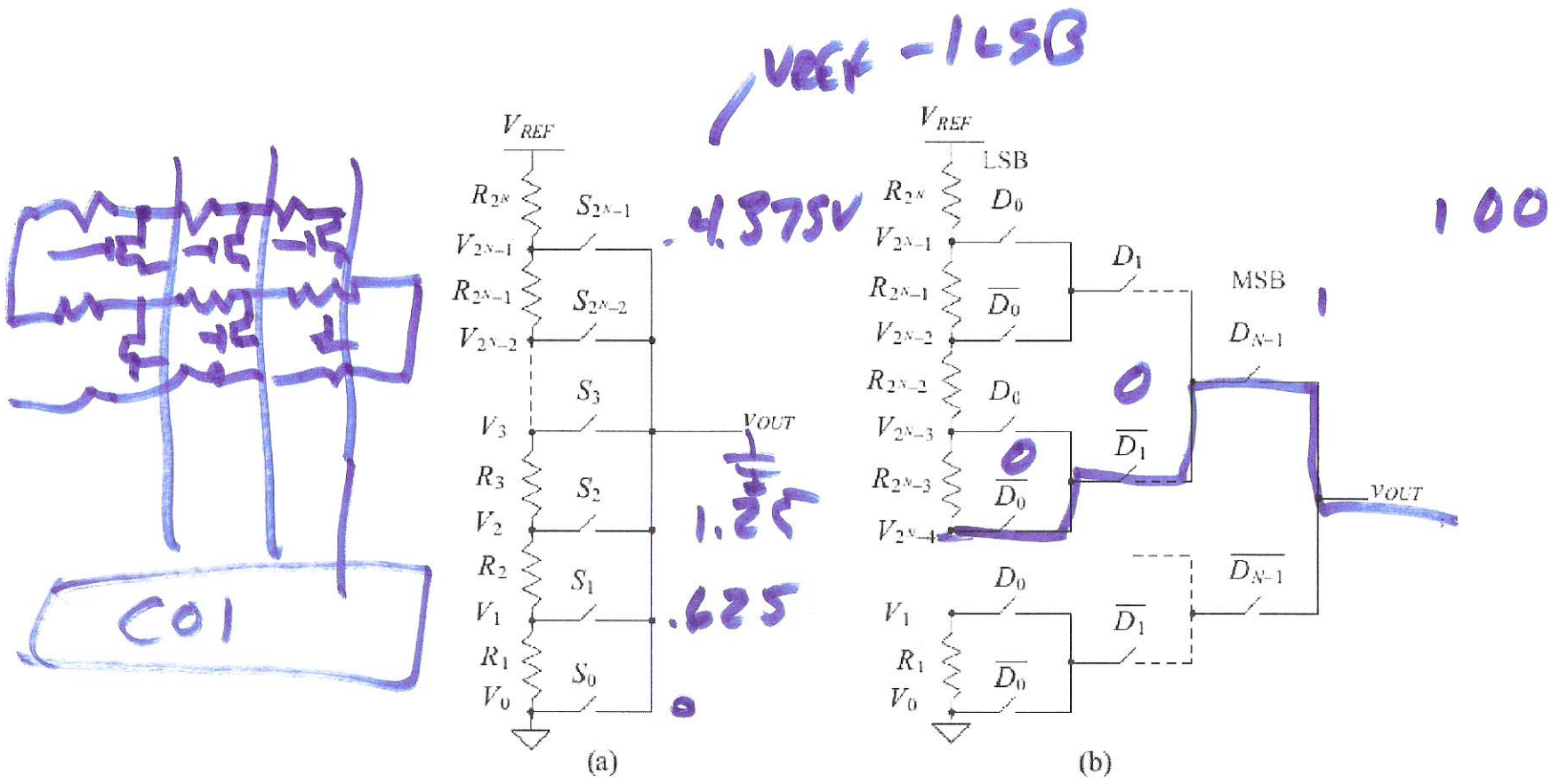


Figure 29.2 (a) A simple resistor-string DAC and (b) the use of a binary switch array to lower the output capacitance.

$$1\text{LSB} = \frac{V_{REF}}{2^N} = \frac{5\text{V}}{2^3} = 0.625$$

$$\frac{\Delta R}{R} = 0.01$$

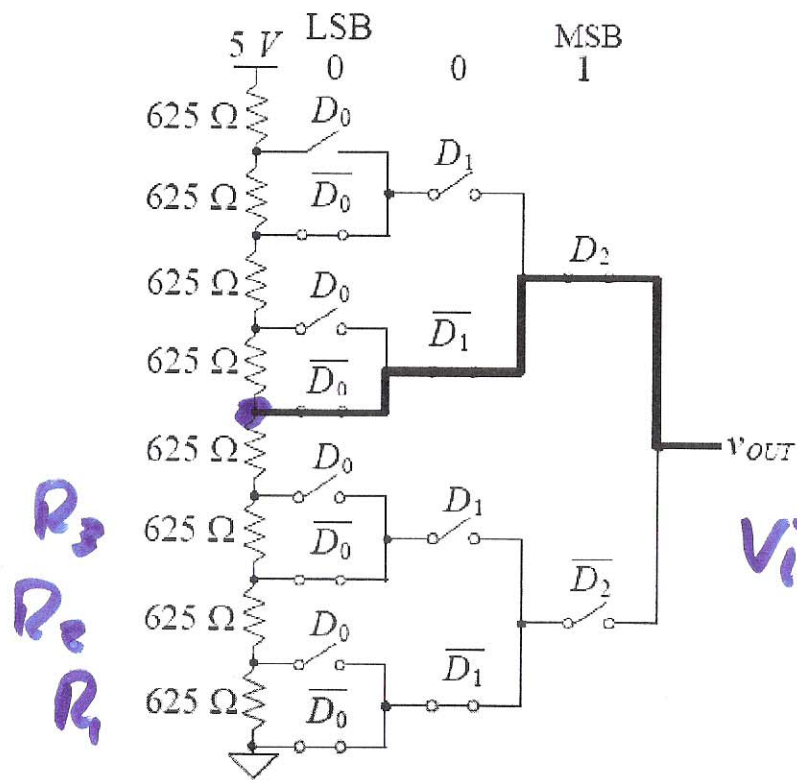

$R_3$   
 $R_2$   
 $R_1$

$$V_i = \frac{\sum_{k=1}^N R_k}{2^N \sum_{k=1}^N R_k} \cdot V_{REF} = \frac{2 \times 20}{5000} \cdot V_{REF}$$

Figure 29.3 A 3-bit resistor string DAC used in Ex. 29.1

$$\frac{\sum_{k=1}^{2^N} R_k}{2^N} = R \quad \leftarrow \text{AVG VALUE}$$

$$R_k = R + \Delta R_k$$

3)

$$V_i = \frac{V_{REF}}{2^N} \cdot \frac{\sum_{k=1}^i (R + \Delta R_k)}{R}$$

$$= \frac{V_{REF}}{2^N} \cdot \frac{1}{R} \left( i \cdot R + \sum_{k=1}^i \Delta R_k \right)$$

What is the ideal value of  $V_i$ ?

$$V_{i,ideal} = \frac{V_{REF}}{2^N} \cdot i$$

$$V_i = V_{i,ideal} + \underset{\substack{\uparrow \\ V_{REF} \\ 2^N}}}{1LSB} \sum_{k=1}^i \frac{\Delta R_k}{R}$$


$$INL = V_i - V_{i,ideal}$$

$$\overline{INL} = \frac{V_{REF}}{2^N} \cdot \sum_{k=1}^i \frac{\Delta R_k}{R}$$

Assume the

$$i < \frac{2^N}{2} \text{ then } \Delta R_k = -\text{MAX } \Delta R$$
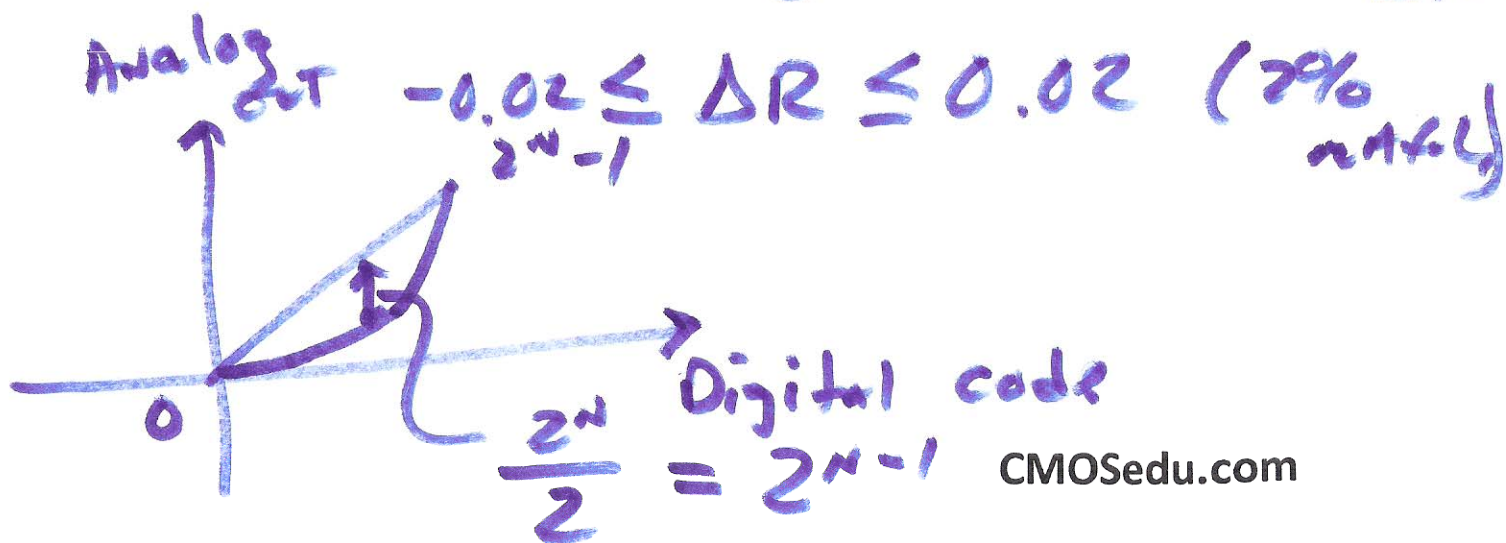
$$i > \frac{2^N}{2} \text{ then } \Delta R_k = +\text{MAX } \Delta R$$





$$INL_{MAX} = \frac{V_{REF}}{2^N} \sum_{k=1}^{2^{N-1}} \frac{\Delta R_k}{R}$$

$$1LSB \rightarrow \frac{V_{REF}}{2^N} \cdot 2^{N-1} \cdot \frac{\Delta R_k}{R} = \frac{V_{REF}}{2} \cdot \frac{\Delta R_k}{R}$$

$$= \frac{1}{2} LSB 2^N \underbrace{\frac{\Delta R_k}{R}}_{\text{mismatch}}$$

CMOS process mismatch  
poly R 1% =  $\frac{\Delta R}{R} = 0.01$

$$INL_{MAX} = \frac{V_{REF}}{2} \cdot 0.01$$

WANT  $\frac{1}{2}$  LSB INL

0.01


$$I_{INL} = \frac{1}{2} \text{ LSB} = \frac{V_{REF}}{2^N} \cdot \frac{1}{2} = \frac{V_{REF}}{2} \frac{\Delta R}{R}$$

$$\frac{\Delta R}{R} < \frac{1}{2^N}$$

for 0.01 mismatch

$N =$ ~~5~~ bits

5 to 6 bits!

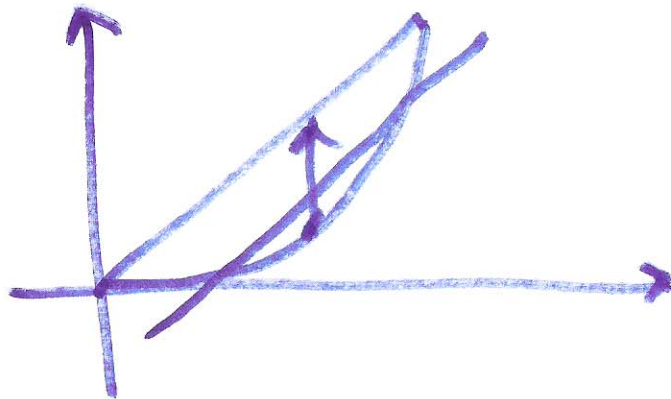

7)

# DNL

$$|V_i - V_{i-1}| =$$

$$\left[ i \cdot \frac{V_{REF}}{2^N} + \frac{V_{REF}}{2^N} \sum_{k=1}^i \frac{\Delta R_k}{R} \right] -$$

$$\left[ (i-1) \cdot \frac{V_{REF}}{2^N} + \frac{V_{REF}}{2^N} \sum_{k=1}^{i-1} \frac{\Delta R_k}{R} \right]$$

$$= \left| \frac{V_{REF}}{2^N} \left( 1 + \frac{\Delta R_{si}}{R} \right) \right|$$

$$DNL = \left( \downarrow \right) - \frac{V_{REF}}{2^N} \Rightarrow DNL = 1 \text{ LSB} \cdot \frac{\Delta R}{R}$$




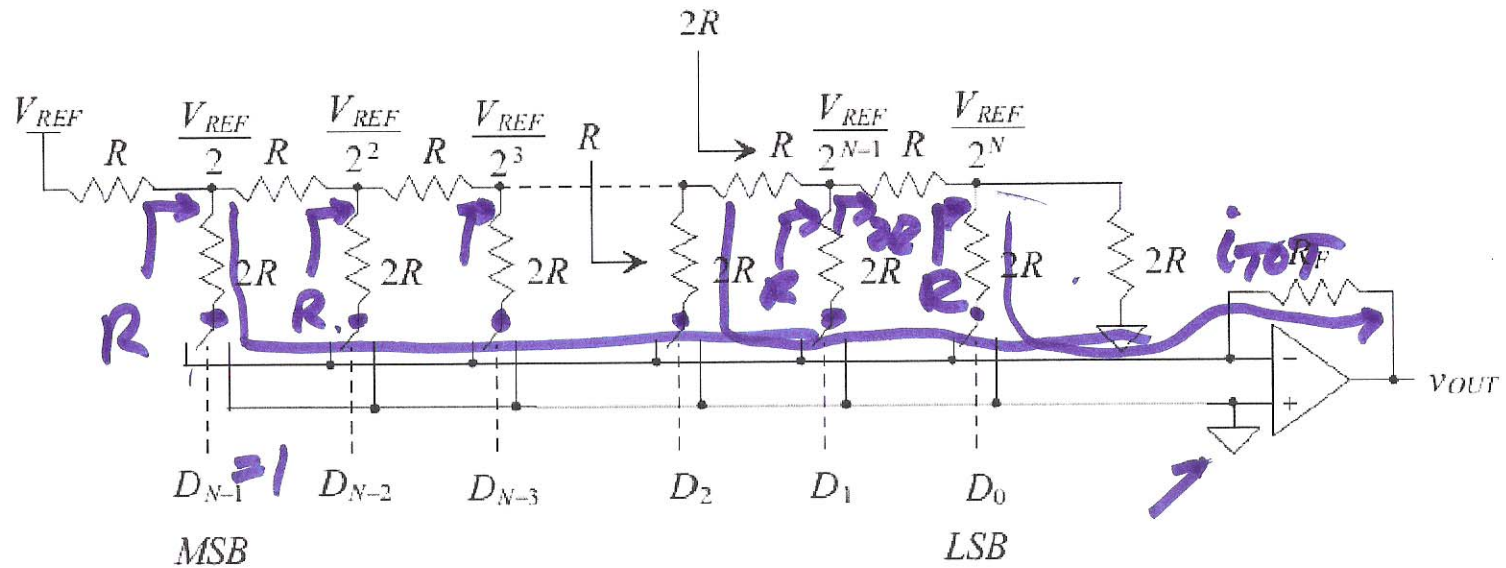


Figure 29.5 An R-2R digital-to-analog converter.

$$V_{OUT} = -i_{TOT} \cdot R_F$$

$$i_{TOT} = \sum_{k=0}^{N-1} D_k \cdot \frac{V_{REF}}{2^{N-k}} \cdot \frac{1}{2R}$$

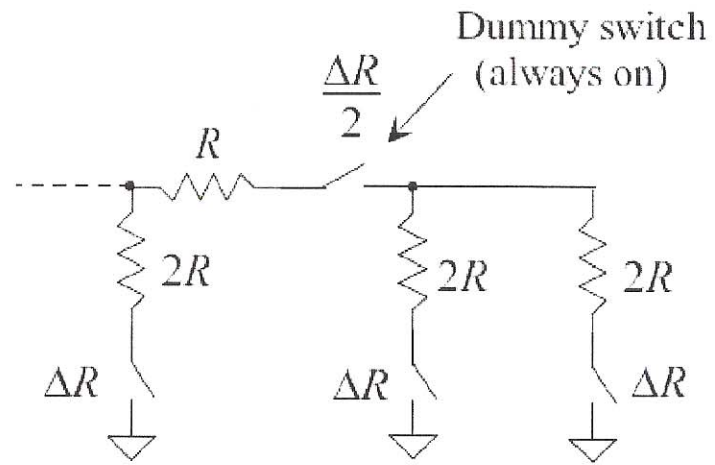

**Figure 29.6** Use of dummy switches to offset switch resistance.

10)

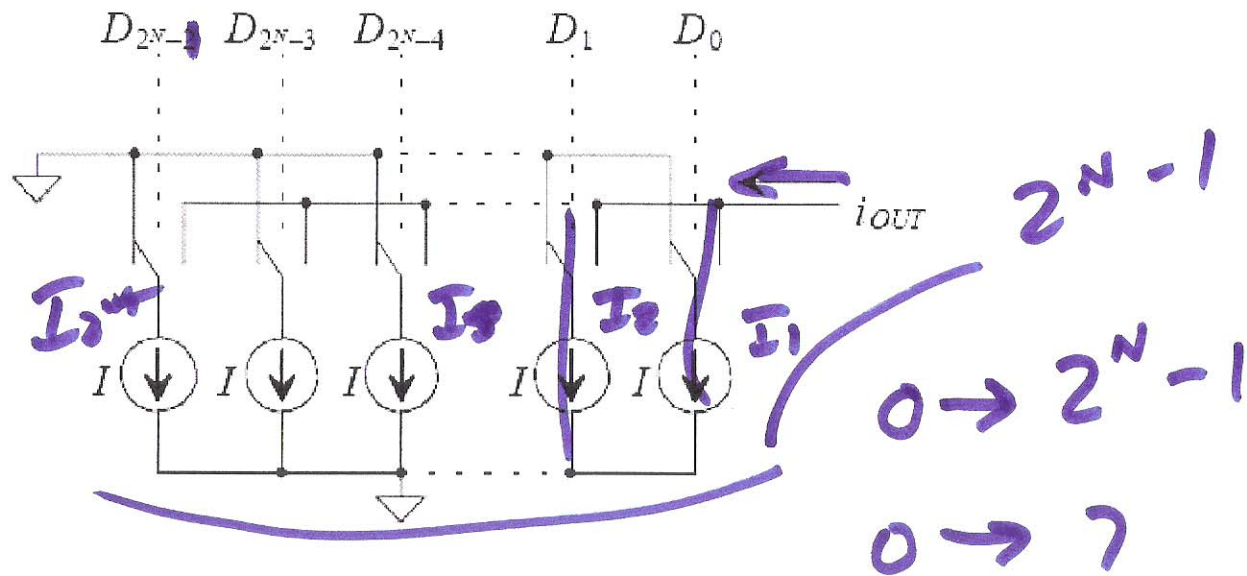


Figure 29.9 A generic current steering DAC.

$I = 1250 = 14A$

000	$\frac{I}{0}$
001	14A
010	24A

Unit elements

$2^N - 1$

$\sum_{k=1}^{2^N - 1} I_k = I(1 + 2 + 4 + \dots + 2^{N-1})$

$I + \Delta I_k$

$I = I_{avg} = \frac{I_k (2^N - 1)}{2^N}$

11)


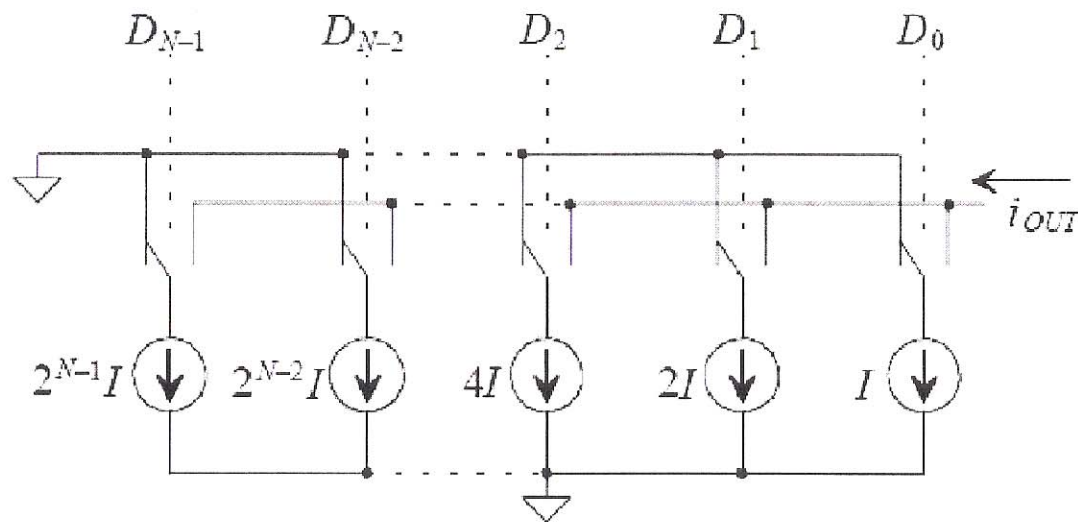


Figure 29.10 A current steering DAC using binary-weighted current sources.

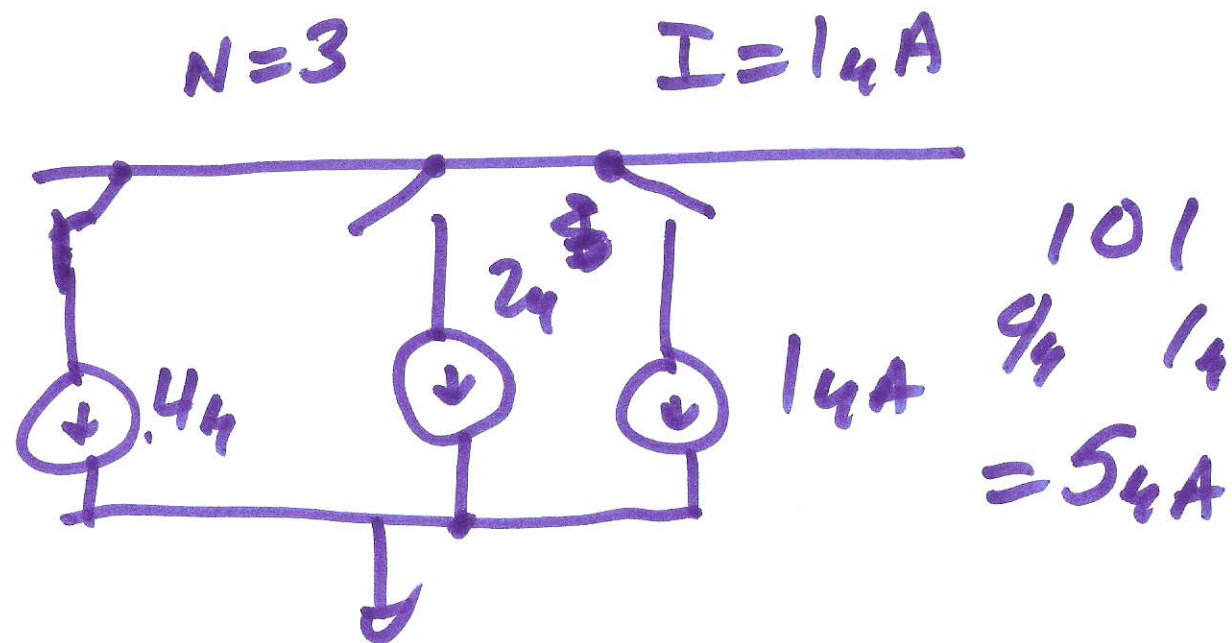

12)

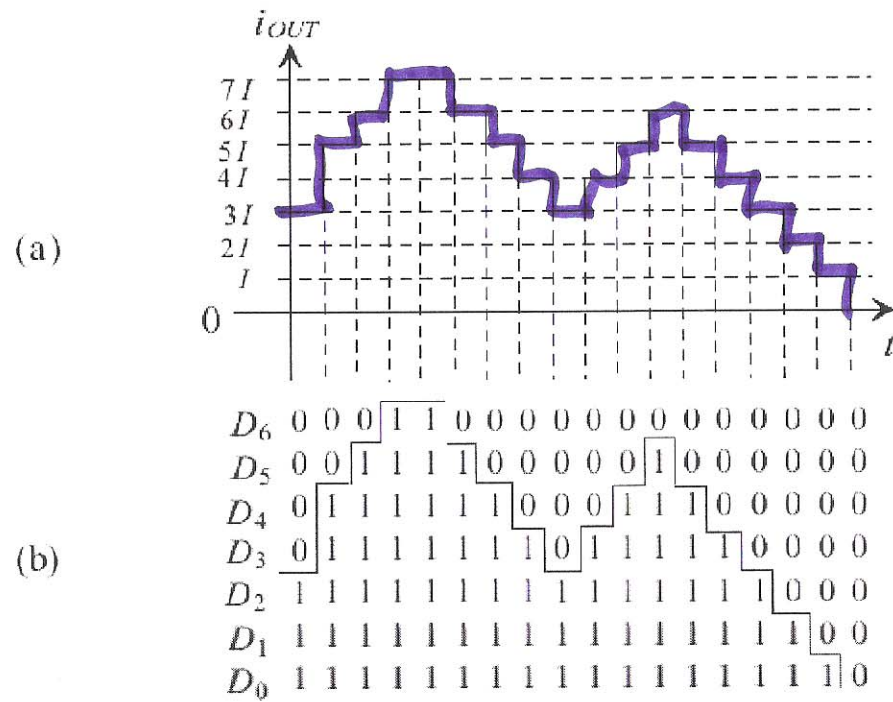


Figure 29.11 (a) Output of a 3-bit current-steering DAC and (b) the thermometer code input.