

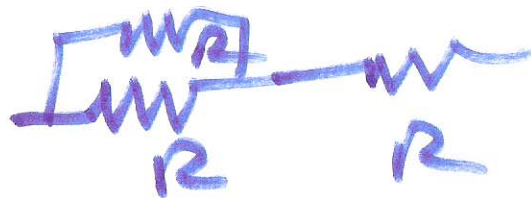
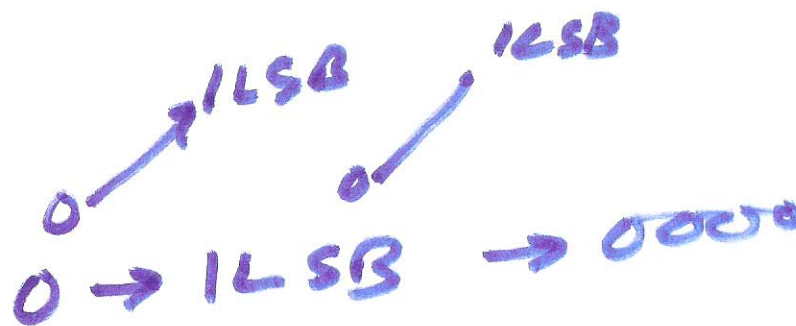



Figure 29.21 Block diagram of a Flash ADC.
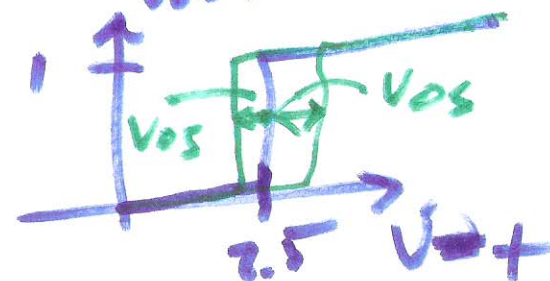
$$\frac{V_{REF}}{2^N} / 2 = \frac{1}{2} \text{ LSB}$$



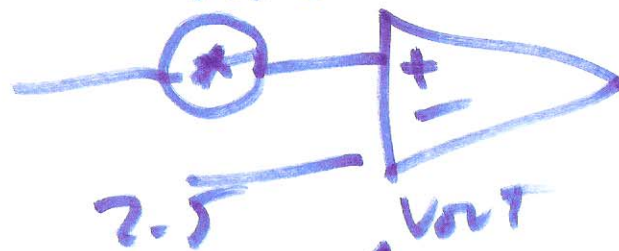29.2 ADCs
 $V_{OS}(\text{can be } + \text{ or } -)$



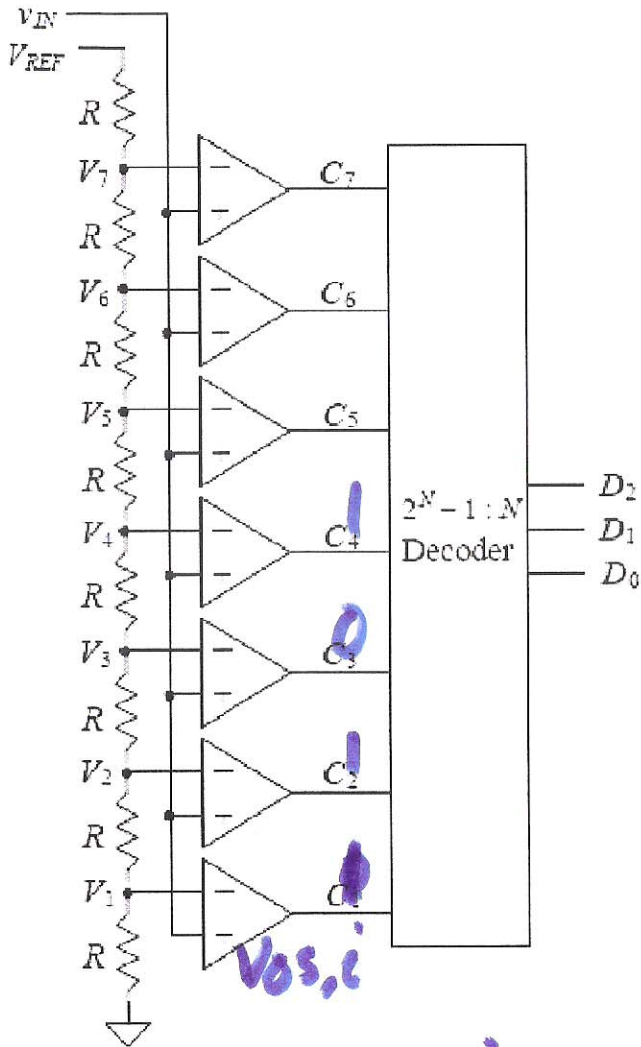

$$V_i = V_{i,ideal} + \frac{V_{REF}}{2^N} \sum_{K=1}^i \frac{\Delta R_K}{R}$$

$$V_{sw,i} = V_i + V_{os,i}$$

$$INL = V_{sw,i} - V_{i,ideal}$$

$$= \frac{V_{REF}}{2^N} \sum_{K=1}^i \frac{\Delta R_K}{R} + V_{os,i}$$

WORST CASE mismatch in middle
 AS BEFORE
 $i = \frac{2^N}{2} = 2^{N-1}$

Figure 29.22 Three-bit Flash A/D converter to be used in Ex. 29.10.

$$V_{i,ideal} = V_{REF} \frac{\sum_{K=1}^i R_K + \Delta R_K}{2^N \cdot R} = \frac{V_{IN}}{2^N} \cdot i \cdot \frac{R}{R}$$

$R_1 = R_2 = R_3$ LSBs

2)

$$I_{NL, worst} = 1 \text{ LSB} \cdot \sum_{k=1}^{2^n-1} \frac{\Delta R_k}{R} + V_{os, i}$$

$$= \frac{V_{REF}}{2^n} \cdot 2^{n-1} \frac{\Delta R_{kmax}}{R} + V_{os, max}$$

$$= \frac{V_{REF}}{2} \cdot \left| \frac{\Delta R_{kmax}}{R} \right| + |V_{os, i}|_{max}$$

if $V_{REF} = 2$

$$= \frac{2}{2} \cdot |0.005| + \frac{10 \text{ mV}}{10 \text{ mV}}$$

8-bits

V_{offset}

5 μ biggest influence
in general

256 comparators

6-bits without calibration

$$DNL_{\text{max}} = \underbrace{V_{i,\text{ideal}} - V_{i-1,\text{ideal}}}_{1\text{LSB}} + \frac{V_{\text{REF}}}{2^n} \cdot \frac{\Delta R_i}{R} + V_{\text{os},i} - V_{\text{os},i-1} - 1\text{LSB}$$

$$DNL_{\text{max}} = \frac{V_{\text{REF}}}{2^n} \cdot \frac{\Delta R_i}{R} + |2V_{\text{os},\text{max}}|$$

\uparrow
 $V_{\text{os},\text{max}} = -V_{\text{os},\text{min}}$

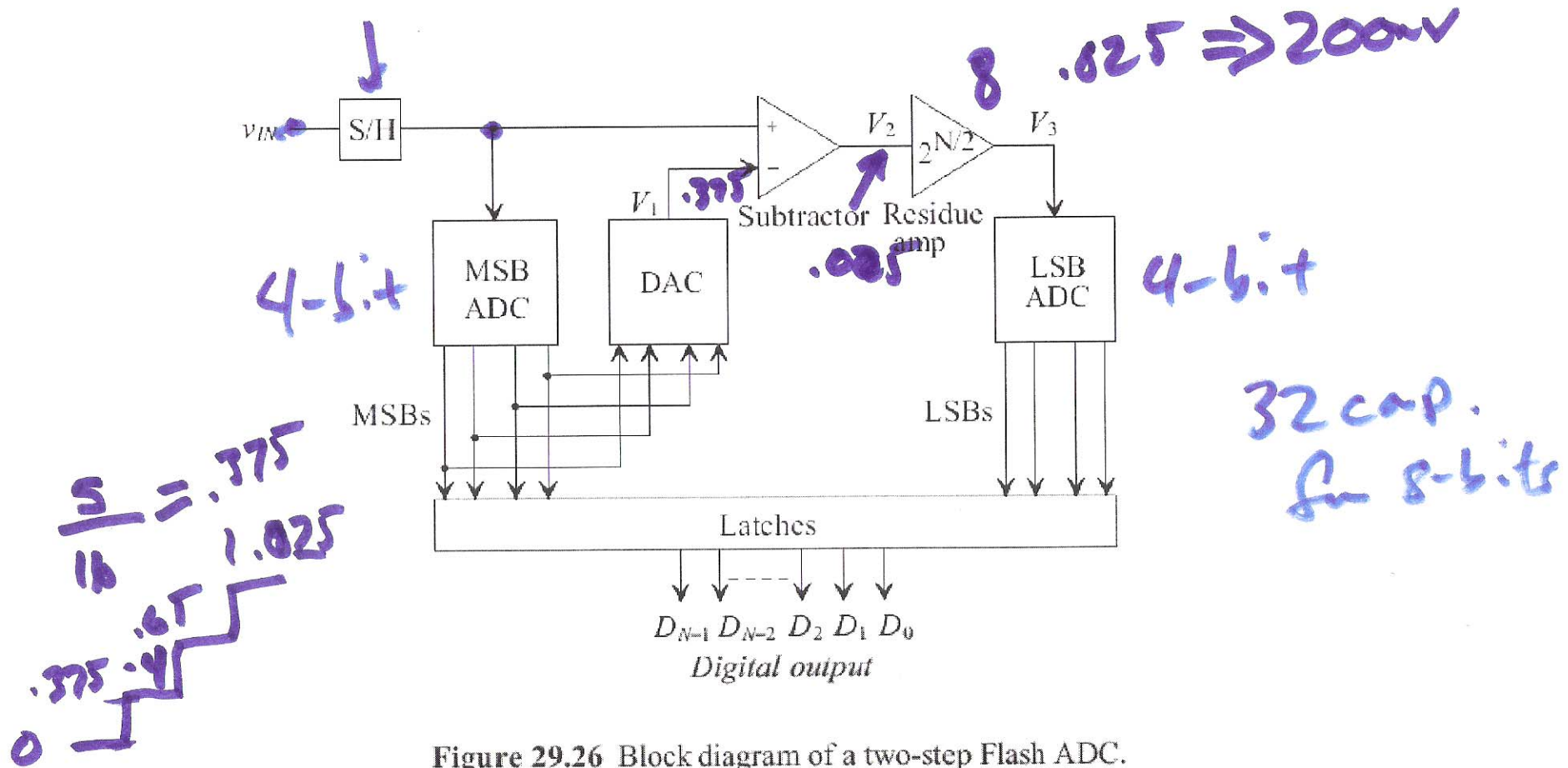


Figure 29.26 Block diagram of a two-step Flash ADC.

8-bit Flash 255 Cap
 FLASH $2^N - 1$ COMPARATORS

5)

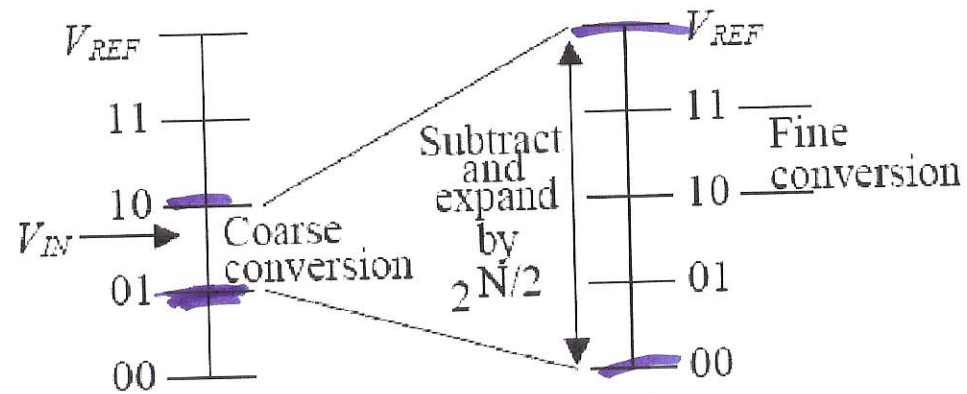


Figure 29.27 Coarse and fine conversions using a two-step ADC.

6)

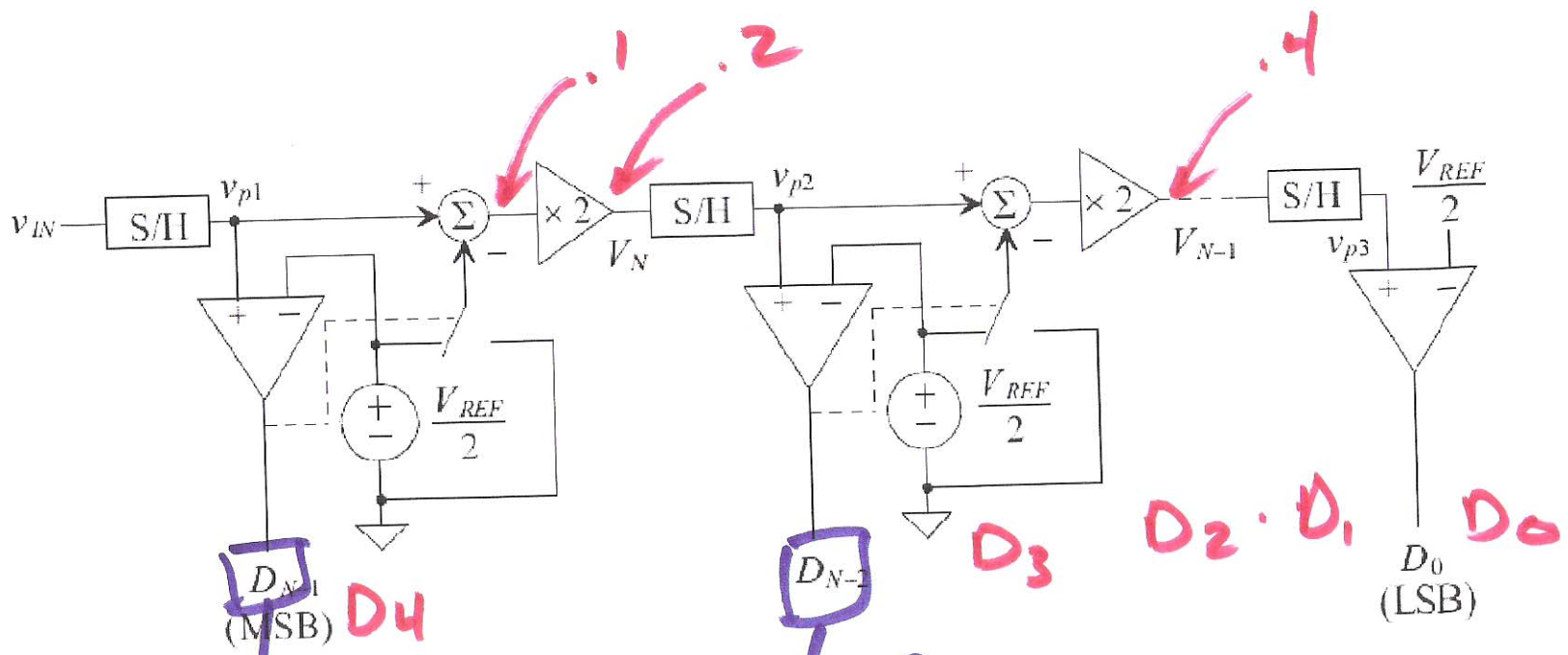


Figure 29.30 Block diagram of a pipeline ADC.

$$\frac{V_{in}}{.6}$$

- $D_4 = 1$
- $D_3 = 0$
- $D_2 = 0$
- $D_1 = 1$

10011

$$V_{REF} = 1 \begin{array}{r} .8 \\ - .1 \\ \hline .3 \end{array}$$

$$\frac{V_{REF}}{2^n} = \frac{1}{32} = 0.03125$$

$$D_0 = 1 \quad 1 + 2 + 16 = \mathbf{19 \cdot 03125}$$



$$A_{CL} = \frac{A_{OL}}{1 + \beta A_{OL}} = \frac{1}{\beta} - \Delta A$$

Accuracy issues in op-amps, ideally $\Delta A = 0$ & $A_{OL} = \infty$

$$\frac{1}{\beta} = 2^N \quad \text{error to } < \frac{1}{2} V_{LSB}$$

$$< \frac{V_{REF}}{2^{N+1}}$$

$$A_{OL} = \frac{1}{\beta} (1 + \beta A_{OL}) - \Delta A (1 + \beta A_{OL})$$

$$= \frac{1}{\beta} + A_{OL} - \Delta A - \beta A_{OL} \cdot \Delta A$$

$$\beta A_{OL} \cdot \Delta A$$

$$A_{OL} (1 + \beta A_{OL})$$

$$= 2^{N+1} - \Delta A$$

$$A_{OL} = \frac{2^{N+1}}{\beta} - \frac{1}{\beta} = \frac{1}{\beta} (2^{N+1} - 1)$$

8)

$$A_{OL} \approx \frac{2^{N+1}}{\beta} \quad \text{for a } \frac{1}{2} \text{ LSB error}$$

for pipeline $\beta = \frac{1}{2}$

$$A_{OL} \Big|_{\text{ideal}} = \frac{1}{\beta}$$

$$V_{out} \left(1 - \frac{1}{2^{N+1}} \right)$$

$$f_{un} \geq \frac{f_{clk} \cdot 2^{N+1}}{\pi \cdot \beta}$$

unity gain freq.

9)