

30.1

 


Figure 30.1 Traditional current-mode R-2R DAC.

- To be added



 


Figure 30.2 Traditional voltage-mode R-2R DAC.

full output swing
 $0 \rightarrow VDD$

 

 Bad if common-mode voltage on op-amp inputs varies




V_{REFP}

$V_{REFn} + 1\text{LSB}$

- To be added

$$V_{REFP} - 1\text{LSB}$$

 

$$\frac{V_{REFP} + V_{REFM}}{2}$$

$$V_{REFP} - \frac{V_{REFP}}{2} - \frac{V_{REFM}}{2}$$

$$I = \frac{-I \cdot R}{R}$$

$$I = \frac{V_{REFP} - V_{REFM}}{-\frac{V_{REFP}}{2} + \frac{V_{REFM}}{2} + \frac{2R}{Z} + \frac{V_{REFP} + V_{REFM}}{Z}}$$


Figure 30.3 Wide-swing current-mode R-2R DAC.


$$-I \cdot R + \frac{V_{REFP} + V_{REFM}}{2}$$

Table 30.1 Summary of experimental results.

	8-bit	10-bit	12-bit
DNL (LSB)	0.150	0.450	2.000
INL (LSB)	0.200	1.000	3.000
Settling time		200 ns	
Power		3.88 mW (driving a 1k load)	
Area (mm ²)		0.045	
$f_{clk,max}$		4 MHz	
Output swing		$0 < V_{out} < VDD (= 1.8 V)$	


- To be added

 

 

D.N.L Analysis:

 
$$\frac{V_{REFP} - V_{REFM}}{2(R + \Delta R)}$$



 6)

$\Delta I =$

$$\frac{V_{REF+} - V_{REF-}}{4(R-\Delta R)} - \frac{V_{REF+} - V_{REF-}}{4\Xi(R+\Delta R)}$$



ΔI

$$\frac{V_{REFP} - V_{REFm}}{2(2(R+\Delta R))} \neq \frac{V_{REFP} - V_{REFm}}{2(2(R-\Delta R))} +$$

$$+ \frac{V_{REFP} - V_{REFm}}{2(2(R+\Delta R))} \neq \frac{V_{REFP} - V_{REFm}}{2(2(R-\Delta R))}$$

8)

UNIV
UNIVERSITY OF NEVADA LAS VEGAS


 


Figure 30.5 Showing how currents sum into the feedback current.

- To be added

 

- To be added


$$1023 \rightarrow 1024$$

$$2047 \rightarrow 2048$$


Figure 30.6 Segmentation in a wide-swing R-2R DAC.

helps DNL

but no help for INL

 


(a) Showing offset voltage in an op-amp.

 

(b) DAC transfer curves showing offset.

Figure 30.7 Showing how an op-amp offset affects the DACs transfer curves.

- To be added

 



 


Figure 30.8 Trimming circuit for DAC offset.

- To be added

 

 
(a) DAC transfer curves before calibration.




(b) DAC transfer curves after offset calibration

Figure 30.10 Showing how INL can be seen as an offset error.

- To be added

 

(a) DAC transfer curves with gain error.

 

(b) DAC transfer curves after offset calibration with gain error.

Figure 30.11 Showing gain error and how it can cause problems in an offset calibration.

- To be added


 
 


Figure 30.12 Trimming the output of the DAC using (a) current and (b) voltage.

- To be added

 

- To be added

 


Figure 30.14 Voltage-mode (5-bit) DAC without an op-amp.

- To be added



 


Figure 30.15 Example output for the 10-bit DAC in Ex. 30.1 showing settling time limitations.

- To be added

 

Current-source-based cell.

 

Resistor-based cell.

Figure 30.18 Basic cell used in a current-mode DAC.

- To be added

 


Figure 30.19 Implementation of a current-mode DAC.

- To be added

 


Figure 30.20 W-2W current mirror.

- To be added