
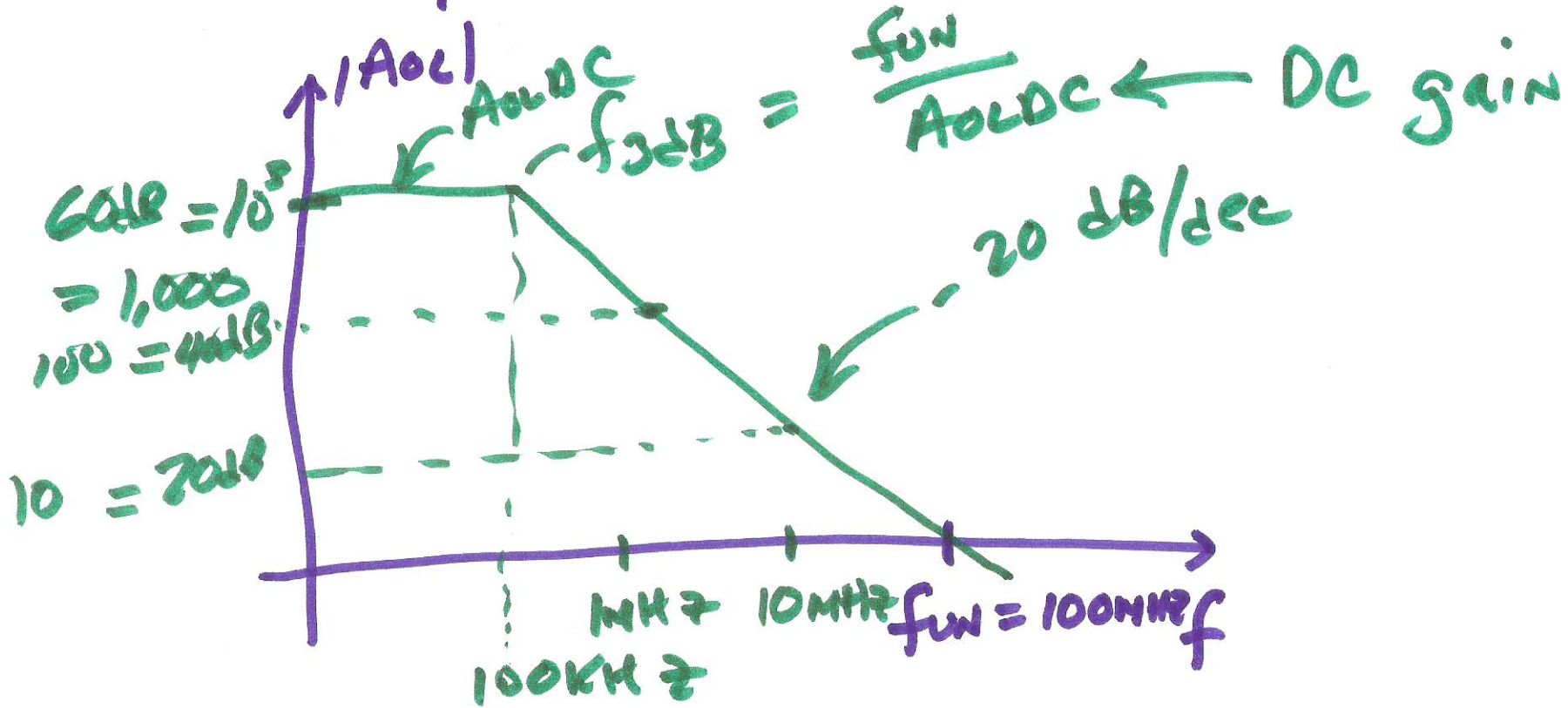


OP-AMPS IN DATA CONVERTERS

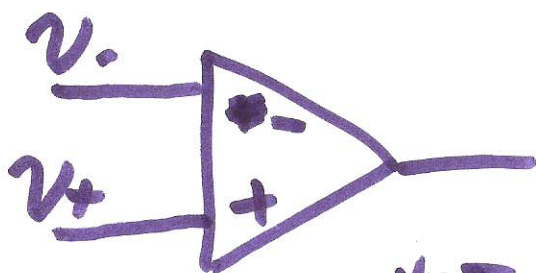

$$A_{OL}(f) = \frac{10^3}{1 + j \cdot \frac{f}{100 \text{ kHz}}}$$




$$v_{out} =$$

$$= A_{OL}(f) \cdot (v_+ - v_-)$$



1)

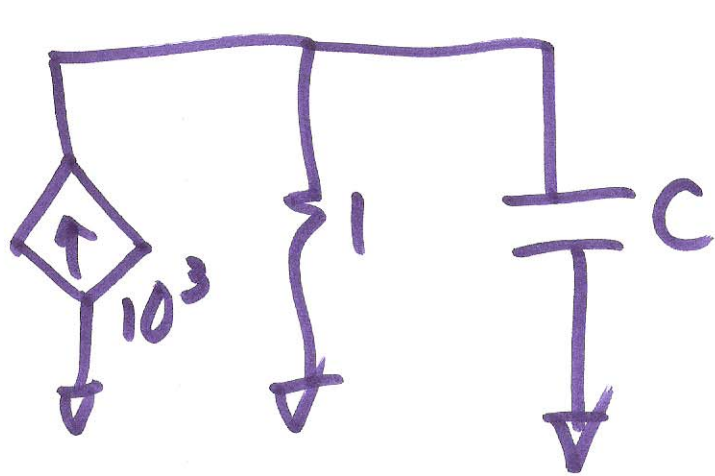

$$f_{3dB} = \frac{1}{2\pi RC}$$

10^5 (with an arrow pointing to the f_{3dB} term)

$$C = \frac{1}{2\pi \cdot 10^5}$$

$$= 159 \cdot 10^{-5}$$

$$= 159 \cdot 10^{-8}$$

$$= 1.59 \cdot 10^{-6}$$

$$\underline{\underline{1.59 \mu F}}$$

$$\frac{10^3}{1 + jf/f_{3dB}}$$

$100kHz$ (with an arrow pointing to the f_{3dB} term)

2)


$$A_{cl} = \frac{f_{uw}}{A_{cl}} = f_{cl}$$

$$f_{uw} = A_{cl} \cdot f_{cl}$$

↑
closed loop

Non-inverting topology

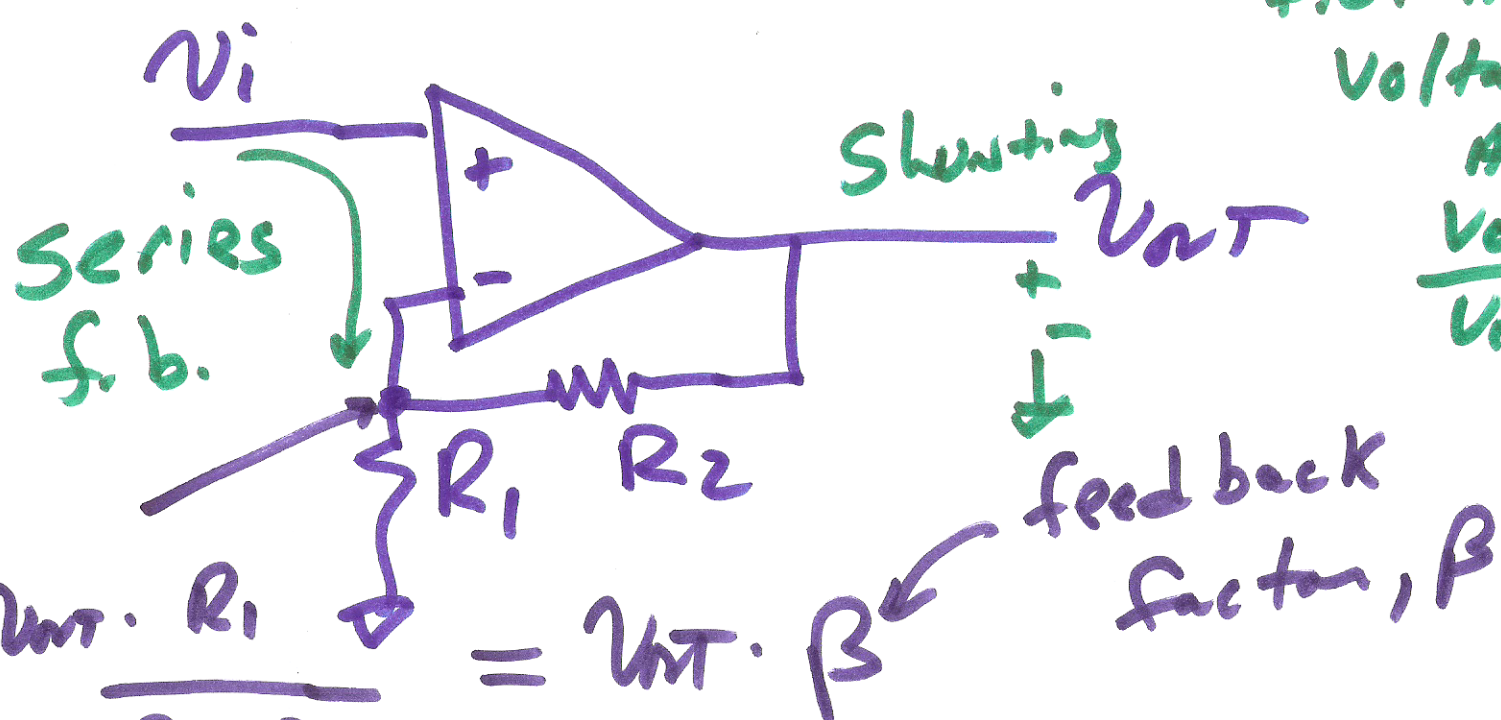Series-shunt
f.b. and
Voltage
and
 $\frac{V_o}{V_i}!$




$$V_f = \frac{V_{out} \cdot R_1}{R_1 + R_2} = V_{out} \cdot \beta$$

β

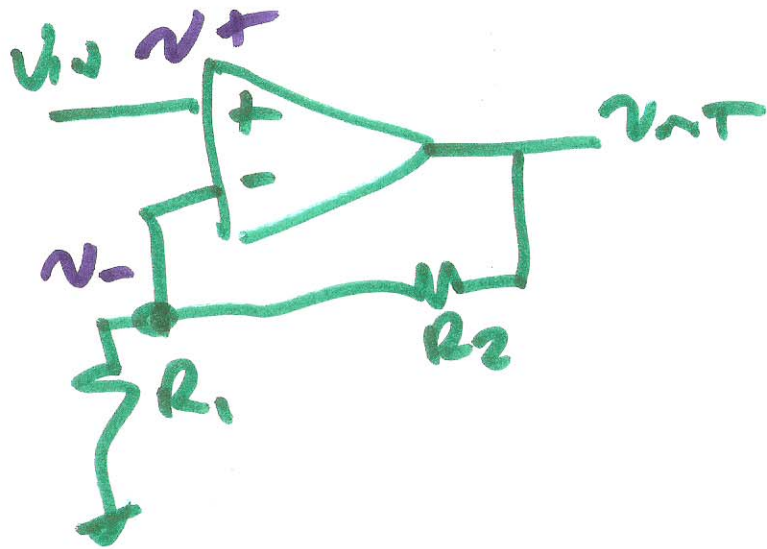3)

$$A_{OL}(f) = \frac{A_{OLDC}}{1 + j \frac{f}{f_{3dB}}}, \quad f_{3dB} = \frac{f_{uL}}{A_{OLDC}}$$



$$\beta \cdot v_{OUT} = v_{in}$$

$$v_{OUT} = A_{OL}(f) \cdot (v_{+} - v_{-})$$

$$\beta \cdot v_{OUT}$$

4)

$$|A_{CL}| \approx \frac{f_{uL}}{f}$$


$$\left| \frac{v_{OUT}}{v_{in}} \right| = |A_{CL}| = \frac{f_{uL}}{f}$$

$$A_{CL} = \frac{v_{OUT}}{v_{in}} = \frac{A_{OL}(f)}{1 + A_{OL}(f) \cdot \beta}$$

$$A_{OL} \approx \frac{A_{OLDC}}{j \frac{f}{f_{3dB}}} = \frac{A_{OLDC}}{f}$$

CMOSedu.com

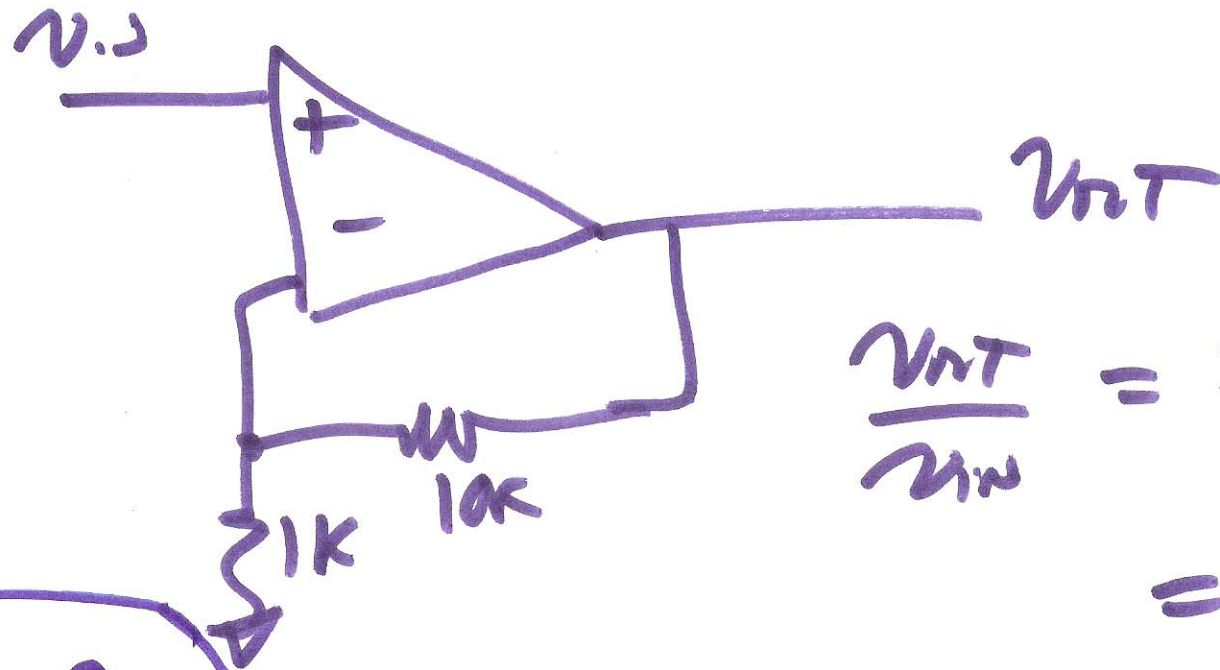$f_{un} = 100 \text{ MHz}$ find f_{3dB} for:



$$\frac{v_{oT}}{v_{in}} = \frac{1k + 10k}{1k}$$

$$= 1 + \frac{10k}{1k}$$

$$A_{CL} = 11$$

$$A_{CL} f_{3dB} = \frac{100 \text{ MHz}}{11}$$


$$f_{3dB} \Big|_{\text{closed loop}} = 9.091 \text{ MHz}$$

$$f_{CL} \Big|_{3dB} = \frac{f_{un}}{A_{CL}}$$

Voltage
AMP
Series-shunt

6)

Inverting Amp

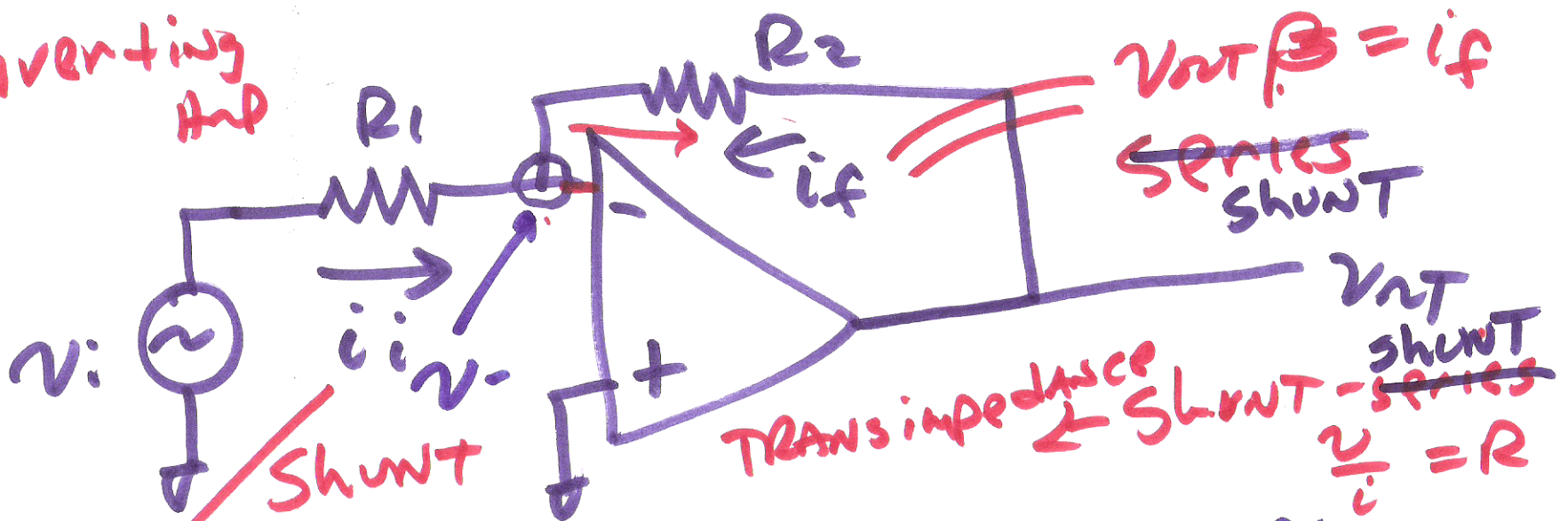

$$\frac{v_i - v_-}{R_1} = - \frac{v_{out} - v_-}{R_2}$$

$$\frac{v_i}{R_1} = i_i$$

$$\beta = -1/R_2$$


$$A_{CL} = \frac{v_{out}}{i_i} = -\frac{1}{R_2}$$

$$|A_{CL}| = \left| \frac{v_{out}}{v_i} \right| = \frac{R_2}{R_1}$$

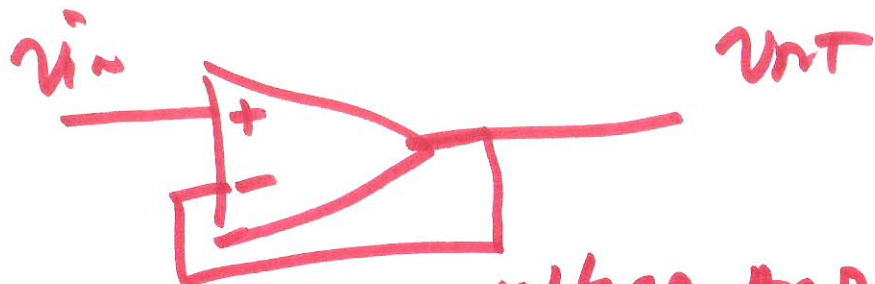7)

$$f_{3dB, CL} \approx \frac{R_1}{R_1 + R_2} \cdot f_{un}$$


$$Gain \cdot BW = \frac{R_2}{R_1 + R_2} \cdot f_{un}$$



voltage amp

$$\left| \frac{v_{out}}{v_{in}} \right| = 1$$

$$f_{CLBW} = f_{un}$$

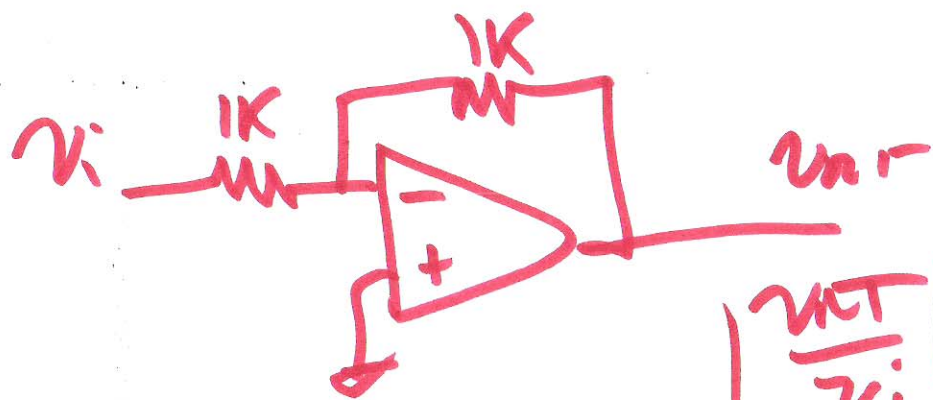

$$\left| \frac{v_{out}}{v_i} \right| = 1$$

$$f_{CLBW} = \frac{f_{un}}{2}$$

8)