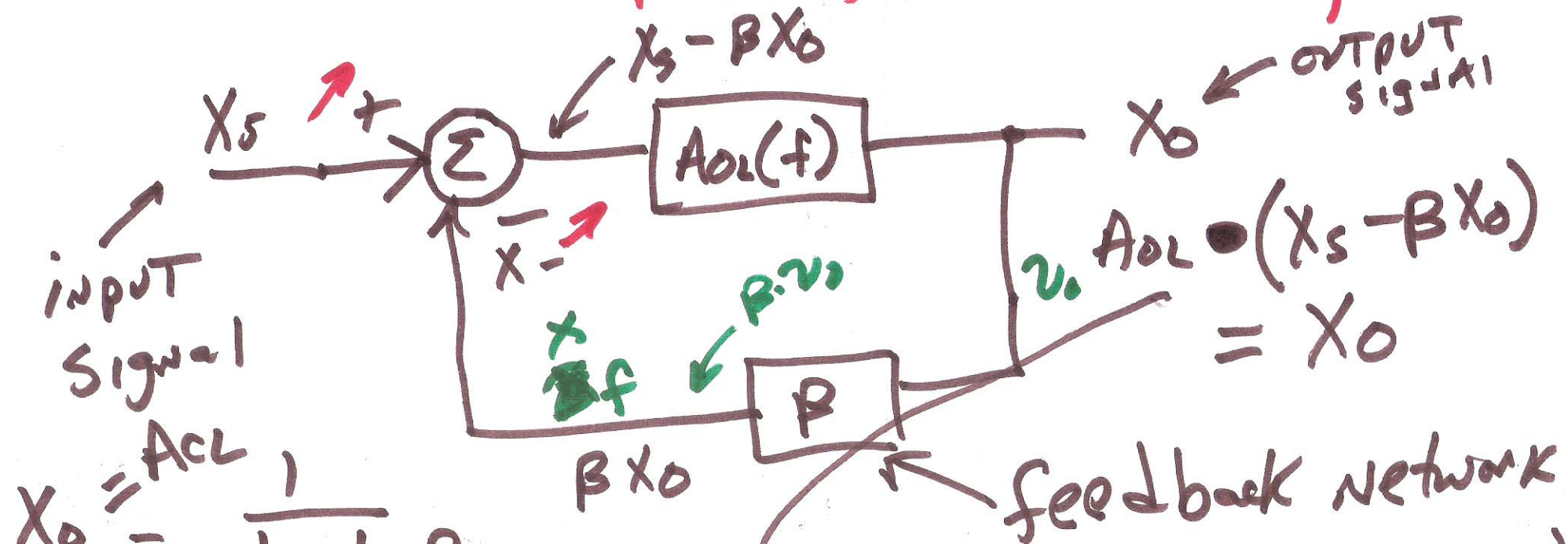


# Sec. 31.1

## The feedback Eq.



$$\frac{X_o}{X_s} = A_{CL} = \frac{1}{\frac{1}{A_{OL}} + \beta}$$

$$A_{OL} \rightarrow \infty \left\{ A_{CL} = \frac{X_o}{X_s} \approx \frac{1}{\beta} \right.$$


$$A_{OL} \cdot X_s = X_o (1 + A_{OL} \beta)$$

$$A_{CL} = \frac{X_o}{X_s} = \frac{A_{OL}}{1 + \beta A_{OL}}$$


$$A_{CL} \geq 10 \quad \beta \geq 0.1$$

$$\beta \cdot A_{OL} = \text{loop gain}$$

$$\beta = \text{feedback factor}$$

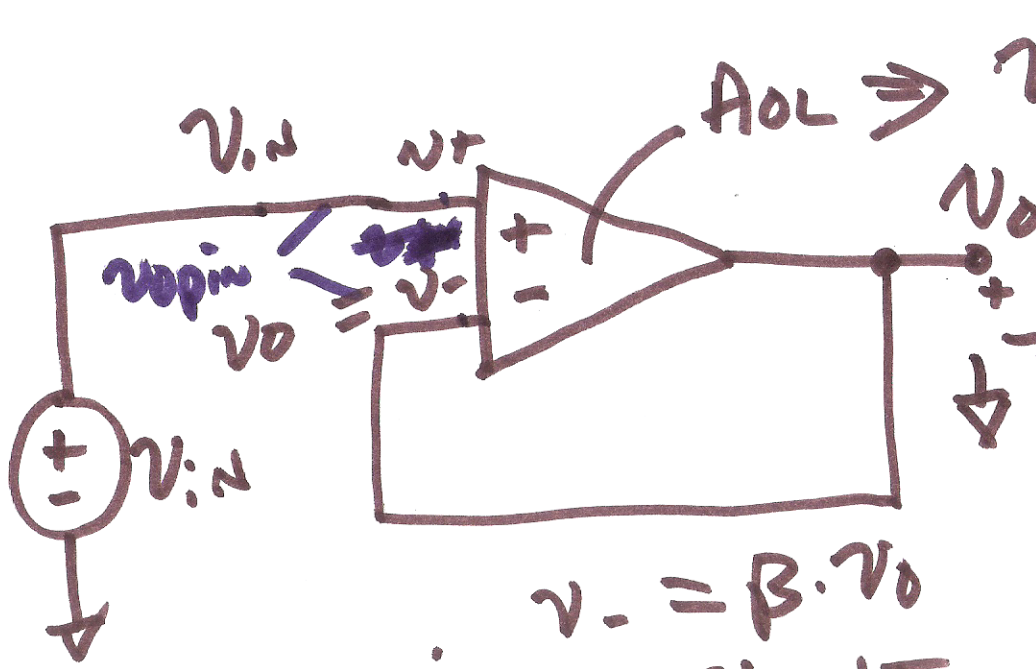

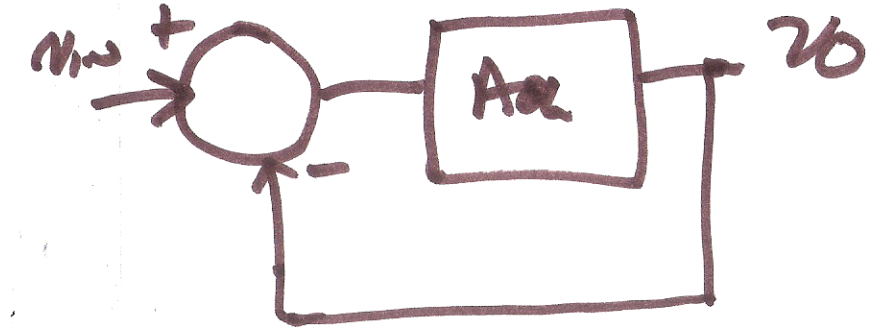$A_{OL} \Rightarrow v_o = A_{OL} (v_+ - v_-)$   
 $= A_{OL} (v_{iN} - v_{out})$   
 open loop gain of op-amp




$v_- = \beta \cdot v_o$   
 SERIES - SHUNT  
 $v_+ - v_- = v_{iN}$   
 $v_{iN} = v_{opin} + v_o$

$\beta = 1$   
 ideally  $v_o = v_i$   
 $v_o = \frac{A_{OL}}{1 + \beta A_{OL}} \cdot v_i$

2)

$v_i$  series - shunt

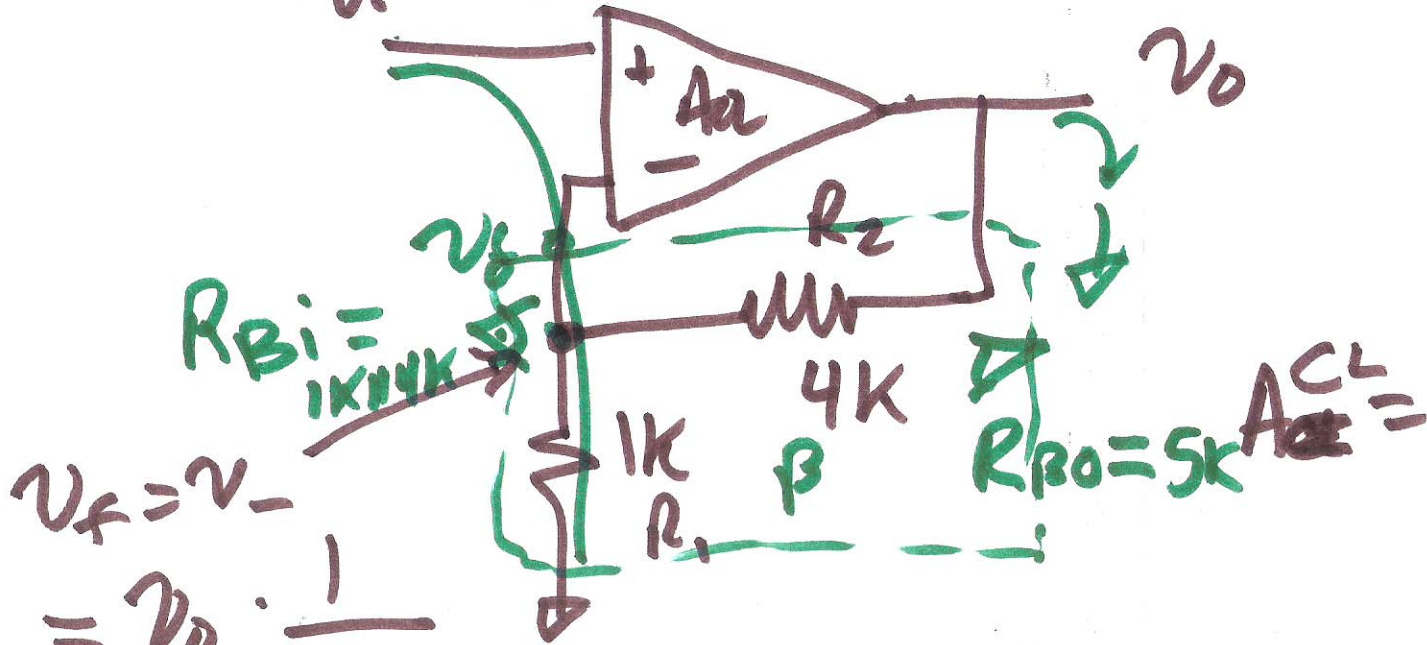


$v_f = v_-$   
 $= v_o \cdot \frac{1}{1+4}$   
 $\beta = \frac{1}{5}$

ideally then

$A_{CL} = 5 = 1 + \frac{R_2}{R_1}$

$Bv_o = \frac{1}{5} v_o$

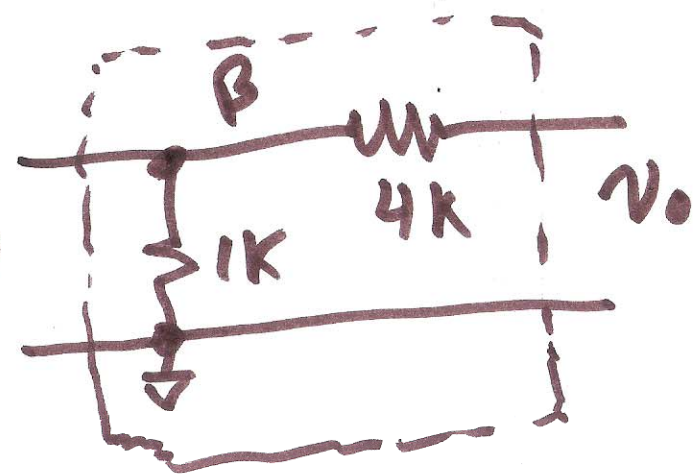


$A_{CL} \Big|_{\text{ideally}} = \frac{1}{\beta}$


$\frac{A_{OL}}{1 + \beta A_{OL}} \rightarrow \frac{1}{5}$

3)



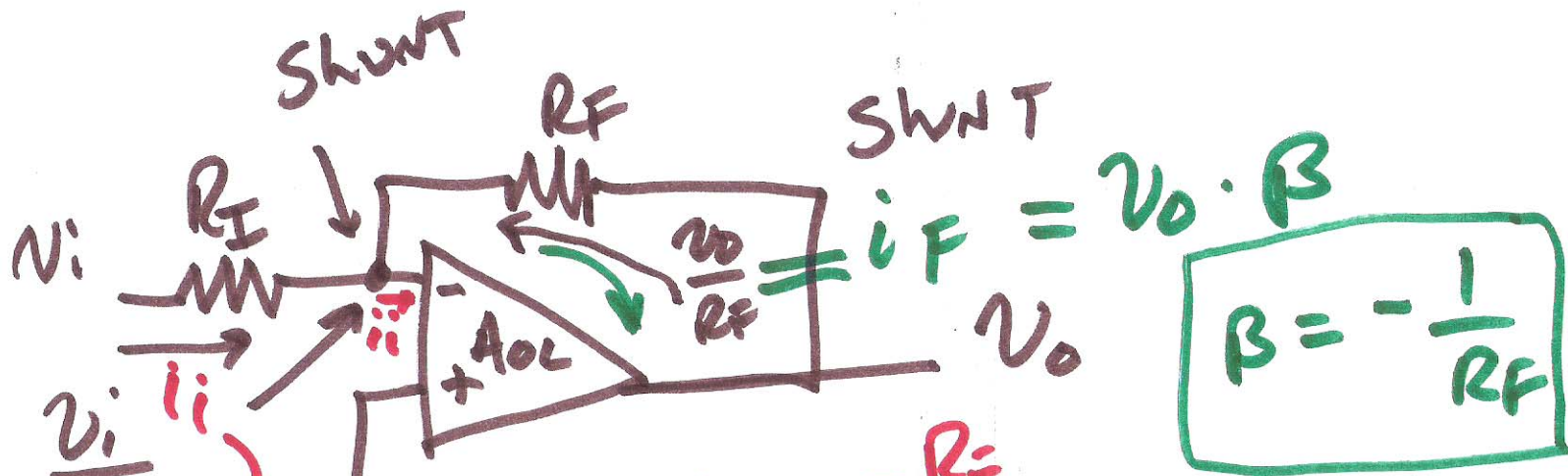


$$A_{cl} = -\frac{R_F}{R_I}$$

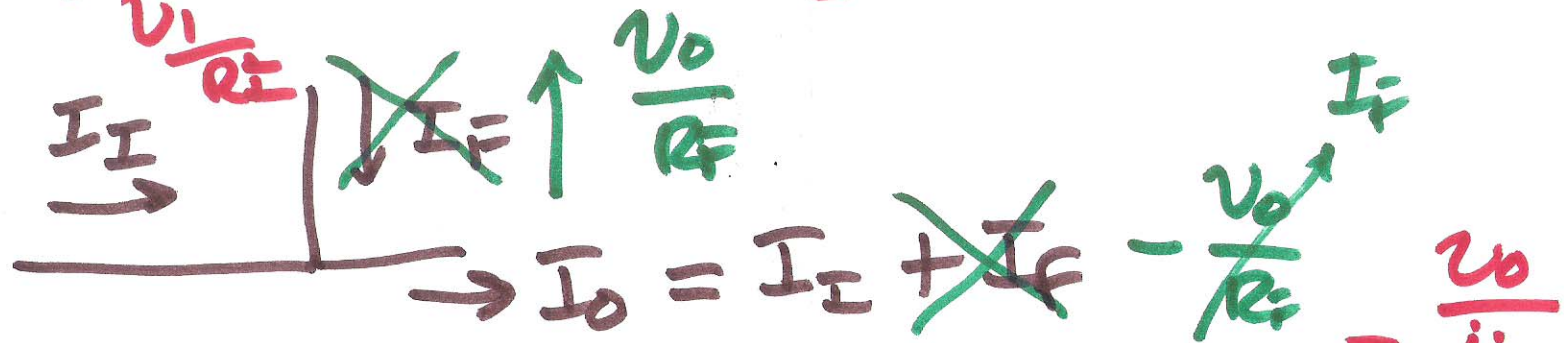


$$A_{cl} = \frac{v_o}{i_i} = \frac{v_o}{v_i/R_I} = \frac{A_{ol}}{1 + A_{ol} \cdot \left(-\frac{1}{R_F}\right)}$$

$$A_{ol} \rightarrow \infty \quad A_{cl} = -\frac{R_F}{R_I}$$


4)

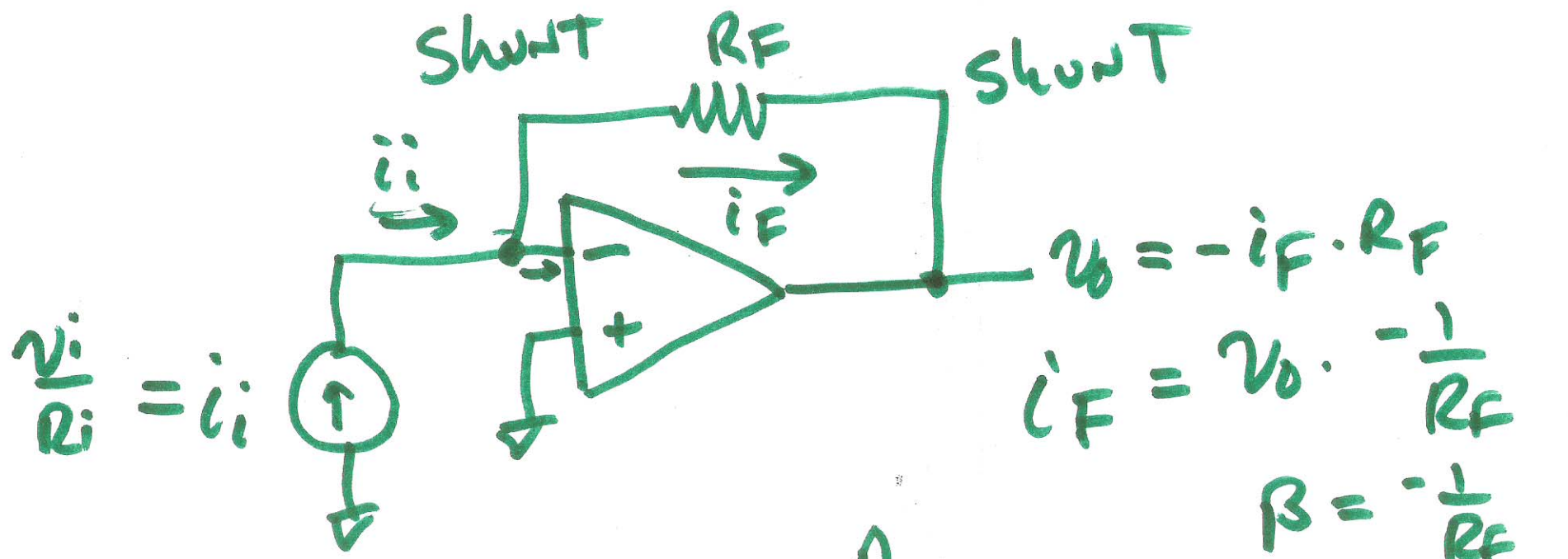

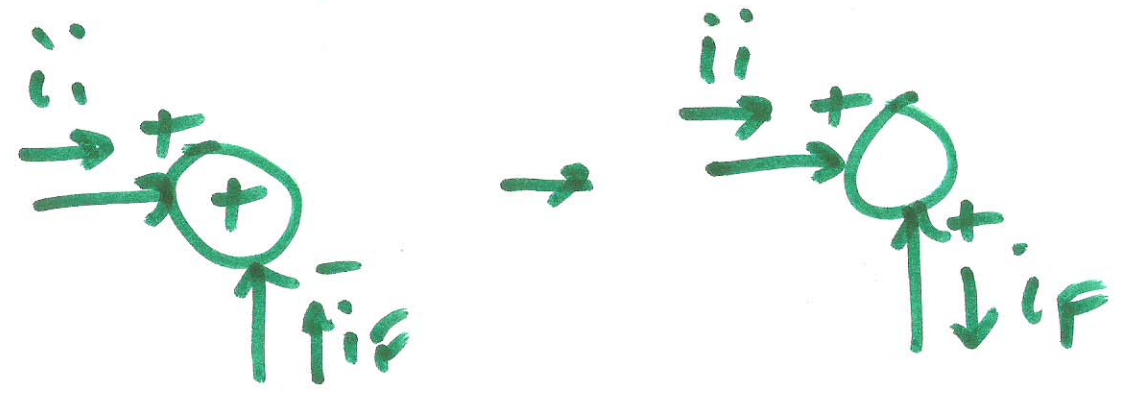
$$A_{CL} = \frac{v_o}{i_i} = \frac{A_{OL}}{1 + A_{OL} \cdot \beta} \Rightarrow \left. \begin{array}{l} -R_F \\ A_{CL} \rightarrow \infty \end{array} \right\}$$




5)

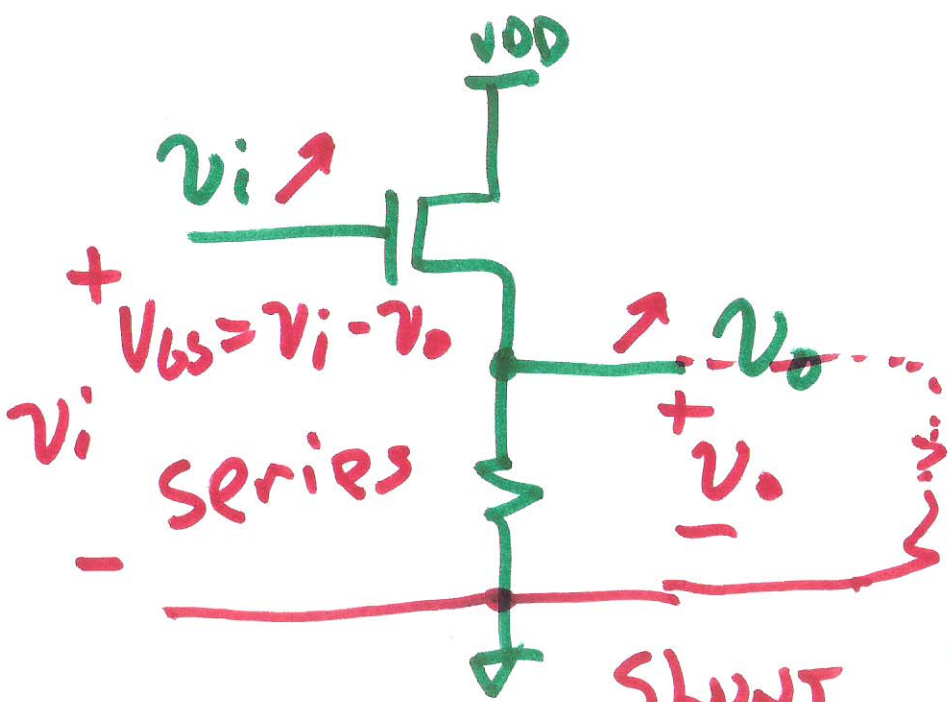

Series-shunt  
V/V

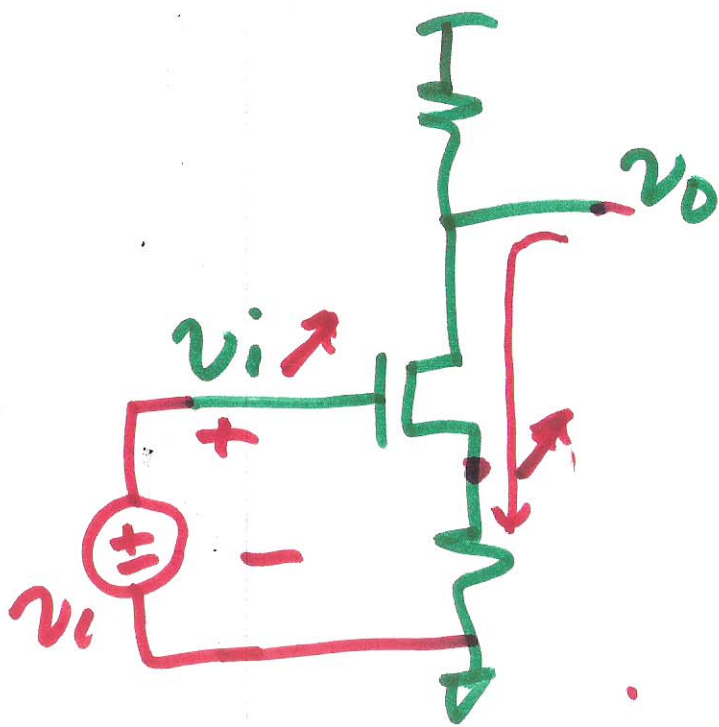

Series - ~~series~~ shunt?

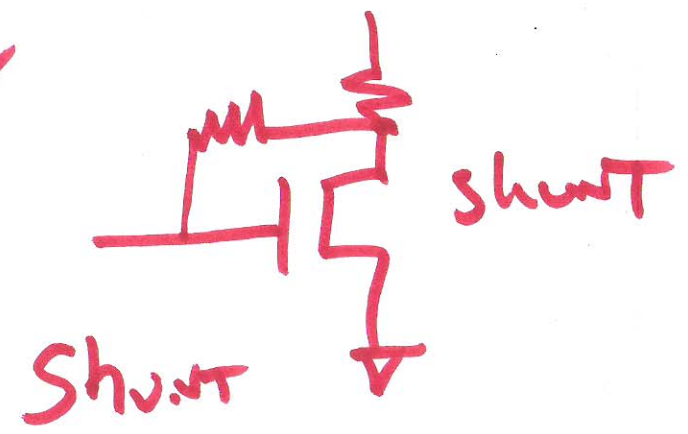

6)