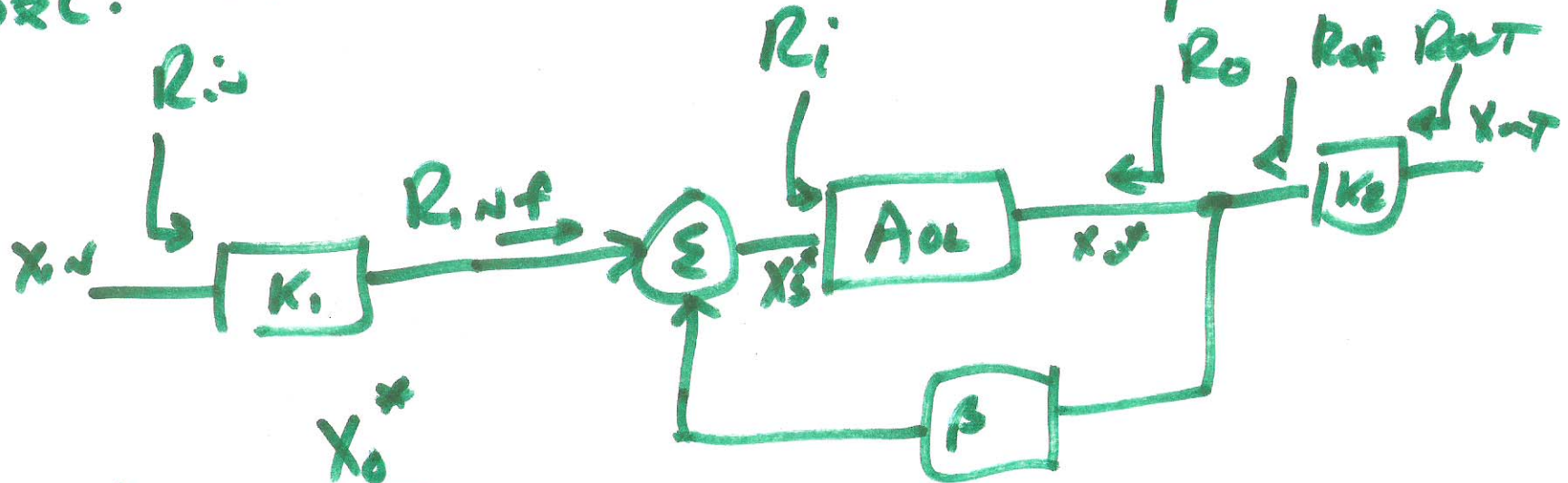



Sec. 31.3.4 Calculating open-loop parameters

Sec. 31.3.5 Calculating closed-loop parameters




$$A_{OL} = \frac{x_o^*}{x_s^*}$$

$$R_i = \frac{v_i^*}{i_i^*}$$

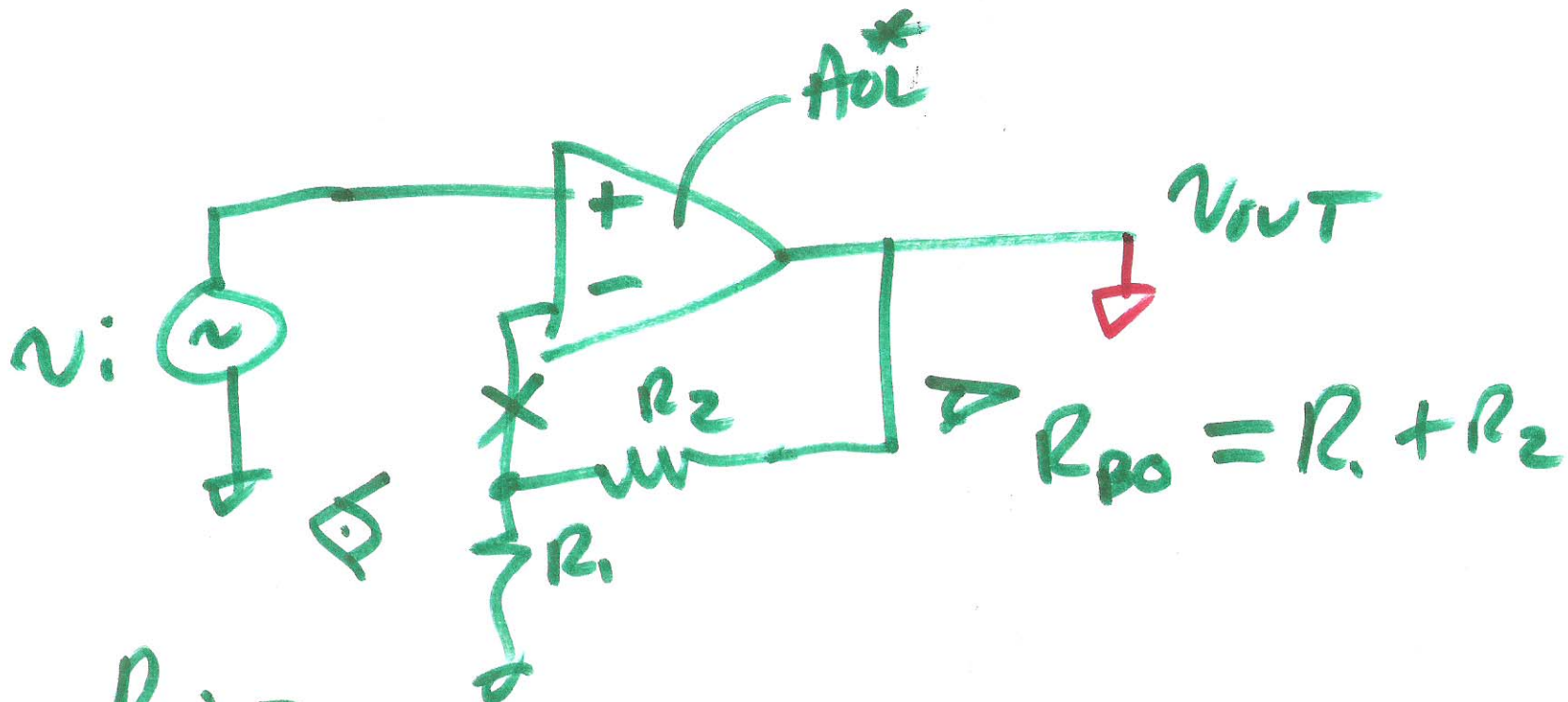

$$R_{BO} = R_1 + R_2$$

$$R_{oi} = R_1 \parallel R_2$$

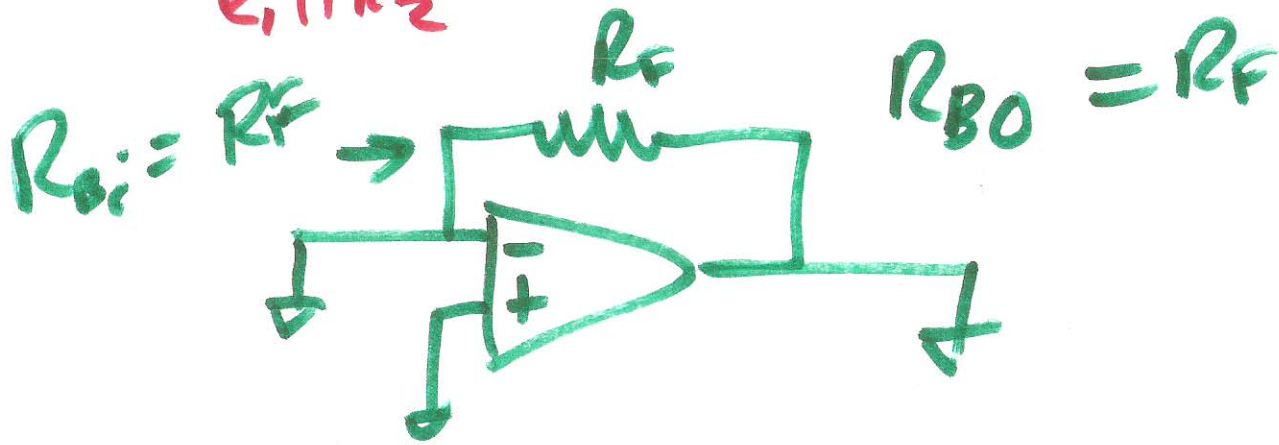


$$R_{oi} = R_f$$

shunt-shunt
f.b. amp

2)

Series-shunt

AOL

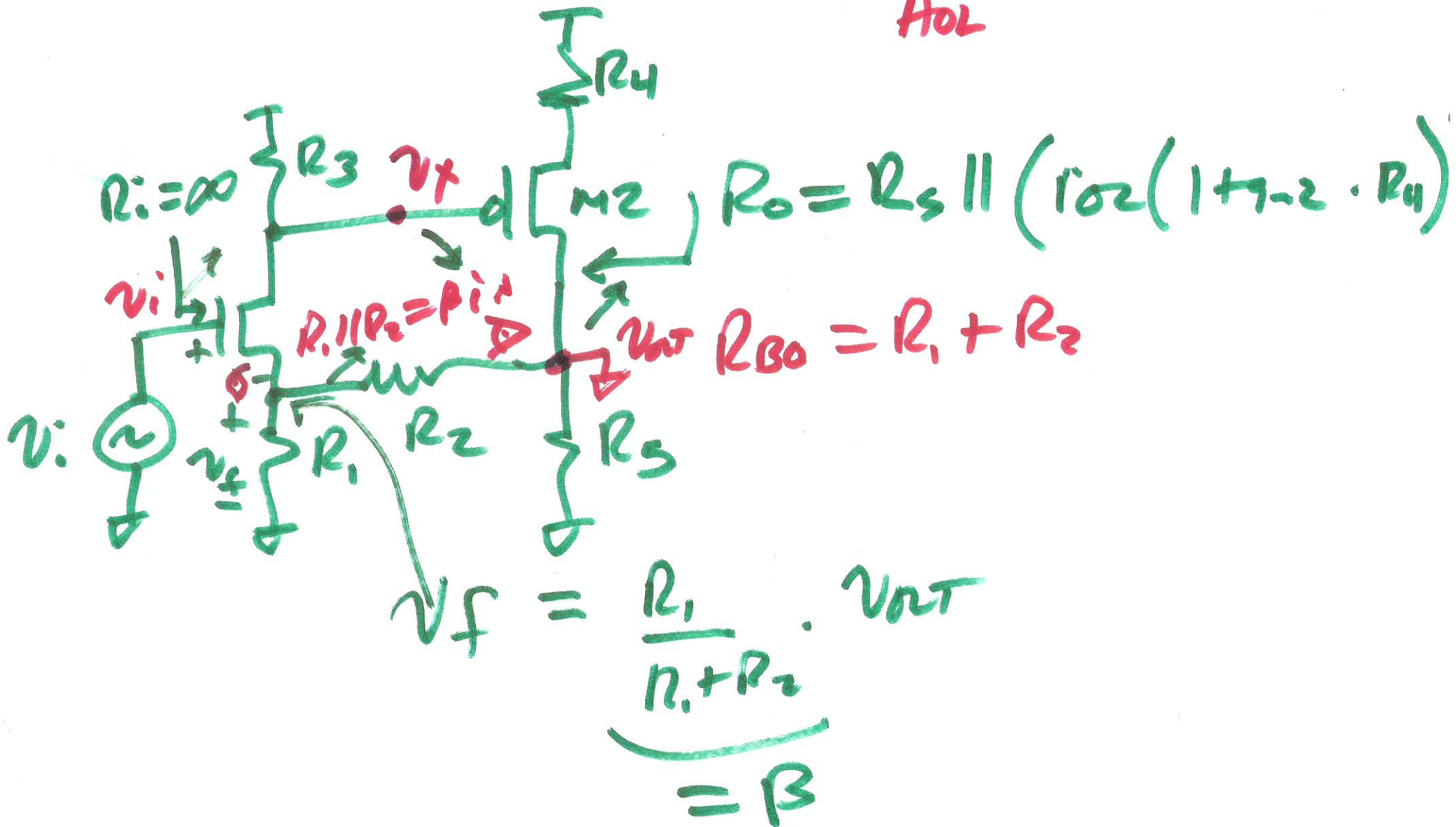

3)


$$\begin{aligned}
 v_x &= -i_d \cdot (R_3 \parallel r_{o1} (1 + g_m \cdot R_1 \parallel R_2)) \\
 &\approx -i_d \cdot R_3 \\
 v_i &= v_{gs1} + i_d \cdot R_1 \parallel R_2 \\
 &= i_d \left(\frac{1}{g_m} + R_1 \parallel R_2 \right)
 \end{aligned}$$

A_{ol}* calculation

$$g_m v_{gs} = i_d$$

$$\frac{v_x}{v_i} \approx \frac{-R_3}{\frac{1}{g_m} + R_1 \parallel R_2}$$

4)

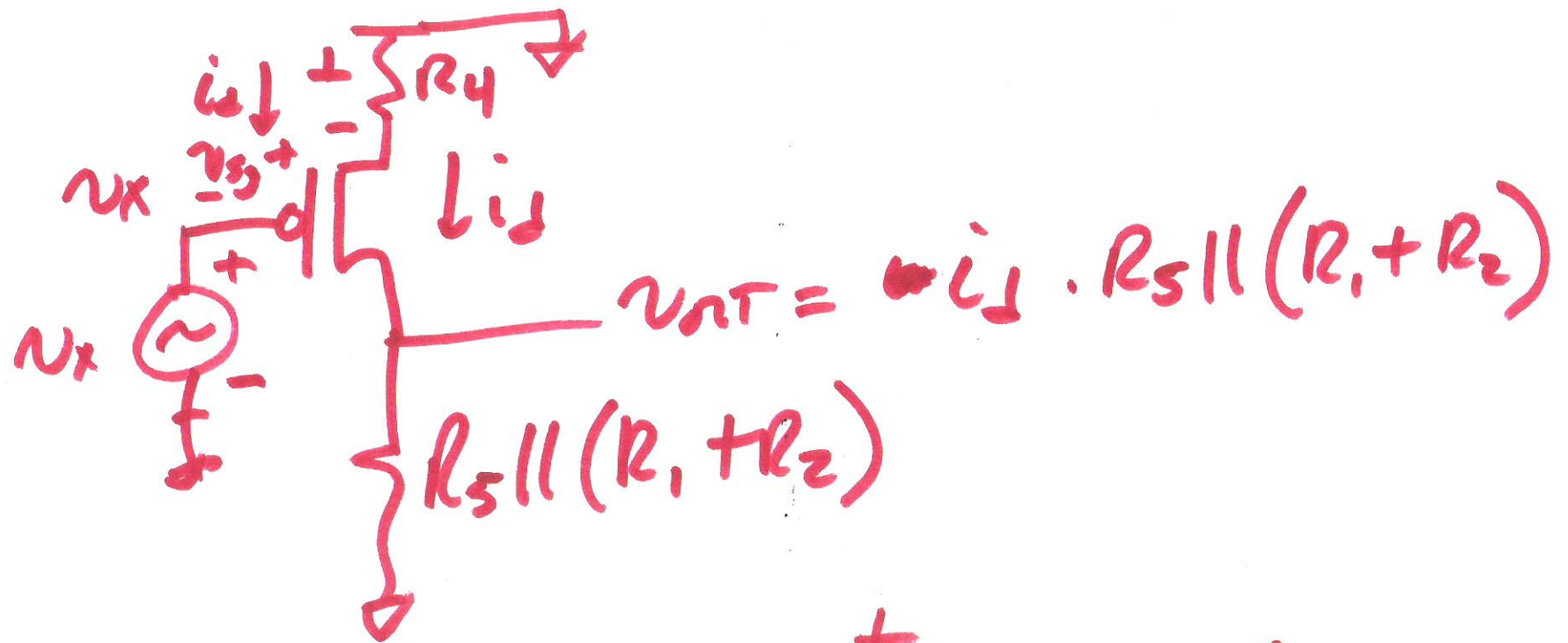

$$v_{out} = i_d \cdot R_5 \parallel (R_1 + R_2)$$

$$i_d \cdot R_4 + v_{s2} + v_x = 0$$

$$i_d \left(R_4 + \frac{1}{g_{m2}} \right) = -v_x$$

$$\frac{v_{out}}{v_x} = - \frac{R_5 \parallel (R_1 + R_2)}{R_4 + \frac{1}{g_{m2}}}$$

5)

$$A_{ol}^* = \frac{v_o}{v_i} = \frac{R_3 \cdot (R_5 \parallel (R_1 + R_2))}{\left(\frac{1}{g_{m1}} + R_1 \parallel R_2\right) (R_4 + \frac{1}{g_{m2}})}$$

v)