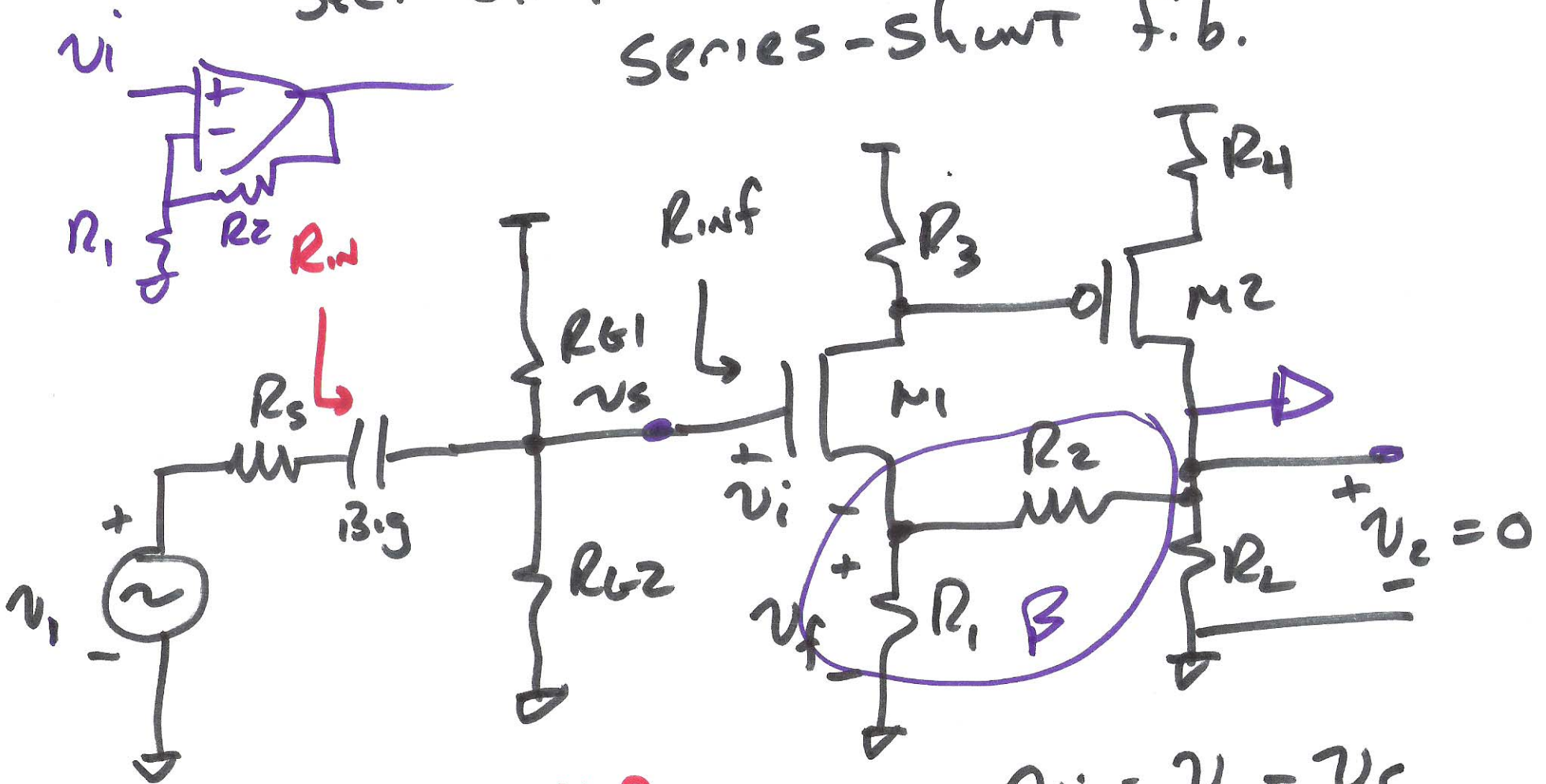


Sec. 31.4

Series-Shunt f.b.




$$R_{in} = R_{B1} \parallel R_{B2}$$

$$v_s = v_i \cdot \frac{R_{B1} \parallel R_{B2}}{R_{B1} \parallel R_{B2} + R_s}$$

$$v_i = v_s - v_f$$

$$\beta = \frac{R_1}{R_1 + R_2}$$

1)

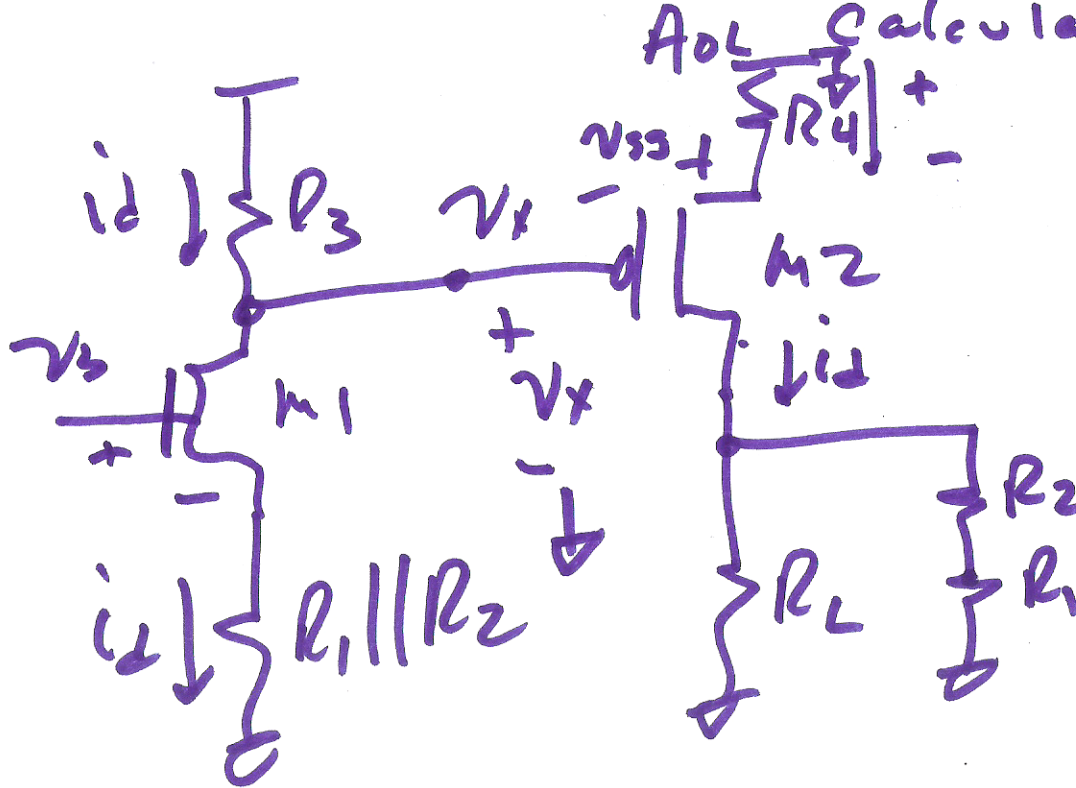

$$g_m V_{sg} = i_d$$

$$i_d \cdot R_4 + V_{sg} + V_x = 0$$

$$V_{out} = i_d (R_2 \parallel (R_1 + R_2))$$

$$V_x = -i_d (R_4 + \frac{1}{g_m})$$

$$\frac{V_{out}}{V_x} = - \frac{R_2 \parallel (R_1 + R_2)}{R_4 + \frac{1}{g_m}}$$

$$V_x = -i_d R_3$$

$$V_s - V_{gs} - i_d (R_1 \parallel R_2) = 0$$

$$V_{gs} = \frac{1}{g_m} i_d$$

$$V_s = i_d \left(\frac{1}{g_m} + R_1 \parallel R_2 \right)$$

$$\frac{V_x}{V_s} = \frac{-R_3}{\frac{1}{g_m} + R_1 \parallel R_2}$$

2)

$$A_{OL} = \frac{v_{out}}{v_s} = \frac{R_3}{\frac{1}{g_{mN}} + R_1 \parallel R_2} \cdot \frac{R_L \parallel (R_1 + R_2)}{R_4 + \frac{1}{g_{mP}}}$$


$$\frac{[-g_{mP} \cdot R_L \parallel (R_1 + R_2)]}{1 + g_{mN}(R_1 \parallel R_2)} \cdot \left[\frac{-g_{mN} R_3}{1 + g_{mP} \cdot R_4} \right]$$


$$A_{OL} = \frac{R_3}{\frac{1}{g_{mN}} + R_1 \parallel R_2} \cdot \frac{R_L \parallel (R_1 + R_2)}{\frac{1}{g_{mP}} + R_4}$$

$$\beta = \frac{R_1}{R_1 + R_2}, \quad A_{CL} = \frac{A_{OL}}{1 + \beta A_{OL}}$$

3)

$$R_{of} \Big|_{\text{series-shunt}} = \frac{R_o}{1 + A_{oc} \cdot \beta} = \left. \begin{aligned} & \frac{r_{op} \parallel (R_1 + R_2)}{1 + \beta A_{oc}} \\ & R_4 = 0 \end{aligned} \right\}$$

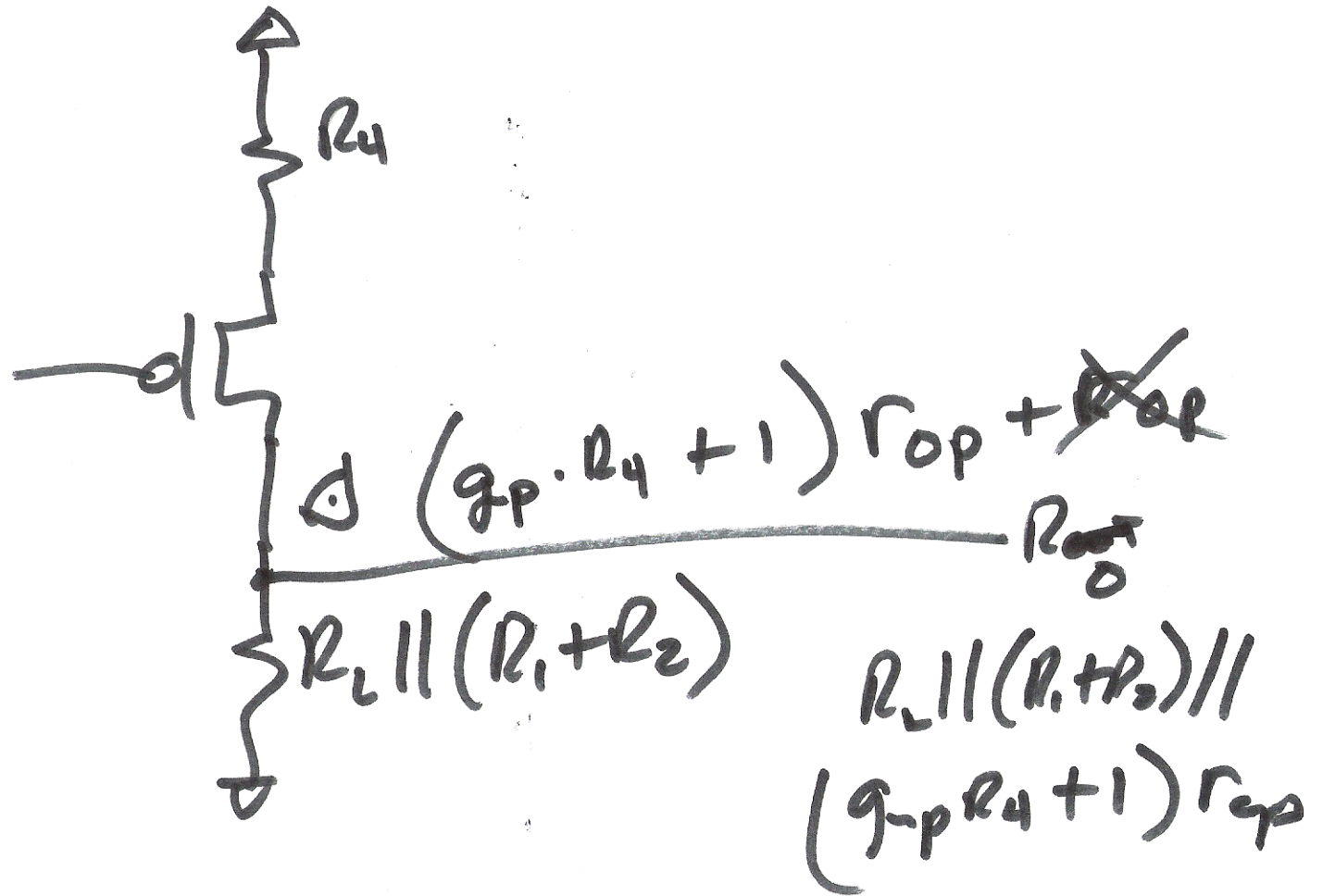


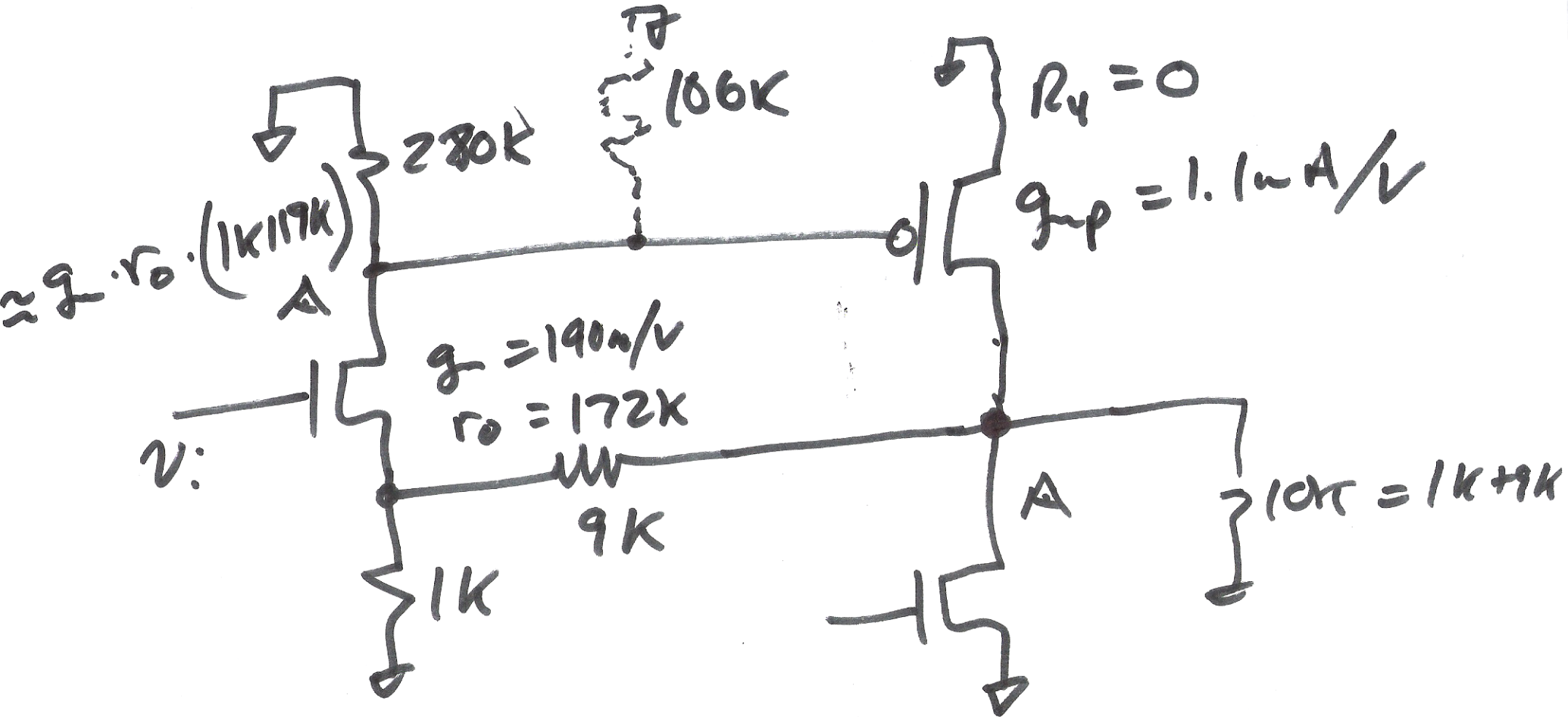

$$r_o(1 + g_m R_s) = 172k(1 + 190\mu(0.0009M\Omega)) \approx 172k$$

$$172k // 280k$$
~~$$190\mu \cdot (0.172M\Omega) (900)$$~~

5)

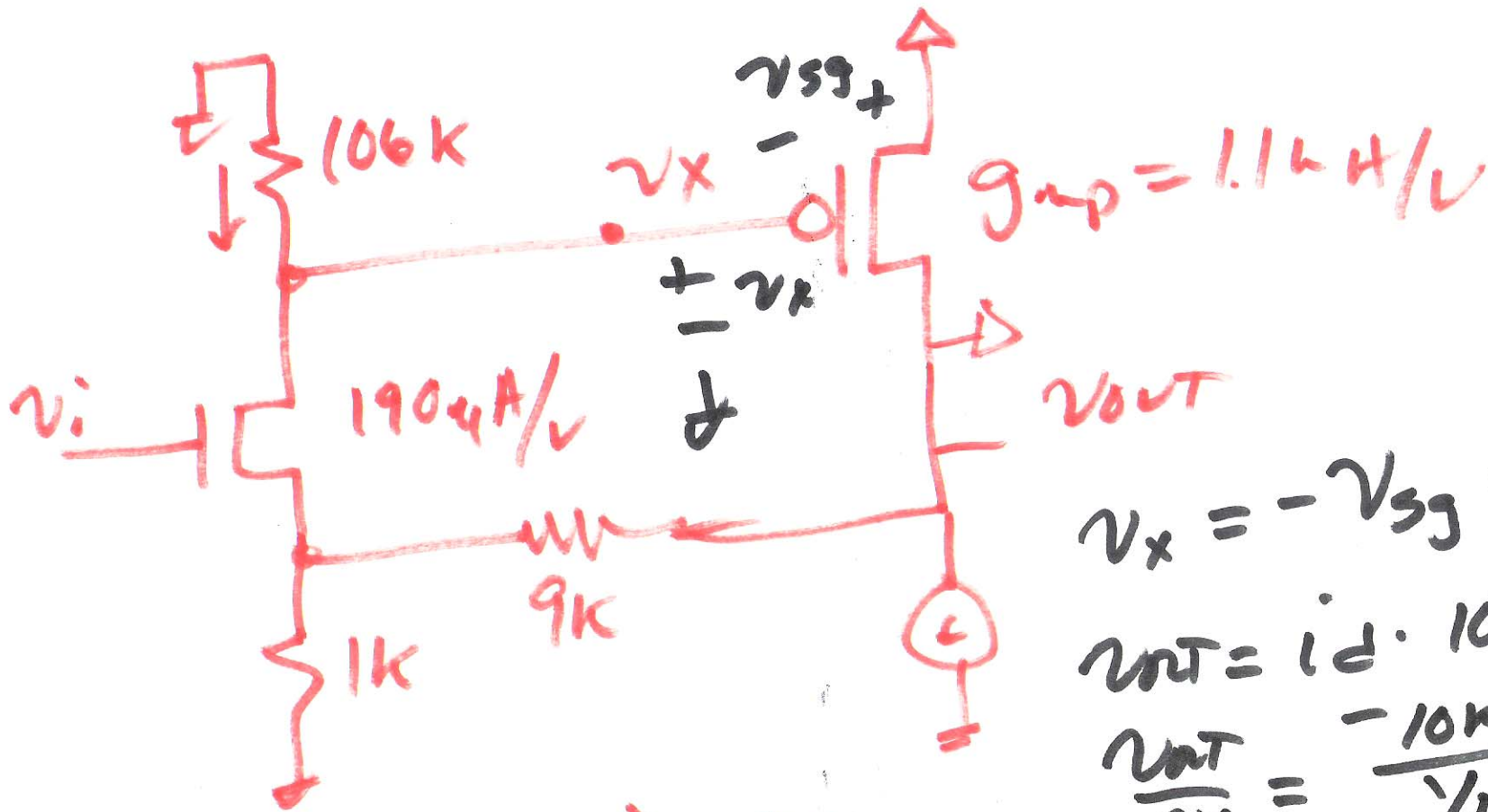

$$v_x = -v_{gs} = -\frac{i_d}{g_m}$$

$$v_{out} = i_d \cdot 10k$$

$$\frac{v_{out}}{v_x} = \frac{-10k}{1/1.1mA} = \underline{\underline{11}}$$

$$v_x = -i_d \cdot 106k$$

$$v_i = v_{gs} + i_d \cdot (1k || 9k)$$

$$\frac{v_x}{v_i} = \frac{-106k}{1/g_m + 900} \approx \frac{-106}{7.4} = \underline{\underline{14.3}}$$


$$A_{vL} = 11 \cdot 14.3 = 157.3$$

6)

$$A_{CL} = \frac{1}{\frac{1}{157} + 0.1} = \underline{\underline{9.4}}$$

$$R_{of} = \frac{10K}{1 + \beta A_{OL}} = \frac{10K}{1 + 0.1 \cdot 157}$$
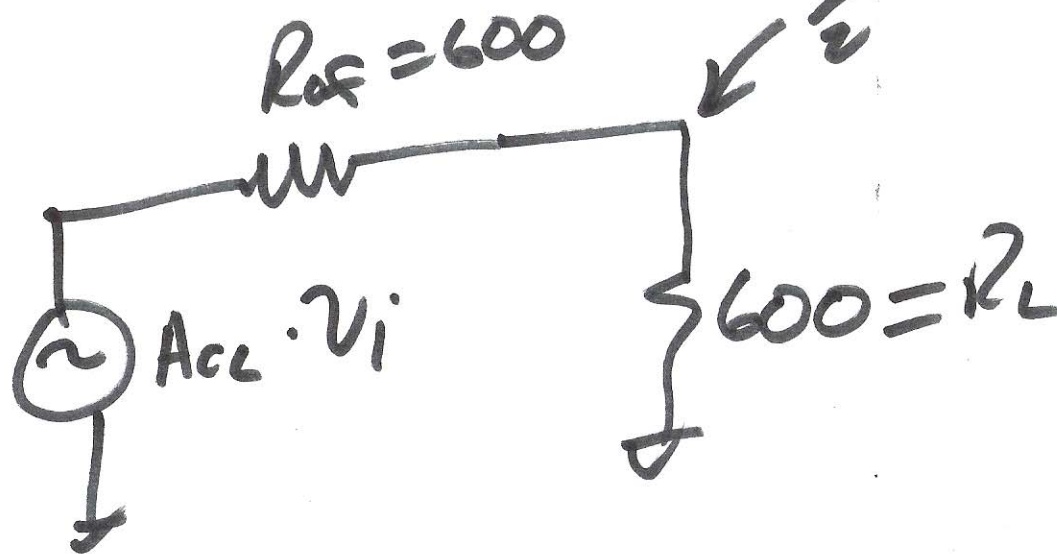
$$\frac{1}{2} A_{CL} \cdot R_{of} = \frac{10K}{16.7} = \underline{\underline{600 \Omega}}$$



7)