

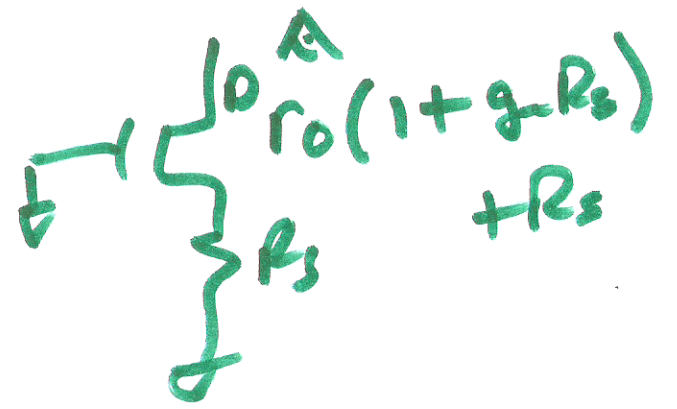




Section 31.5 Shunt-Shunt f.b.

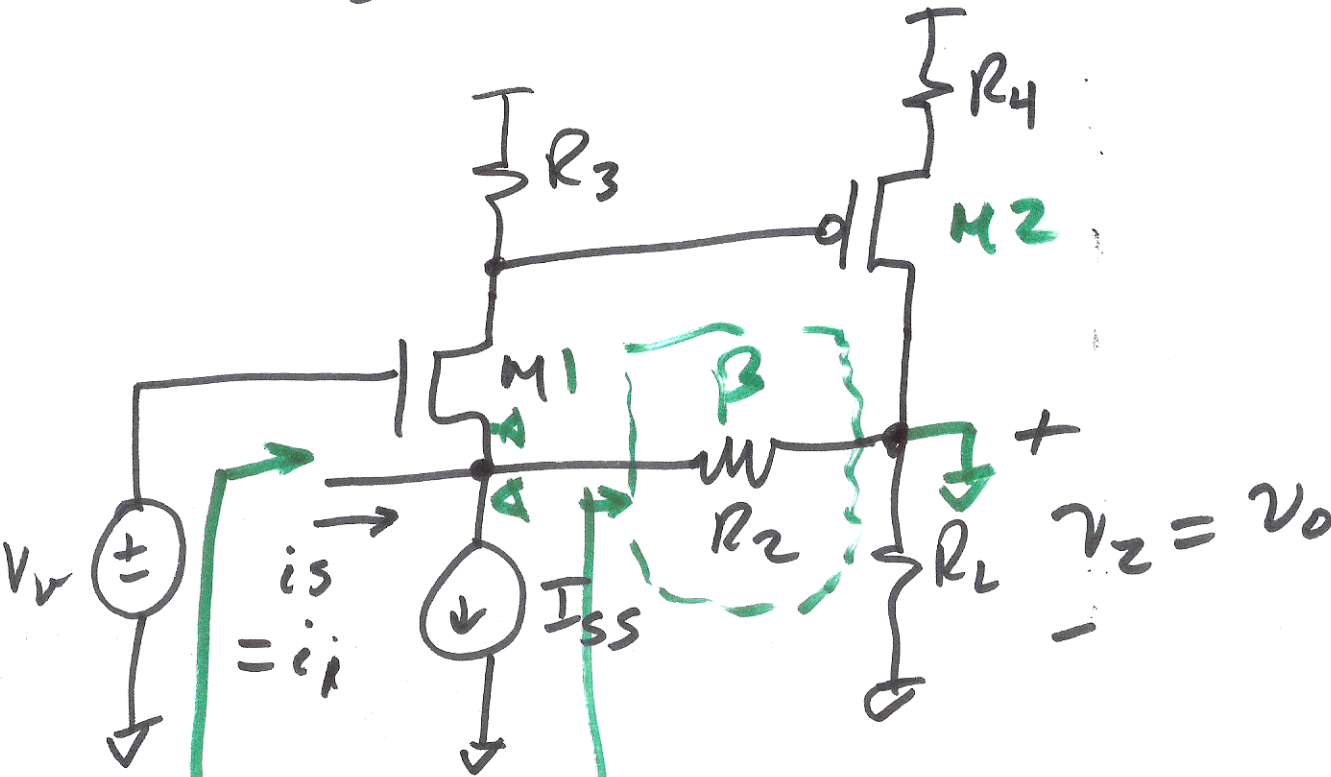

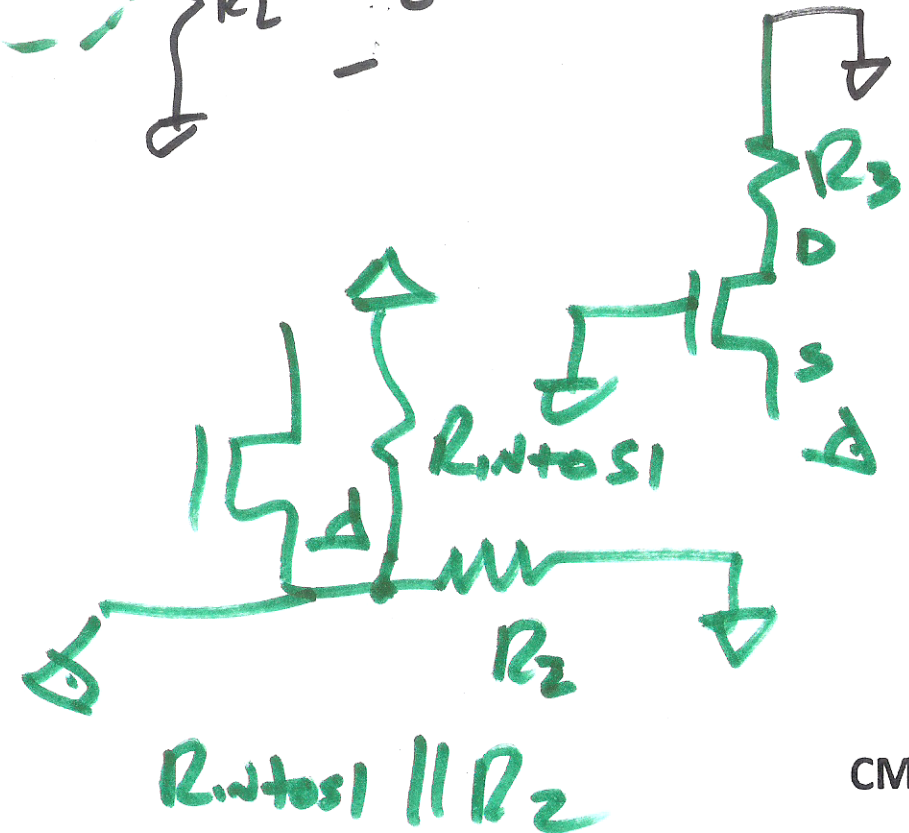$R_i = R_2 \parallel R_{in} \parallel R_{si}$
 $R_{si} = R_2$
 NO f.b.



1)

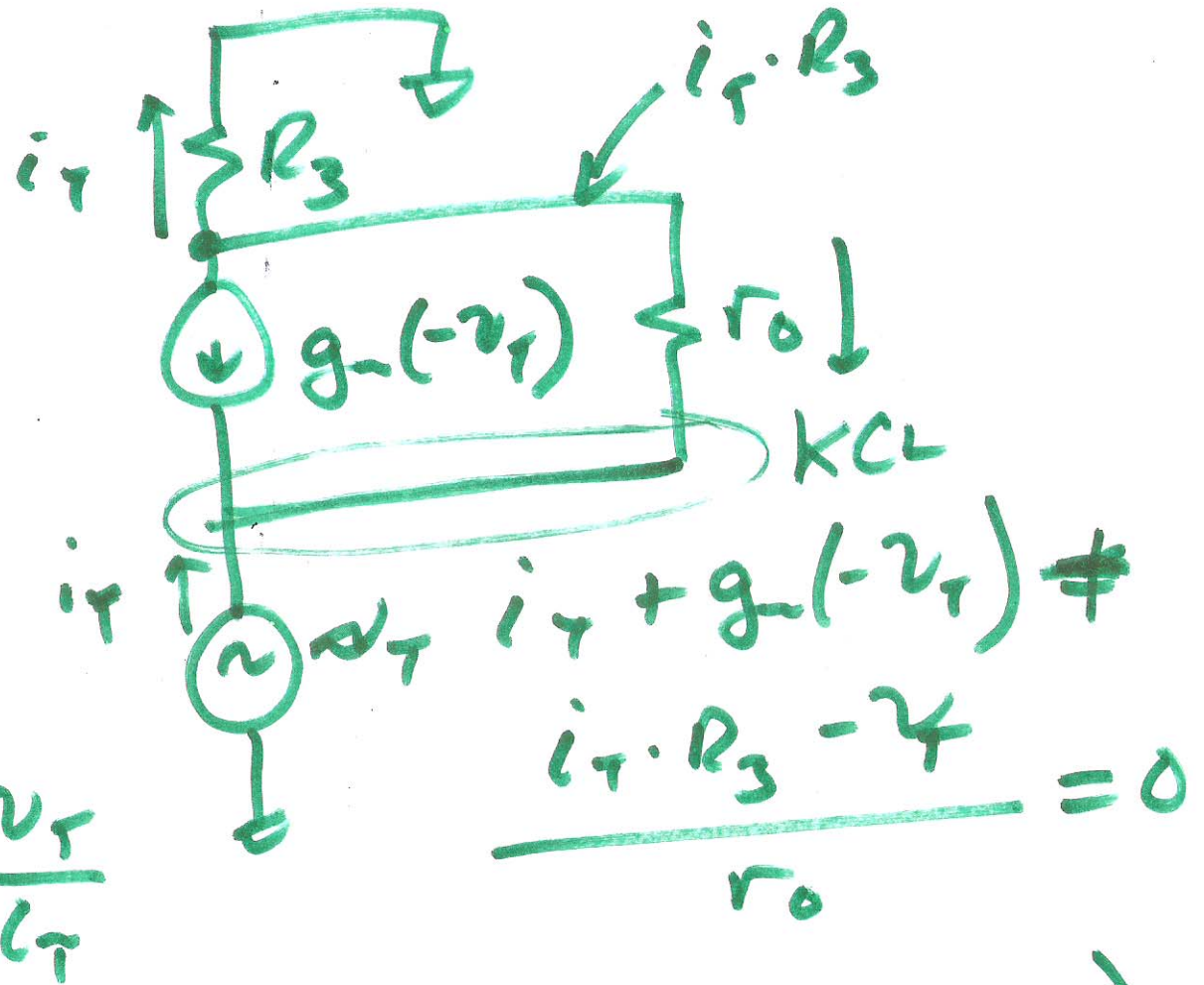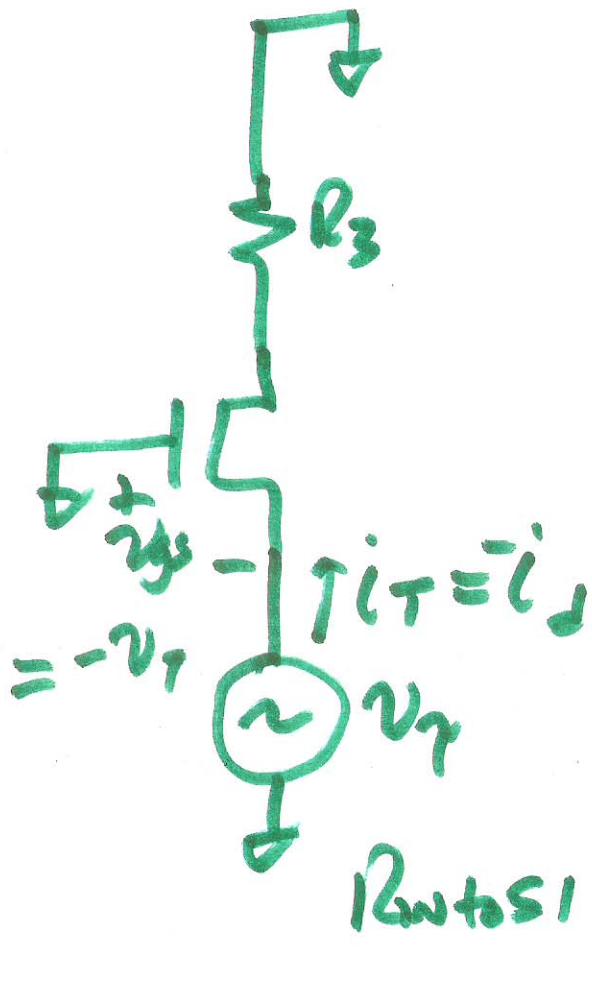

$$i_T \left(1 + \frac{R_3}{r_o} \right) = v_T \left(g_m + \frac{1}{r_o} \right)$$

2)

$$\frac{v_T}{i_T} = \frac{\left(1 + \frac{R_3}{r_o}\right)}{g_m + \frac{1}{r_o}} = r_{o11} \frac{1}{g_m} \cdot \left(1 + \frac{R_3}{r_o}\right)$$



$$\frac{\frac{1}{g_m} \cdot r_o}{\frac{1}{g_m} + r_o} = r_{o11} \frac{1}{g_m} = \frac{1}{g_m + \frac{1}{r_o}}$$

special case $R_3 = r_o$

$$\frac{v_T}{i_T} = 2 \frac{1}{g_m}$$

$$\frac{1 + \frac{r_{oP}}{r_{oN}}}{g_{mN} + \frac{1}{r_{oN}}}$$

CMOSedu.com

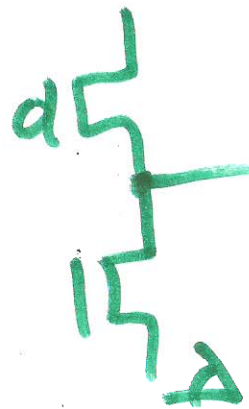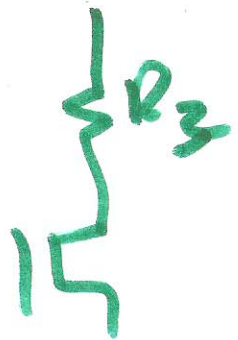

3)

$$\text{open-ckt gain} = g_m \cdot r_o$$

$$= \frac{r_o}{\frac{1}{g_m}}$$

We want
transistors

is



$$\frac{1}{g_m} \ll r_o$$

$$r_o \gg \frac{1}{g_m}$$

$$g_m \gg \frac{1}{r_o}$$

$$\frac{v_T}{i_T} \approx \frac{1}{g_m} \left(1 + \frac{R_3}{r_o} \right)$$
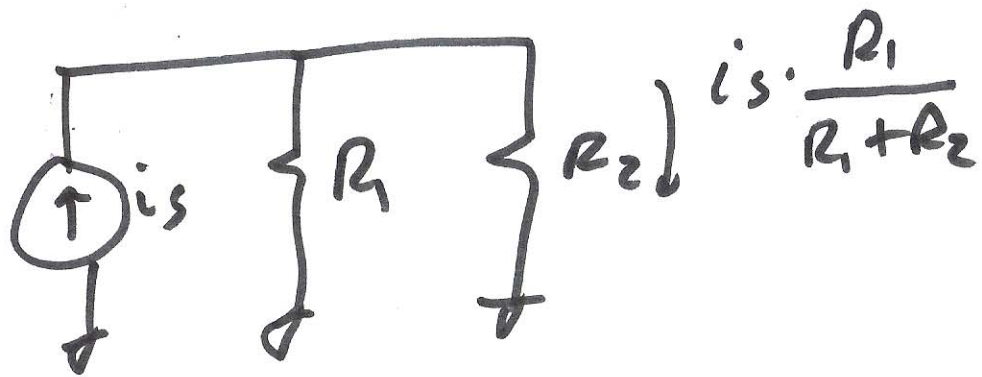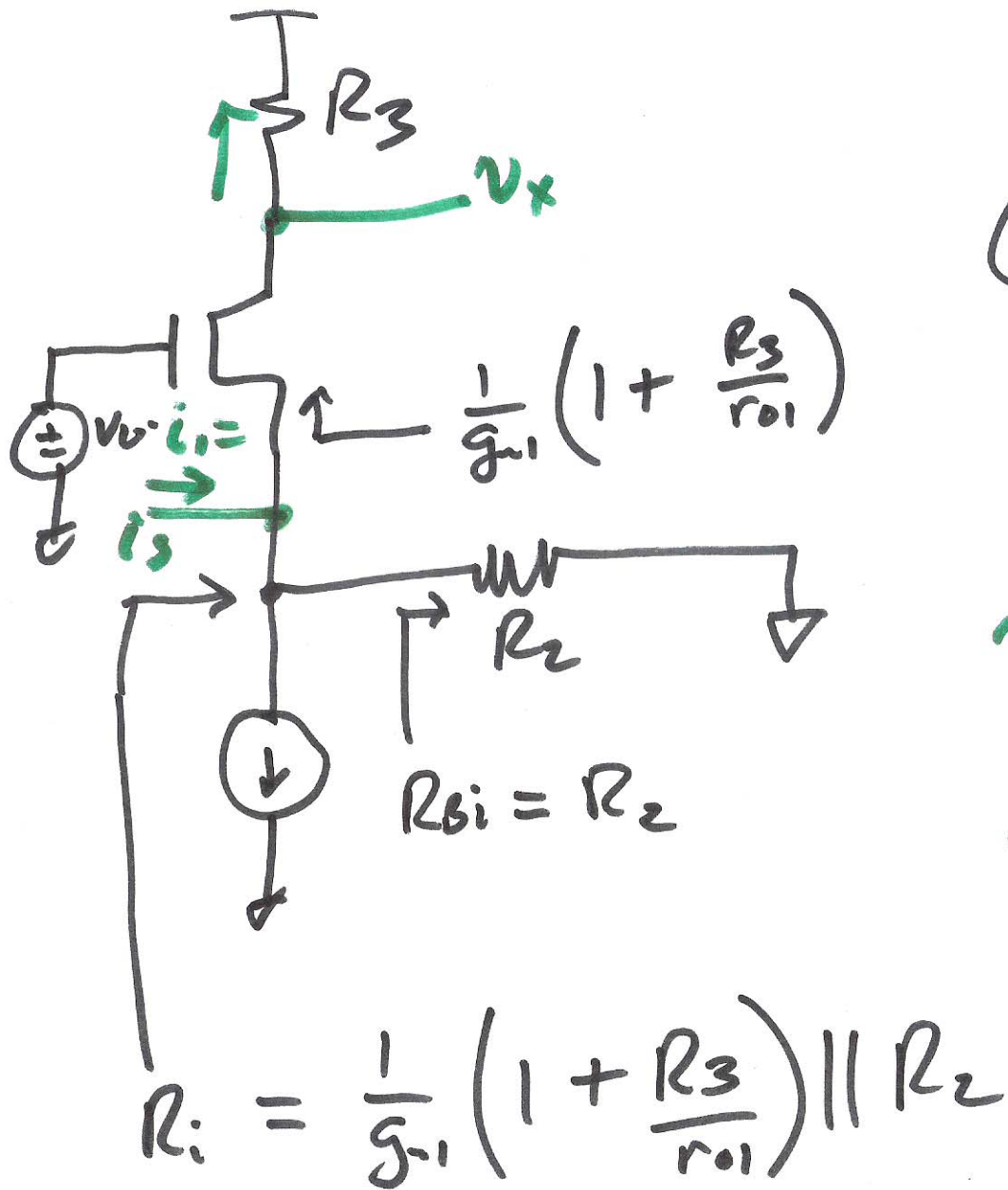
$$\approx \frac{1}{g_{mN}} \left(1 + \frac{r_{op}}{r_{on}} \right)$$




$$v_x = R_3 \left(i_s \cdot \frac{R_2}{R_2 + \frac{1}{g_{m1}} \left(1 + \frac{R_3}{r_{o1}} \right)} \right)$$

$$\frac{v_x}{i_s} = \frac{R_2 \cdot R_3}{R_2 + \left(\frac{1}{g_{m1}} \left(1 + \frac{R_3}{r_{o1}} \right) \right)}$$


$$A_{OL} = \frac{v_o}{i_s}$$

5)


$$i_d \cdot R_4 + v_{sg} + v_x = 0$$

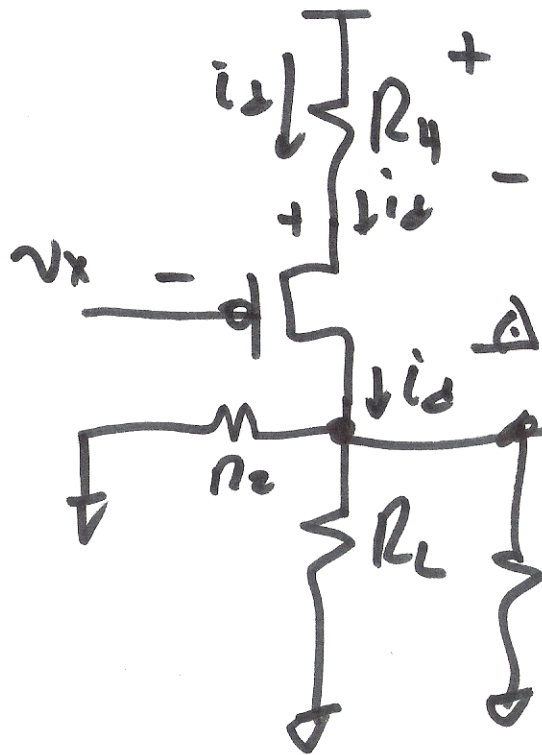
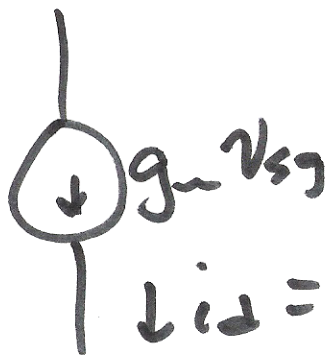
$$v_o = i_d \cdot R_2 \parallel R_L \parallel (r_{op}(1 + g_{mp} \cdot R_4) + R_4)$$




6)

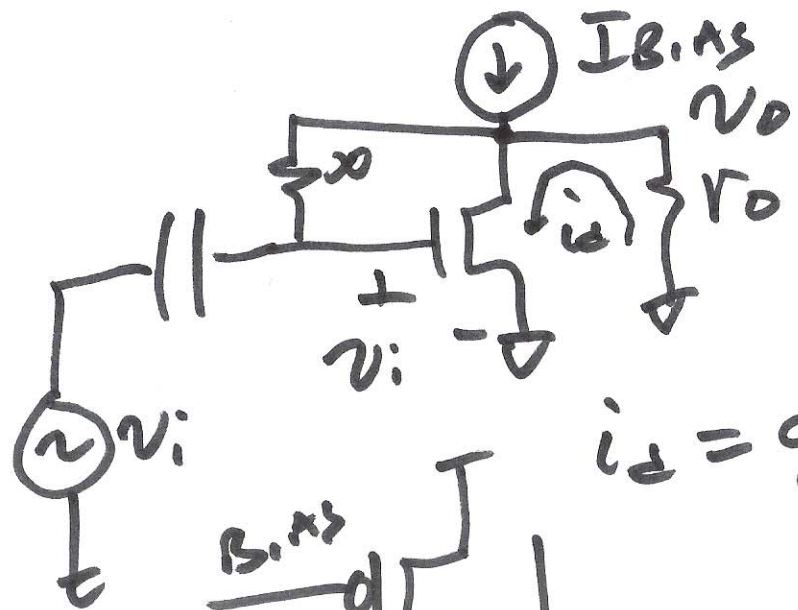

$$\Rightarrow v_o = -i_d \cdot r_o = -g v_i \cdot r_o$$



$$i_d = g v_{gs} = g v_i$$

$$\frac{v_o}{v_i} = -g r_o$$

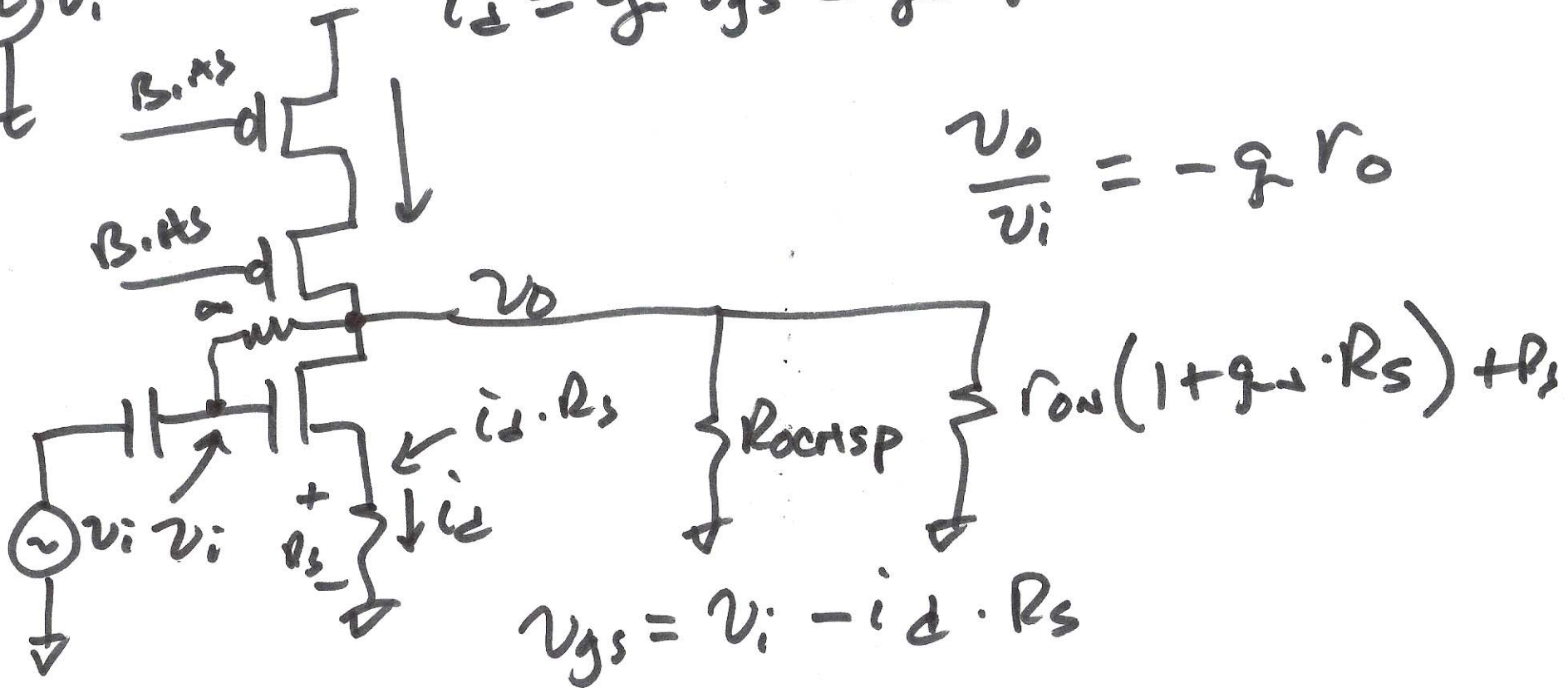

$$v_{gs} = v_i - i_d \cdot R_s$$

$$r_{on}(1 + g_m \cdot R_s) + R_o$$

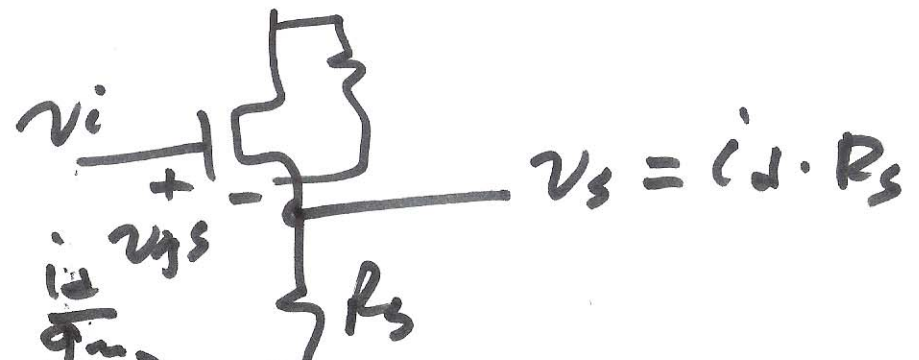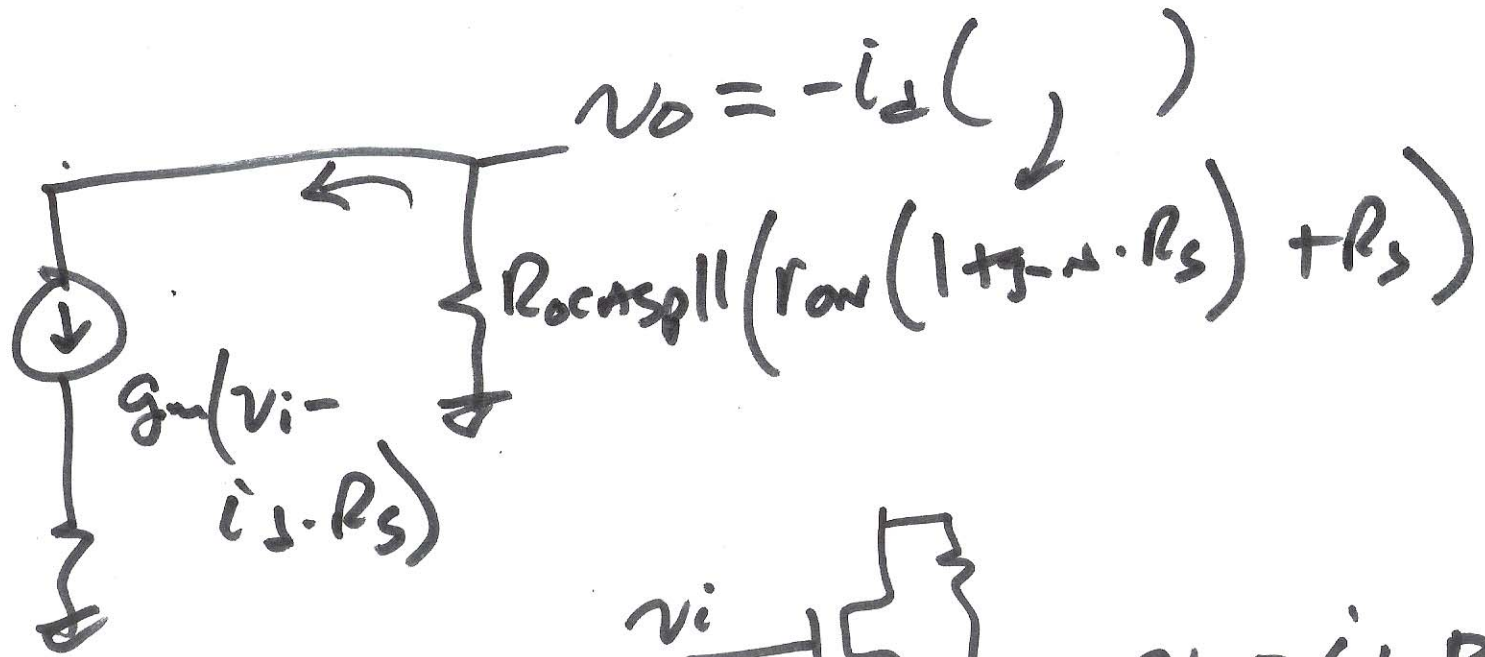



$$v_o = -R_{ocnspl} (r_{on} (1 + g_m \cdot R_s) + R_s) i_d$$

$$\frac{v_o}{v_i} = \frac{-R_{ocnspl} (r_{on} (1 + g_m \cdot R_s) + R_s)}{\frac{1}{g_m} + R_s}$$

$$v_i = v_{gs} + i_d \cdot R_s$$

$$v_i = i_d \left(\frac{1}{g_m} + R_s \right)$$

8)

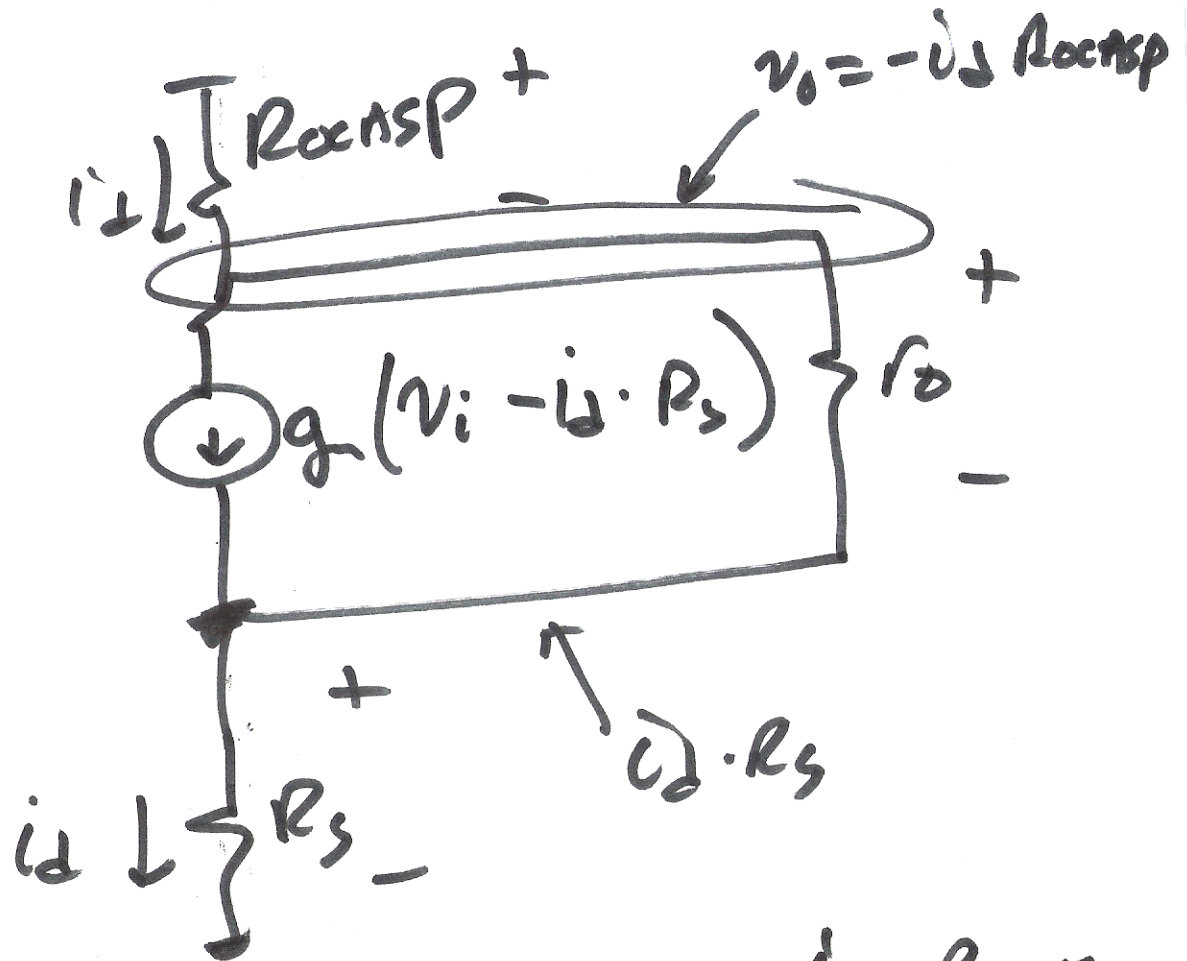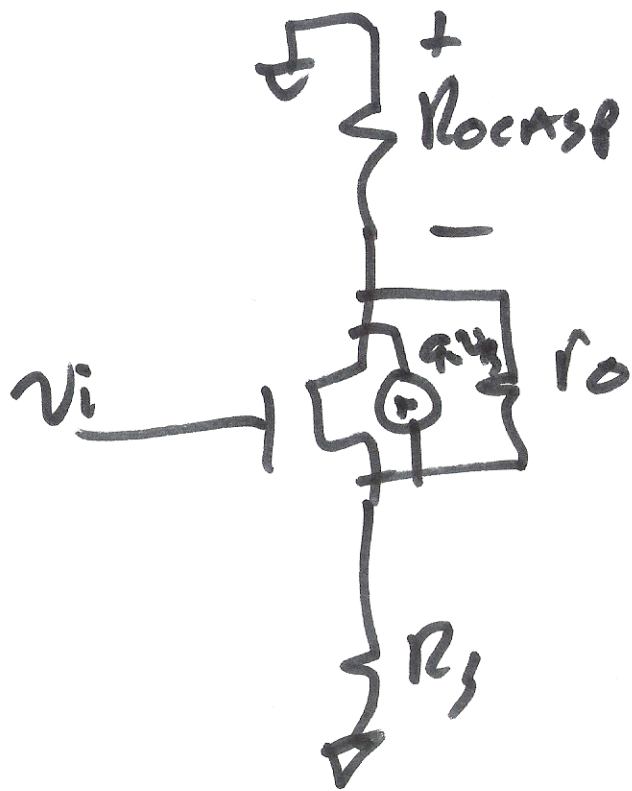

$$i_d = g_m (v_i -$$

$$i_d \cdot R_{ocnsp} + r_o (i_d - g_m (v_i - i_d R_s)) + i_d \cdot R_s$$

$$v_o = -i_d \cdot R_{ocnsp}$$


9)

$$\cancel{v_i} - v_o + r_o \left(-\frac{v_o}{R_{oNS}} - g_m v_i - g_m \frac{v_o R_s}{R_{oNS}} \right)$$

$$\cancel{v_i} - \frac{v_o R_s}{R_{oNS}} = 0$$

$$v_o \left(\frac{R_s}{R_{oNS}} + g_m \frac{R_s}{R_{oNS}} \cdot r_o + \frac{r_o}{R_{oNS}} + 1 \right) =$$
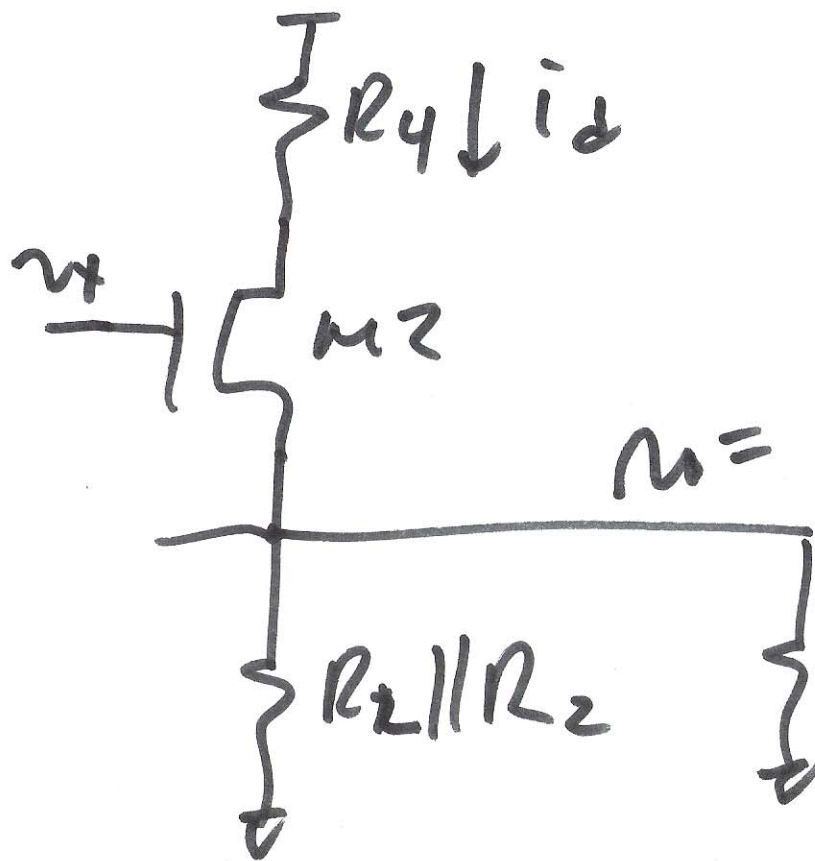
$$\frac{v_o}{v_i} = \frac{-g_m v_i}{\frac{R_s}{R_{oNS}} + g_m \frac{R_s}{R_{oNS}} \cdot r_o + \frac{r_o}{R_{oNS}} + 1}$$



$$R_4 \cdot i_d + v_{sg} + v_x = 0$$

$$v_x = -i_d \left(R_4 + \frac{1}{g_m} \right)$$

$$r_{op} \left(1 + \frac{R_4}{r_{op}} \right) + R_4$$

$$v_o = \frac{-R_2 \parallel R_2 \parallel \left(r_{op} \left(1 + \frac{R_4}{r_{op}} \right) + R_4 \right)}{R_4 + \frac{1}{g_m}}$$

$$A_{v2} = \frac{v_x}{i_s} \cdot \frac{v_o}{v_x} = \frac{-R_2 \parallel R_3 \parallel (r_{op}(1 + \frac{R_4}{r_{op}}) + r_{t4})}{R_4 + \frac{1}{g_m}}$$

$$\cdot \frac{R_2 R_3}{R_2 + \left(\frac{1}{g_m} \left(1 + \frac{R_3}{r_{o1}}\right)\right)}$$

$$= \frac{10k \cdot 10k \cdot 150k}{\frac{6.5k}{4} \cdot (10k + 2 \cdot 6.5k)}$$

$$= \frac{100 \cdot 150k}{\frac{6.5}{4} \cdot 23} = \frac{100}{143} \cdot 150k \approx \underline{\underline{100k}}$$

$$n=4$$

12)