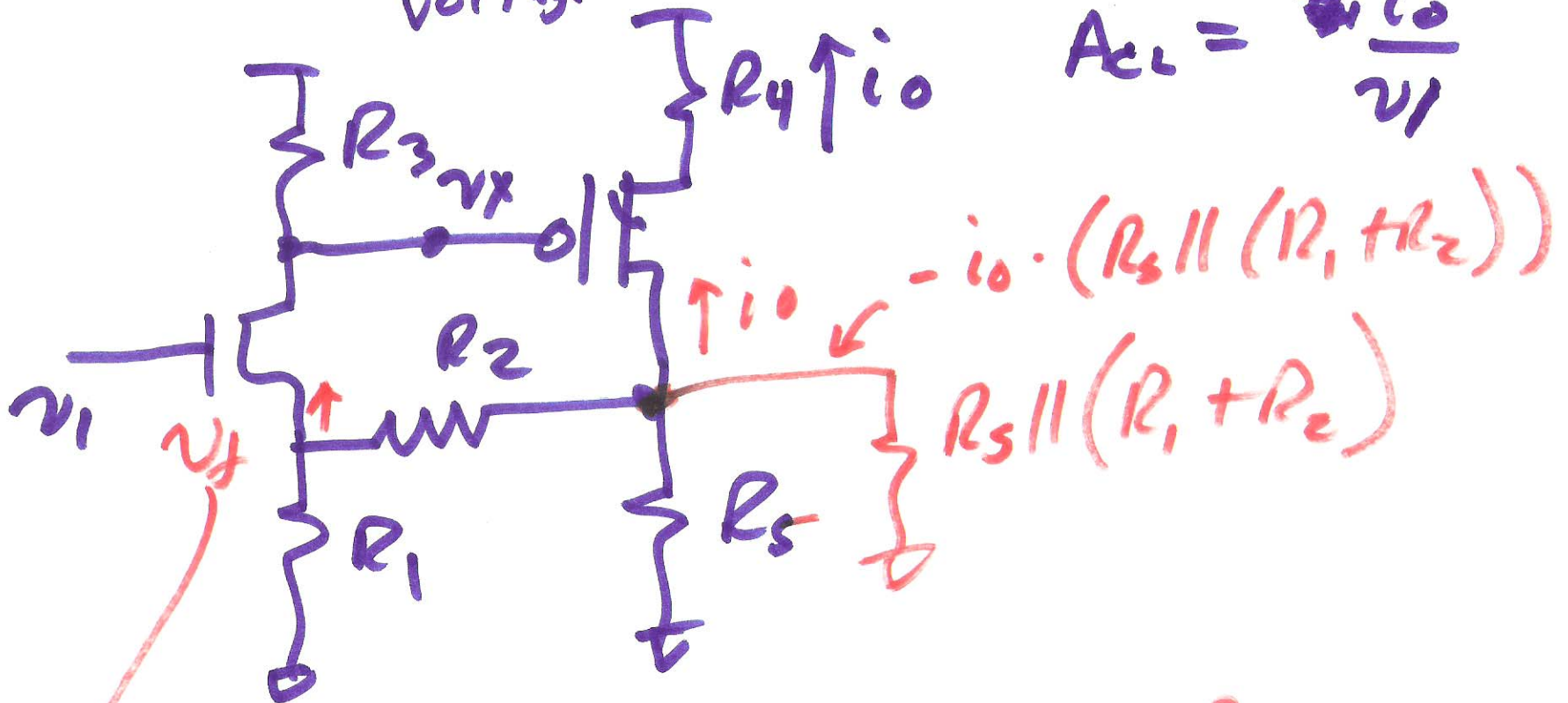


Sec. 31.6

Series - Series f.b. AMP
 voltage current


$$A_{CL} = \frac{v_o}{v_i}$$



$$v_f = -i_o \cdot (R_s \parallel (R_1 + R_2)) \cdot \frac{R_1}{R_1 + R_2}$$


$$\beta = \left(\frac{i_o}{v_f} \right)^{-1} = \frac{-R_s \cdot (R_1 + R_2)}{R_s + R_1 + R_2} \cdot \frac{R_1 + R_2}{R_1}$$
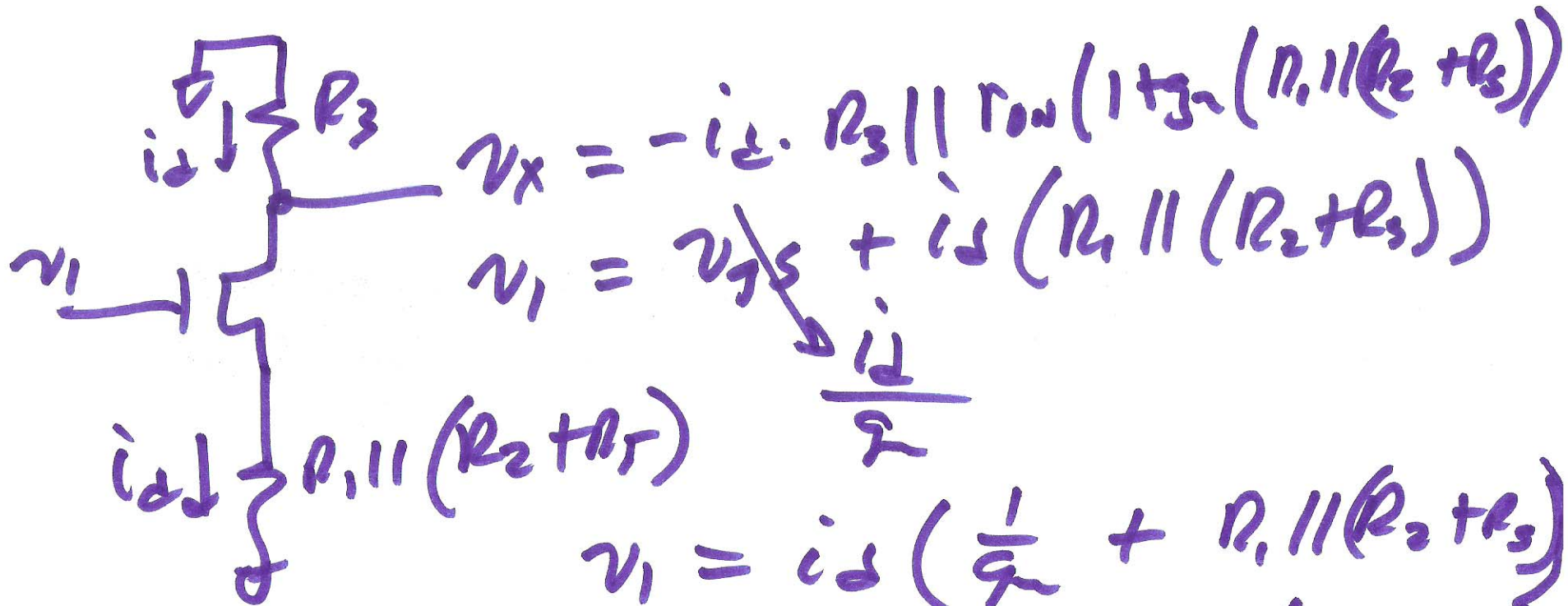
$$\beta = \frac{-R_1 \cdot R_5}{R_5 + R_1 + R_2}$$



$$\frac{v_x}{v_i} = \frac{-R_3 \parallel r_{out} (1 + g_m (R_1 \parallel (R_2 + R_5)))}{\frac{1}{g_m} + R_1 \parallel (R_2 + R_5)}$$

2)

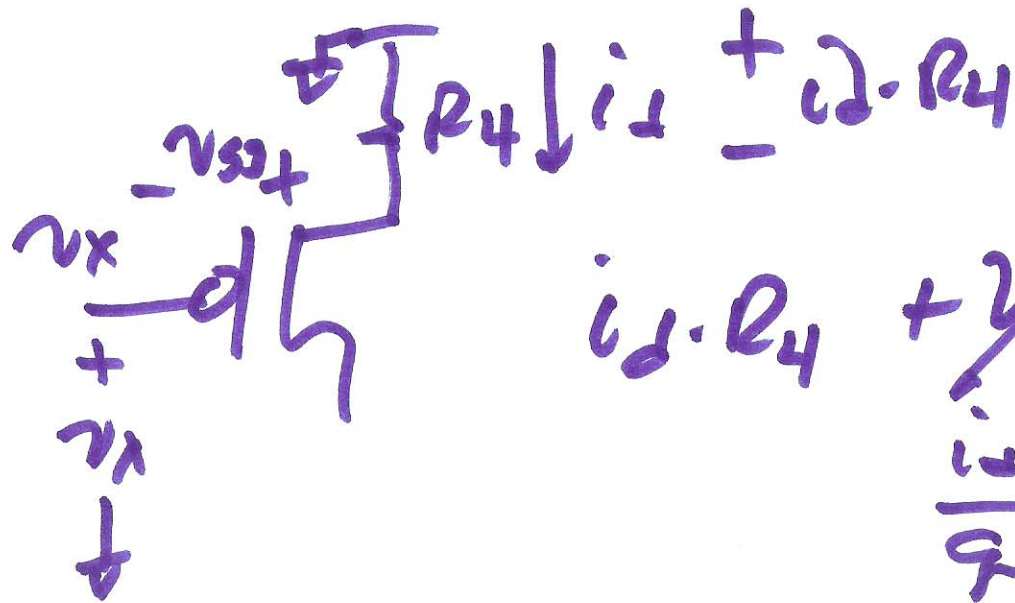

$$R_4 i_d + v_x = 0$$


$$i_d R_4 + \frac{v_x}{g_m} + v_x = 0$$

$$-v_x = i_d \left(R_4 + \frac{1}{g_m} \right)$$

$$-\frac{i_d}{v_x} = \frac{i_d}{v_x} = -\frac{1}{R_4 + \frac{1}{g_m}}$$

$$\frac{i_d}{v_x} = \frac{1}{R_4 + \frac{1}{g_m}} \cdot \frac{R_3 \parallel R_{intd}}{\frac{1}{g_m} + R_1 \parallel (R_2 + R_3)}$$

3)

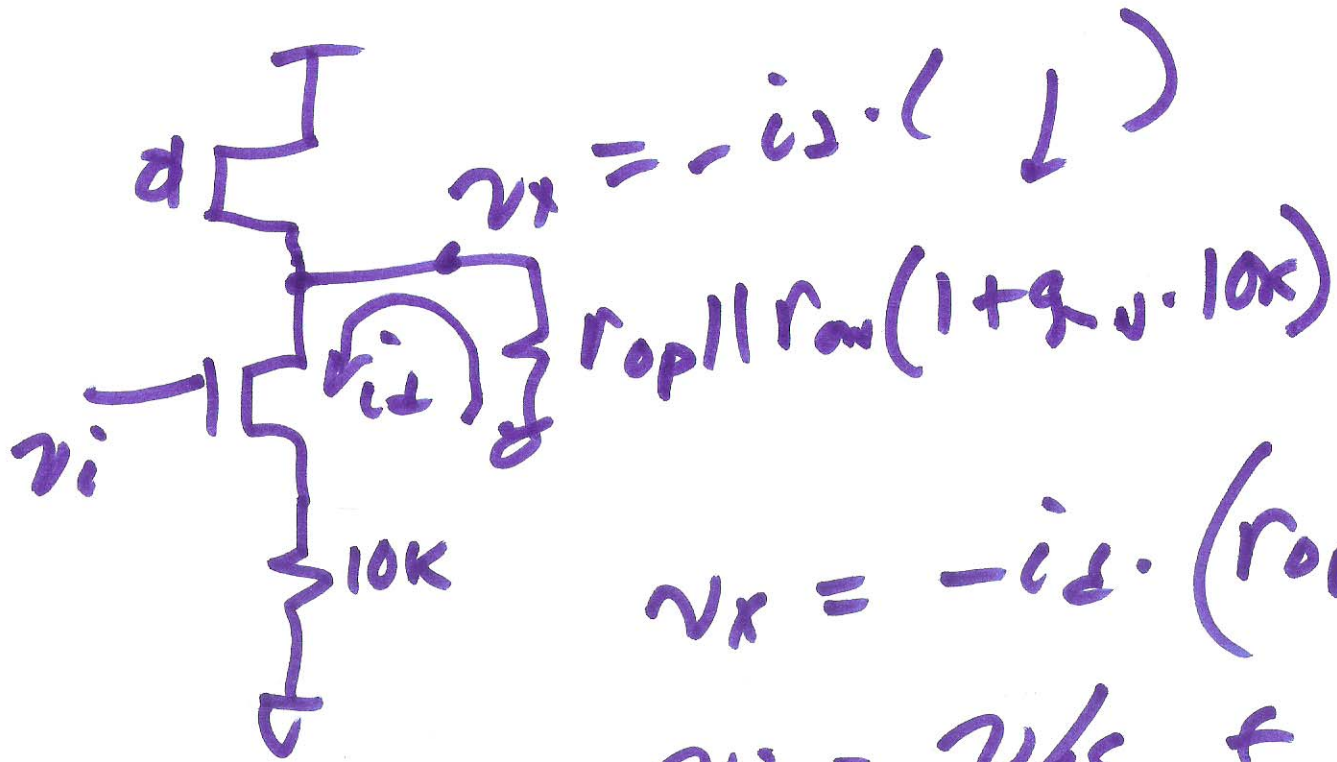

$$v_x = -i_d \cdot (\downarrow)$$

$$r_o \parallel r_D (1 + g_m \cdot 10K)$$


$$v_x = -i_d \cdot (r_o \parallel r_D (1 + g_m \cdot 10K) + i_d \cdot 10K)$$

$$\frac{v_x}{v_i} = \frac{r_o \parallel r_D (1 + g_m \cdot 10K)}{\frac{1}{g_m} + 10K}$$

$$v_i = \frac{v_x / g_m}{i_d} = i_d \left(\frac{1}{g_m} + 10K \right)$$

=

4)

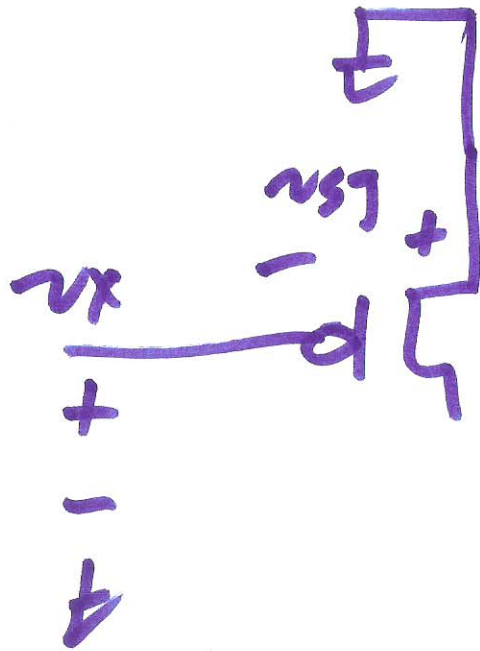

$$v_{sg} = -v_x$$

$$\frac{i_d}{g_{mP}} = -v_x$$

$$-\frac{i_o}{g_{mP}} = -v_x$$

$$g_{mP} v_x = i_o$$

$$i_o = \frac{r_{op} || r_{on} (1 + g_{mP} \cdot 10k)}{\frac{1}{g_{mP}} + 10k} \cdot g_{mP} \quad 3.6 \frac{\mu A}{V}$$

$$\approx \frac{r_{op}}{10k} \cdot g_{mP} \approx \frac{200k}{10k} \cdot 183 \frac{\mu A}{V}$$

5)

$$R_o = \frac{1}{g_{mP}} \approx \frac{1}{3.6 \mu A} = 300 \Omega$$


$$10k \parallel R_{o5} \approx 10k$$

$$R_{of} = \frac{300 \left(1 + \frac{\mu_n \cdot 3.6 \mu A}{10k} \right)}{1 + \frac{\mu_n \cdot 3.6 \mu A}{10k}}$$

$$\approx \frac{300 \cdot 36}{10k} = 300(1 + 36)$$

$$\approx \underline{\underline{10k}}$$

6)

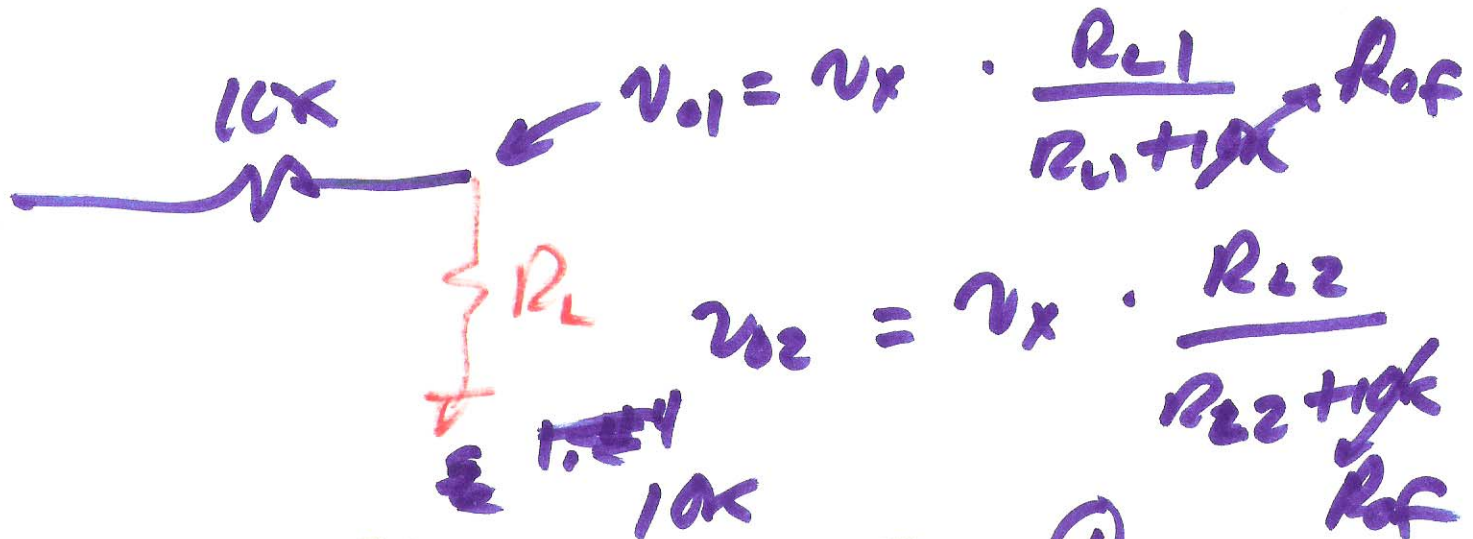

$$.77 = v_x \cdot \frac{10k}{10k + R_{of}} \quad (1)$$

$$1.4 = v_x \cdot \frac{20k}{20k + R_{of}} \quad (2)$$

$$\frac{(2)}{(1)} \Rightarrow 1.81 = \frac{20k}{10k} \cdot \left(\frac{20k + R_{of}}{10k + R_{of}} \right)$$

$$.905(10k + R_{of}) = 20k + R_{of}$$

$$9.05k + 9.05 R_{of} = 20k + R_{of}$$

||



$$\frac{1.4}{.77} = \frac{\frac{20k}{20k + R_{of}}}{10k}$$

$$1.81 = 2 \cdot \frac{10k + R_{of}}{20k + R_{of}}$$

$$.905(20k + R_{of}) = 10k + R_{of}$$

$$18.1k + .905 R_{of} = 10k + R_{of}$$

$$8.1k = .1 R_F$$

$$R_F = 81k$$

8)