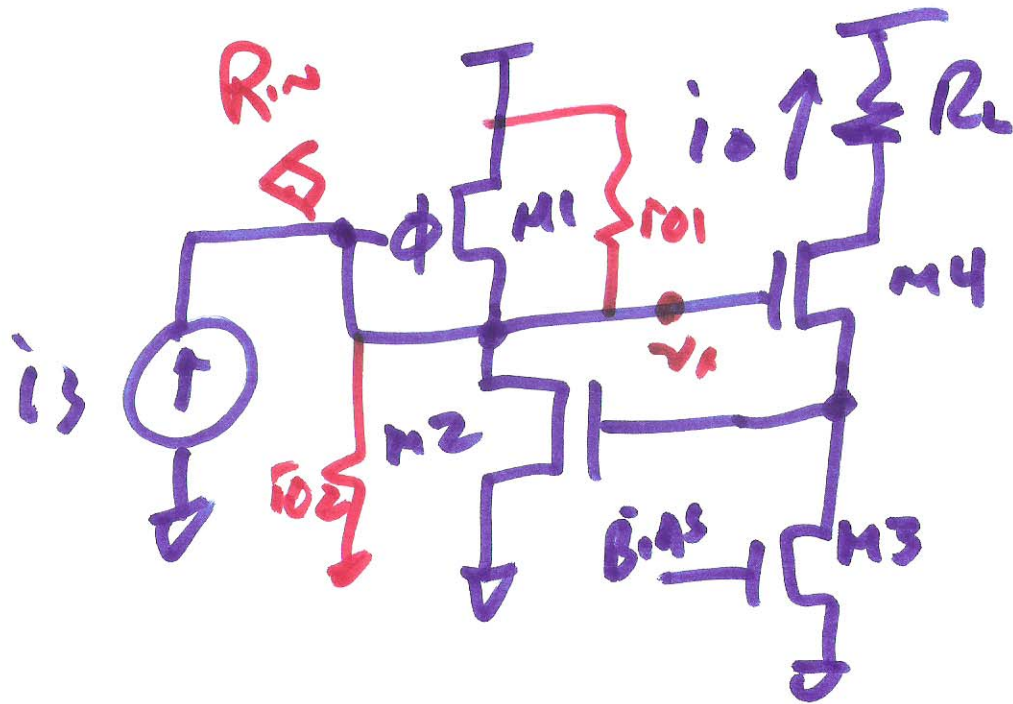



59:55

Section 31.7

the current Amplifier


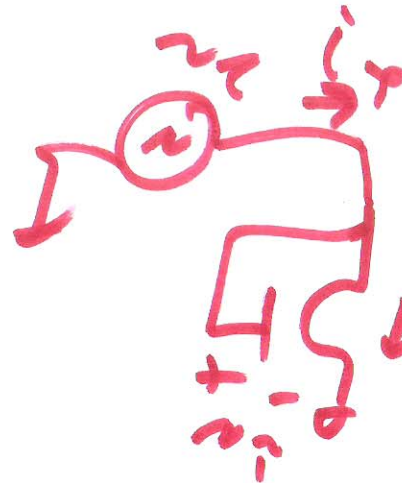
$$R_o = r_{o1} \parallel r_{o2} \parallel \frac{1}{g_m}$$



$$g_m v_T = i_T$$



$$\frac{v_T}{i_T} = \frac{1}{g_m}$$

Shunt - series


$$v_x = i_s \cdot (r_{o1} \parallel r_{o2} \parallel \frac{1}{g_m})$$

$$\frac{v_x}{i_s} = r_{o1} \parallel r_{o2} \parallel \frac{1}{g_m}$$

1)

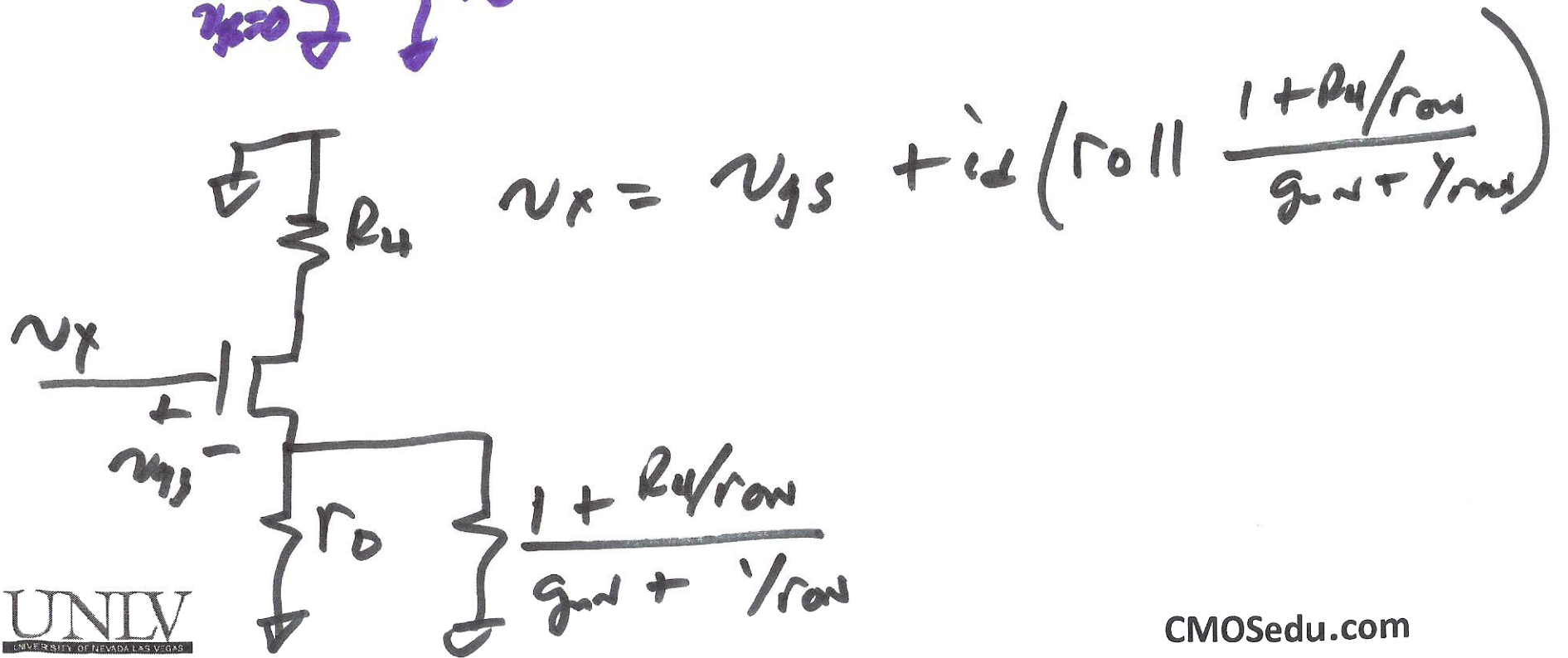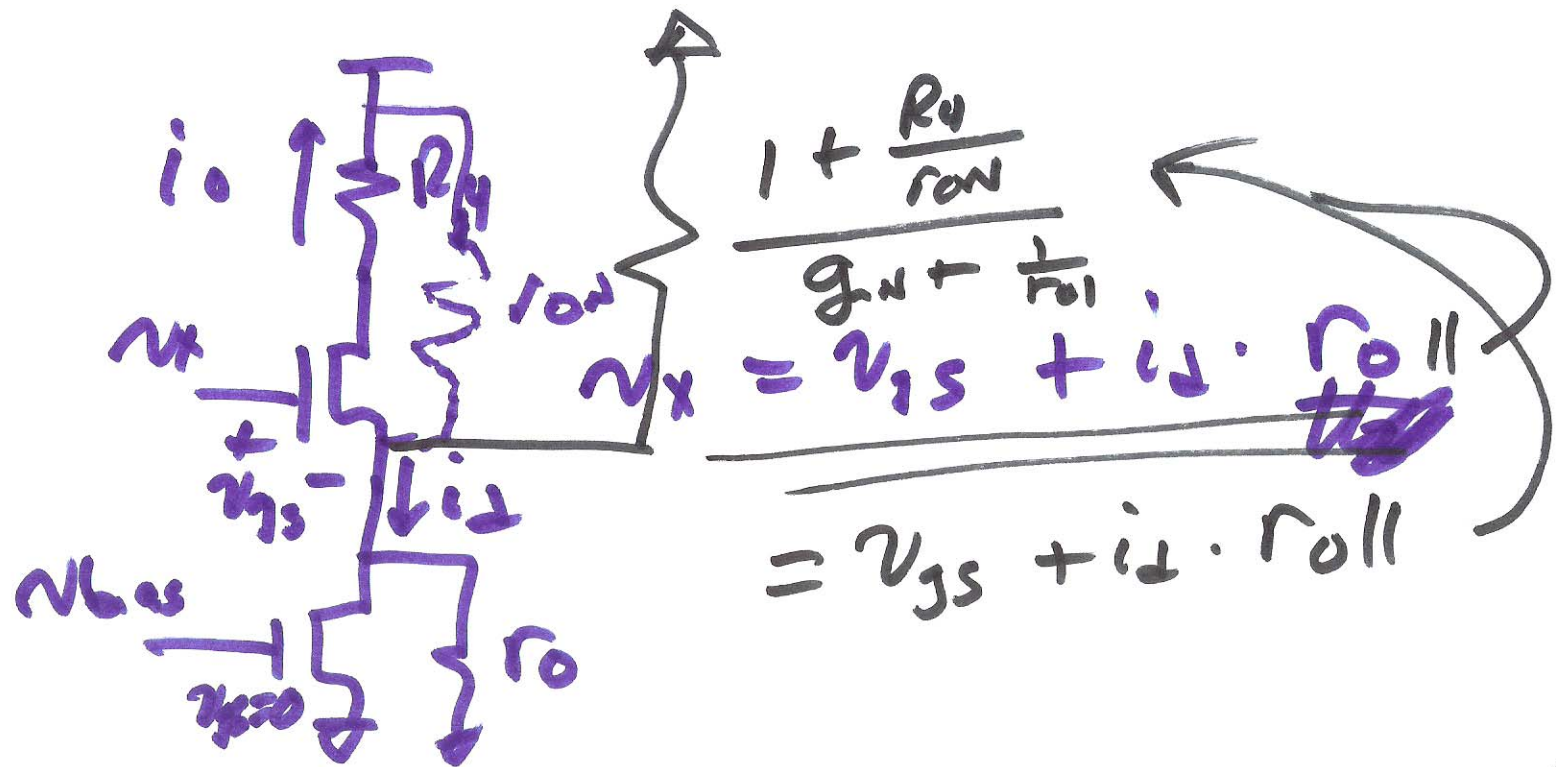

2)

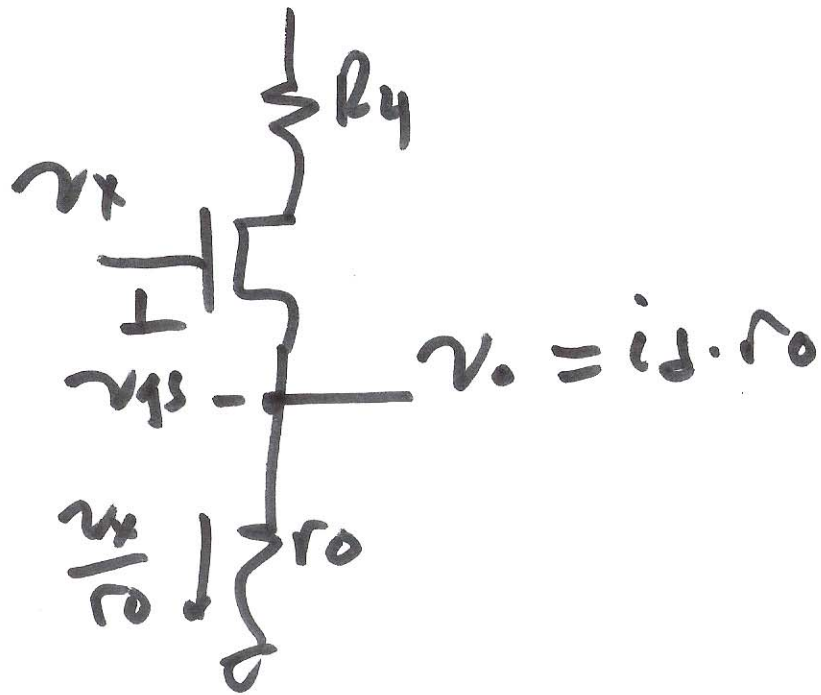

$$v_x = v_{gs} + i_o r_o$$

$$v_x = i_o \left(\frac{1}{g_m} + r_o \right)$$

$$\frac{i_o}{v_x} = \frac{1}{\frac{1}{g_m} + r_o}$$

$$\approx \frac{1}{r_o}$$

$$\frac{i_o}{v_x} = \frac{1}{r_o} \cdot r_o \parallel r_o \parallel \frac{1}{g_m}$$

$$\approx \frac{1}{g_m \cdot r_o} \text{ (no units)}$$

$$R_{in} = r_{on} || r_{op}$$

$$v_x = i_s \cdot r_{on} || r_{op}$$

$$i_o = \frac{v_x}{r_o}$$


$$A_{ol} = \frac{i_o}{v_x} \cdot \frac{v_x}{i_g}$$

$$= \frac{1}{r_{on}} \cdot r_{on} || r_{op}$$

$$r_{on} = r_{op}$$

$$= \frac{1}{\cancel{r_{on}}} \cdot \frac{\cancel{r_{on}} \cdot r_{op}}{r_{on} + r_{op}}$$

$\frac{1}{50k} \cdot 100k$

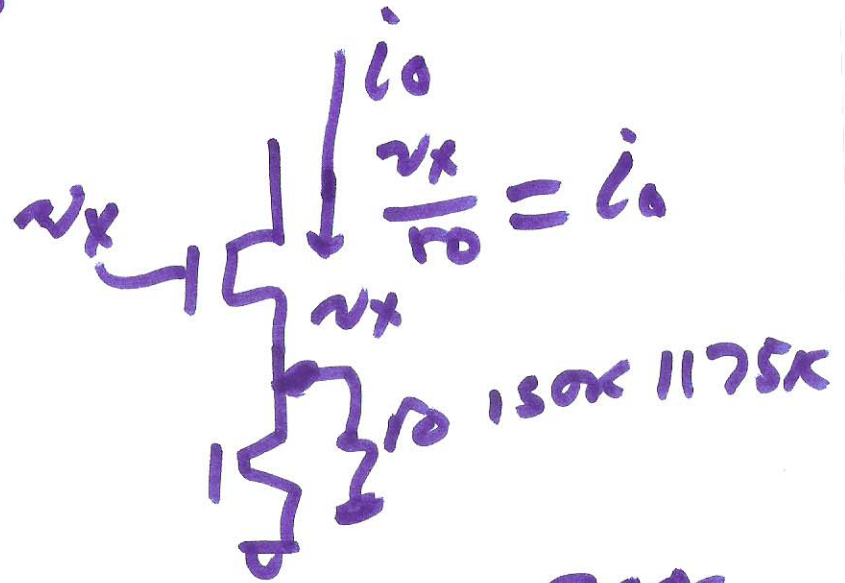


$$r_{o1} = 200k$$

$$r_{o3} = 200k$$

$$\boxed{\frac{1}{2} = A_{ol}}$$

CMOSedu.com

-6dB → -20dB

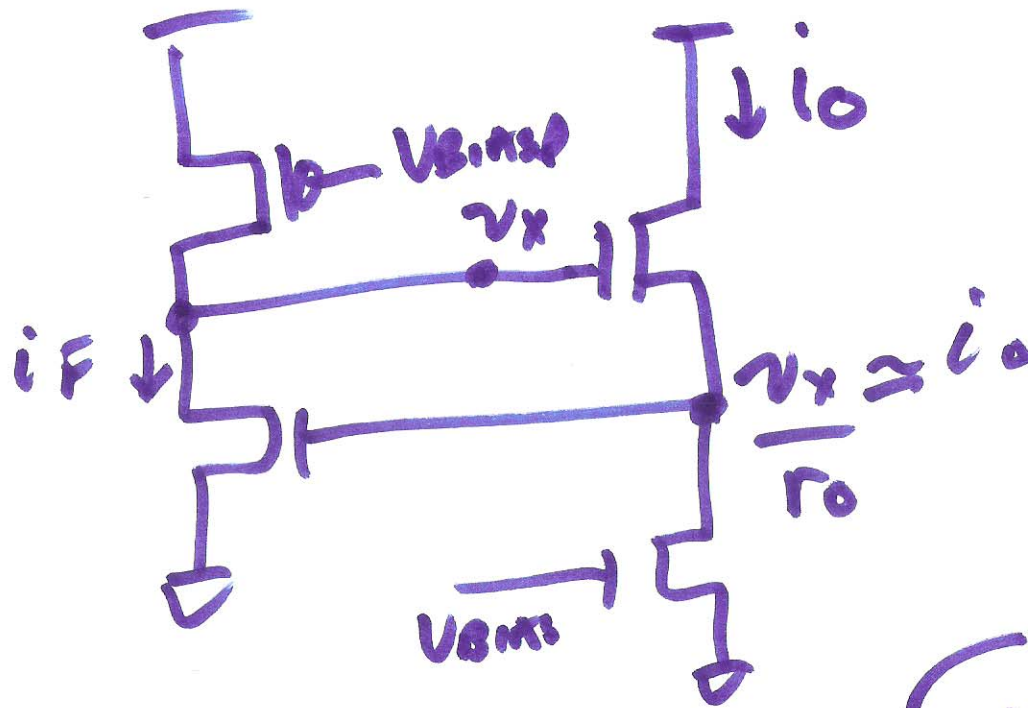

our spice example.

$$i_F = g_m v_x = \underbrace{g_m r_{O3}}_{\beta} i_O$$

$$\beta \cdot i_O = i_F$$

$$\beta = \frac{180 \mu A}{V} \cdot \frac{150k}{.15}$$


$$\beta = 207$$

$$A_{CL} = \frac{\frac{1}{2}}{\frac{\frac{1}{2} \cdot \frac{37}{2} + 1}} = \frac{1}{2} \frac{1}{\frac{37}{2} + 1} \approx .035$$

$$= \frac{\frac{1}{2}}{13.5 + 1} = \frac{1}{2} \left(\frac{1}{14.5} \right)$$

$$.035 \Rightarrow \approx 30\text{dB}$$

$$R_{\text{out}} = \frac{r_{\text{on}} || r_{\text{op}}}{1 + \beta \cdot A_{CL}} = \frac{200\text{k} || 200\text{k}}{1 + 27 \cdot \frac{1}{2}} = \frac{100\text{k}}{14.5} = \underline{\underline{6.9\text{k}}}$$

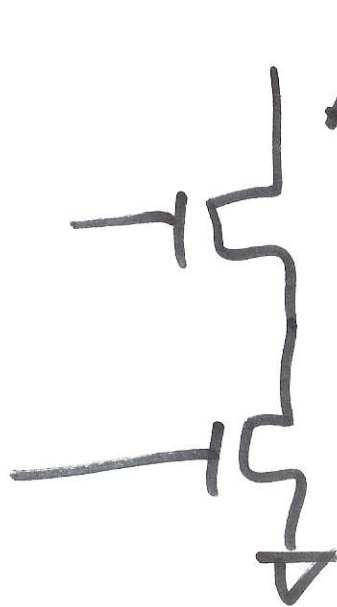


$$A_{\text{rocas}} = g_m r_o^2$$

$$R_{\text{of}} = \frac{g_m r_o^2}{1 + 27 \cdot \frac{1}{2}}$$

$$= \frac{190\mu \cdot 150\text{k} \cdot 150\text{k}}{14.5}$$

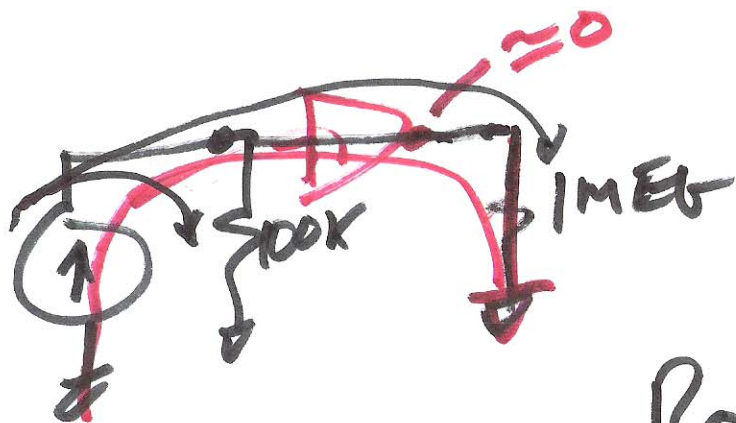~~$R_{\text{of}} = 300\text{k}$~~ I'm tired :)
wrong!



$$R_{\text{of}} = g_m r_o^2 \left(1 + 27 \cdot \frac{1}{2} \right)$$

$$= 190\mu \cdot 150\text{k} \cdot 150\text{k} \cdot 14.5$$

$$R_{\text{of}} = 62\text{ME}\Omega$$

CMOSedu.com