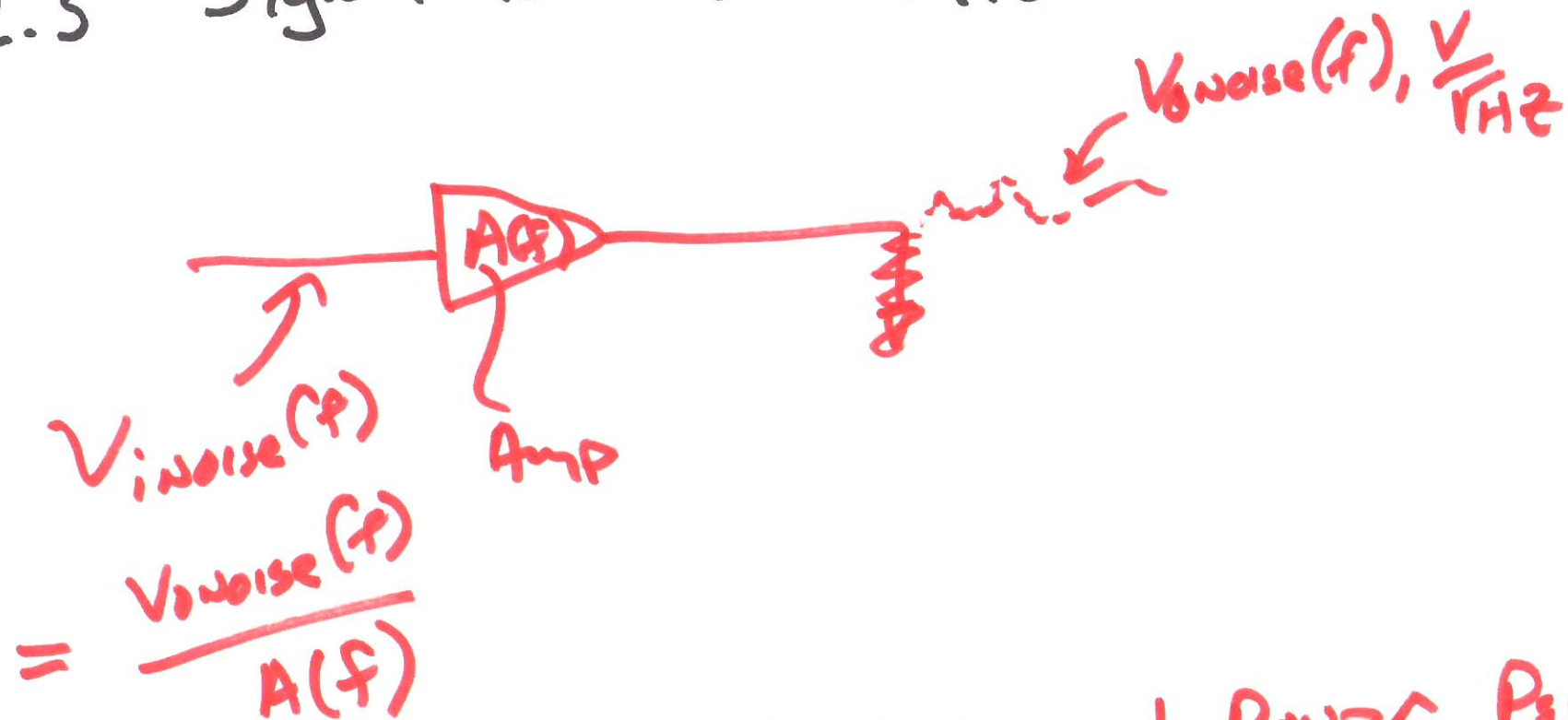


## 8.2.3 Signal-to-Noise Ratio




$$\text{SNR} = \frac{\text{desired signal power, } P_{\text{signal}}}{\text{undesired signal (noise), } P_{\text{noise}}}$$

$$= 10 \log \frac{P_{\text{signal}}}{P_{\text{noise}}} \rightarrow P_{\text{signal}} = \frac{V_{\text{sig, rms}}^2}{1 \Omega}$$


$$SNR = 10 \log \frac{P_s}{P_{noise}} = 20 \log \frac{\sqrt{P_s}}{\sqrt{P_{noise}}}$$
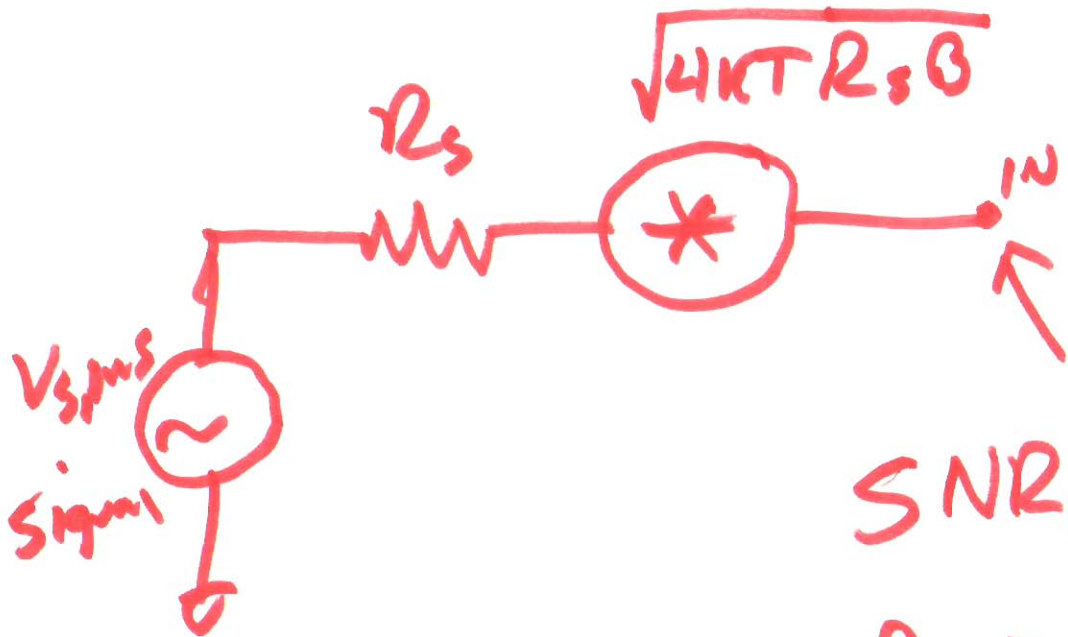
$$= 20 \log \frac{V_{s, rms}}{U_{noise, rms}}$$



$$SNR_{in} = \frac{V_{s,rms}^2}{4kTR_sB}$$

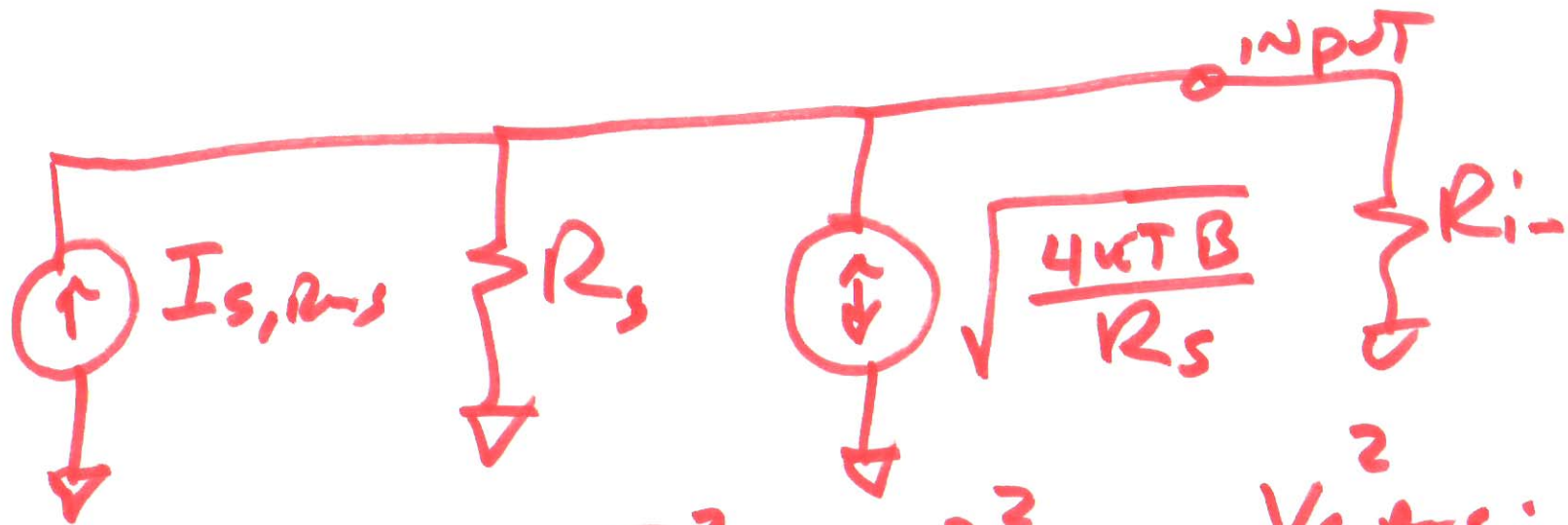$R_s \rightarrow 0, SNR \rightarrow \infty$   
Academic  
(in SPICE)




$$SNR_{in} = \frac{I_{s, rms}^2 \cdot R_s^2}{4kTB \cdot R_s^2} = \frac{V_{s, rms}^2}{4kTR_s \cdot B}$$


$$V_{s, rms}^2 \cdot \left[ \frac{R_{in}^2}{(R_s + R_{in})^2} \right]$$

SNR =
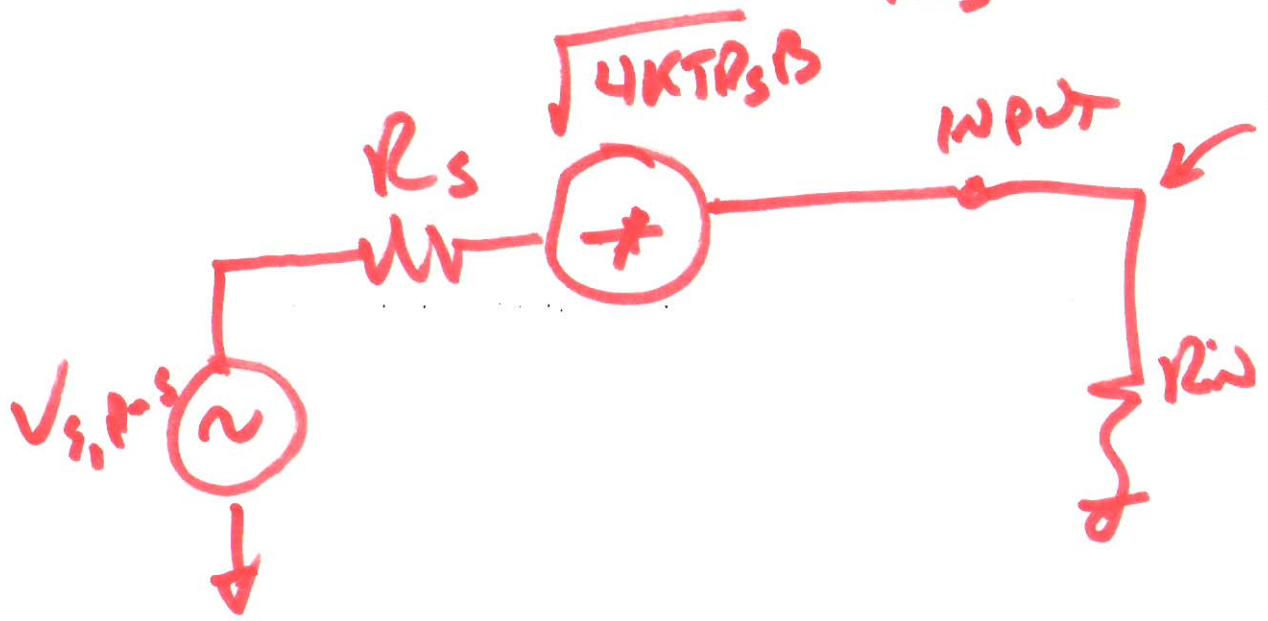
$$4kTR_s B \cdot \left[ \frac{R_s^2}{(R_s + R_{in})^2} \right]$$




3)

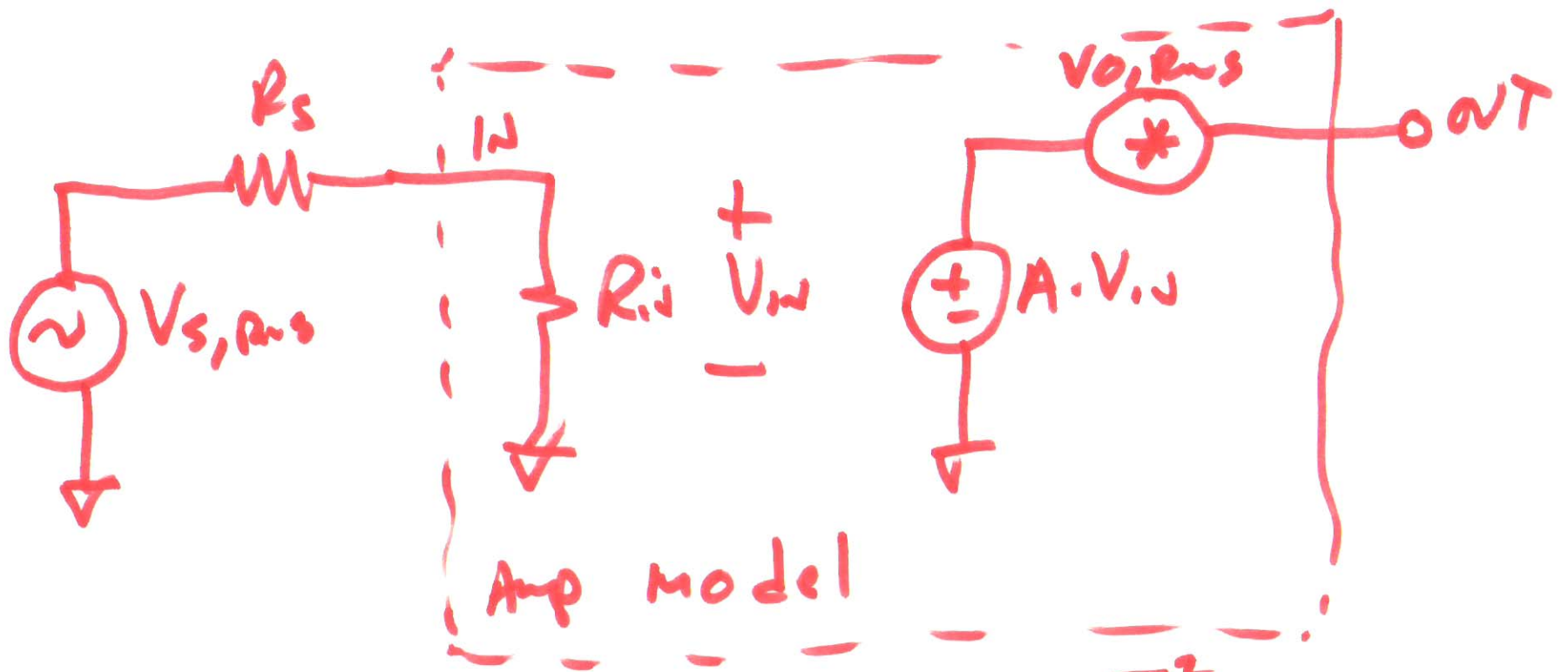

$$SNR_{out} = \frac{V_{s, rms}^2 \cdot \left[ \frac{\beta_j}{R_s + R_{i,j}} \right]^2 A^2}{V_{o, rms}^2}$$

4)

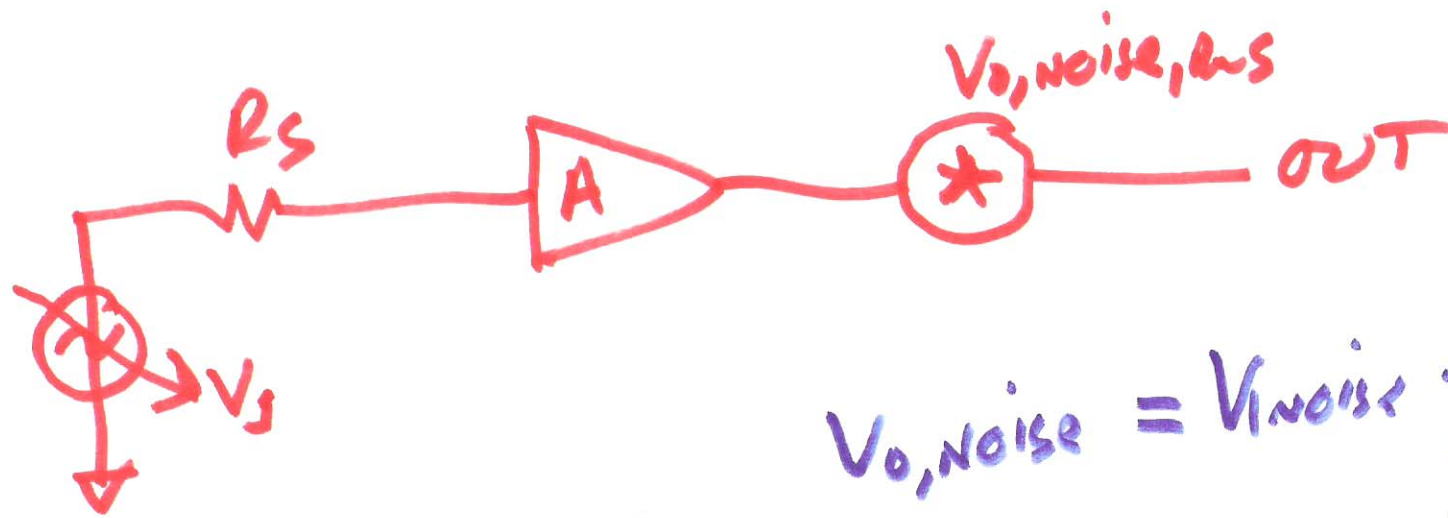


INPUT-referred

$$V_{o,noise} = V_{noise} \cdot \frac{R_i}{R_i + R_s} \cdot A$$


$$R_i = \infty$$

$$V_{noise} = \frac{V_{o,noise}}{A}$$

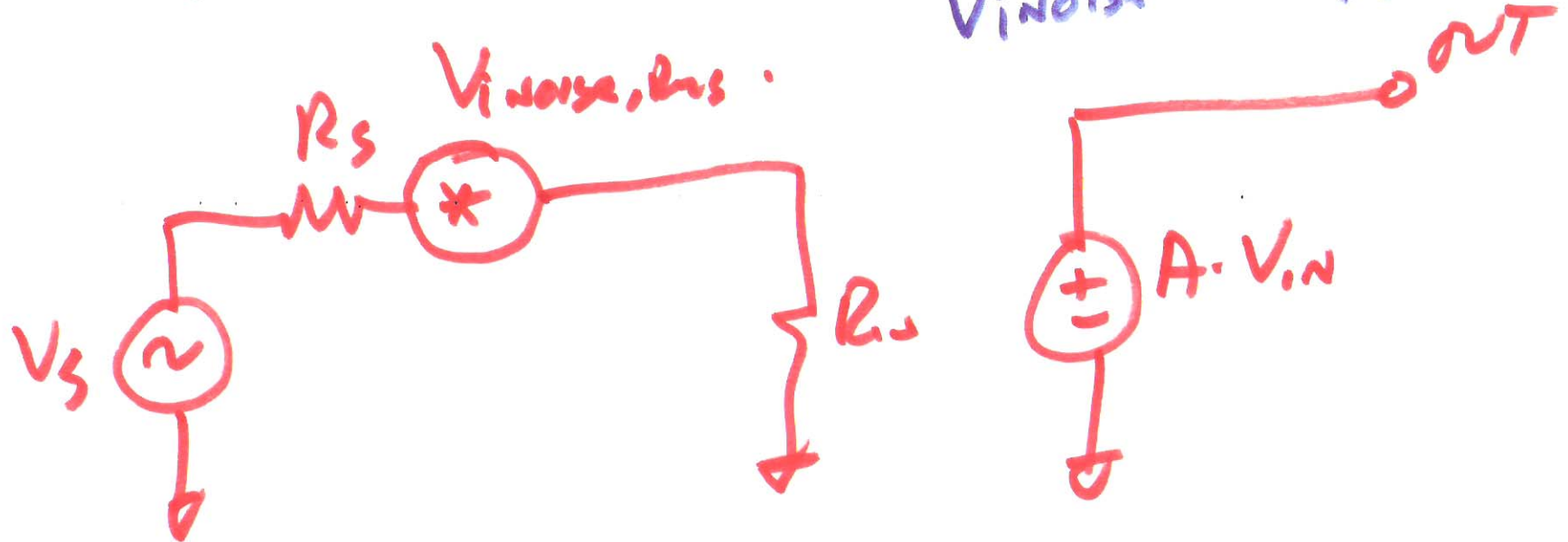


5)

# EXAMPLE

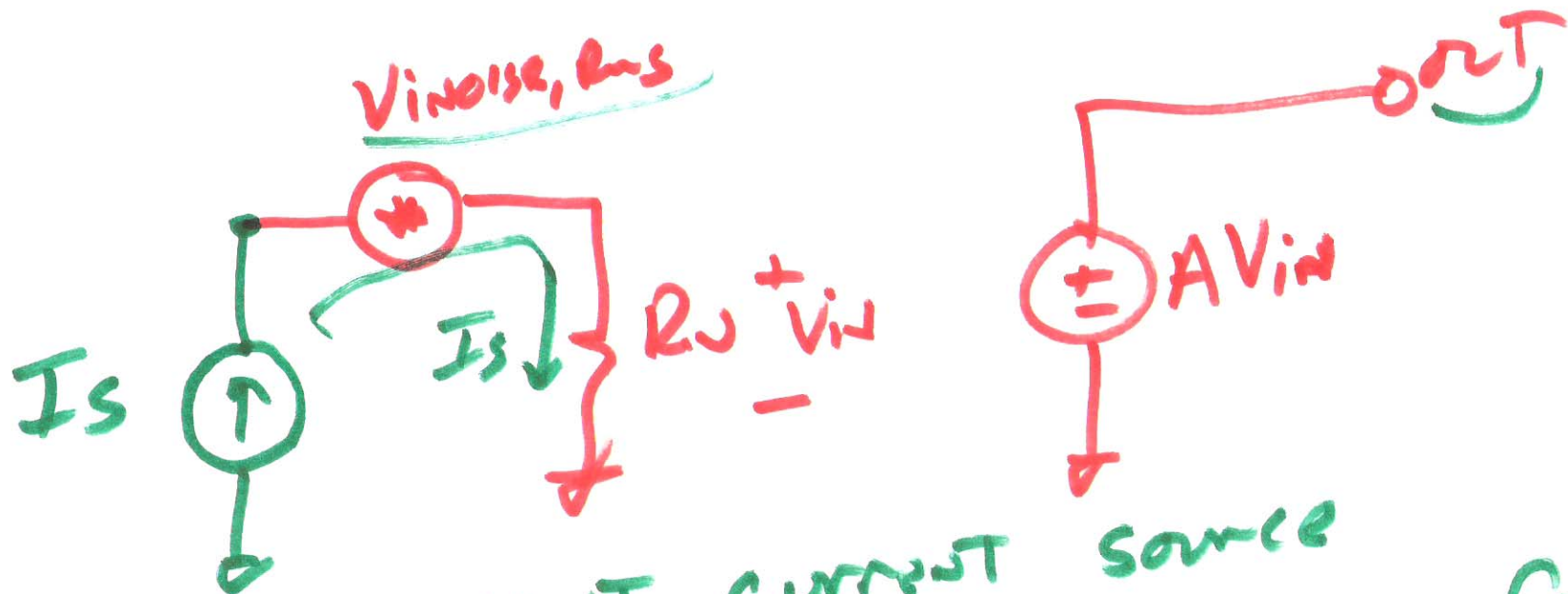

INPUT CURRENT SOURCE  
OUTPUT IS NOISE FREE!

Better input noise model

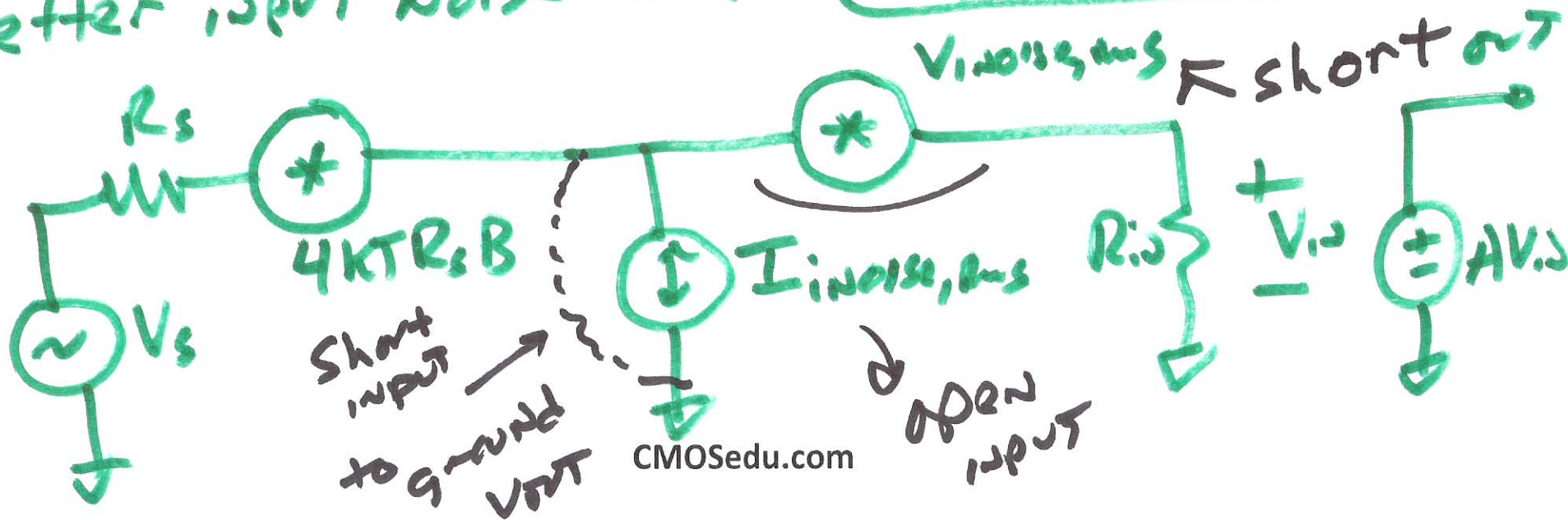

$4kTR_s B$   
short input to ground  $V_{in}$

OPEN INPUT

$$V_{O,NOISE}^2 = 4kTR_s \cdot B \cdot \left[ \frac{R_{IN}}{R_{IN} + R_s} \right]^2 A^2 +$$

$$I_{i,NOISE,AVS}^2 \cdot \left[ \frac{R_s \cdot R_{IN}}{R_s + R_{IN}} \right]^2 \cdot A^2 +$$

$$V_{i,NOISE,AVS}^2 \cdot \left[ \frac{R_{IN}}{R_{IN} + R_s} \right]^2 A^2$$

NOISE Figure

$$NF = 10 \log \frac{\overbrace{SNR_{IN}}^{F = \text{NOISE FACTOR}}}{SNR_{OUT}}$$

$$NF = 3 \text{ dB}$$

$$\begin{aligned} SNR_{IN} &= 70 \text{ dB} \\ SNR_{OUT} &= 67 \text{ dB} \end{aligned}$$



Optimum  $R_s$

$$NF = 10 \log \frac{V_{o,noise,rms}}{4kTR_s \cdot B \left[ \frac{R_n}{R_n + R_s} \right]^2 \cdot A^2}$$

$$NF = 10 \log F$$

Noise Factor

$R_s \rightarrow \text{Big}, NF \rightarrow \text{Big}$   
 $R_s \rightarrow 0, NF \rightarrow \text{Big}$

So what is  $R_{s,opt}$

Optimum source  
resistance

to minimize NF?

8)



$$F = \frac{4kTR_s B + I_{noise, R_s}^2 + V_{noise, R_s}^2}{4kTR_s B}$$

$$\frac{\delta F}{\delta R_s} = 0, \text{ solve } R_{s, opt}$$

$$\frac{\delta F}{\delta R_s} = \left( 1 + \frac{I_{noise, R_s}^2 \cdot R_s}{4kT B} + \frac{V_{noise, R_s}^2 R_s^{-1}}{4kT B} \right) = 0$$

$$0 = \frac{\delta}{\delta R_s} \left( I_{noise, R_s}^2 \cdot R_{s, opt} + V_{noise, R_s}^2 R_{s, opt}^{-1} \right)$$

a)

$$\begin{aligned}
 & I_{\text{noise, rms}}^2 + 2 I_{\text{noise, rms}} \cdot R_{s, \text{opt}} \cdot \frac{\delta I_{\text{noise}}}{\delta R_s} \\
 & - V_{\text{noise, rms}}^2 R_{s, \text{opt}}^{-2} + R_{s, \text{opt}}^{-1} \cdot 2 V_{\text{noise, rms}} \cdot \frac{\delta V_{\text{noise}}}{\delta R_s} \\
 & = 0
 \end{aligned}$$

$$I_{\text{noise, rms}}^2 = \frac{V_{\text{noise, rms}}^2}{R_{s, \text{opt}}^2}$$

$$R_{s, \text{opt}} = \frac{V_{\text{noise, rms}}}{I_{\text{noise, rms}}}$$

$$F_{opt} = 1 + \frac{(V_{noise,rms} \cdot I_{noise,rms})/2}{kTB}$$

