

Figure 8.31 Input-referred noise for the TLC220x low-noise op-amp.

$$V_{1/f}^2(f) = \frac{F_{NN}}{f} \cdot V^2$$

$$\frac{F_{NN}}{1} = \frac{(56 \text{ nV})^2}{1}$$

$$F_{NN} = 3.14 \times 10^{-15} \text{ V}^2$$

$$V_{\text{noise, rms}}^2 = \int_{f_L}^{f_H} \frac{F_{NN}}{f} \cdot df = F_{NN} \cdot \ln \frac{f_H}{f_L}$$

$$f_H = 100 \text{ GHz}$$

$$f_L = 10^{-10} \text{ Hz}$$

once/320 years



))

$$\ln \frac{100 \text{ GHz}}{10^{-10} \text{ Hz}} \approx 49$$

$$V_{\text{noise, rms}} = 7 \cdot \sqrt{FNN}$$

$$\frac{KT}{C} \quad N_{\text{EB}} = \frac{\pi}{2} f_{3\text{dB}}$$

Example 8.15

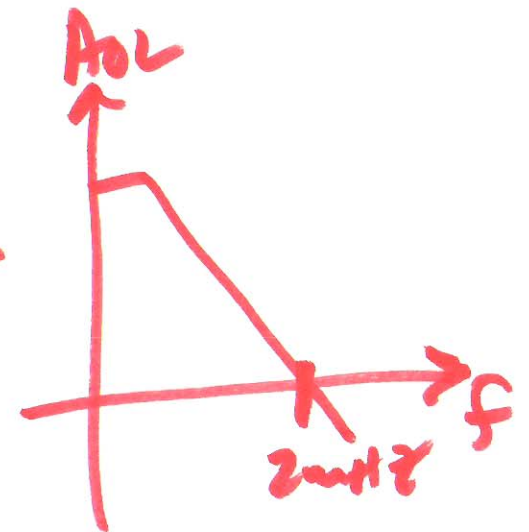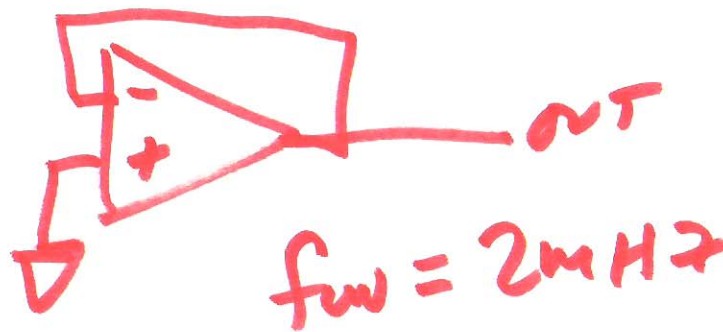

2)


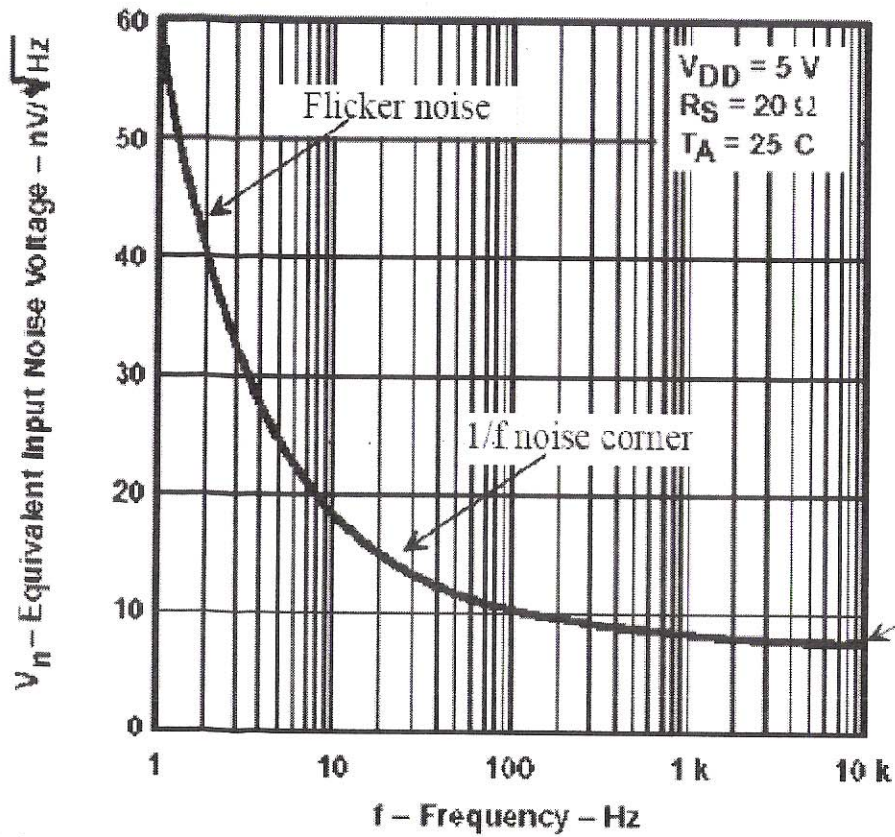


Figure 8.31 Input-referred noise for the TLC220x low-noise op-amp.

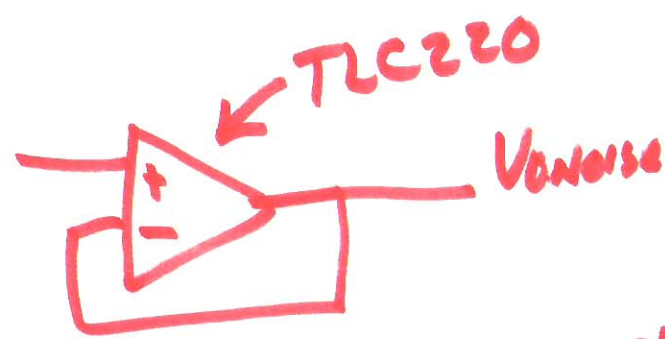

$$V_{noise}^2(f) = \frac{3.14 \times 10^{-15} V^2}{f \text{ Hz}} + 64 \times 10^{-18} \frac{V^2}{\text{Hz}}$$

OUTPUT NOISE PSD

$$V_{noise, rms}^2 = 49 \cdot 3.14 \times 10^{-15} + 64 \times 10^{-18} \frac{V^2}{\text{Hz}} \cdot 2 \text{ MHz} \cdot \frac{\pi}{2}$$


$$GAIN \cdot BW = f_{3dB}$$

$$V_{noise, rms} = \underline{\underline{154 \mu V}} = V_{noise, rms}$$

Thermal

5)



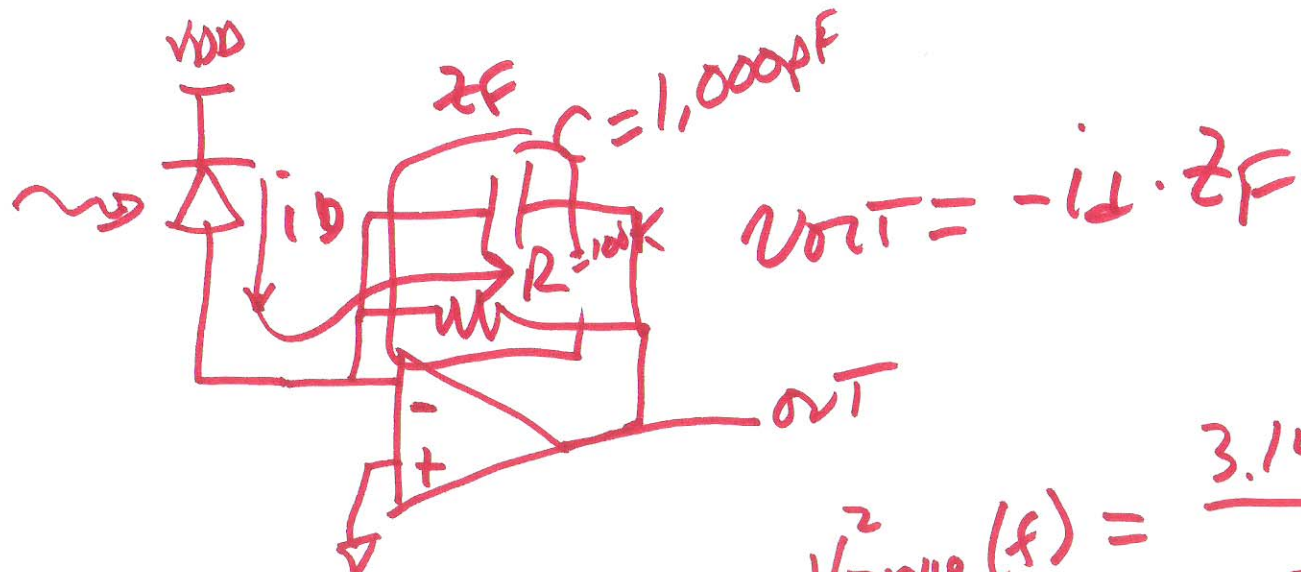

$$V_{noise}^2(f) = \frac{3.14 \times 10^{-15} \text{ V}^2}{f, \text{ Hz}} + 64 \times 10^{-18} \frac{\text{V}^2}{\text{Hz}}$$

$$+ \frac{4KT}{100K} \cdot \frac{100K \cdot \frac{1}{j\omega 1000PF}}{100K + \frac{1}{j\omega 1000PF}}$$

NOISE CKT



$$64 \times 10^{-18} \frac{\text{V}^2}{\text{Hz}}$$

$$+ \frac{3.14 \times 10^{-15} \text{ V}^2}{f}$$

$$|A(f)| = \left| \frac{v_{out}}{i_d} \right| = \frac{R_F}{1 + j\omega R_F C}$$

$$V_{\text{noise, rms}}^2 = 49 \cdot 3.14 \times 10^{-15} + 64 \times 10^{-18} \cdot \frac{\pi}{2} \cdot 2\text{MHz}$$

$$+ \frac{kT}{CE} =$$

$$V_{\text{noise, rms}} \approx 14.34 \text{ V}$$

$$\rightarrow 154 \times 10^{-15} + 200 \times 10^{-12} + 4 \times 10^{-12}$$

Noise free  $\rightarrow$  Op-Amp



$$V_{\text{noise, rms}} = \sqrt{4 \times 10^{-12}}$$

$$= \underline{\underline{2 \mu\text{V}}}$$


# Random Telegraph Signal Noise

(RTS)


Popcorn, Burstnoise

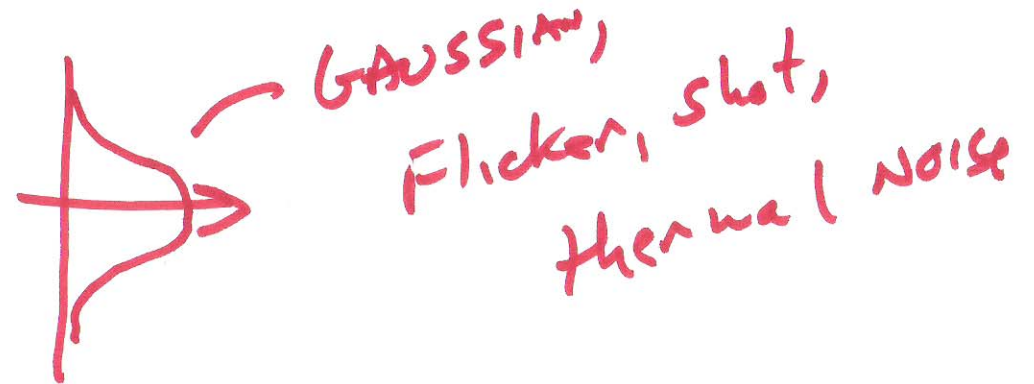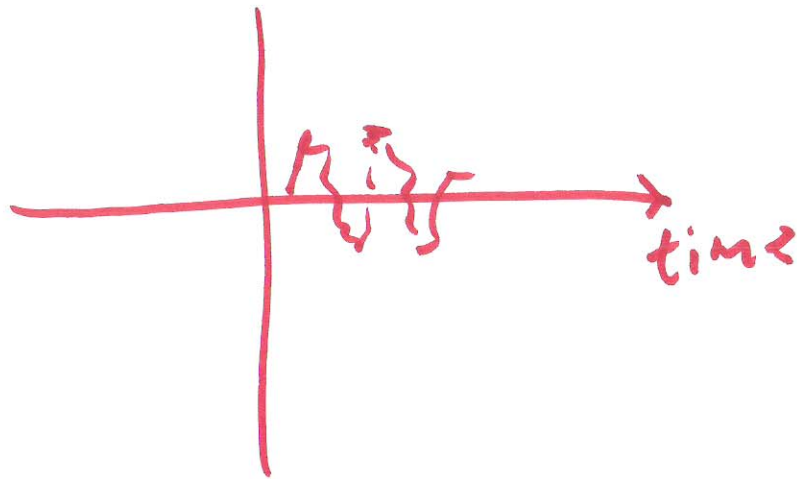

RTS  $\rightarrow$  Not Gaussian


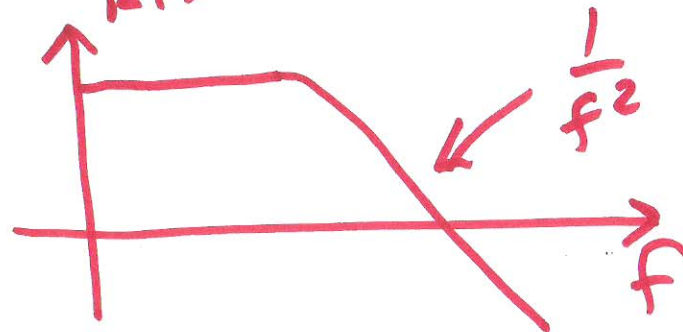


b)

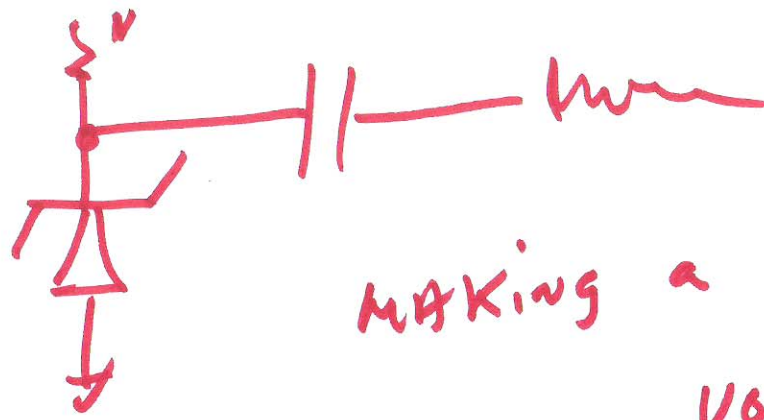

MAKING a LOW-NOISE  
VOLTAGE REFERENCE  
USING ZENER

Avalanche

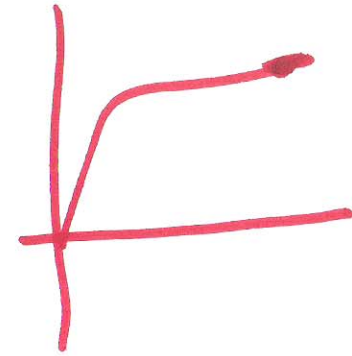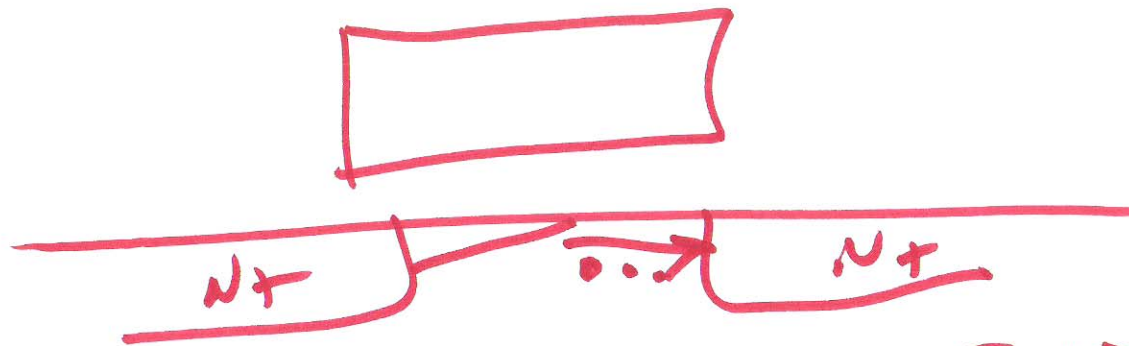

IMPACT IONIZATION

HIGHER  $V_{DS}$

→