

Ex. 9.5

$$i_d = g_m v_{gs}$$

$$I_D = \frac{K_P \cdot W}{2 \cdot L} (V_{GS} - V_{THN})^2$$

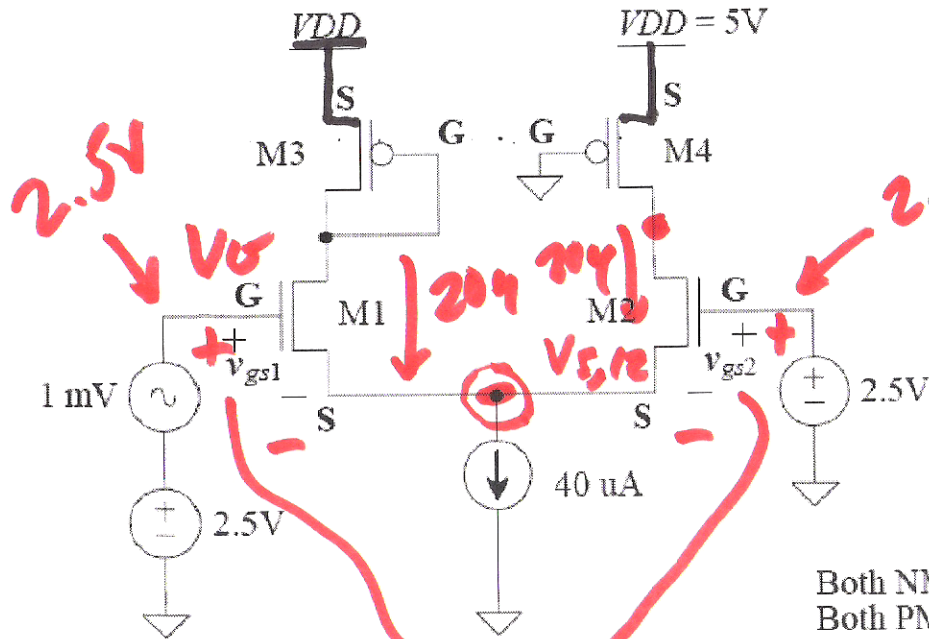


Figure 9.17 Circuit discussed in Ex. 9.5.

$$V_{GS} = \sqrt{\frac{2I_D \cdot L}{W \cdot K_P}} + V_{THN}$$

$$= \sqrt{\frac{2 \cdot 20 \mu A \cdot 2}{10 \cdot 120 \mu A}} + 0.8$$

$$V_{GS} = 1.058$$

$$\begin{aligned} I_{D1} &= I_{D2} = 20 \mu A \\ V_{GS1} &= V_{GS2} = 2.5V \\ V_{S1,2} &= 1.058V \end{aligned}$$

$$V_{GS} = V_G - V_S = 1.058 = 2.5 - V_S$$

$$V_S = 1.442$$

$$V_{SG} > V_{THP}$$

for saturation, PMOS


$$V_{SD} \geq V_{SG} - V_{THP} = V_{SD, SAT}$$

$$V_{SD} = V_{SG}, 0 \geq V_{THP}$$

M3 in saturation

$$V_{SG} = \sqrt{\frac{2I_D \cdot L^2}{K_{PP} \cdot W_3}} + V_{THP}$$

$$= 1.158$$

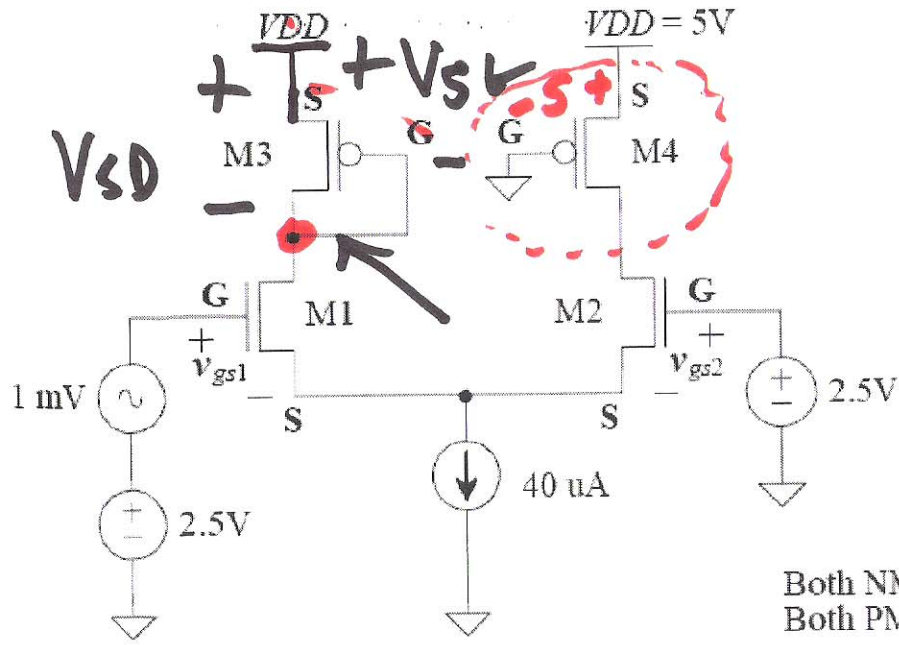

Both NMOS are 10/2
Both PMOS are 30/2

Figure 9.17 Circuit discussed in Ex. 9.5.

for M1 to be in sat.

$$V_{D1} = V_{DD} - V_{SG}$$


$$V_{D1} = 5 - 1.158 = 3.842$$

$$V_{DS1} > V_{GS1} - V_{THN}$$

$$3.842 - 1.442 > 2.5 - 1.442$$

Yes, M1 in saturation
1.7
CMOSedu.com

2)

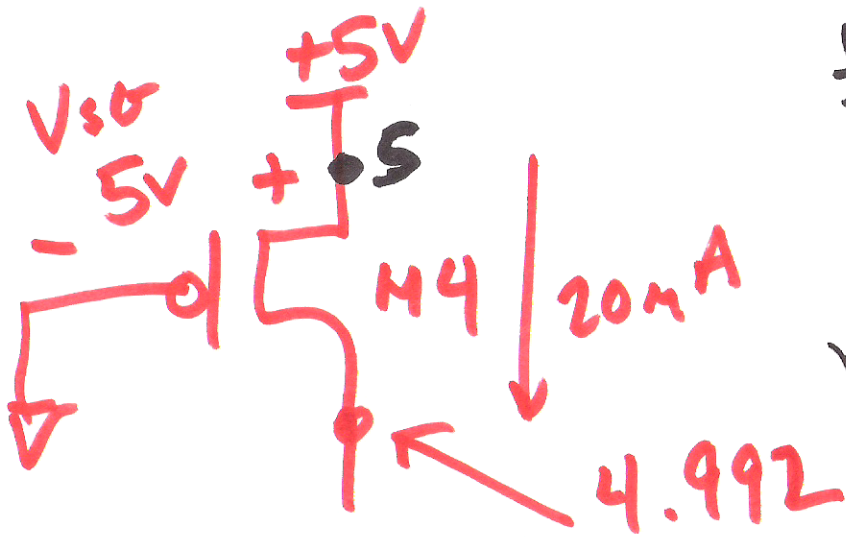

for triode operation

for SAT

$$V_{SD} \geq V_{SG} - V_{THP}$$

$$V_S - V_D \geq 5 - .9$$

$$V_{DD} - V_D \geq 4.1$$

$$V_D \leq .9V$$


$$I_D = K_P \cdot \frac{W}{L} \cdot \left((V_{GS} - V_{THP}) V_{SD} - \frac{V_{SD}^2}{2} \right)$$

$$20 = 40 \cdot \frac{30}{2} \left((5 - .9) V_{SD} - \frac{V_{SD}^2}{2} \right)$$

M4 is in triode!

$$V_{SD} = 8.13 \text{ mV}$$


3)

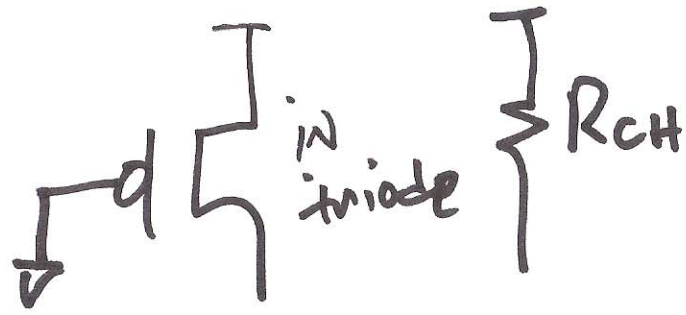

$$\frac{\delta(I_D + i_d)}{\delta v_{SD}} = \frac{\delta}{\delta v_{SD}}$$

$$I_D + i_d = K P_p \frac{W}{L} ((V_{GS} + v_{gs} - V_{TH}))^2$$
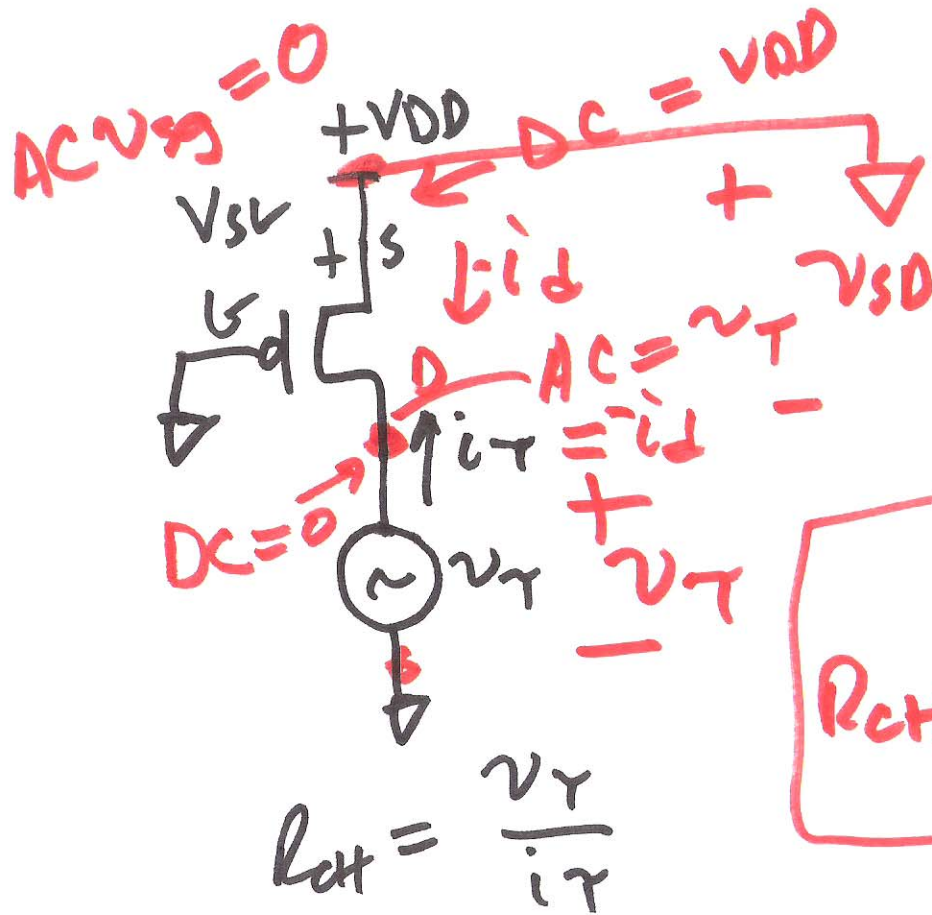
$$R_{CH} = \frac{v_{SD}}{i_d} = \frac{-v_T}{-i_T} + \frac{v_{SD}}{(V_{SD} + v_{SD})^2}$$



$$R_{CH} = \frac{1}{K P_p \frac{W}{L} (V_{GS} - V_{TH})}$$


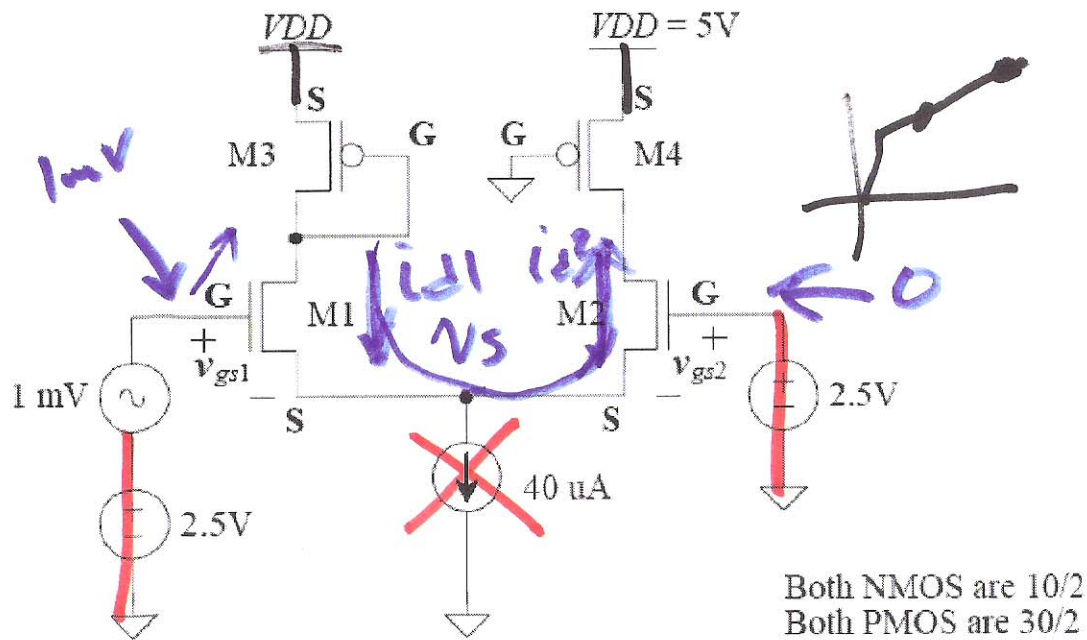


Figure 9.17 Circuit discussed in Ex. 9.5.

$$20 \mu A \rightarrow 20.1 \mu A = I_{D1}$$

$$19.9 \mu A = I_{D2}$$

S)

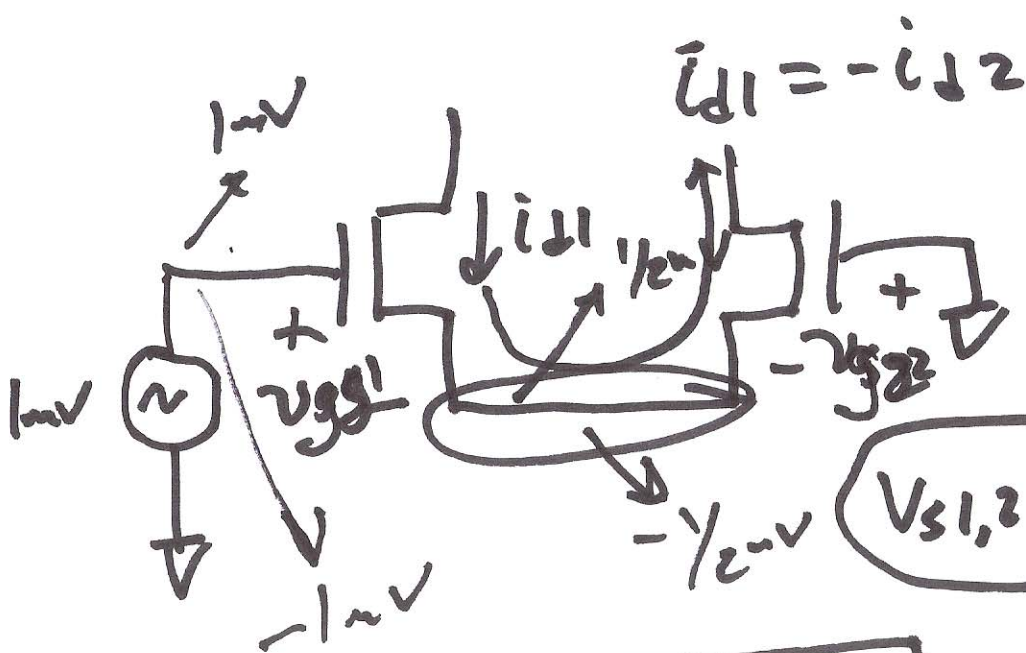

$$g_{m1} v_{gs1} = i_{D1}$$

$$g_{m2} v_{gs2} = i_{D2}$$

$$g_{m1} = g_{m2}$$

$$v_{s1,2} = \frac{1}{2} \mu\text{V}$$

$$i_{D1} = -i_{D2}$$

$$v_{gs1} = -v_{gs2}$$

$$\frac{1}{2} \mu\text{V} = -\left(-\frac{1}{2} \mu\text{V}\right)$$


$$g_{m1} = \sqrt{2 \cdot k_p \cdot \frac{W}{L} \cdot 20\mu\text{A}}$$

$$= 150 \mu\text{A}$$

$$i_{D1} = g_m v_{gs} = 150 \mu\text{A} \cdot \frac{1}{2} \mu\text{V}$$

$$i_{D1} = 75 \mu\text{A}$$


$$i_{D2} = -75 \mu\text{A}$$

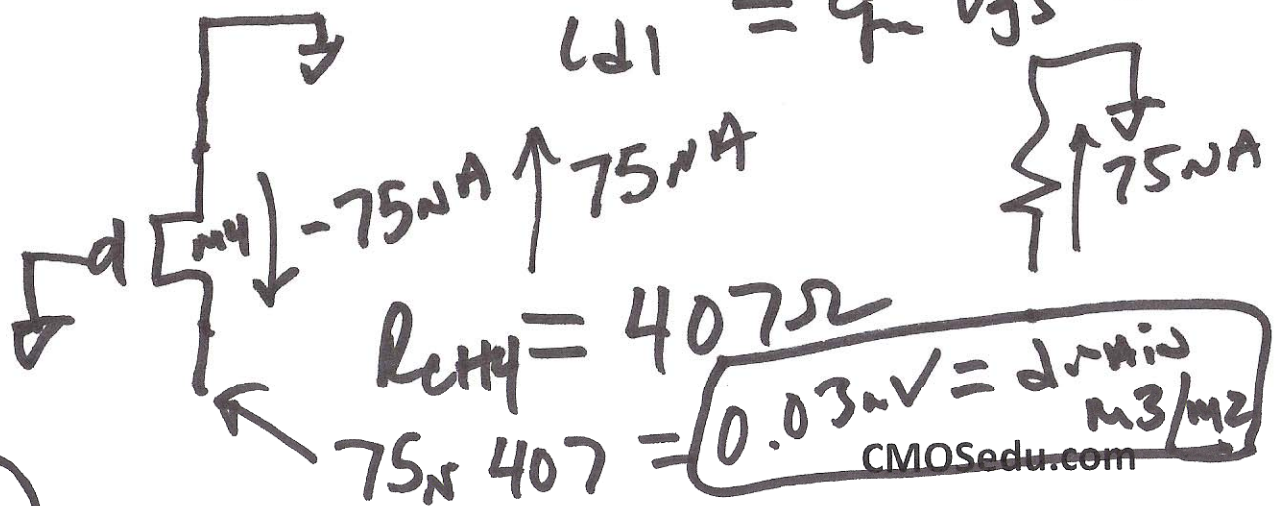

$$R_{cm4} = 407 \Omega$$

$$75 \mu\text{A} \cdot 407 = 0.03 \mu\text{V} = \text{drain}$$

6)

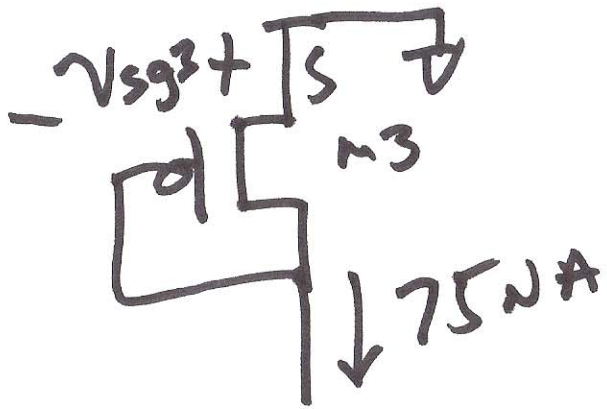

$$i_d = g_m V_{sg}$$

$$V_{sg} = \frac{1}{g_{mp}} \cdot i_d$$

$$g_{mp} = 150 \mu\text{A/V}$$

$$V_{sg} = -\frac{1}{2} \text{ mV}$$

drains, M1
or M3

