


Short channel MOSFETS

General Design (a starting point)

Long-channel devices

$$V_{DS,SAT} = V_{GS} - V_{THN}$$

doesn't work for short-channel MOSFETS

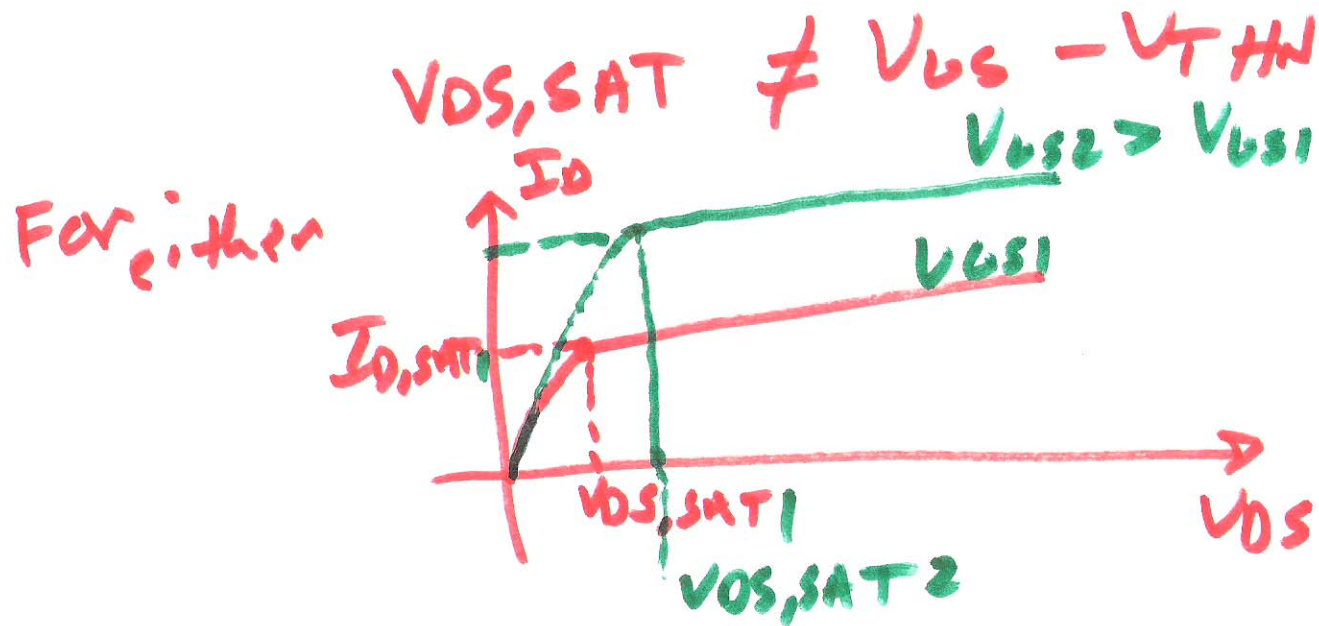

1)

$$f_T \Big|_{\text{long-channel}} = \frac{3\mu_n}{4\pi} \cdot \frac{V_{DS,sat}}{L^2} = \frac{3\mu_n}{4\pi L^2} (V_{DS} - V_{TH}) \quad (9.36)$$

for long or short-channel devices

$$V_{OV} = V_{DS} - V_{TH}$$

How do we select V_{OV} ?

for general design

in book (short channel) $V_{OV} \Rightarrow 5\% \text{ of } V_{DD}$


$$V_{OV} = 70 \text{ mV}$$

$$V_{TH} = 280 \text{ mV}$$

$$V_{DS} = 350 \text{ mV}$$

For High-Speed Design

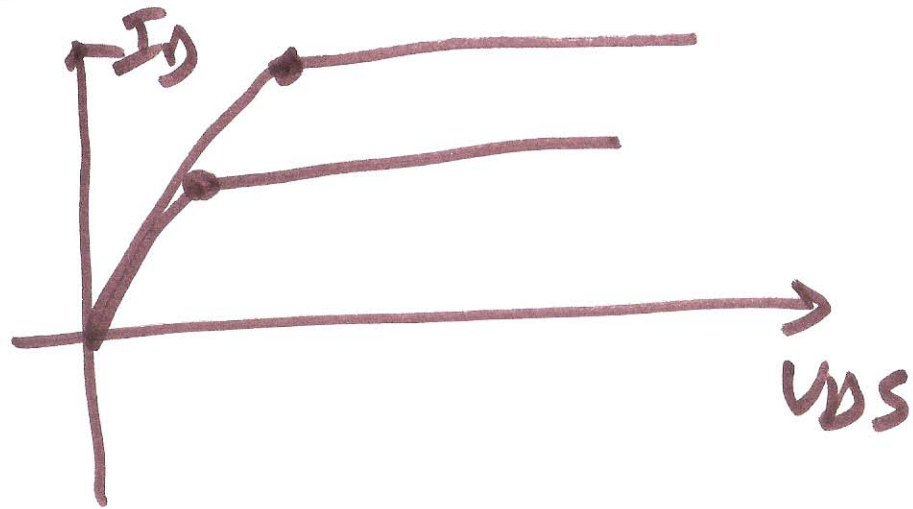$V_{ov} \rightarrow 10\%$ or more of V_{DD}



fan-shunt channel

$$f_T \approx \frac{g_m}{2\pi C_{gs}} \propto \frac{V_{ov}}{L}$$

for high-speed
use small
 $L!$

For short-channel devices

$$I_D \neq \frac{\beta}{2} (V_{GS} - V_{TH})^2, \quad g_m = \sqrt{2\beta I_D} = \beta (V_{GS} - V_{TH})$$

SQUARE-law equations \uparrow long channel

don't work!


$$i_D = v_{SAT} \cdot C_{ox} \cdot W (V_{GS} - V_{TH} - v_{DSSAT})$$

short channel

$$g_m = v_{SAT} \cdot C_{ox} \cdot W$$

independent of L

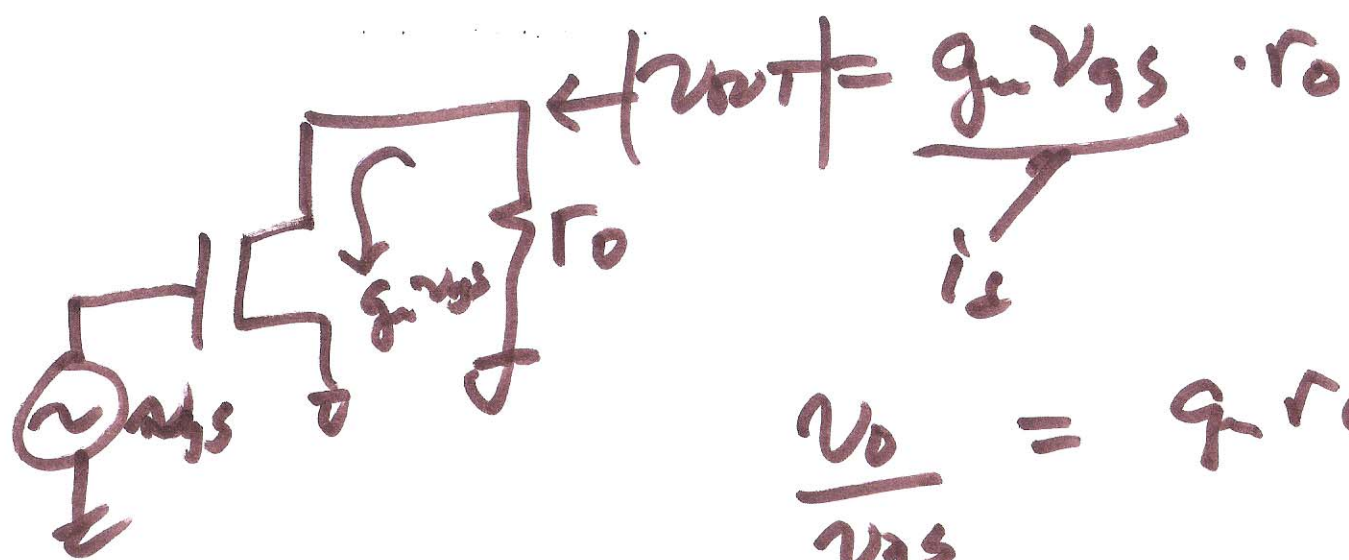g_m is dependent on L because v_{SAT} is dep on L !




$$\frac{v_o}{v_{gs}} = g_m r_o \quad \leftarrow \text{open-ckt gain!}$$

Long-channel devices

$$g_m r_o = \sqrt{2k_p \frac{W}{L} \cdot I_D} \cdot \frac{1}{\lambda I_D} = \frac{\sqrt{2k_p \frac{W}{L}}}{\lambda}$$

$g_m r_o \leftarrow \text{gain}$

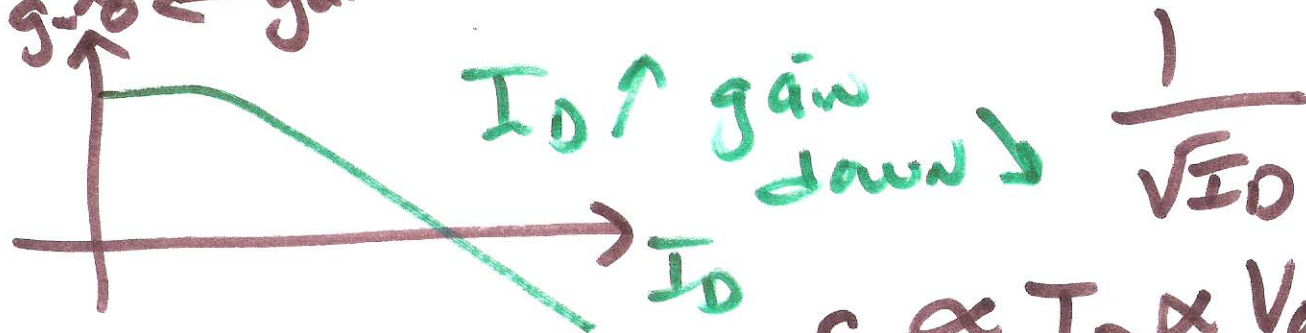

$$f_T \propto I_D \propto V_{ov}$$

$$V_{ov} \uparrow \rightarrow I_D \uparrow \rightarrow f_T \uparrow$$

5)

$$g_m r_o = \frac{K P_n \cdot \frac{W}{L} (V_{GS} - V_{THN})}{\lambda \underbrace{\frac{K P_n \cdot \frac{W}{L} (V_{GS} - V_{THN})^2}{2}}_{I_D}} = \frac{2}{\lambda (V_{GS} - V_{THN})}$$

$$= \frac{2}{\lambda \cdot V_{OVN}}$$

GAIN \cdot $f_T = GFT$ $V_{OVN} \uparrow$ $I_D \uparrow$ $f_T \uparrow$ $g_m r_o \downarrow$

$$g_m r_o \cdot f_T = \frac{34n}{4\pi L^2} \cdot V_{OVN}$$

$$= \frac{2}{\lambda V_{OVN}} \cdot V_{OVN} = GFT = \frac{34n}{2\pi L^2 \lambda}$$

$$\propto \frac{4n}{L^2}$$

6)

TO INCREASE BOTH SPEED
AND GAIN the only "tweak"
is Length!

$$GFT \propto \frac{\mu_n}{L^2}$$

In book

Best \rightarrow GFT for long-channel
for slow designs use old CMOS

$$= 750 \cdot 900 \text{ MHz} \approx 700 \text{ GHz}$$

Short channel GFT

$$= 25 \cdot 6 \text{ GHz} = 150 \text{ GHz}$$

for high-speed use Small/new
CMOS
Technology

33.57

7)