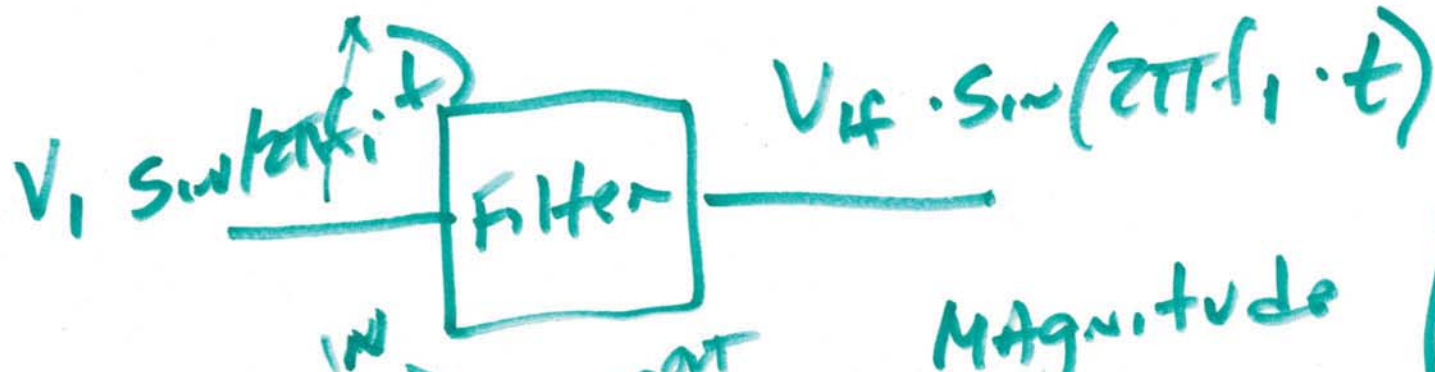


Ch. 3 Integrator building blocks

CMOS mixed-signal circuit Design



Magnitude $\left| \frac{V_{if}}{V_i} \right|$

$$\angle \frac{V_{if}}{V_i} = \theta = \frac{\Delta t}{T} \cdot 360^\circ$$

1)

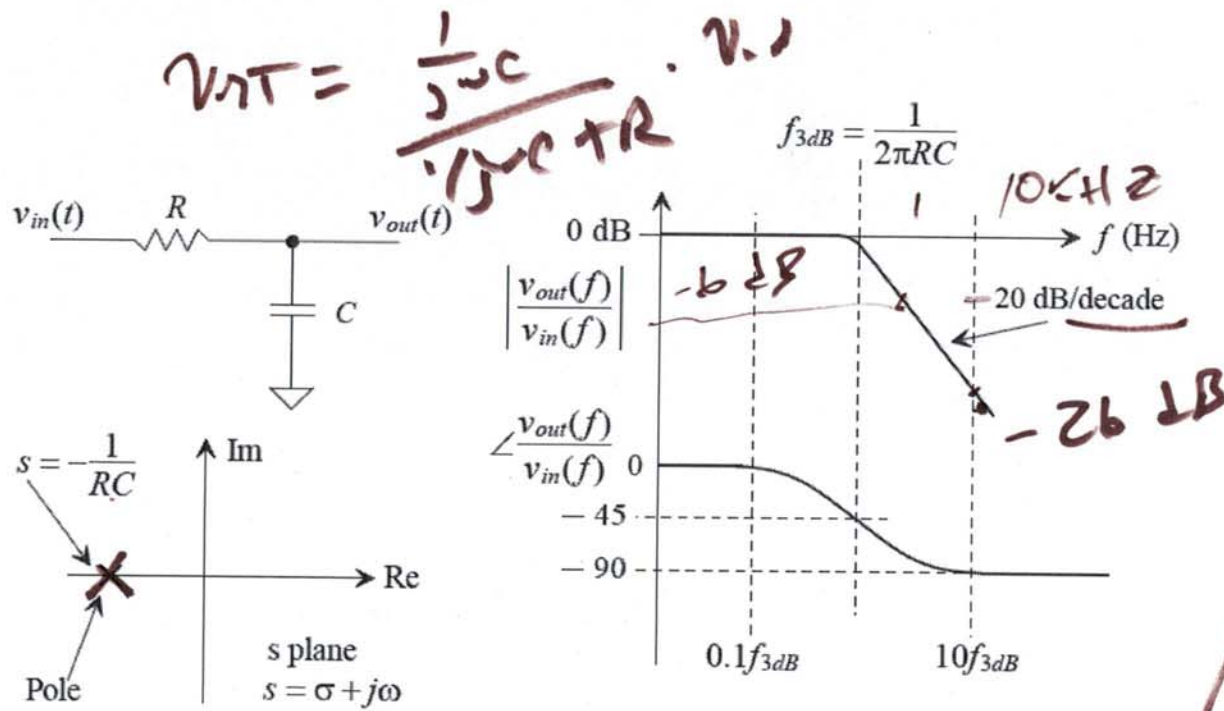


Figure 3.1 First-order lowpass filter.

$$\frac{V_{out}}{V_{in}} = \frac{1}{1 + j\omega RC}$$

$$s = j\omega = -\frac{1}{RC}$$

2)

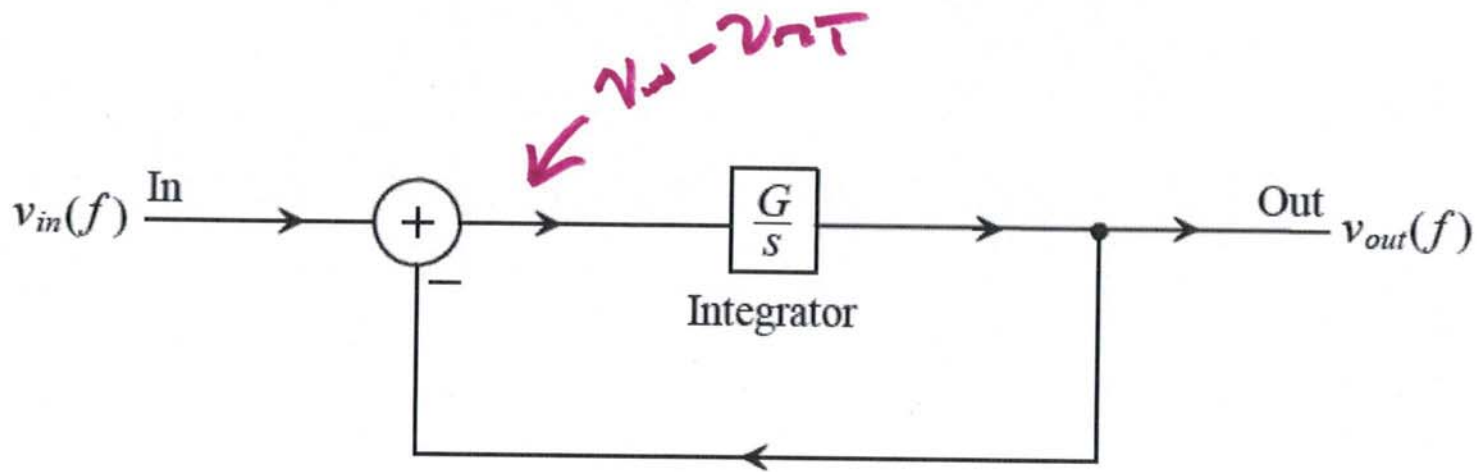


Figure 3.2 Block diagram of an integrator-based lowpass filter.

$$v_{out} = (v_{in} - v_{out}) \frac{G}{s}$$

$$v_{out} \left(1 + \frac{G}{s} \right) = v_{in} \cdot \frac{G}{s}$$

$$\frac{v_{out}}{v_{in}} = \frac{1}{1 + \frac{s}{G}}$$

$$G = \frac{1}{RC}$$

$$\left| \frac{v_{out+} - v_{out-}}{v_{in+} - v_{in-}} \right| = \frac{v_{out+}}{v_{in+}}$$

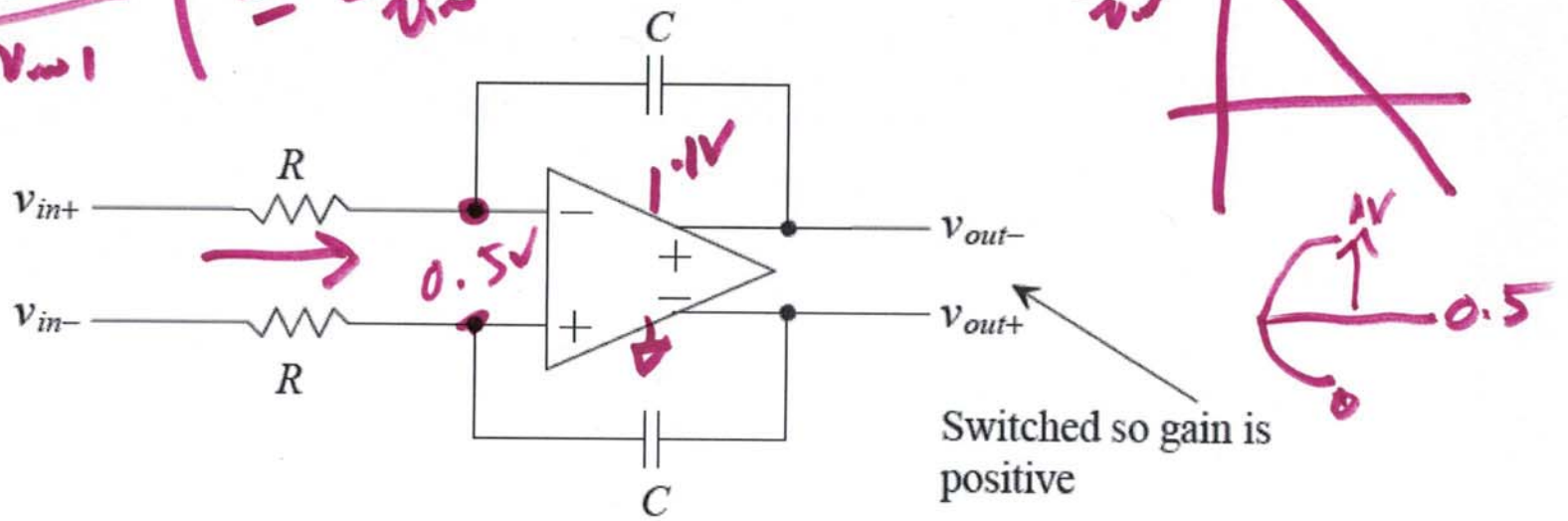


Figure 3.3 A continuous-time analog integrator (CAI).

$$\frac{v_{in} - 0}{R} = \frac{v_{out} - 0}{1/j\omega C} \Rightarrow \frac{v_{out}}{v_{in}} = \frac{-1}{j\omega RC}$$

= $\frac{-1}{j\omega RC}$

SWAPPING the OUTPUTS $\frac{1}{j\omega RC}$



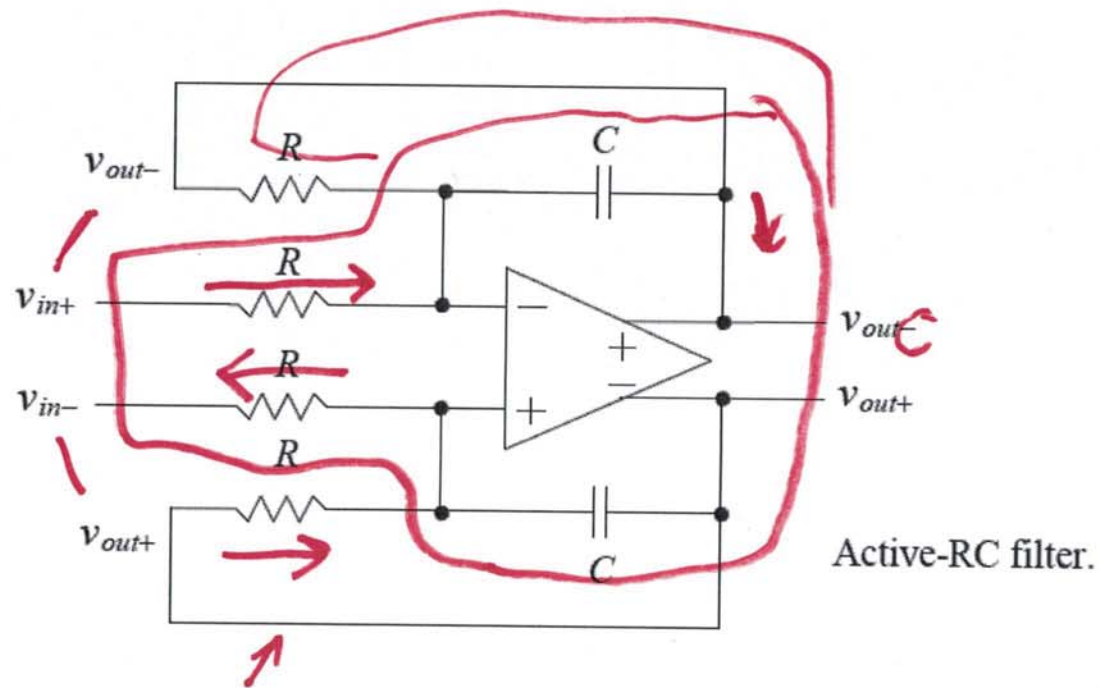


Figure 3.4 Implementation of a first-order lowpass filter using a CAI.

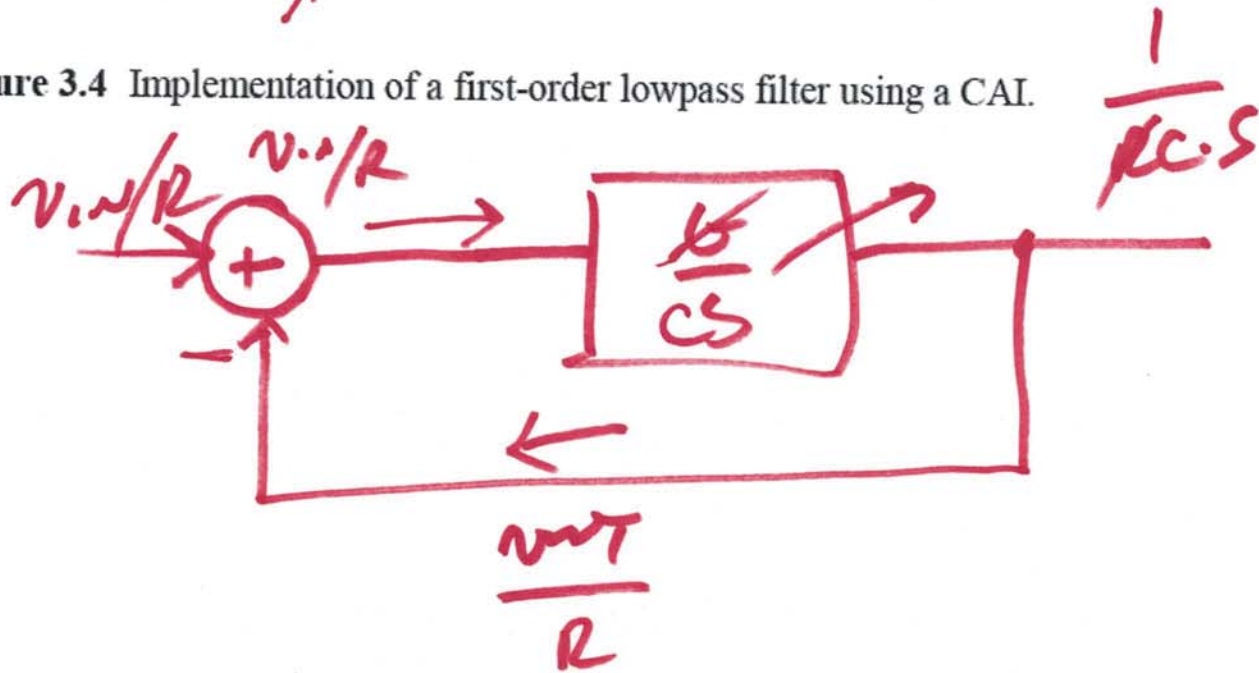


5)

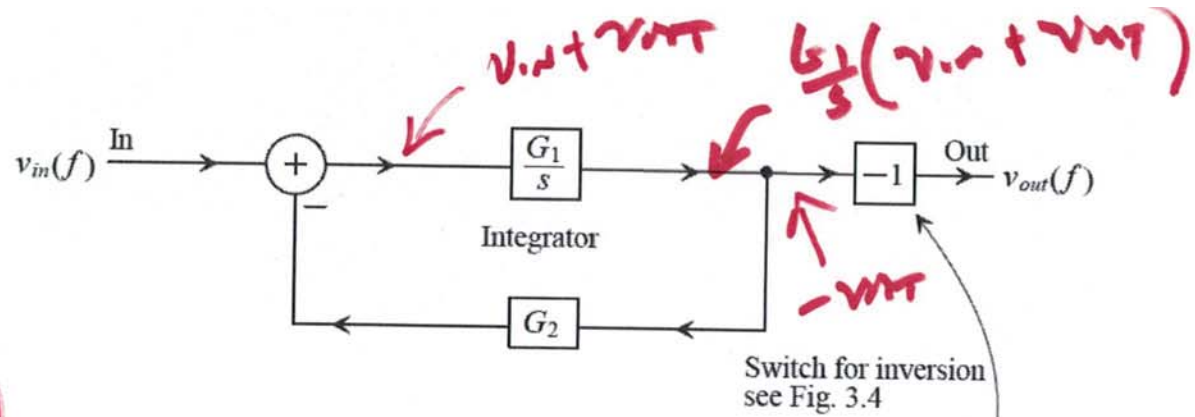

$$\frac{v_{out}}{v_{in}} = \frac{1}{1 + \frac{s}{G_1 \cdot G_2}}$$
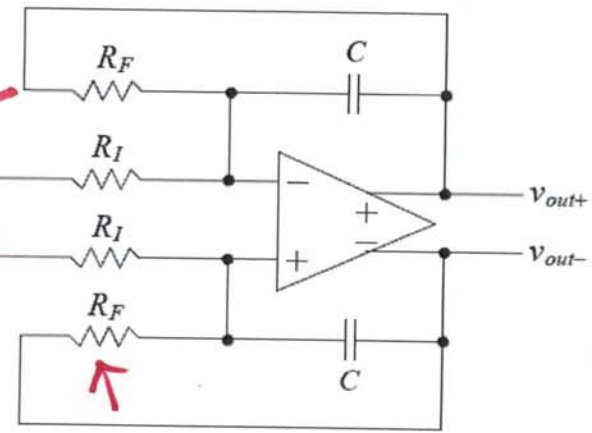
$$= \frac{\frac{R_F}{R_I}}{1 + s R_F C}$$



$$G_1 = \frac{1}{R_I C}$$

$$G_2 = \frac{R_I}{R_F}$$


$$f_{3dB} = \frac{G_1 G_2}{2\pi}$$

Figure 3.6 Integrator-based first-order filter.

$$v_{out} = (-1) \cdot \frac{G_1}{s} (v_{in} + G_2 \cdot (+v_{out}))$$

$$v_{out} \left(1 + \frac{G_1 G_2}{s} \cdot v_{out} \right) = \frac{G_1}{s} \cdot v_{in}$$

6)

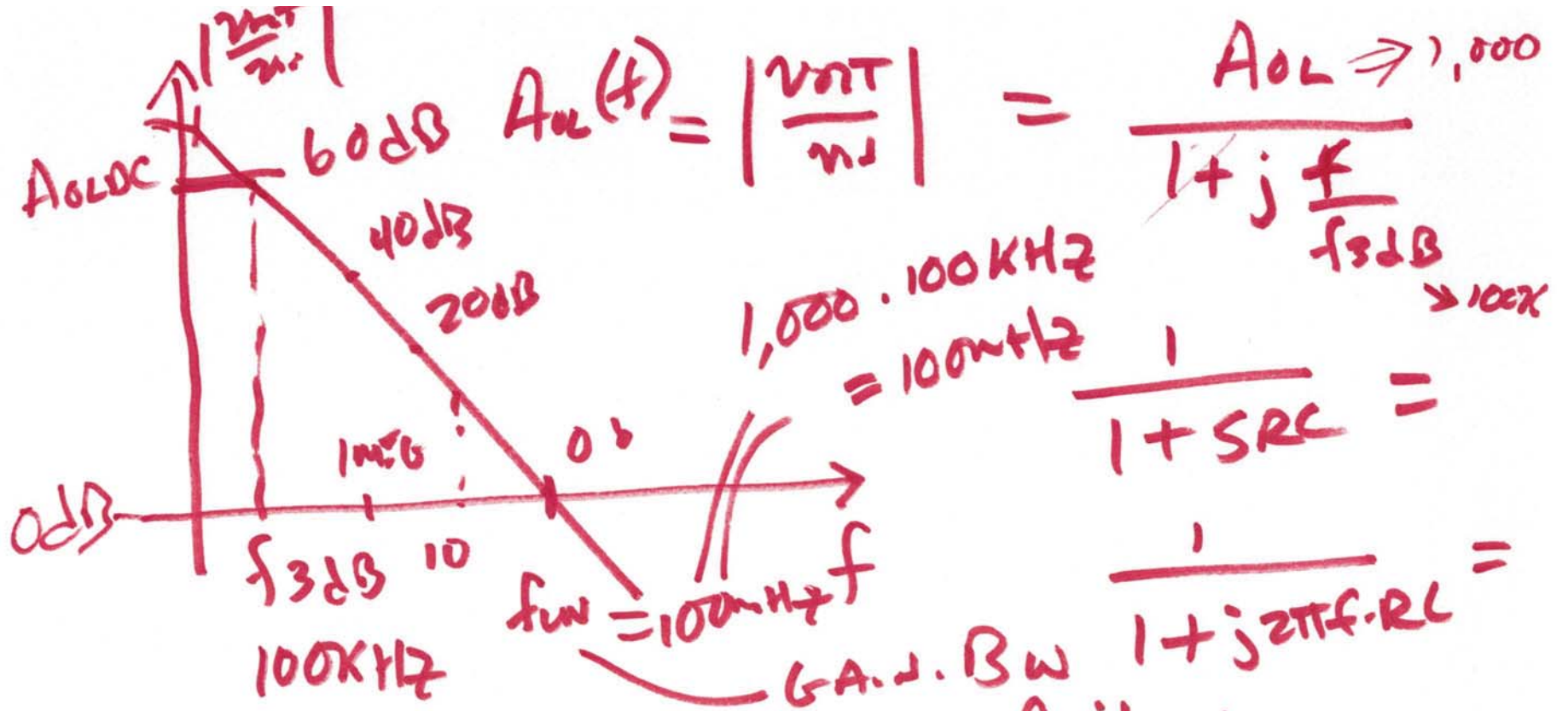

$$A_{OL}(f) \approx \frac{A_{OLDC}}{j \cdot \frac{f}{f_{3dB}}}, \quad f \gg f_{3dB}$$

$$\approx \frac{A_{OLDC} f_{3dB}}{j \cdot f} = \frac{f_{unity}}{j \cdot f}$$

$$\frac{1}{1 + sRC} = \frac{1}{1 + j 2\pi f \cdot RC} = \frac{1}{1 + j \frac{f}{f_{3dB}}}$$

$$f_{3dB} = \frac{1}{2\pi RC}$$



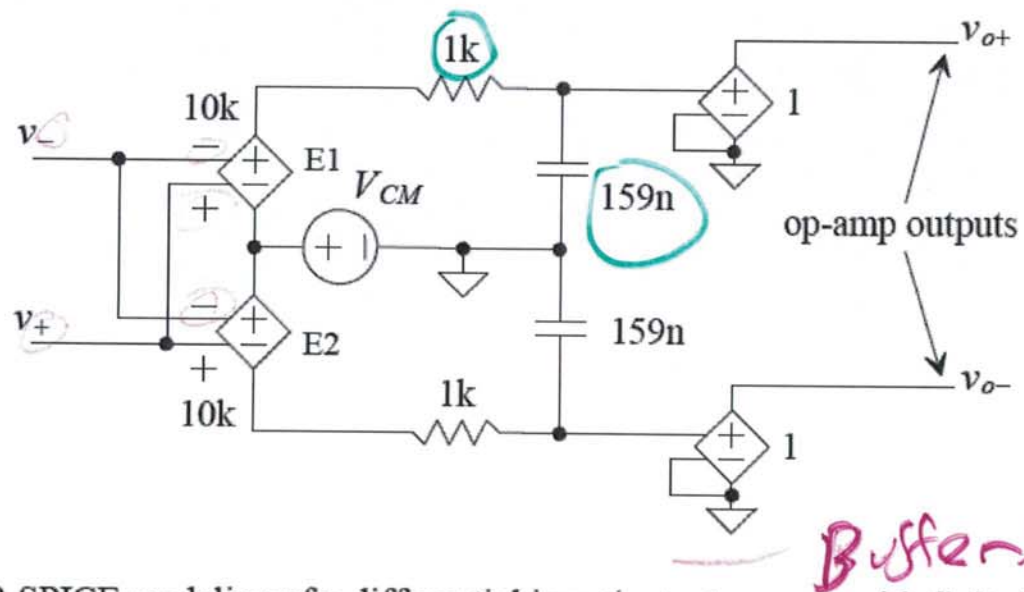


Figure 3.8 SPICE modeling of a differential input/output op-amp with finite bandwidth.

87


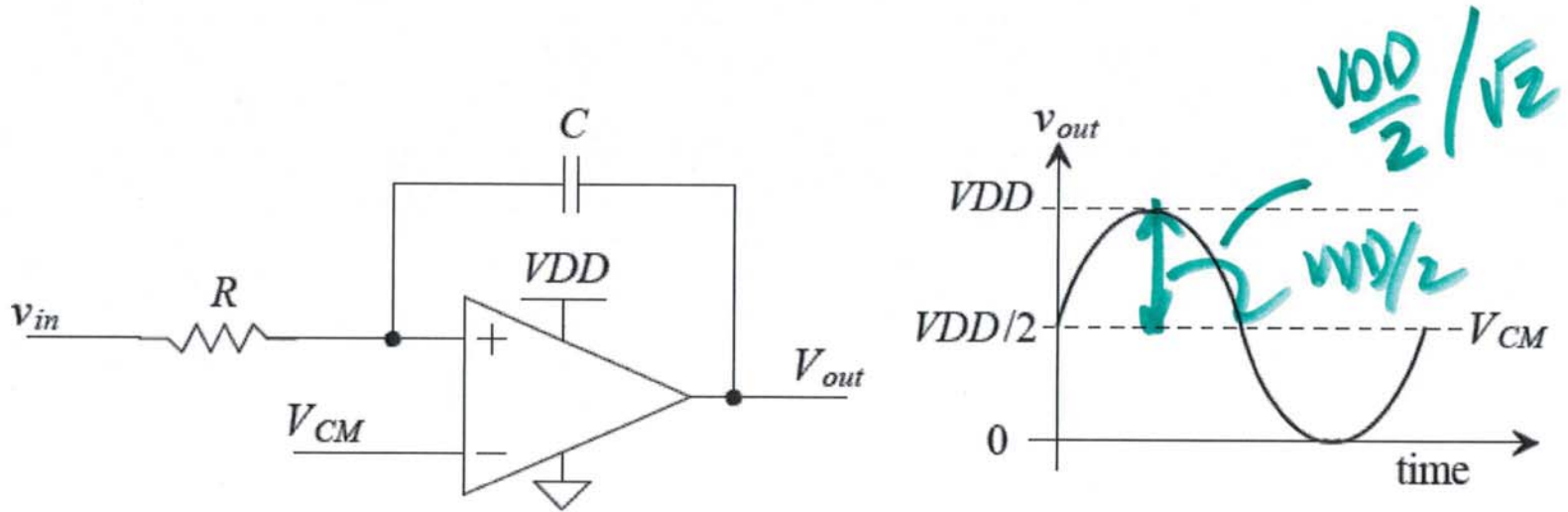


Figure 3.11 Estimating maximum possible SNR of an active-RC filter.

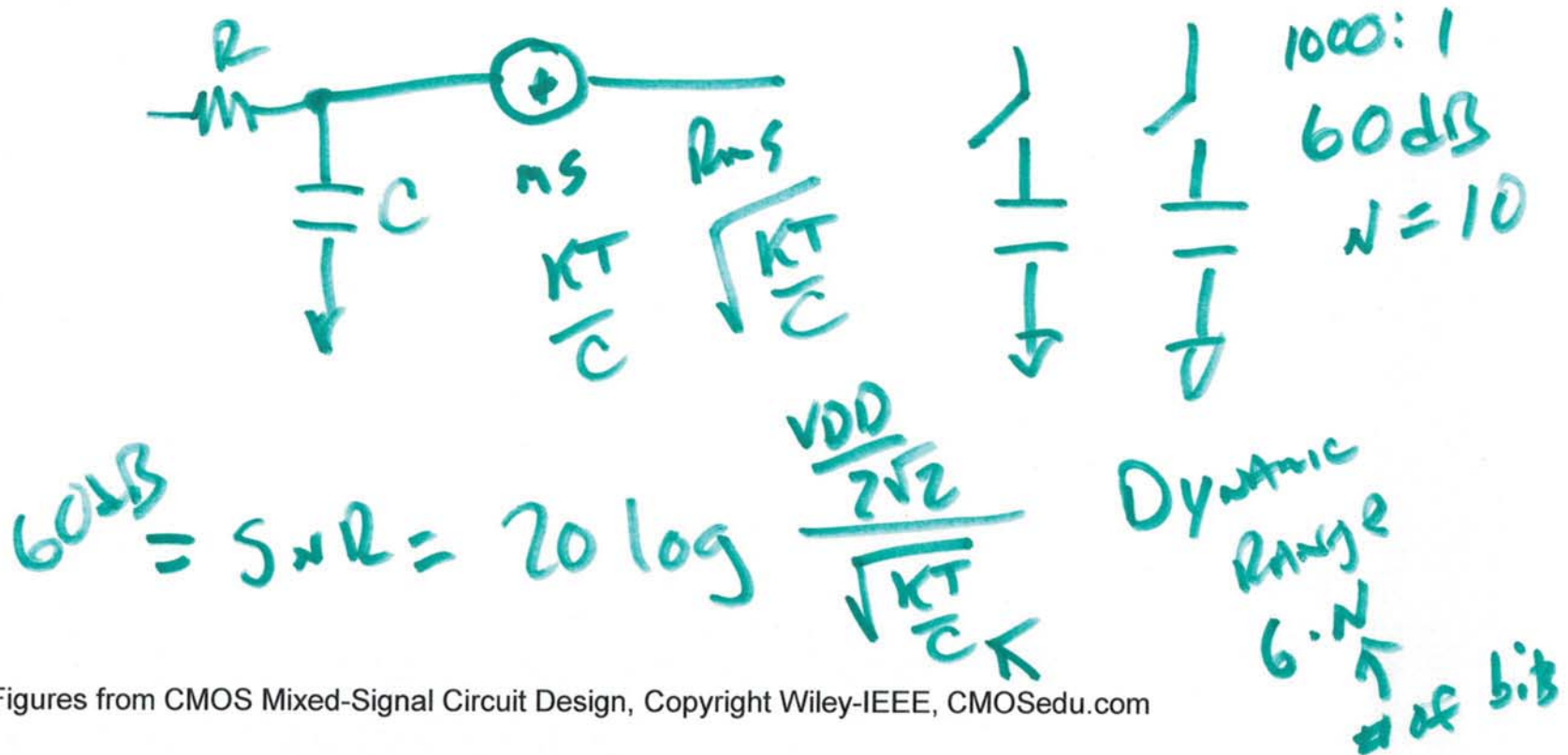

9)