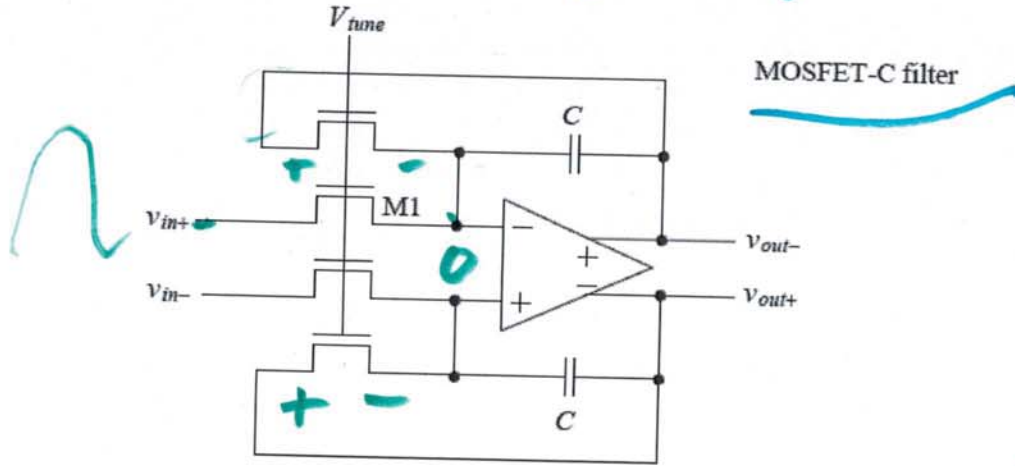


Integrator building blocks

JAN. 21, 2016

RC-integrator



MOSFET-C filter


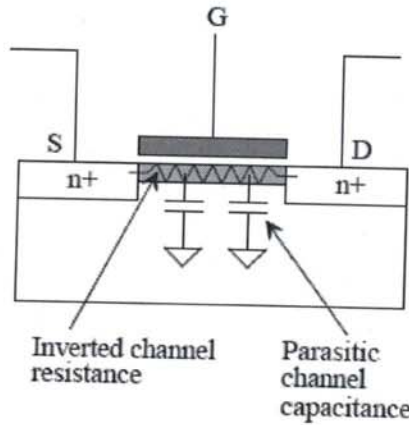
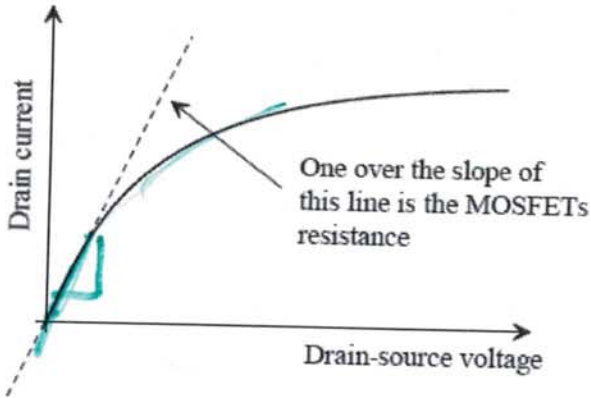
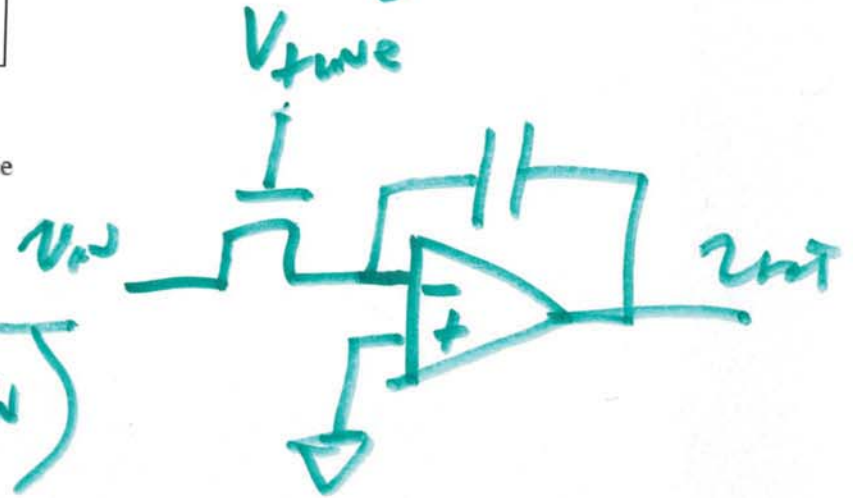


Figure 3.12 A first-order MOSFET-C filter.
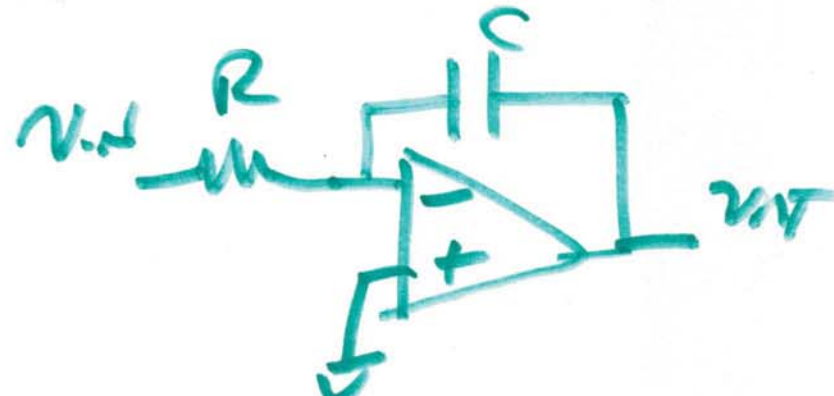
$$R_{ch} = \frac{1}{k_p \frac{W}{L} (V_{TUNE} - V_{THN} - v_{in})}$$



$$R_{CH} = \frac{1}{K_P \cdot \frac{W}{L} (V_{TUNE+} - V_{TUN-} - V_{in})}$$


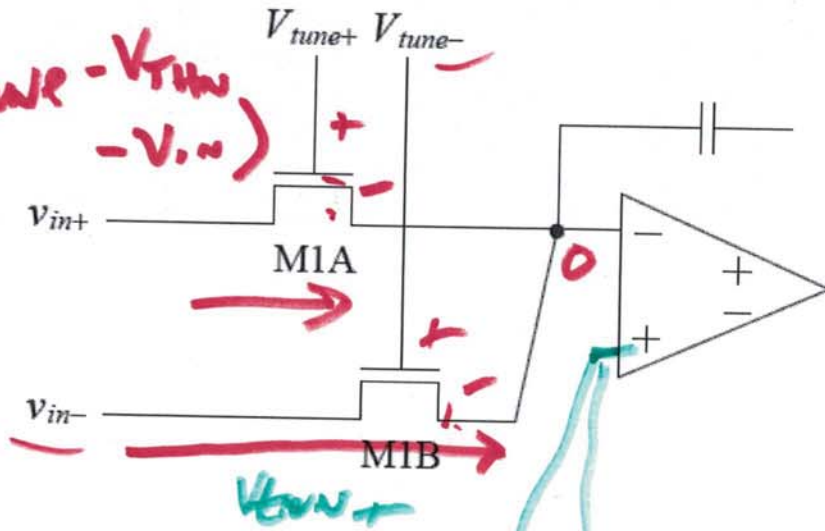


Figure 3.13 Linearizing MOSFET resistors.

$$\frac{.62 V_{TUN+}}{\frac{1}{2} \cdot \frac{1}{2}} = \frac{.62 V_{TUN+}}{.25}$$
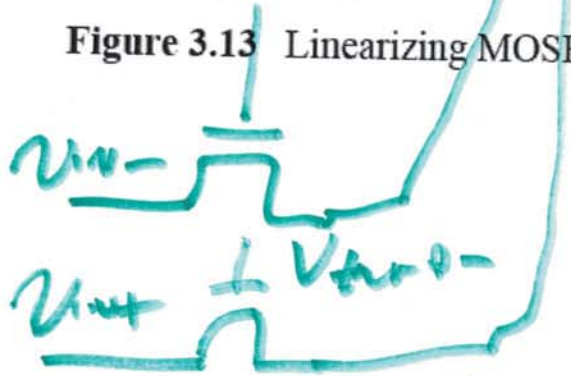
$$V_{in+} = -V_{in} - V_{TUNE+} = V_{TUNE-}$$



$$\frac{V_{out+}}{R_{N1}} = K_P \cdot \frac{W}{L} \cdot V_{TUNE}$$

$$= \frac{V_{out+}}{R_{CH}} + \frac{V_{out-}}{R_{CH}} = V_{in+} \left(K_P \cdot \frac{W}{L} (V_{TUNE+} - V_{TUN-} - V_{in+}) \right) - V_{in-} \left(K_P \cdot \frac{W}{L} (V_{TUNE+} - V_{TUN-} + V_{in-}) \right)$$

2)



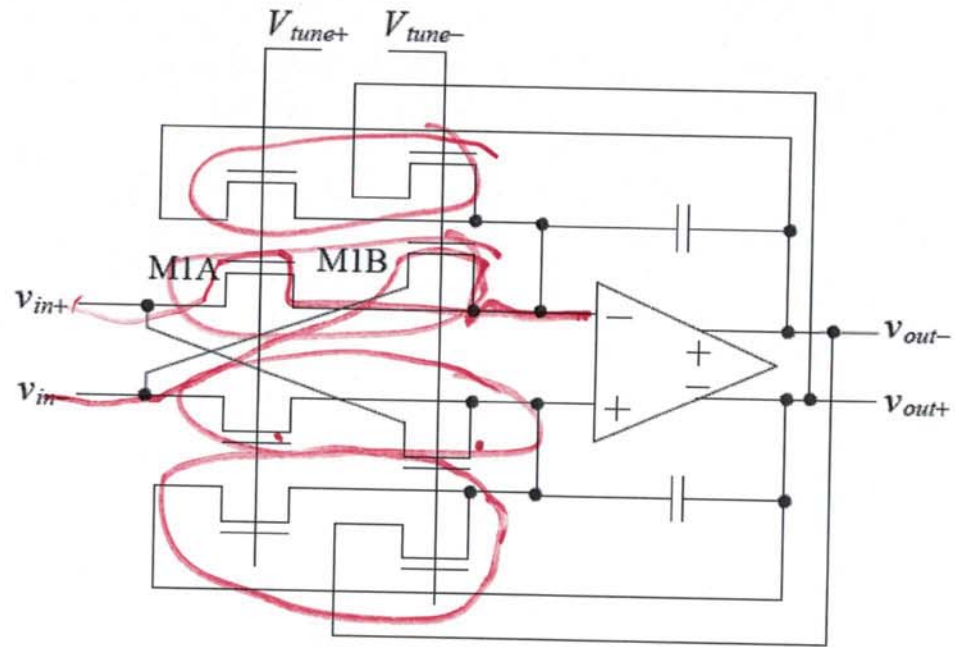


Figure 3.14 First-order MOSFET-C filter using linearized MOSFET resistors.


3)

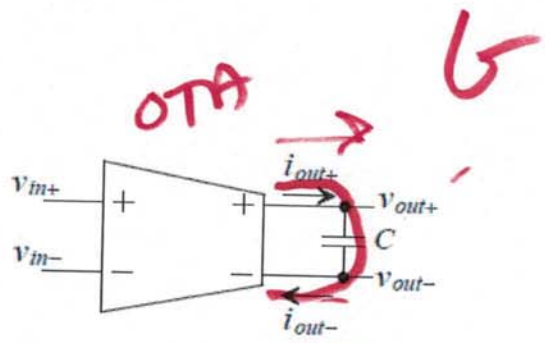

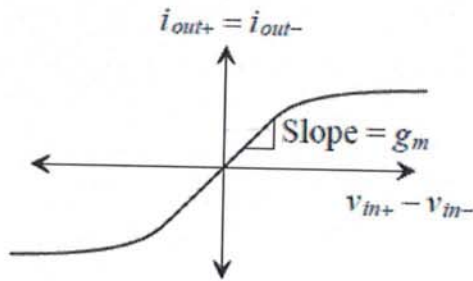(a) Schematic symbol of an OTA or transconductor.



(b) Transfer curves for an OTA.

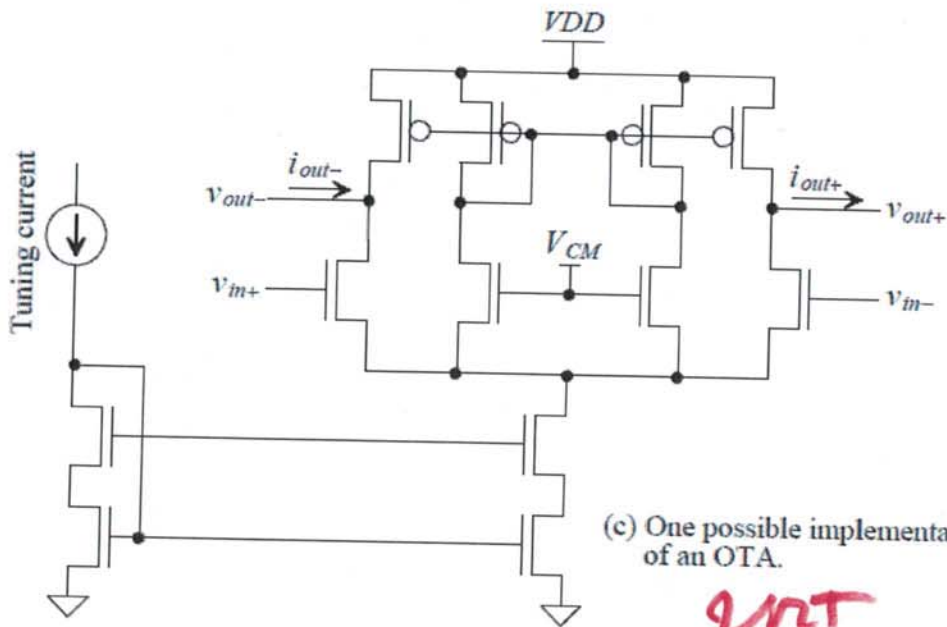

(c) One possible implementation of an OTA.

Figure 3.15 Showing an implementation of an OTA and transfer curves.

$g_m - C$
OTA - C

$$V_{out+} = i_{out+} \cdot \frac{1}{j\omega C}$$

$$+ V_{out-}$$

$$V_{out+} - V_{out-} = \frac{i_{out+}}{j\omega C}$$

$$i_{out+} = g_m \cdot (V_{in+} - V_{in-})$$

$$\frac{v_{out}}{v_{in}} = \frac{v_{out+} - v_{out-}}{v_{in+} - v_{in-}} = \frac{g_m}{j\omega C}$$

$$= \frac{1}{\frac{1}{g_m} \cdot C \cdot j\omega}$$

$$G = \frac{1}{RC}$$

1)


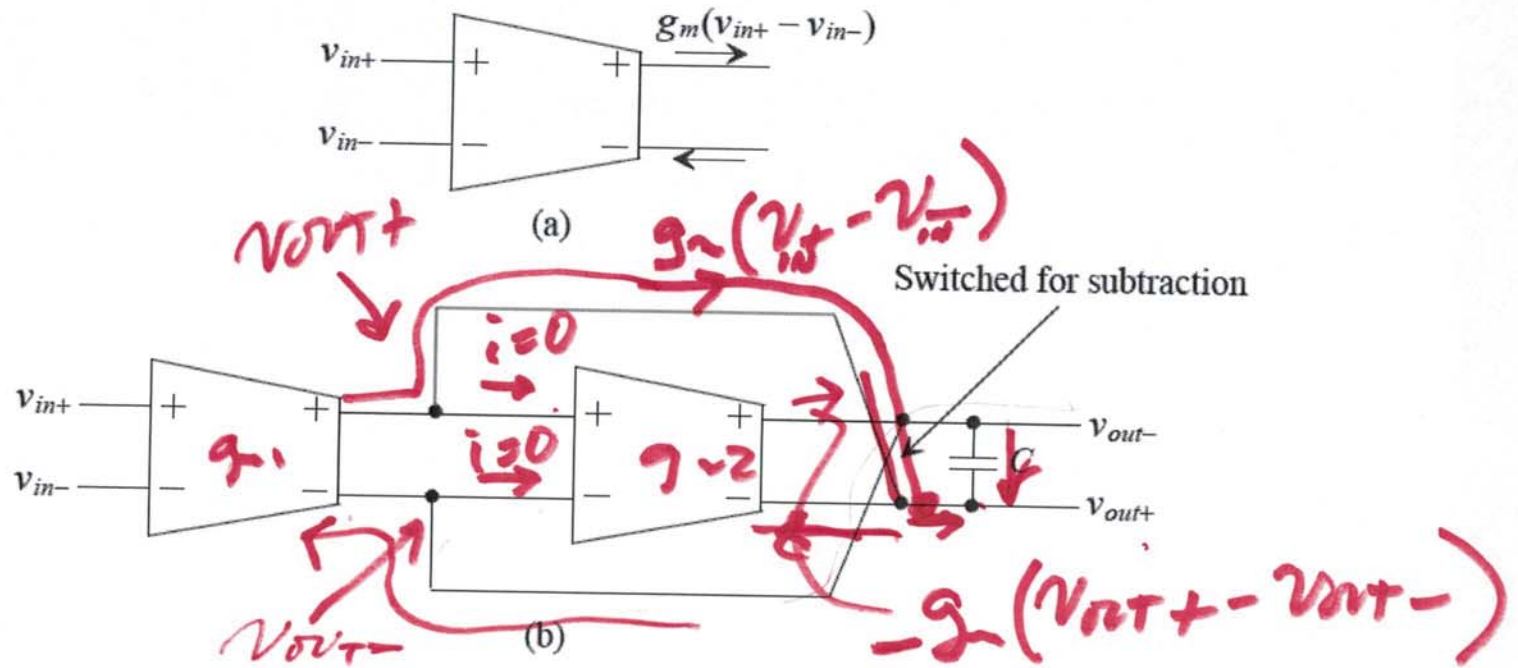
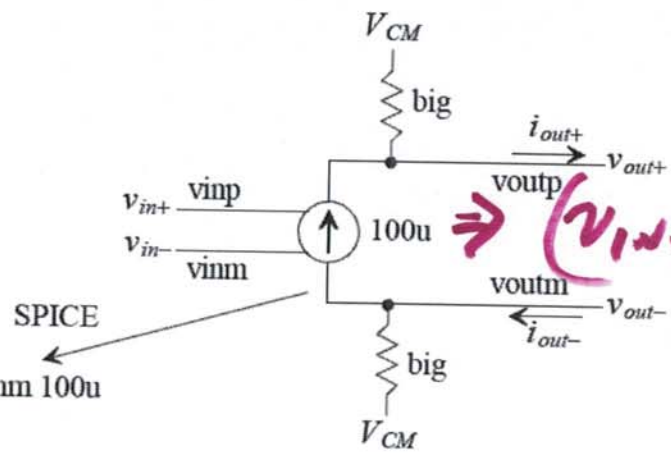


Figure 3.16 Implementing a first-order filter using transconductors.
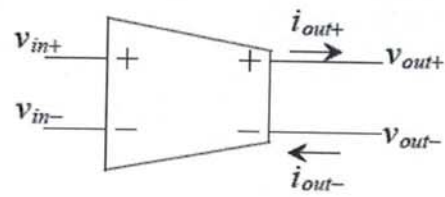
$$\begin{aligned}
 0 &= g_2(v_{in+} - v_{in-}) - g_2(v_{out+} - v_{out-}) + \frac{(v_{out-} - v_{out+})}{\frac{1}{j\omega C}} \\
 &= g_2(v_{in+} - v_{in-}) - (v_{out+} - v_{out-})(g_2 + j\omega C) \\
 \frac{v_{out+} - v_{out-}}{v_{in+} - v_{in-}} &= \frac{g_2}{g_2 + j\omega C} = \frac{1}{1 + j\omega C \cdot \frac{1}{g_2}}
 \end{aligned}$$




G1 voutm voutp vinp vinm 100u

Notice how SPICE defines positive current flow as current flowing from the + terminal to the - terminal

Figure 3.17 Modeling an ideal transconductor in SPICE using a voltage-controlled current source.

$\Rightarrow (v_{in+} - v_{in-}) 100\mu$
 \downarrow
 g_m
 $\frac{1}{R} = 10K$

6)

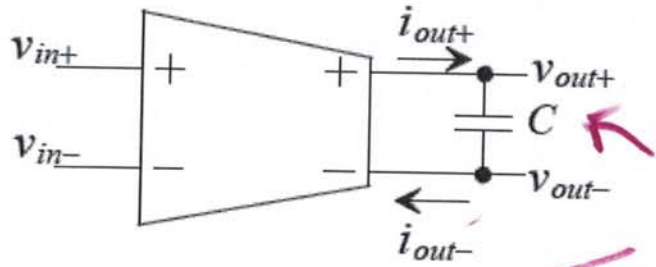

$$v_{nt+} - v_{nt-} = \frac{1}{j\omega C} \cdot i_{out+}$$

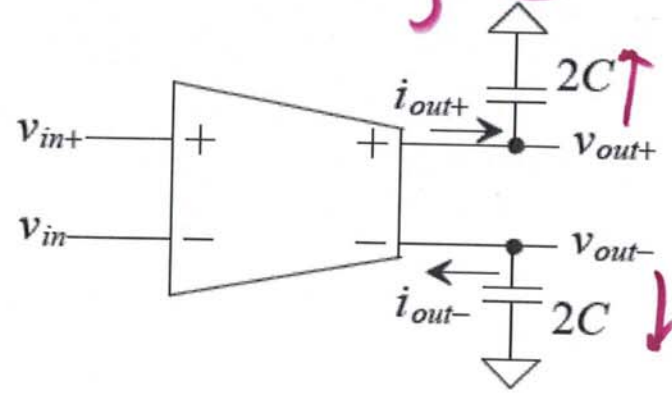


Figure 3.19 Showing how we break the capacitor up to provide a load for the CMFB circuit.

$$i_{out+} = (v_{out+} - v_{out-}) \cdot \frac{1}{j\omega C} \Rightarrow v_{out+} - v_{out-} = j\omega C \cdot i_{out+}$$

$$i_{out+} = \frac{v_{out+}}{1/j\omega 2C}$$

$$i_{out-} = \frac{v_{out-}}{1/j\omega 2C} = i_{out+}$$

$$v_{out+} - v_{out-} = \frac{2 v_{out+}}{j\omega 2C}$$

$$-v_{out-} = \frac{i_{out+}}{j\omega 2C}$$

1)

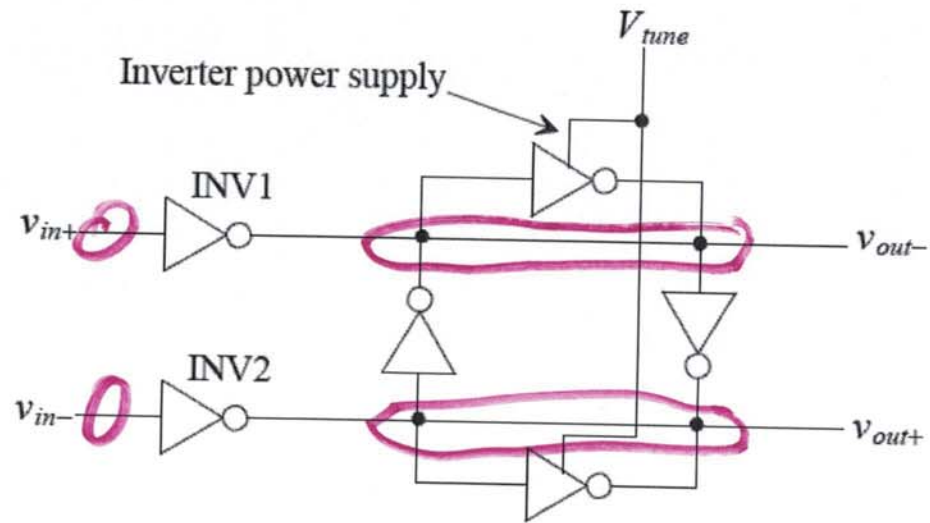


Figure 3.20 High-frequency transconductor.

8)

$$\frac{C_I}{C_F} \frac{z^{-1}}{1 - z^{-1}} = \frac{C_I}{C_F} \frac{1}{z - 1} = \frac{C_I}{C_F} \frac{1}{s \cdot T_{CLK}} = \frac{C_I}{C_F} \cdot f_{CLK} \cdot \frac{1}{s}$$

gain

$$z = e^{j2\pi f \cdot T_{CLK}}$$



$$= 1 + \frac{j2\pi f \cdot T_{CLK}}{s} + \frac{(j2\pi f \cdot T_{CLK})^2}{2!} + \dots$$

$$f \ll \frac{1}{T_{CLK}}$$

$$z \approx 1 + s \cdot T_{CLK}$$

$f \ll f_{CLK}$

9)

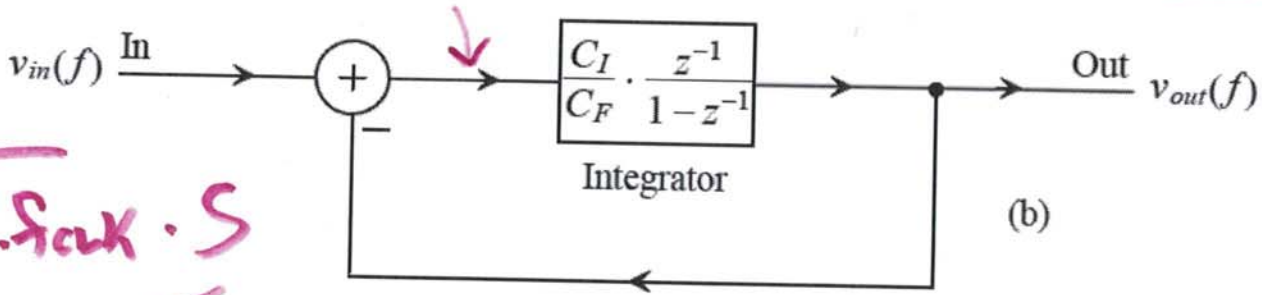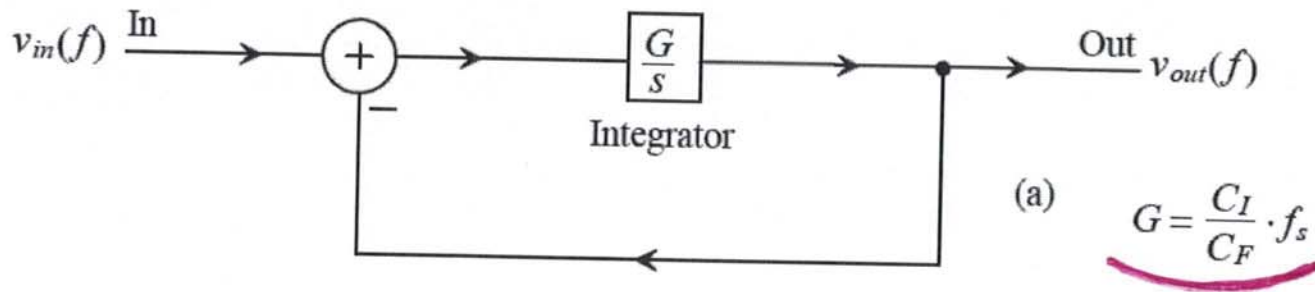

$$\frac{1}{1 + \frac{C_F}{C_I} \cdot f_{cut} \cdot s}$$

Figure 3.21 Block diagram of an integrator-based lowpass filter. (a) Continuous-time and (b) the discrete-time equivalent.

$$(v_{in} - v_{out}) \cdot \frac{C_I}{C_F} \cdot \frac{z^{-1}}{1 - z^{-1}} = v_{out}$$

$$\frac{v_{out}}{v_{in}} = \frac{1}{1 + \frac{C_F(1 - z^{-1})}{C_I \cdot z^{-1}}}$$

$$= v_{out} \left(1 + \frac{C_I}{C_F} \cdot \frac{z^{-1}}{1 - z^{-1}} \right)$$

$$\frac{1}{1 + \frac{C_F}{C_I} \cdot \left(\frac{1 - z^{-1}}{z^{-1}} \right)}$$

$$z z 1 + s \cdot f_{cut}$$

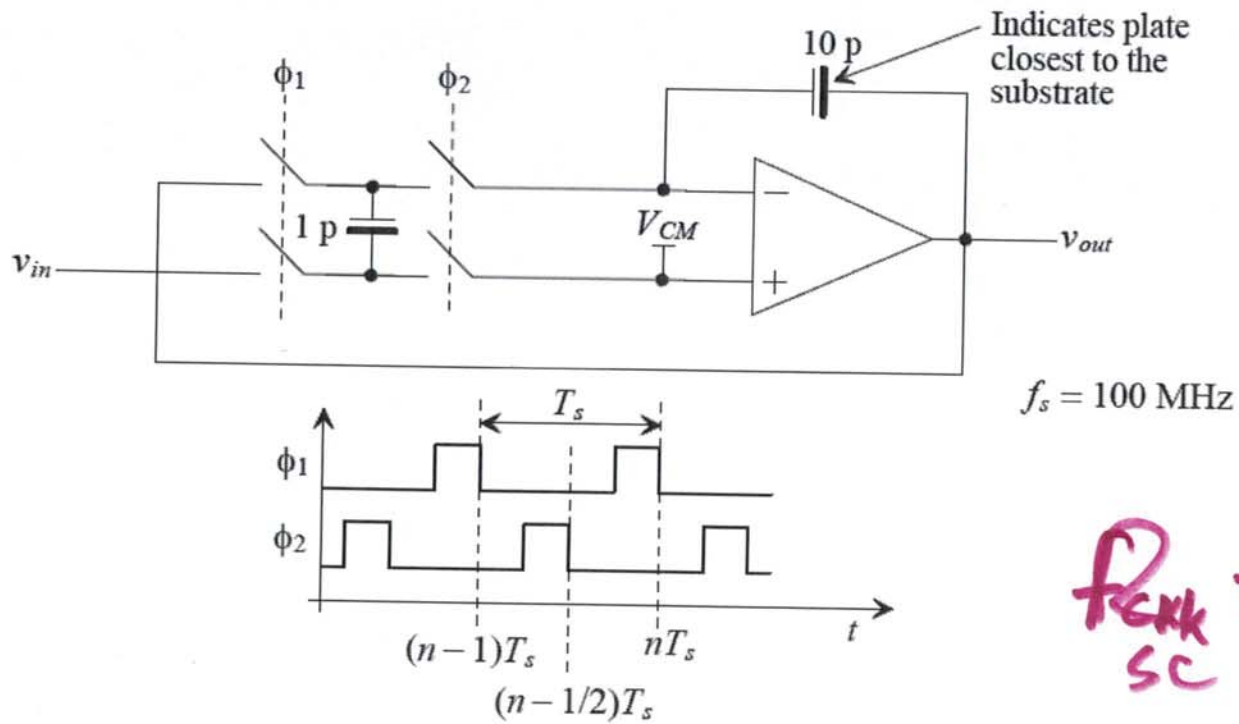


Figure 3.22 A switched capacitor, first-order filter similar to the one described in Ex. 3.1.

$$R_{sc} = \frac{1}{108 \cdot 10^{-12}}$$

$$R_{sc} = 10 \text{ K}$$

$$f_{clk} = 1.59 \text{ MHz}$$

is 100 MHz

→ 1.59 MHz

11)

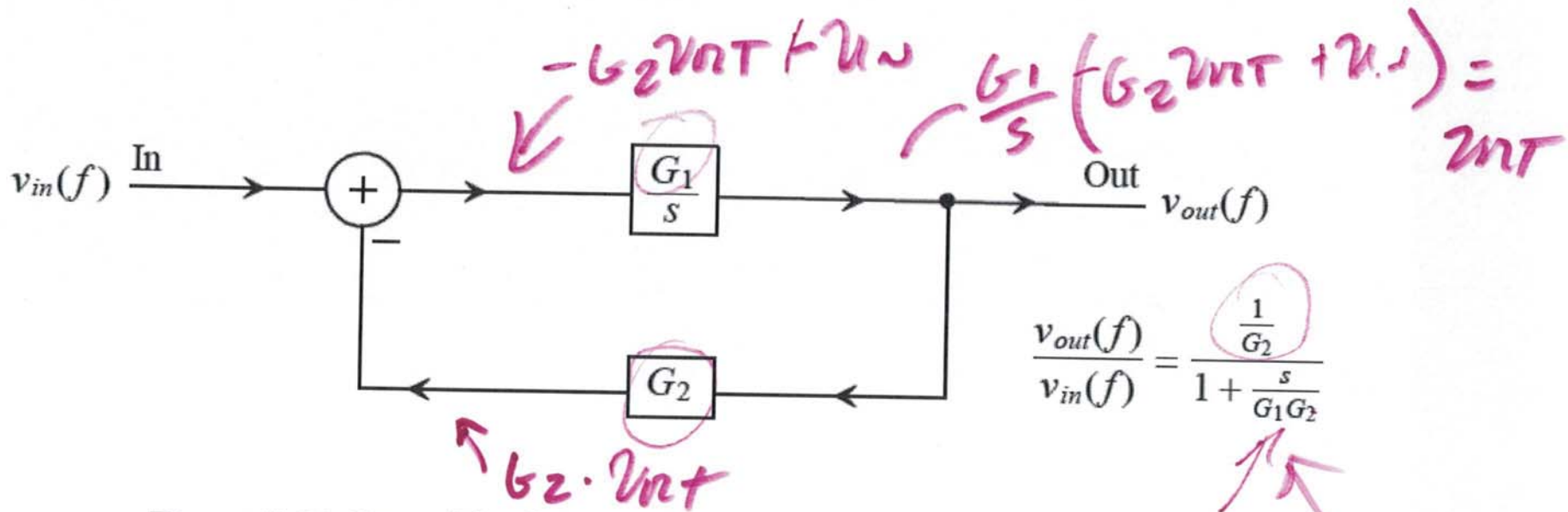


Figure 3.24 General implementation of a lowpass first-order filter.

$$v_{out} \left(1 + \frac{G_1 G_2}{s} \right) = v_{in} \cdot \frac{G_1}{s}$$

$$\frac{v_{out}}{v_{in}} = \frac{\frac{G_1}{s}}{1 + \frac{G_1 G_2}{s}} \cdot \frac{s}{G_1 G_2} = \frac{1}{G_2} \cdot \frac{s}{s + G_1 G_2}$$

(2)

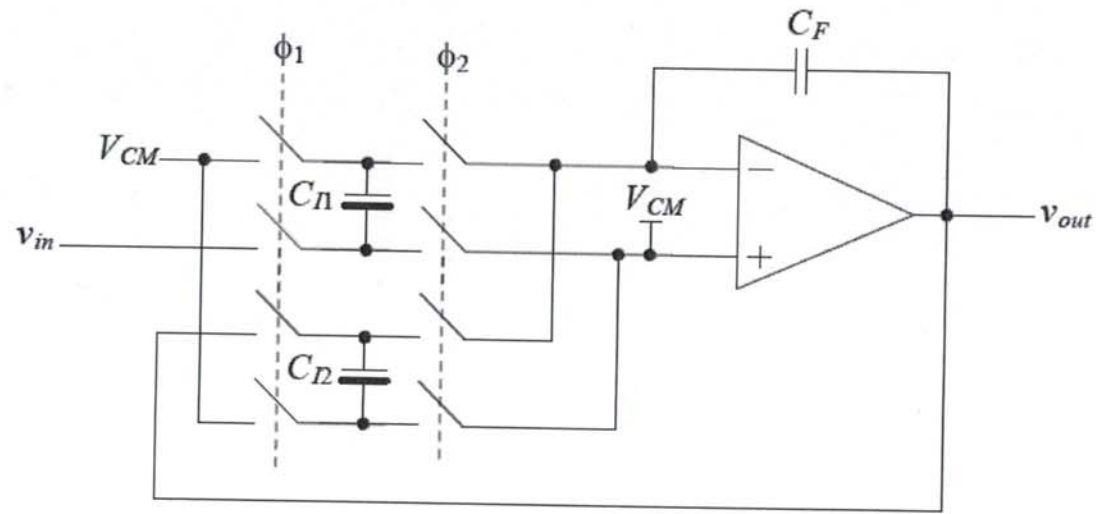


Figure 3.25 Implementation of the block diagram shown in Fig. 3.24.

$$G_1 = \frac{C_{I1}}{C_F} \cdot f_s$$

$$G_2 = \frac{C_{I2}}{C_F} \cdot f_s \cdot \frac{1}{G_1} = \frac{C_{I2}}{C_{I1}}$$

13)

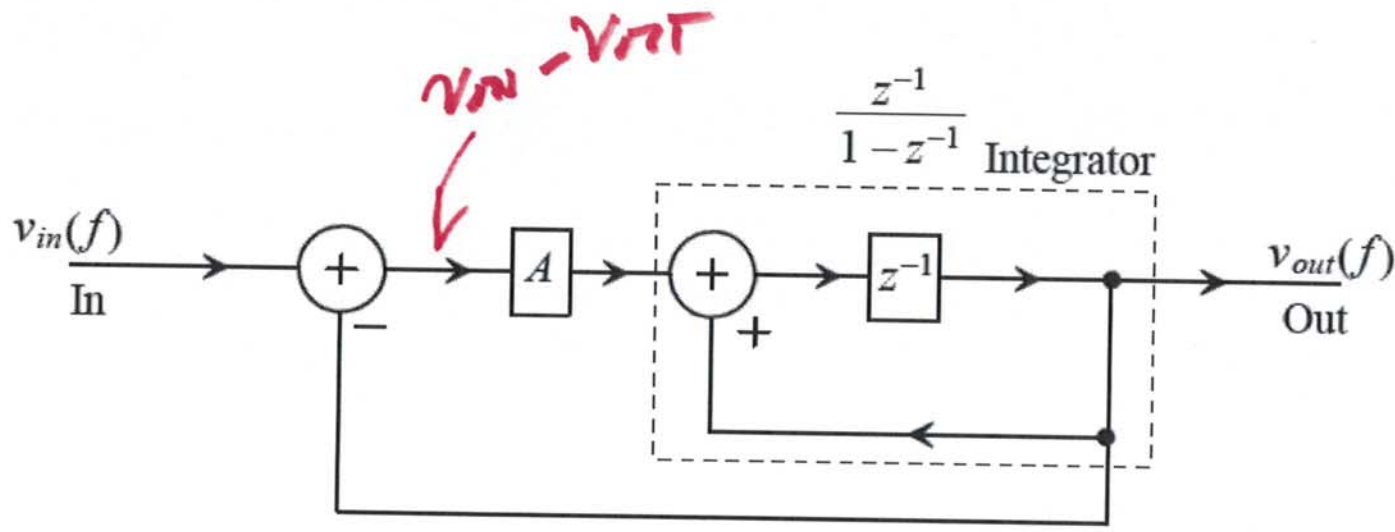


Figure 3.26 Digital block diagram of an integrator-based discrete-time lowpass filter.

$$v_{out} = (v_{in} - v_{out})A \cdot \frac{z^{-1}}{1 - z^{-1}}$$

$$\frac{v_{out}}{v_{in}} = \frac{A}{z - (1 - A)}$$

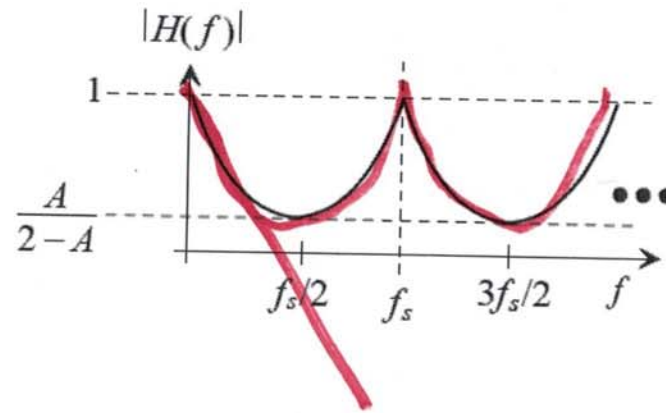
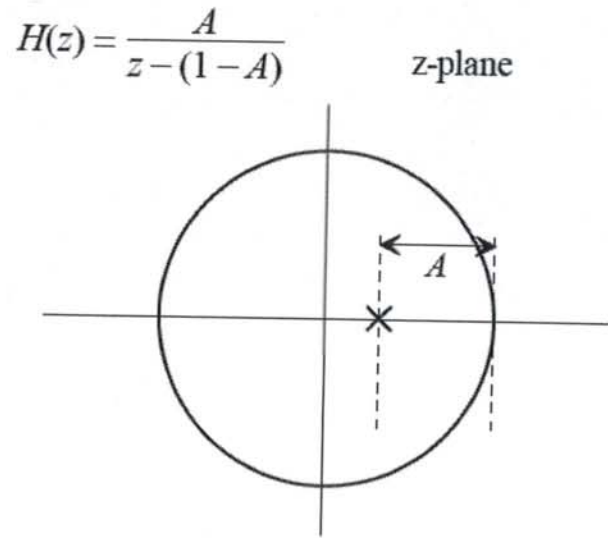


Figure 3.27 The z-plane representation and magnitude response of a first-order discrete-time filter.

15)