

Filtering topologies



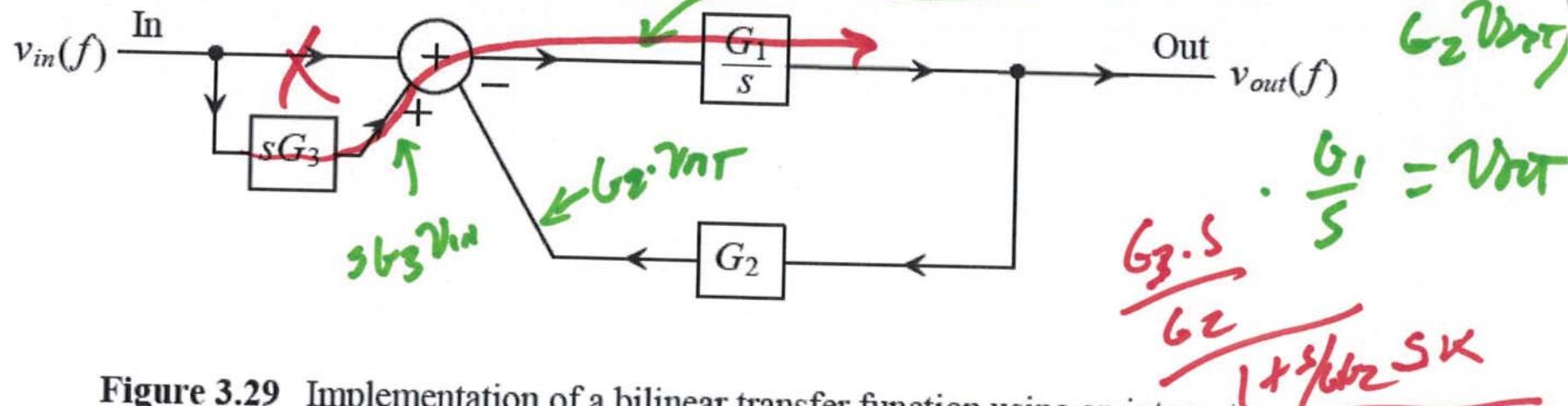


Figure 3.29 Implementation of a bilinear transfer function using an integrator.

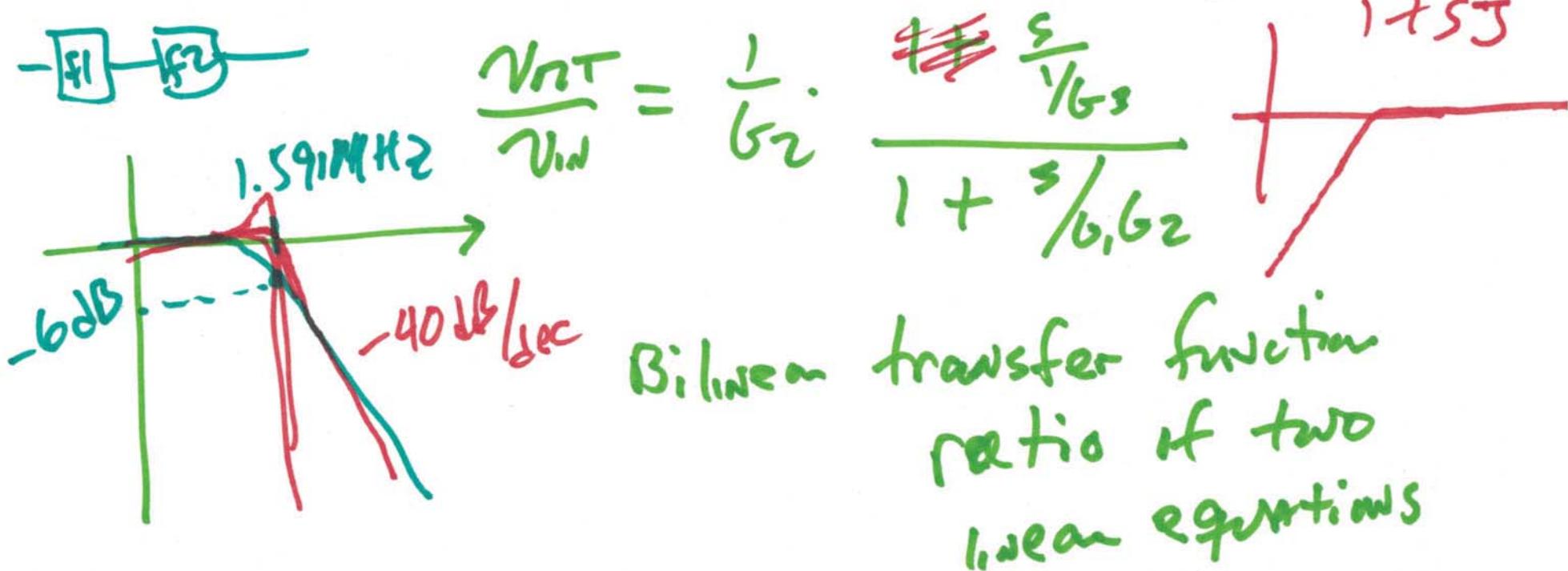

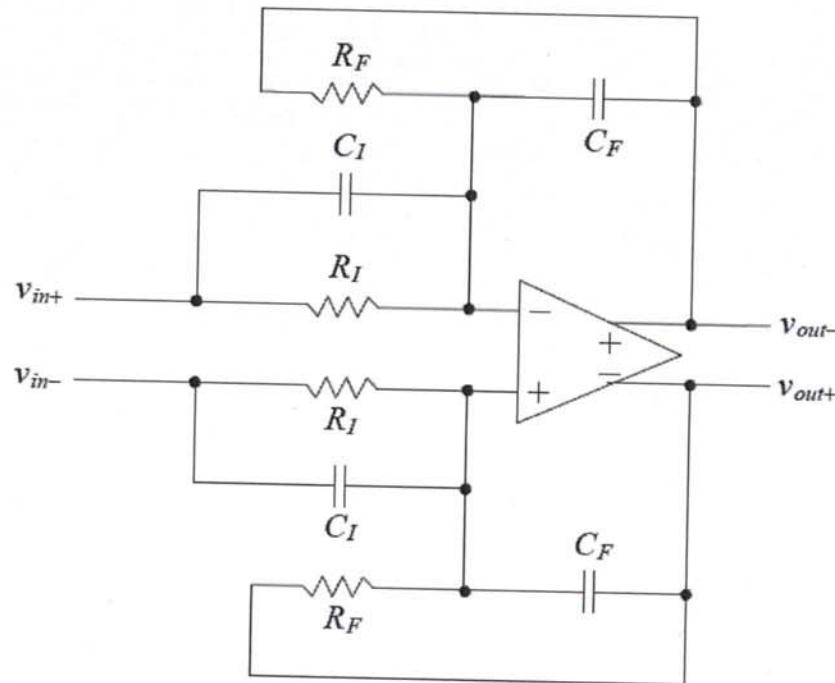

$$\frac{V_{out}}{V_{in}} = \frac{1}{G_2} \cdot \frac{1 + \frac{s}{G_3}}{1 + \frac{s}{G_1 G_2}}$$

$$G_1 = \frac{1}{R_I C_F}$$

$$G_2 = \frac{R_I}{R_F}$$

$$G_3 = R_I C_I$$

$R_I \rightarrow \infty$

$G_1 \rightarrow 0$

$G_2 \rightarrow \infty$

$G_3 \rightarrow \infty$

Figure 3.30 Implementation of an active-RC bilinear transfer function filter.

$$\frac{R_F}{R_I} \cdot \frac{1 + s R_I C_I}{1 + s R_F C_F}$$

$$\xrightarrow{R_I \rightarrow \infty} 1 + s R_F C_F$$

$$\xrightarrow{R_F / R_I} \frac{R_F / R_I + s R_F C_I}{1 + s R_F C_F}$$

$$\xrightarrow{R_F / R_I} \frac{1 + s R_F C_I}{1 + s R_F C_F}$$


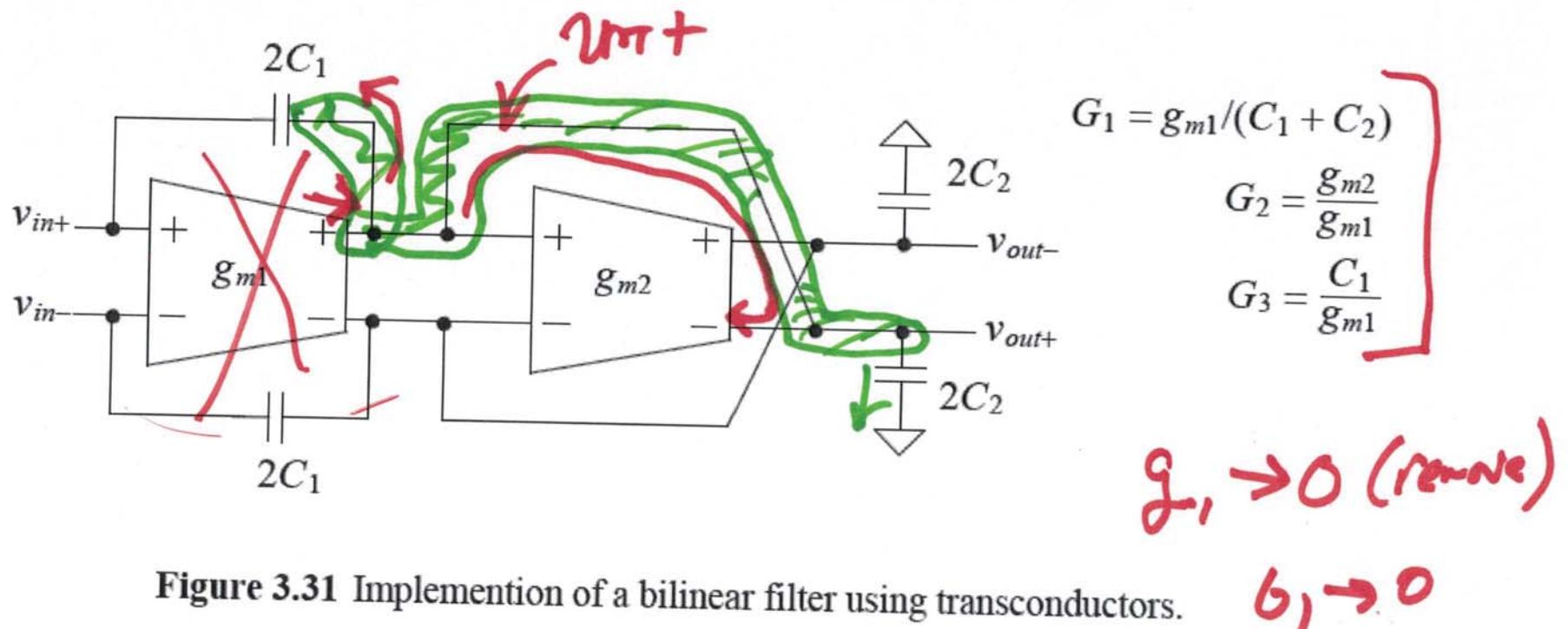


Figure 3.31 Implementation of a bilinear filter using transconductors.

$$\begin{aligned}
 & g_{m1}(\gamma_{n1}) \\
 &= \frac{\gamma_{nT} - \gamma_{n1}}{\gamma j \omega C_1 / 2} + \gamma_{nT} \cdot g_2 + \frac{\gamma_{nT}}{\gamma j \omega 2C_2}
 \end{aligned}$$

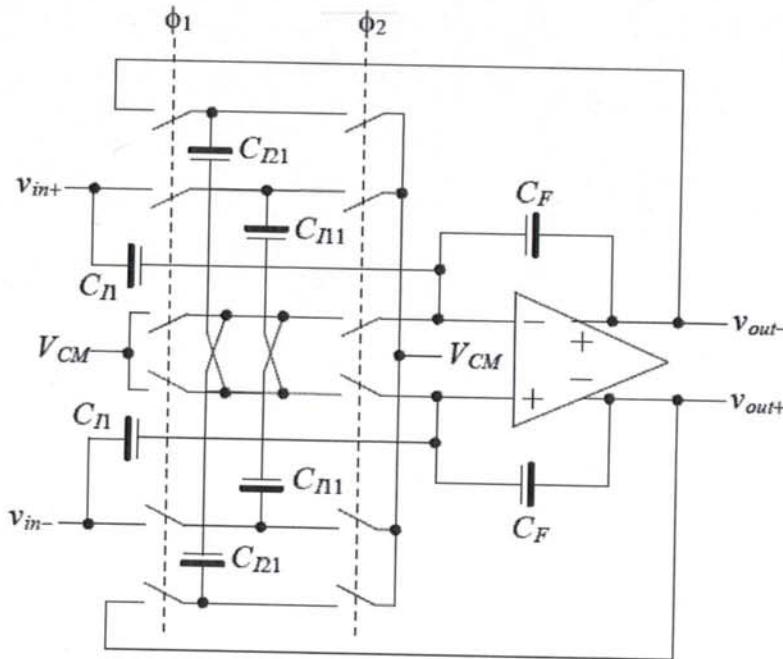$g_1 \rightarrow 0$
 $g_2 \rightarrow 0$
 $g_3 \rightarrow \infty$



$$G_1 = \frac{C_{L1}}{C_F} \cdot f_s$$

$$G_2 = \frac{C_{D1}}{C_{L1}}$$

$$G_3 = \frac{C_L}{C_{L1} \cdot f_s}$$

$$\frac{v_{out}(f)}{v_{in}(f)} = \frac{1}{G_2} \cdot \frac{1 + \frac{s}{1/G_3}}{1 + \frac{s}{G_1 G_2}}$$

Figure 3.32 Implementation of a bilinear filter using switched capacitors.

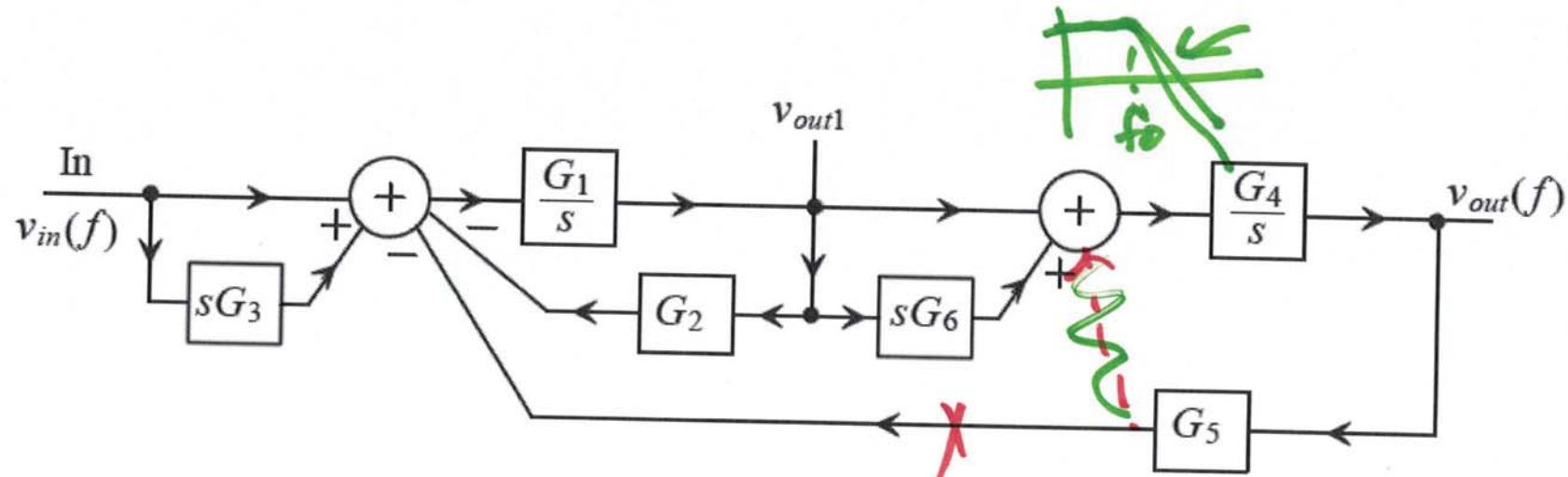


Figure 3.33 Implementation of a biquadratic transfer function using two integrators.

$$\frac{V_{out}}{V_{in}} = \frac{a_2 s^2 + a_1 s + a_0}{s^2 + \left(\frac{2\pi f_0}{Q}\right)s + (2\pi f_0)^2}$$

Bigotry

$$\omega_n = 2\pi f_0$$

Natural


Energy stored

✓ 12

$$900K \xrightarrow{3dB} \text{A} \xrightarrow{3dB} 1.1 \text{MHz} =$$

inverter
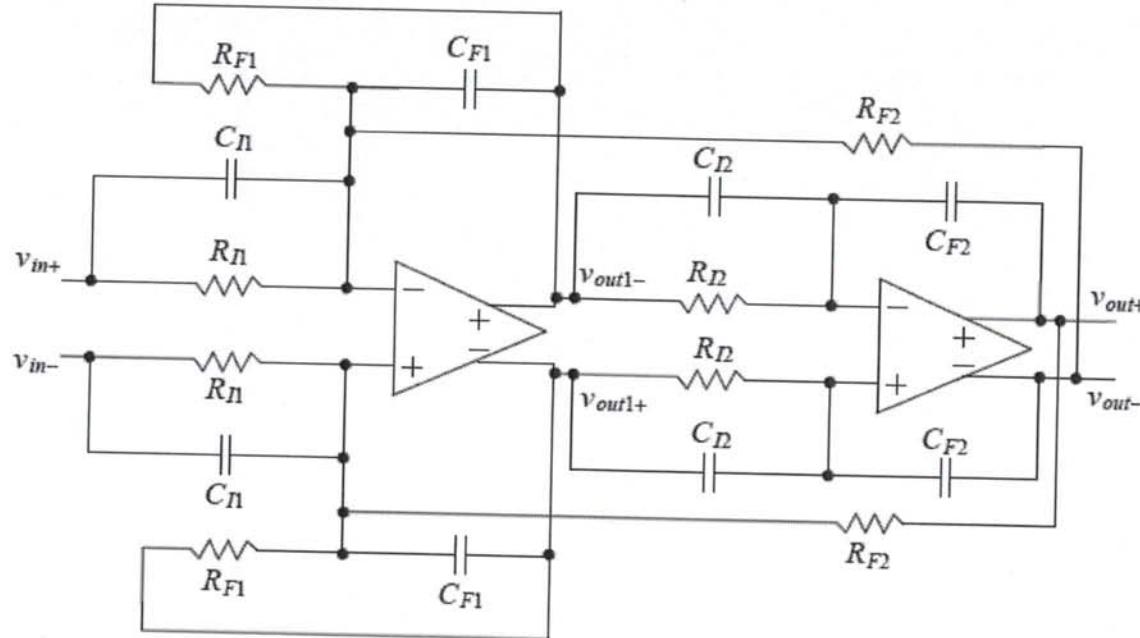
$$\frac{f_0}{B_w} = \frac{1/\mu F}{250K} = 5$$




$$G_1 = \frac{1}{R_n C_{F1}} \quad G_2 = \frac{R_n}{R_{F1}} \quad G_3 = R_n C_n \quad G_4 = \frac{1}{R_D C_{F2}} \quad G_5 = \frac{R_n}{R_{F2}} \quad G_6 = R_D C_D$$

$$a_2 = \frac{C_n C_D}{C_{F1} C_{F2}} \quad a_1 = \frac{C_n}{R_D C_{F1} C_{F2}} + \frac{C_D}{R_n C_{F1} C_{F2}} \quad a_0 = \frac{1}{R_n C_{F1} R_D C_{F2}}$$

$$\frac{\omega_0}{Q} = \frac{2\pi f_0}{Q} = \frac{1}{R_{F1} C_{F1}} + \frac{C_D}{C_{F1} R_{F2} C_{F2}} \quad f_0 = \frac{1}{2\pi} \cdot \sqrt{\frac{1}{C_{F1} R_D C_{F2} R_{F2}}}$$

Figure 3.34 Implementation of the active-RC biquadratic transfer function filter.

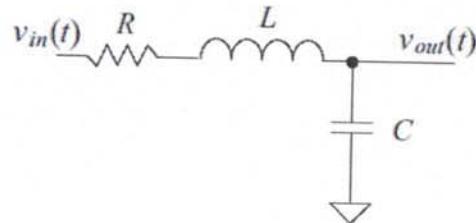

$$\frac{v_{out}}{v_{in}} = \frac{\frac{1}{LC}}{s^2 + s\frac{R}{L} + \frac{1}{LC}}$$

$$f_0 = \frac{1}{2\pi\sqrt{LC}}$$

$$Q = \frac{1}{R}\sqrt{\frac{L}{C}}$$


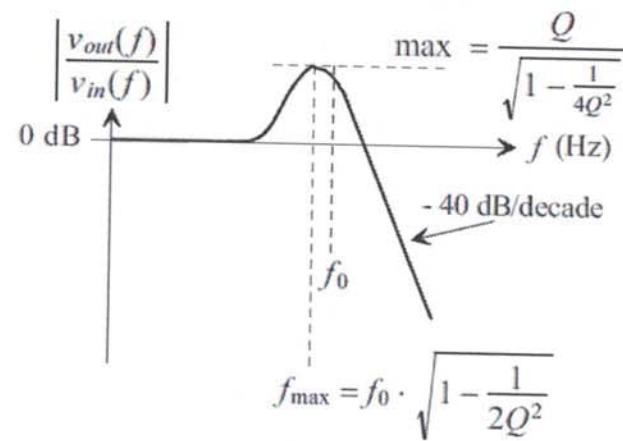


Figure 3.35 Second-order lowpass filter.

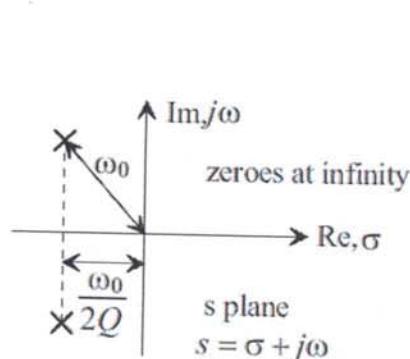

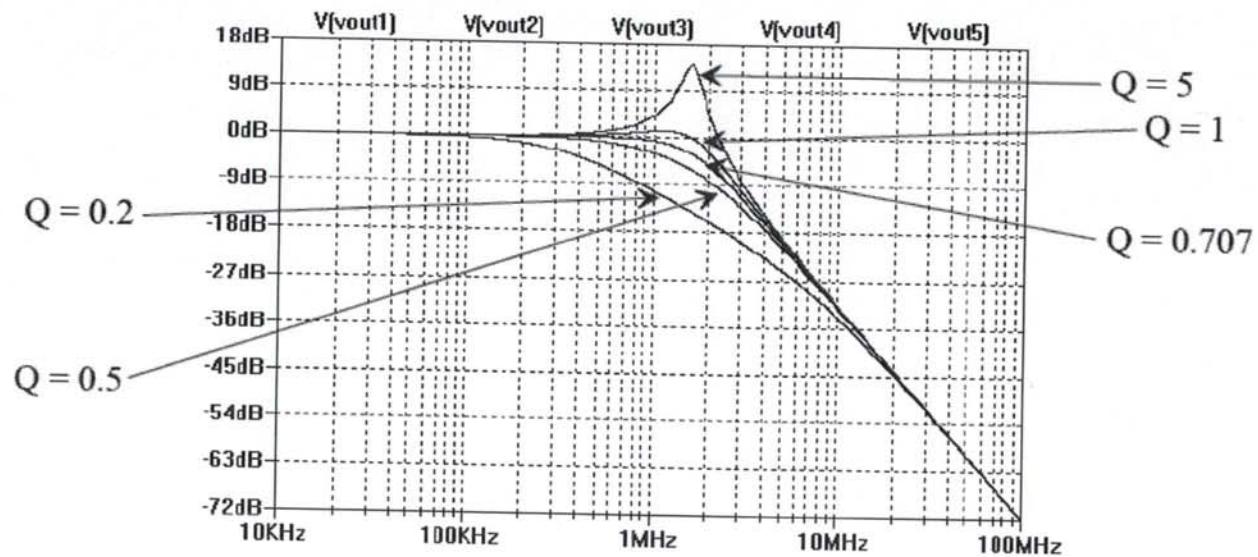


Figure 3.37 The effect of Q on the frequency response of a second-order lowpass filter.

SAW