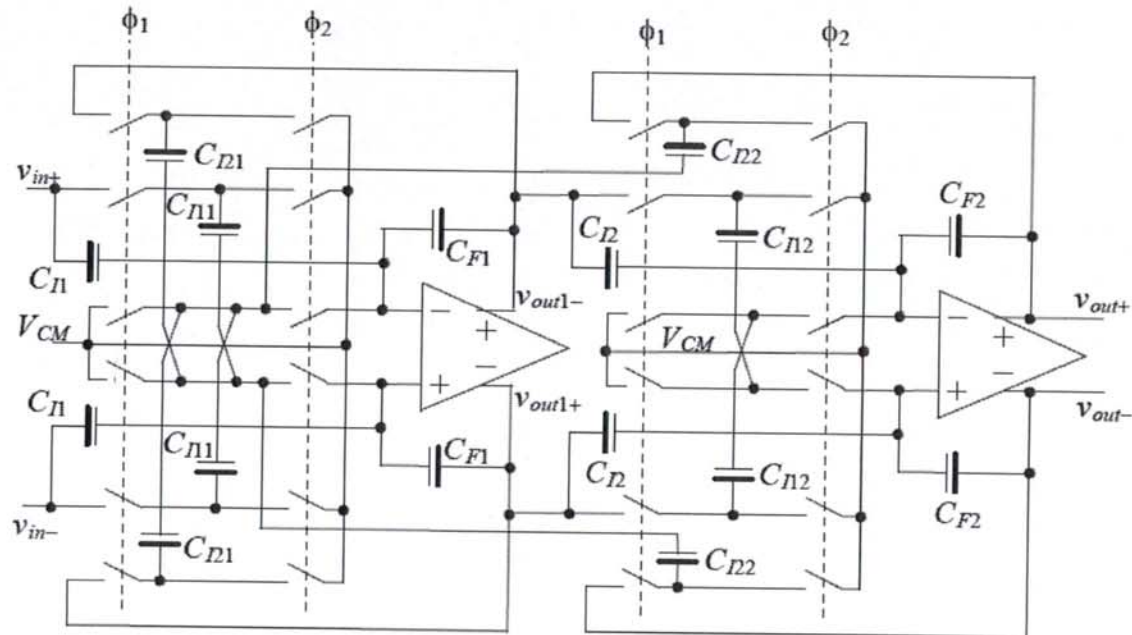


Figure 3.39 Second-order bandpass filter.

S.L.

$$\frac{v_{out}}{v_{in}} = \frac{a_1 s + a_0}{s^2 + \left(\frac{2\pi f_0}{Q}\right) s + (2\pi f_0)^2} = \frac{s b_1 b_3 b_4 + b_1 b_4}{s^2 + b_1 b_2 s + b_1 b_4 b_5}$$



$$G_1 = \frac{C_{N1}}{C_{F1}} \cdot f_s \quad G_2 = \frac{C_{D1}}{C_{N1}} \quad G_3 = \frac{C_N}{C_{N1}} \cdot f_s \quad G_4 = \frac{C_{N2}}{C_{F2}} \cdot f_s \quad G_5 = \frac{C_{D2}}{C_{N1}} \quad G_6 = \frac{C_D}{C_{N2}} \cdot f_s \quad \leftarrow$$

Figure 3.43 Implementing a biquad filter using switched capacitors.

$Hi-Q$ $Q = \frac{\pi f_0}{b_1 b_2}$ 3.77
 $Q \propto R_F$ $R_{sc} = \frac{1}{f_c}$
 $G \propto \frac{1}{R}$

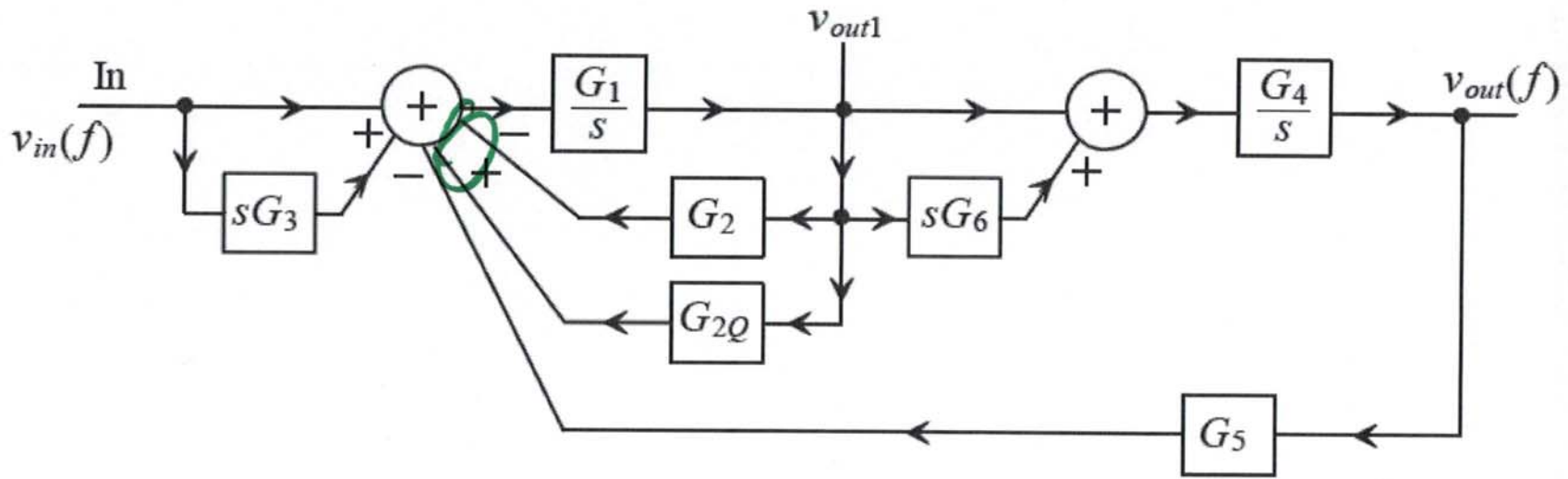


Figure 3.44 Implementation of a "high-Q" biquadratic transfer function.

$$v_{out1} \cdot (G_{2Q} - G_2)$$

3)

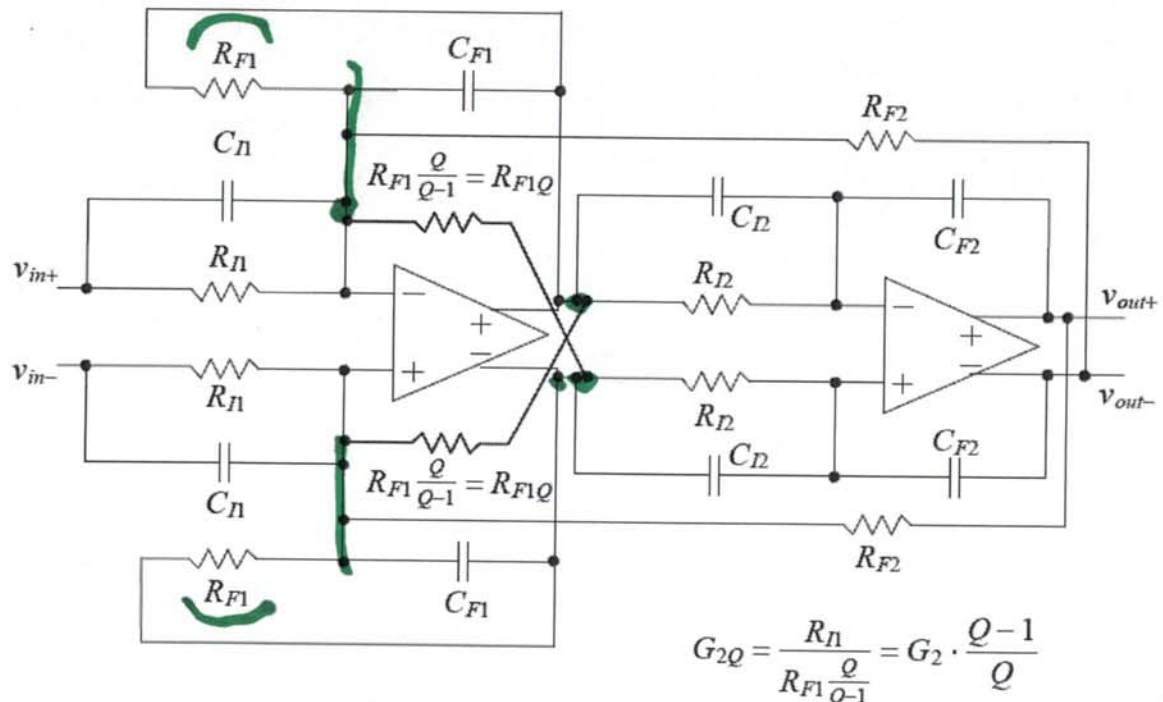


Figure 3.45 Implementation of the "high-Q" active-RC biquadratic transfer function filter. The bold lines indicate the added components.

4)

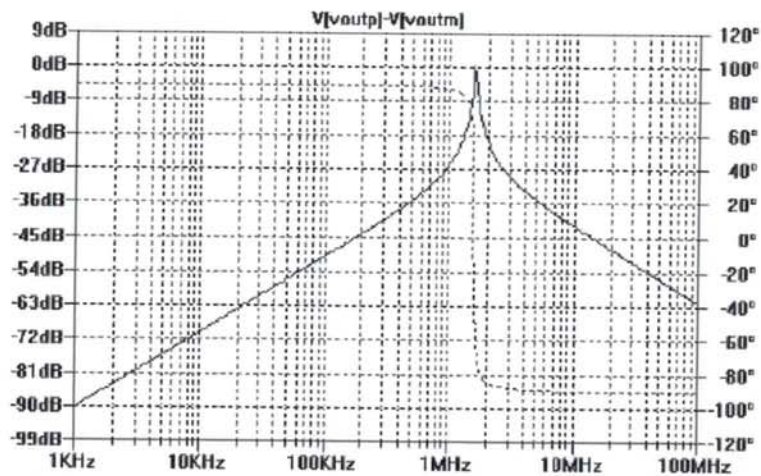
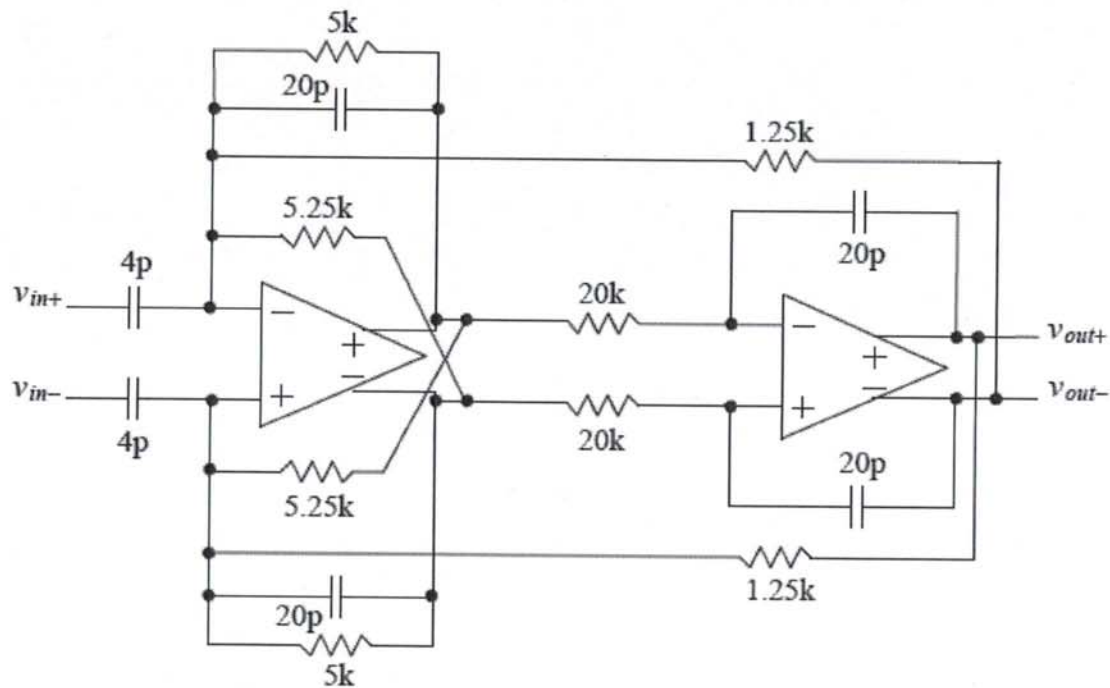


Figure 3.46 Bandpass filter discussed in Ex. 3.13.

5)


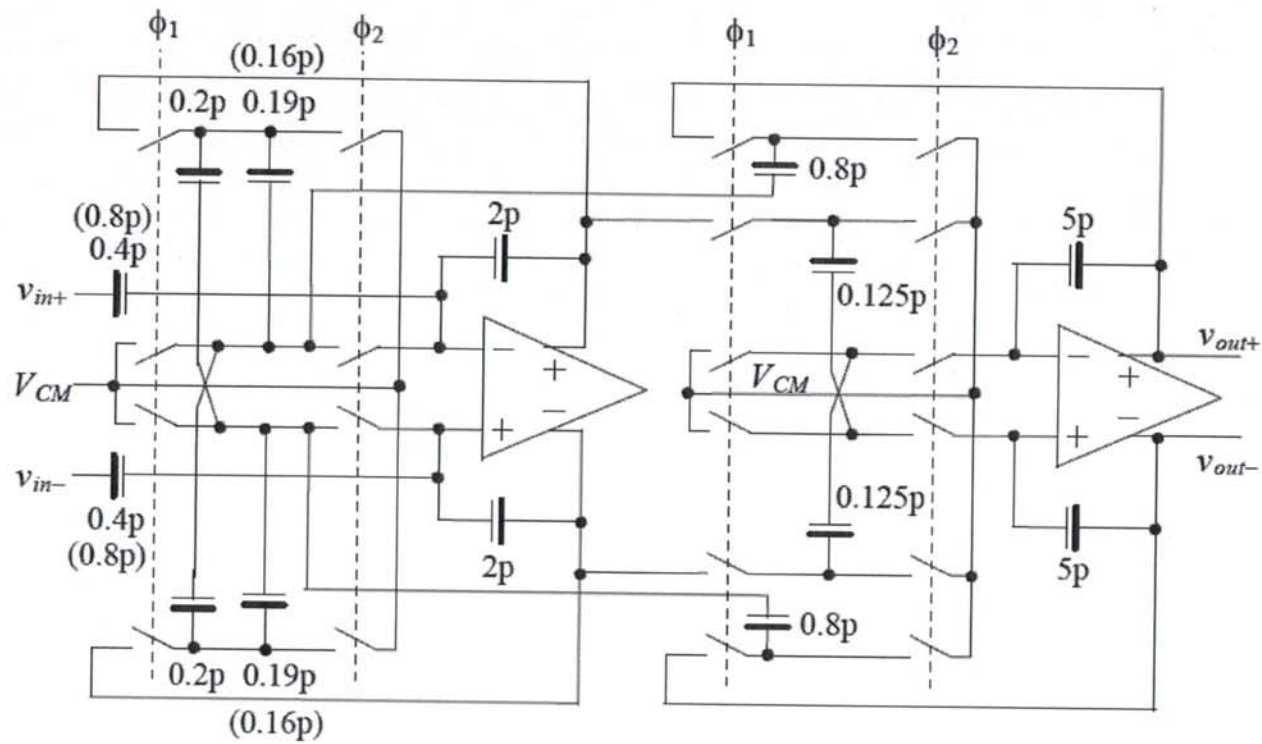


Figure 3.47 Switched-capacitor implementation of a high-Q filter; see Ex. 35.14.

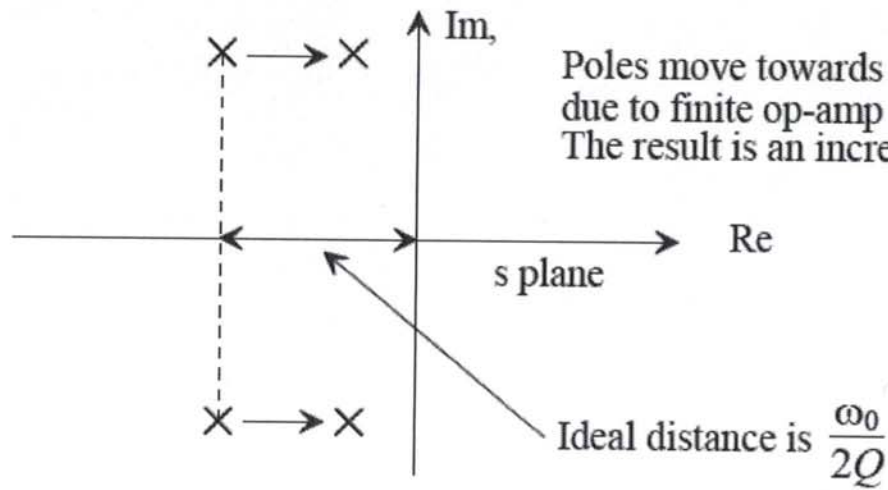

$$A_{OL}(s) = \frac{A_{OL}}{1 + j\frac{f}{f_{3dB}}}$$

$$\approx \frac{1}{j\frac{f}{f_{3dB}}}$$

Figure 3.50 Showing Q peaking resulting from the op-amp finite gain bandwidth product.


Q peaking related to finite BW of op-amp
 $f_{3dB} = \frac{f_{3dB}}{A_{OL}}$

$$\frac{1}{s} \rightarrow \frac{1}{s \left(1 + \frac{s}{\pi f_{3dB}}\right)}$$

$$\frac{1}{s \left(1 + \frac{s}{\pi f_{3dB}}\right) + p_1} \cdot \frac{1}{s \left(1 + \frac{s}{\pi f_{3dB}}\right) + p_2}$$

$$s\left(1 + \frac{s}{2\pi f_w}\right) + p_1 = s + p_1 + \frac{s^2}{2\pi f_w}$$
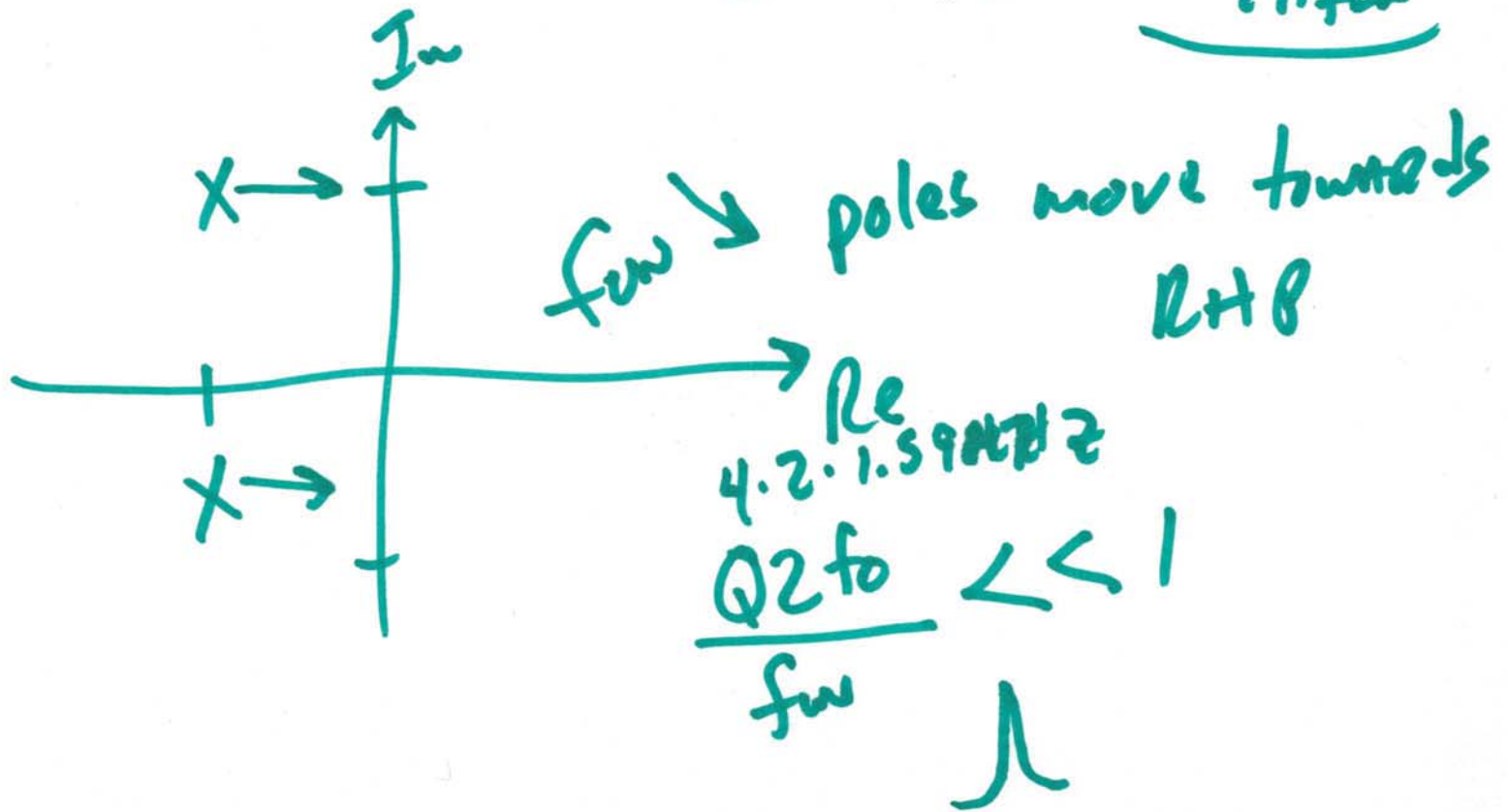
$$= s + p_1 + \frac{-(2\pi f)^2}{2\pi f_w}$$



8



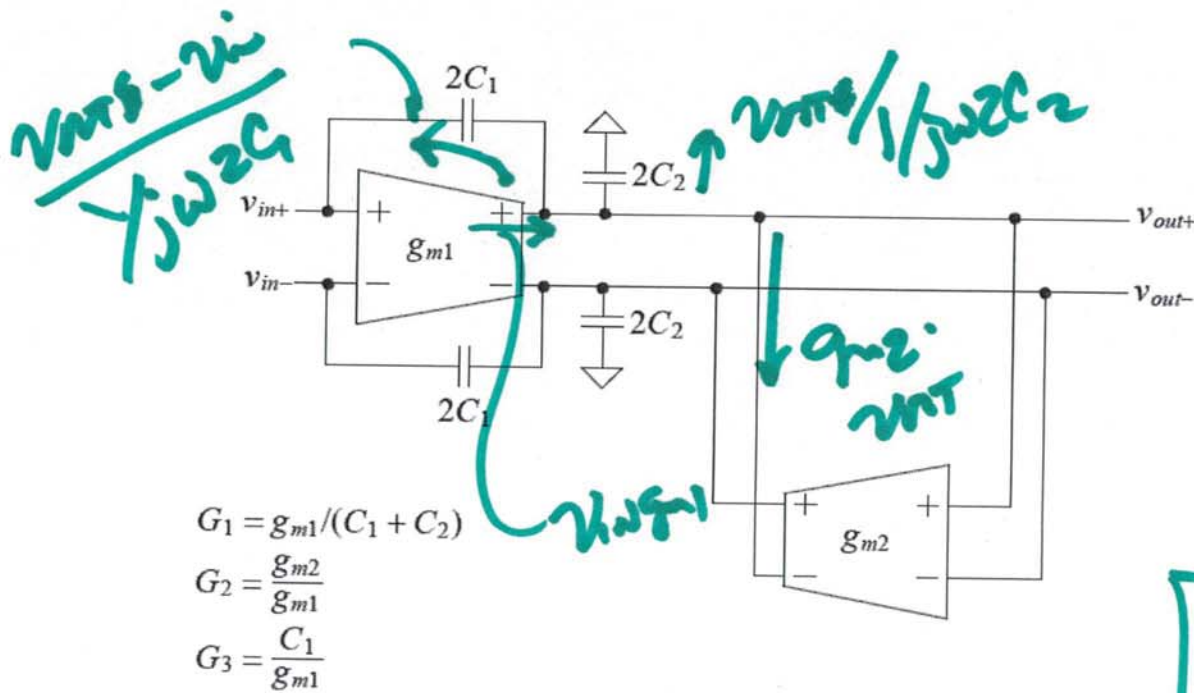


Figure 3.52 Redrawing the bilinear filter shown in Fig. 3.31.

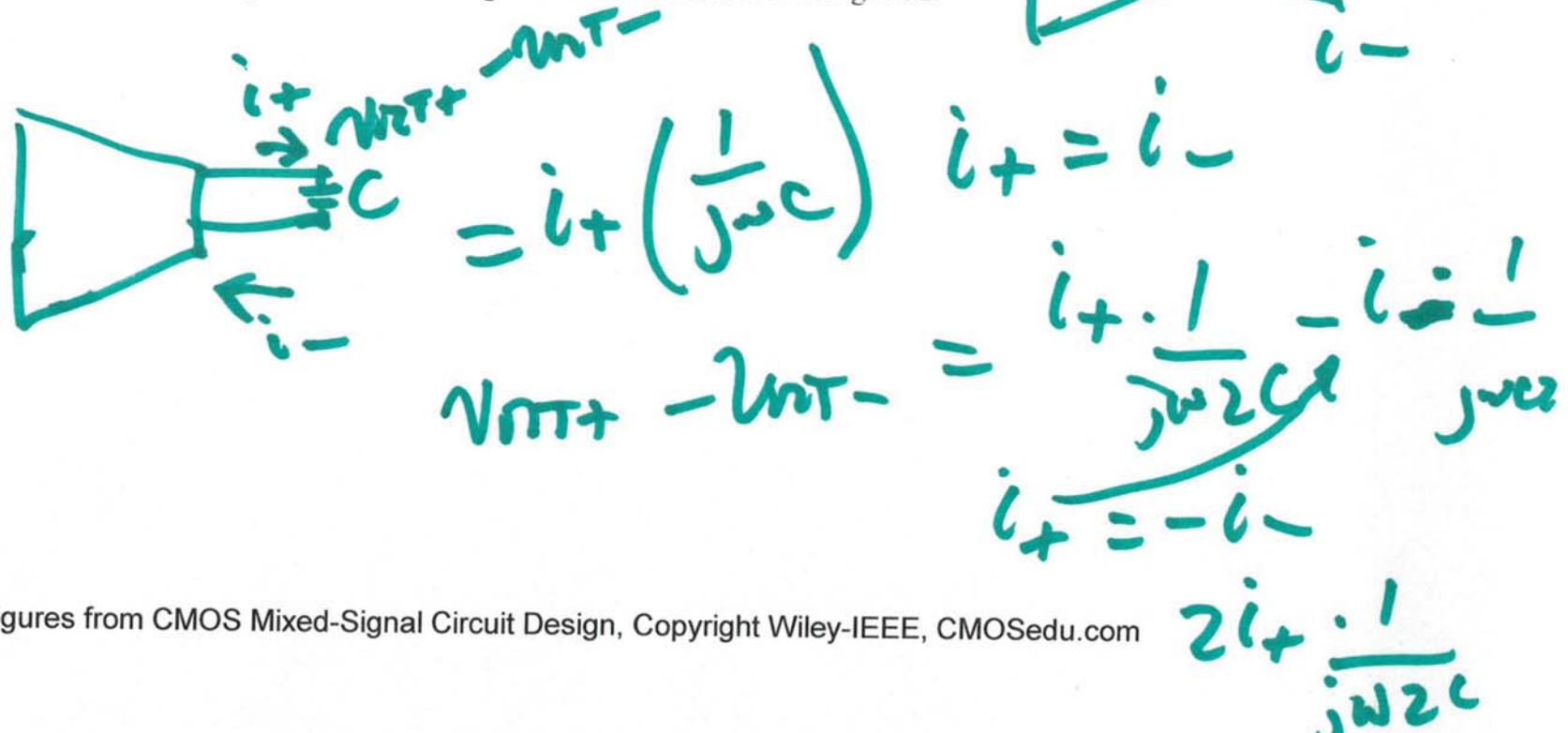

a)

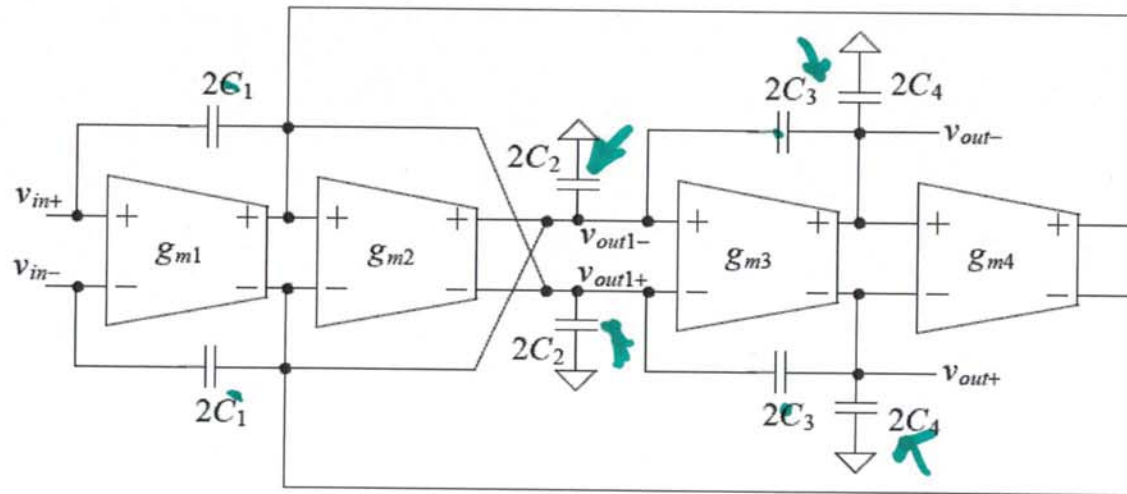

$$G_1 = g_{m1}/(C_1 + C_2) \quad G_2 = \frac{g_{m2}}{g_{m1}} \quad G_3 = \frac{C_1}{g_{m1}} \quad G_4 = g_{m3}/(C_3 + C_4) \quad G_5 = \frac{g_{m4}}{g_{m1}} \quad G_6 = \frac{C_3}{g_{m3}}$$

Figure 3.53 Implementing a biquadratic filter using transconductors.

10)