




ECG 722

CMOS mixed-signal

9/26/14

Low pass Sinc Filters

Accumulate & Dump

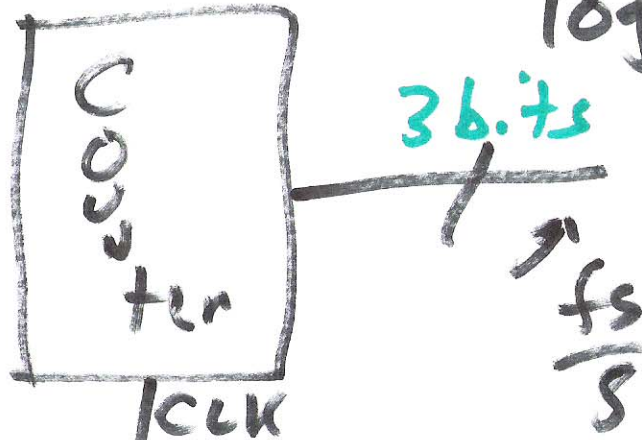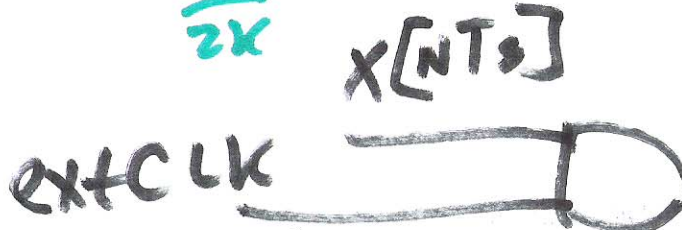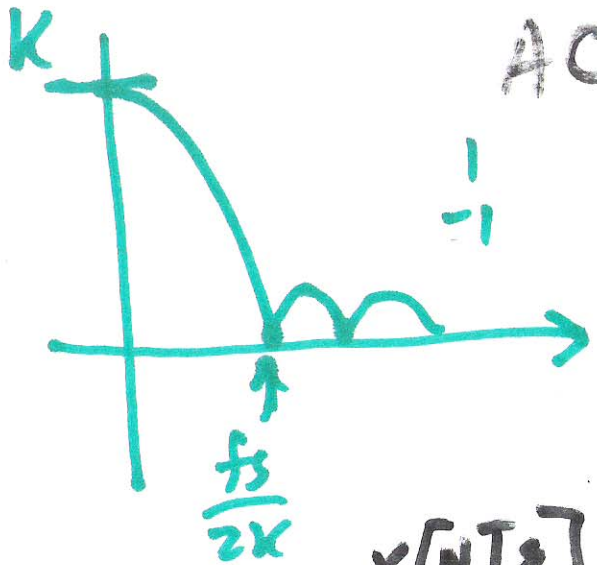

$\log_2 K : K = 256$


$K = 8$

$\log_2 2^3 = 3\text{-bit}$


$\log_2 2^8 = 8\text{-bit}$

$11110000 \frac{f_s}{8}$
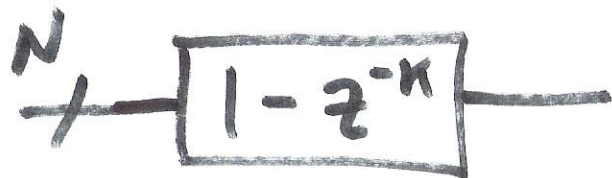
$$\begin{array}{r} 10011100 \\ \frac{72}{11} T_f \quad 4 \\ \hline 10101010 \\ \frac{273}{2} = \frac{f_s}{2} \end{array}$$



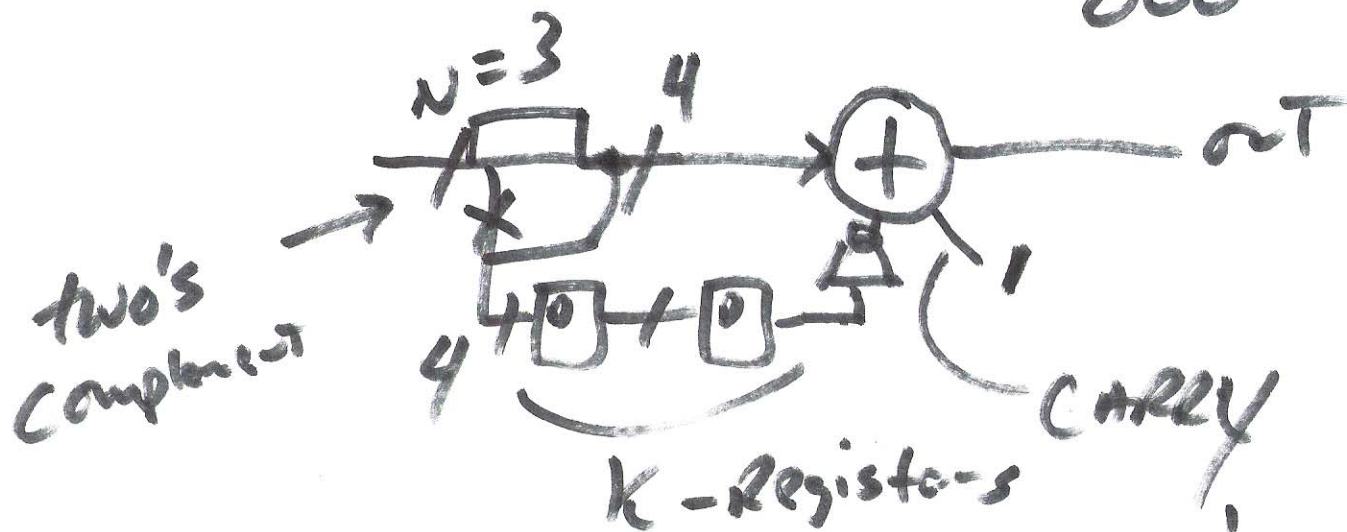$111 \quad 0011 \rightarrow +3$
 $100 \quad 000 \rightarrow 0$
 $000 \quad 1100 \rightarrow -4$



two's complement

$\begin{array}{r} 3 \\ -(-4) \\ \hline +7 \rightarrow 0111 \end{array}$

$+3$
 $-(-4)$

\rightarrow

0011
 0000
 $\quad \quad \quad 1$

~~00~~
 0111 yay!

2)

Change into two's complement and extend sign bit by 1.

Extend the sign-bit by $2 = \log_2 K - 1$

Change back to binary offset format.


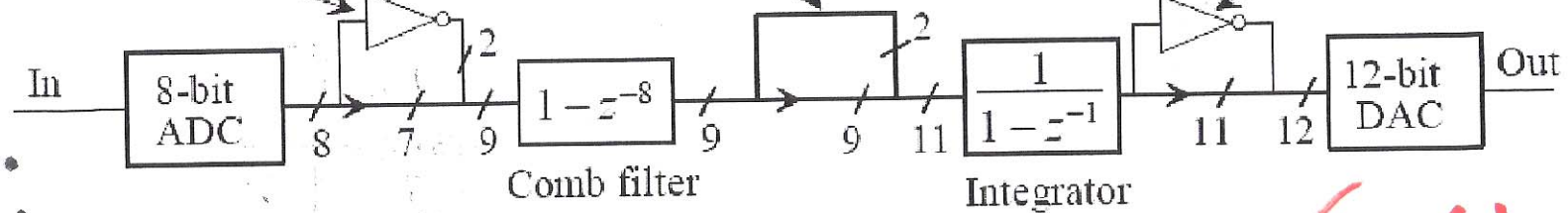


Figure 4.14 Digital filter sketch for Ex. 4.3.

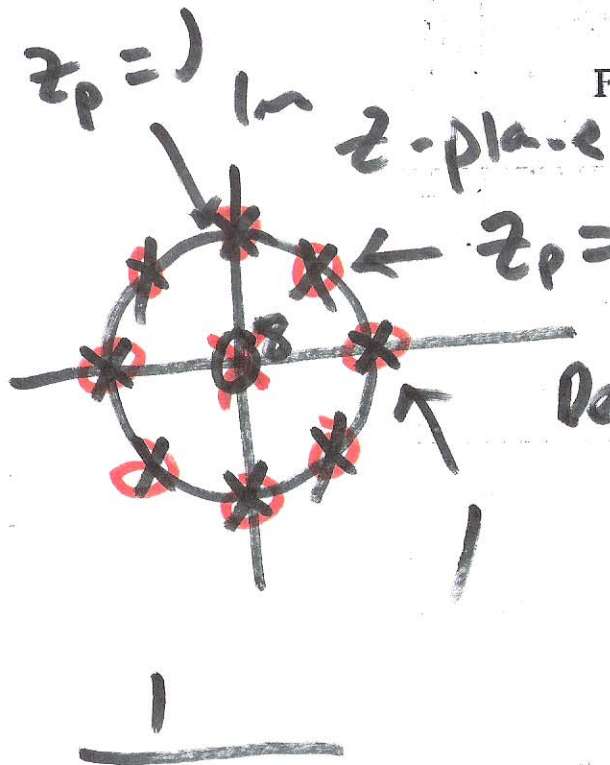

z-plane

$$z_p = .707 + j.707$$

$$(1 - z^{-8}) =$$


$$\left(\frac{z^8 - 1}{z^8} \right) =$$

$$\left(z + \frac{1}{\sqrt{2}} + j \frac{1}{\sqrt{2}} \right)$$


$$(z + j) \cdot \left(z - \frac{1}{\sqrt{2}} - j \frac{1}{\sqrt{2}} \right)$$

$$\frac{(z-1)(z+1)(z-j)(z+j)}{z^8}$$

3)


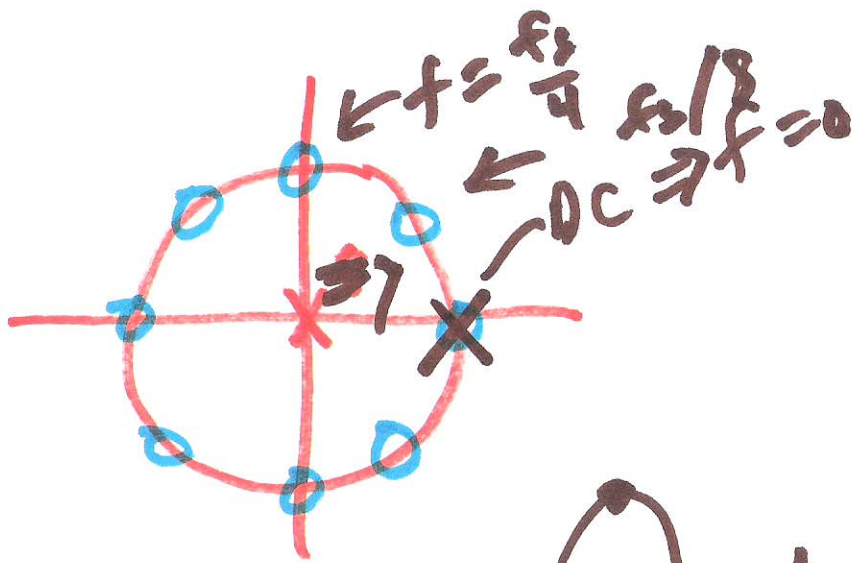


$$1 - z^{-8} = \frac{z^8 - 1}{z^8}$$

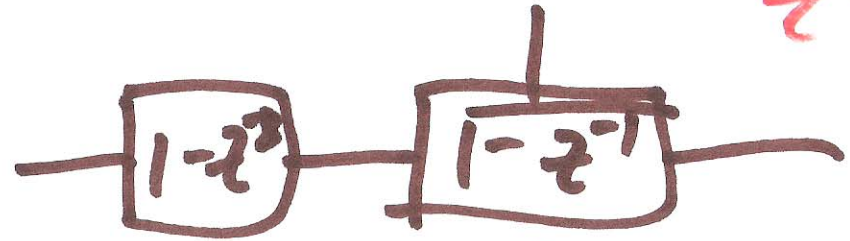

$$\frac{z}{z - 1}$$




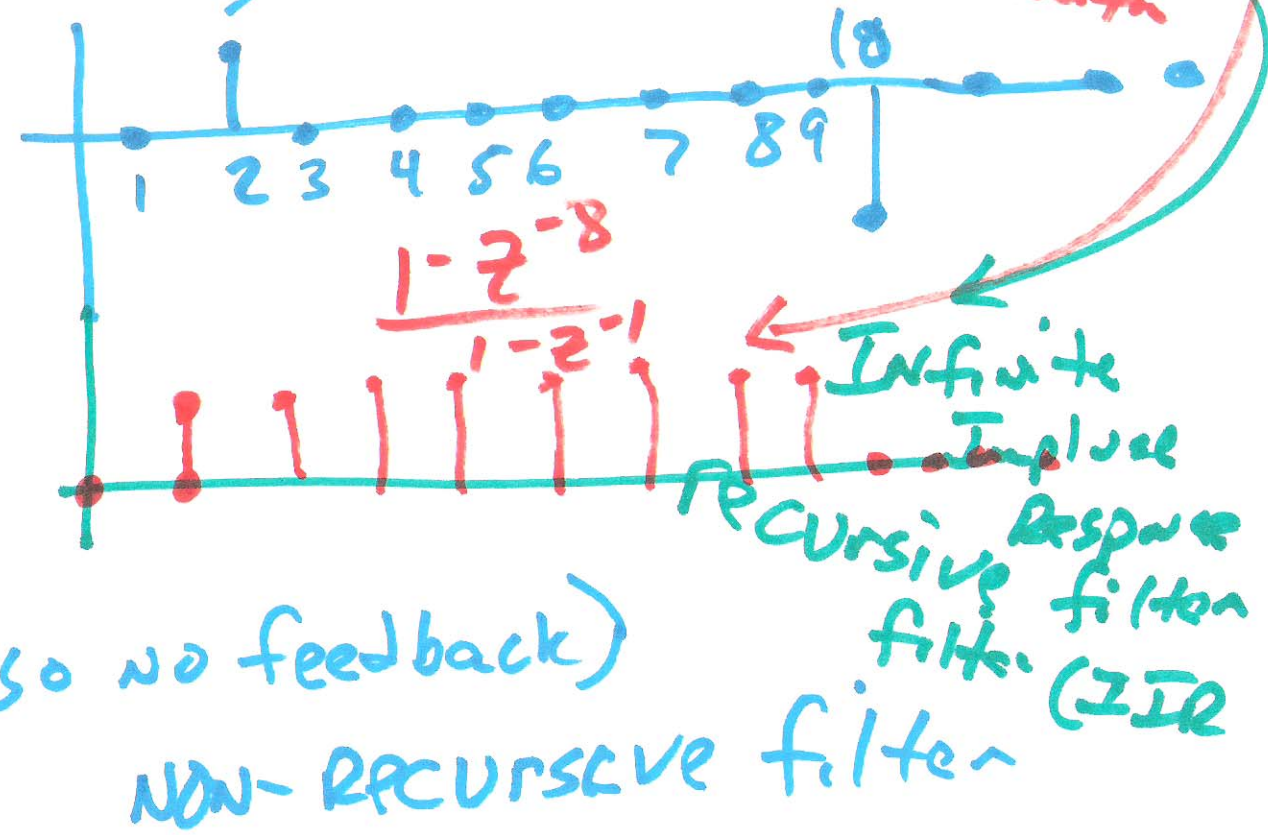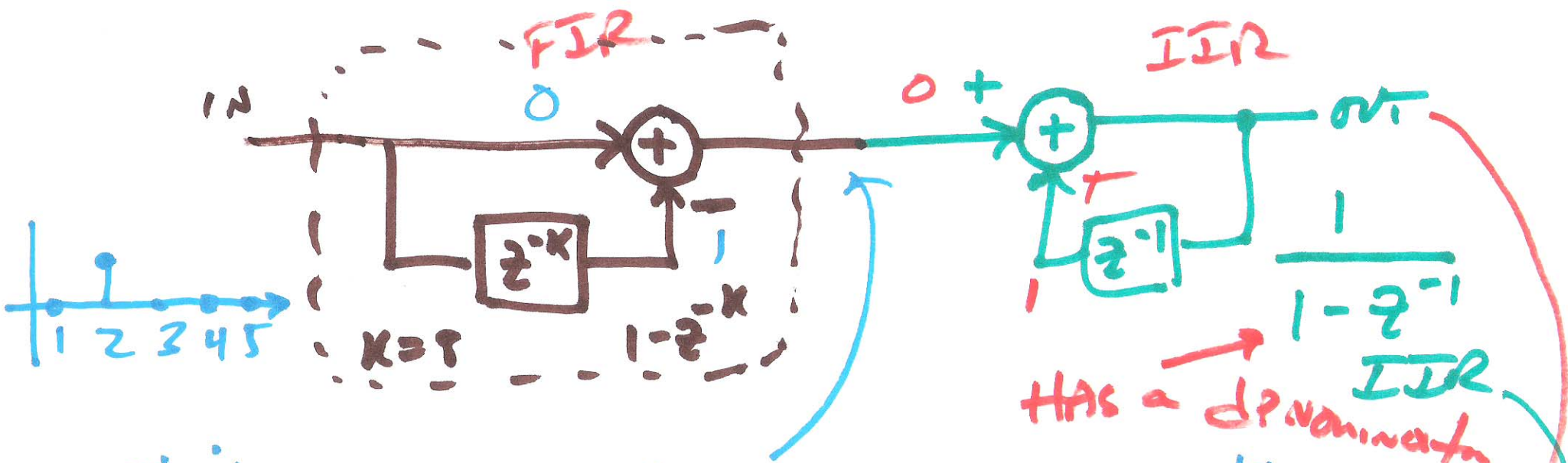

6)

Stable Digital filter.

has poles inside the unit circle

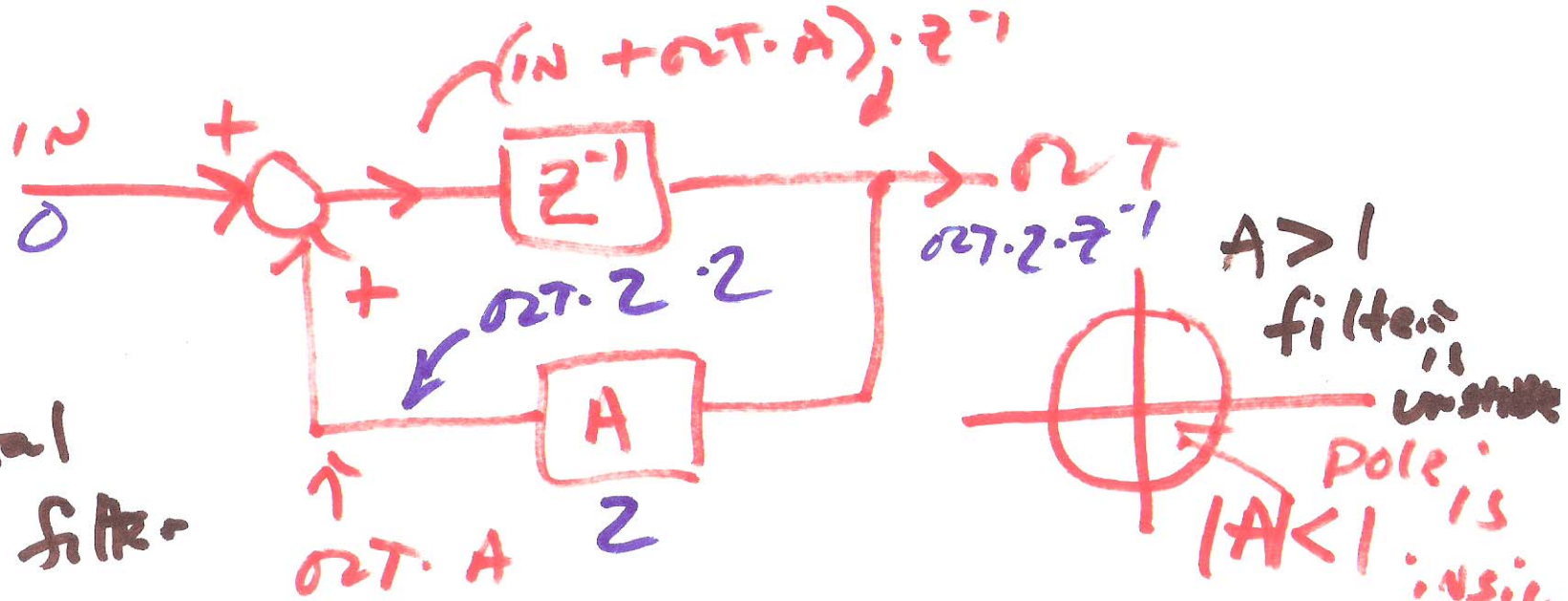

$$OUT = (IN + OUT \cdot A) z^{-1}$$

the unit circle

$$OUT (1 - A z^{-1}) = IN z^{-1}$$

$$\frac{OUT}{IN} = \frac{z^{-1}}{1 - A z^{-1}} = \frac{1}{z - A}$$

6)


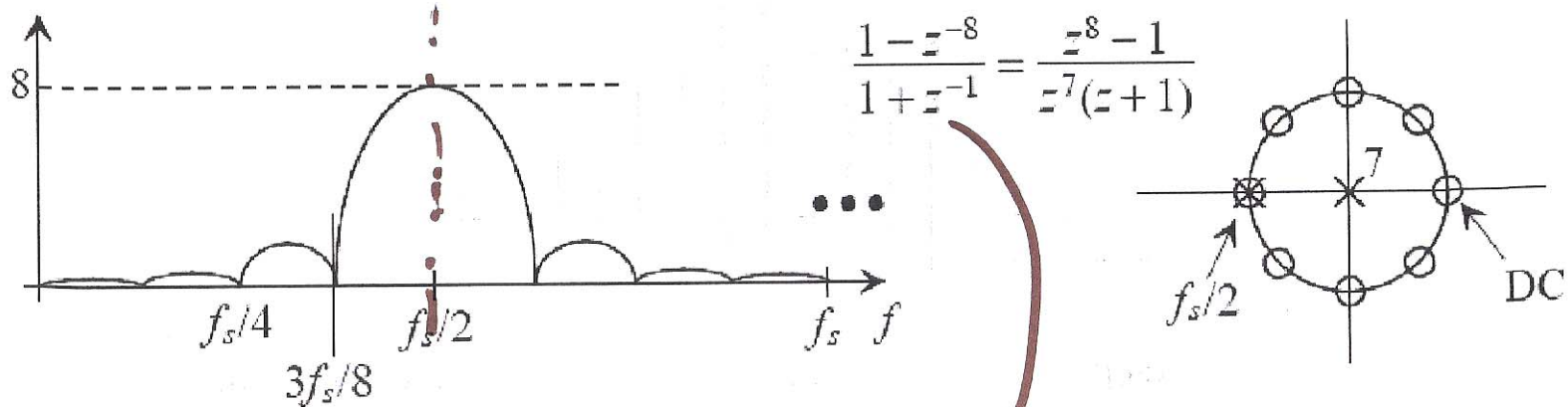


Figure 4.19 A highpass filter implementation using a comb filter.

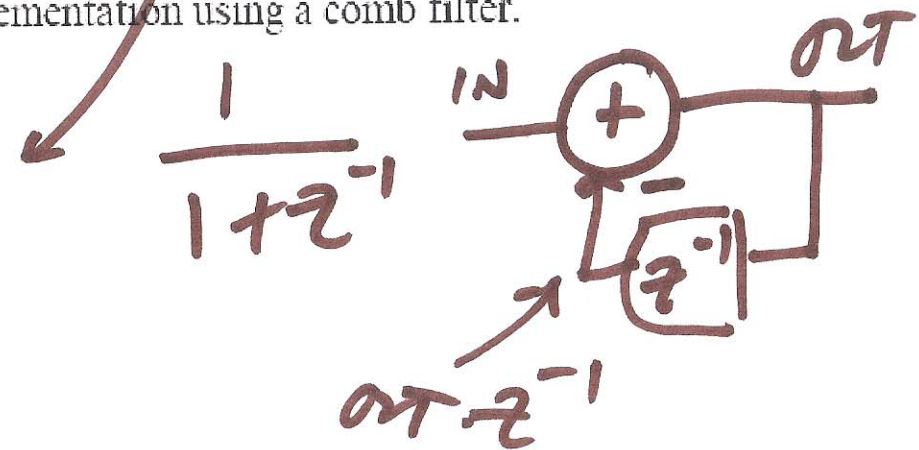

$$\frac{OUT}{IN} = \frac{1}{1+z^{-1}} \quad OUT = IN - OUT \cdot z^{-1}$$

$$OUT(1+z^{-1}) = IN$$

7)

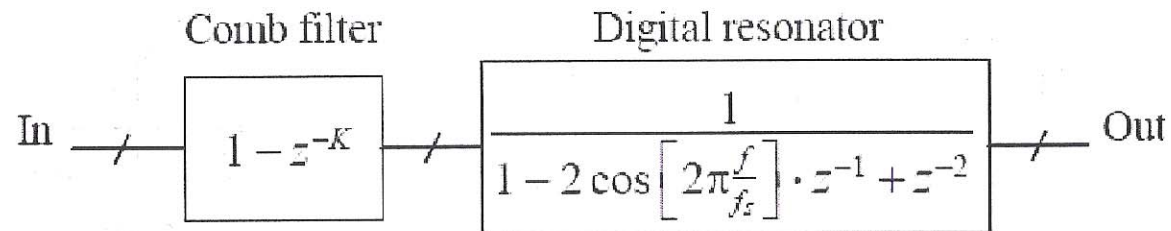


Figure 4.20 Implementing a sinc-shaped bandpass filter.

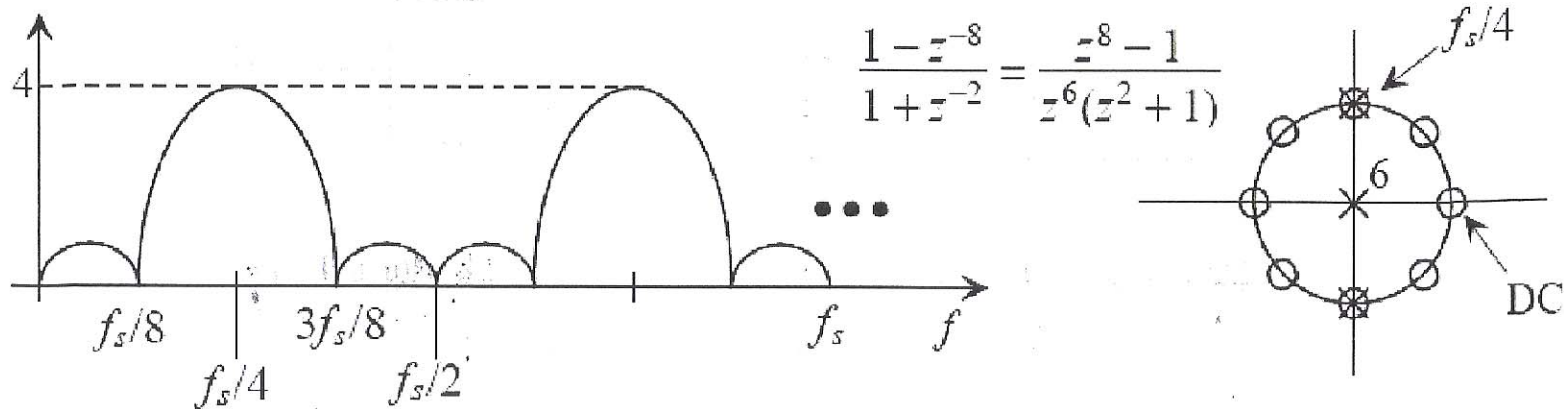


Figure 4.21 A bandpass filter implementation using a comb filter and digital resonator.

$$\frac{1}{1+z^{-2}} \Rightarrow \frac{z^2}{z^2+1} = \frac{z^2}{(z+j)(z-j)}$$

9)


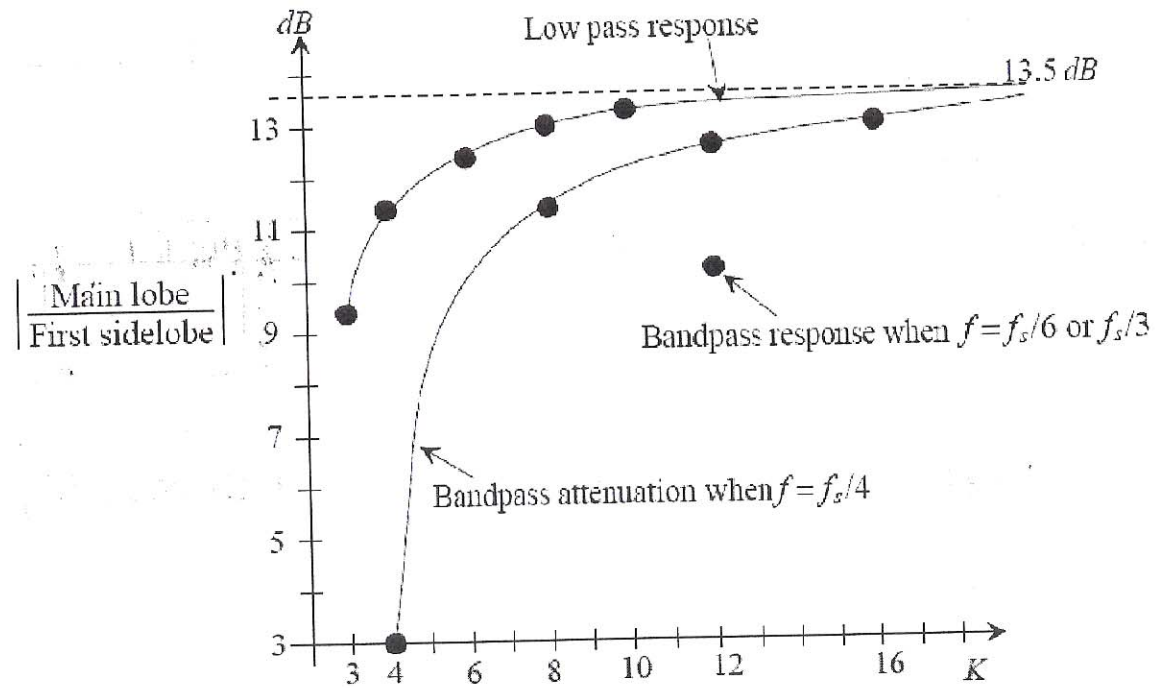


Figure 4.22 Lowpass and bandpass filter attenuation versus number of comb filter zeroes, K.

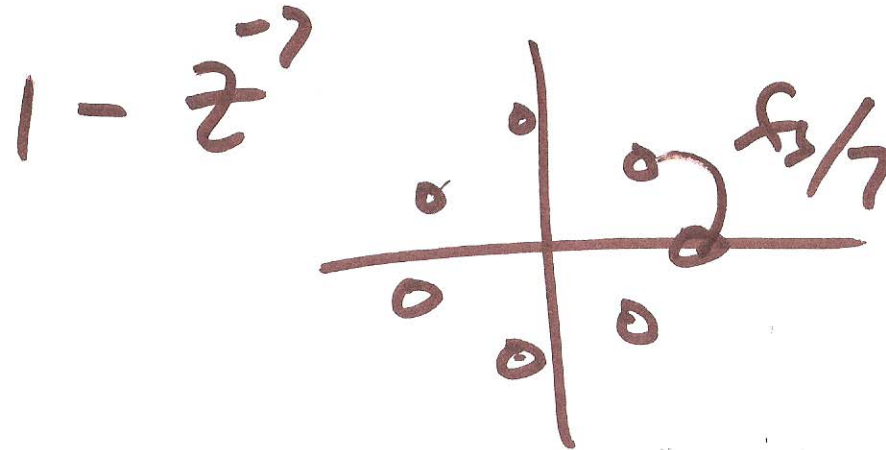


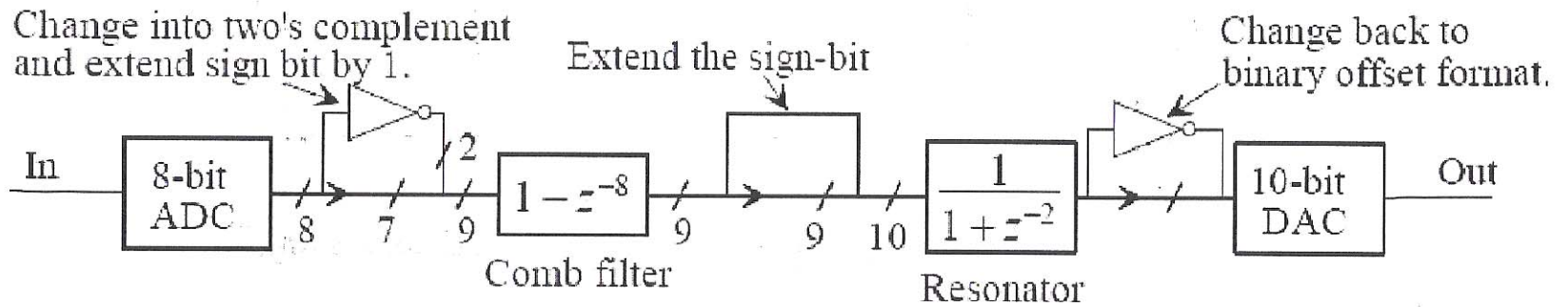


Figure 4.24 Digital filter sketch for Ex. 4.7.

$$f_s/4$$

$$f_s = 100\text{mHz}$$

ii)

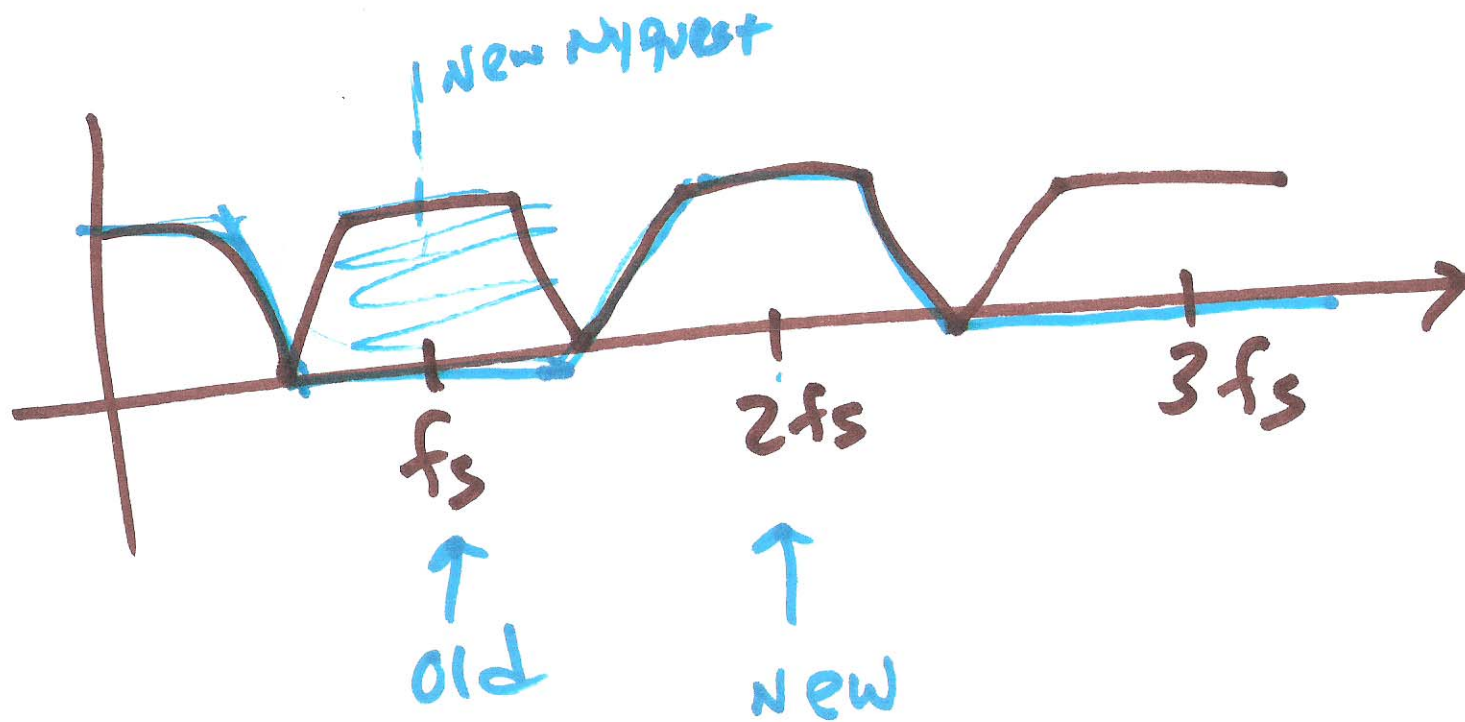

12)

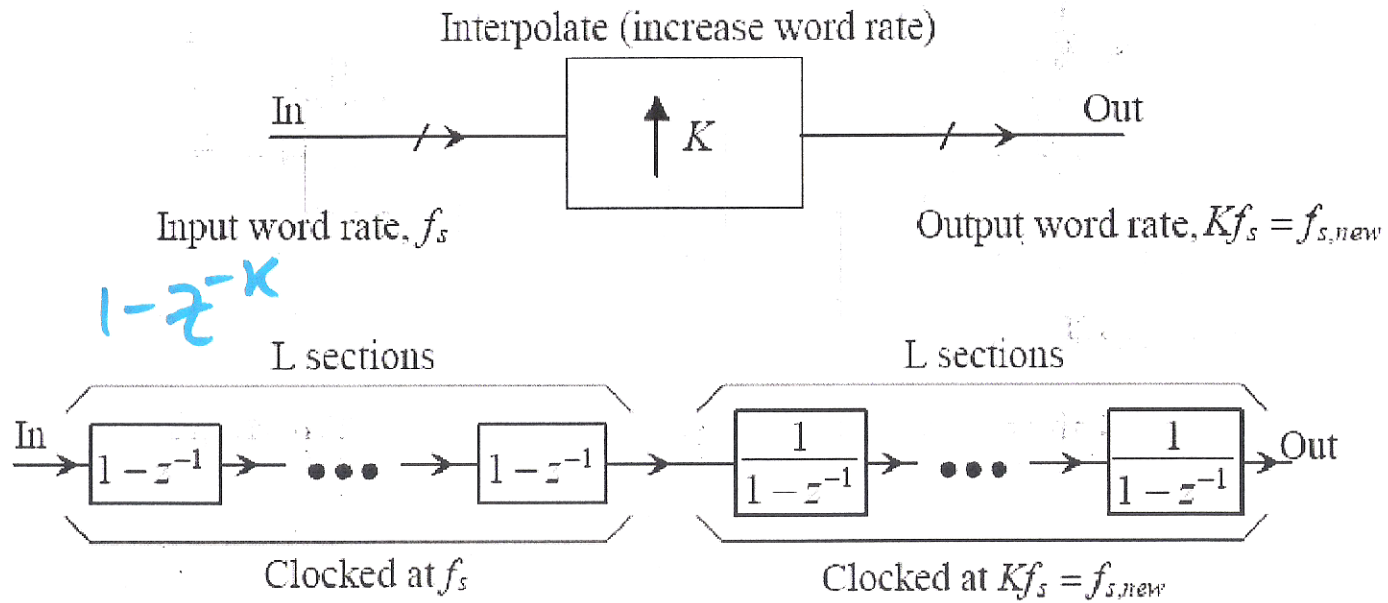


Figure 4.28 Interpolating using Sinc filters for image removal.

$$1\text{-delay} = k\text{-delays}$$

$$T_s \qquad \qquad \qquad \frac{T_s}{k}$$

13)