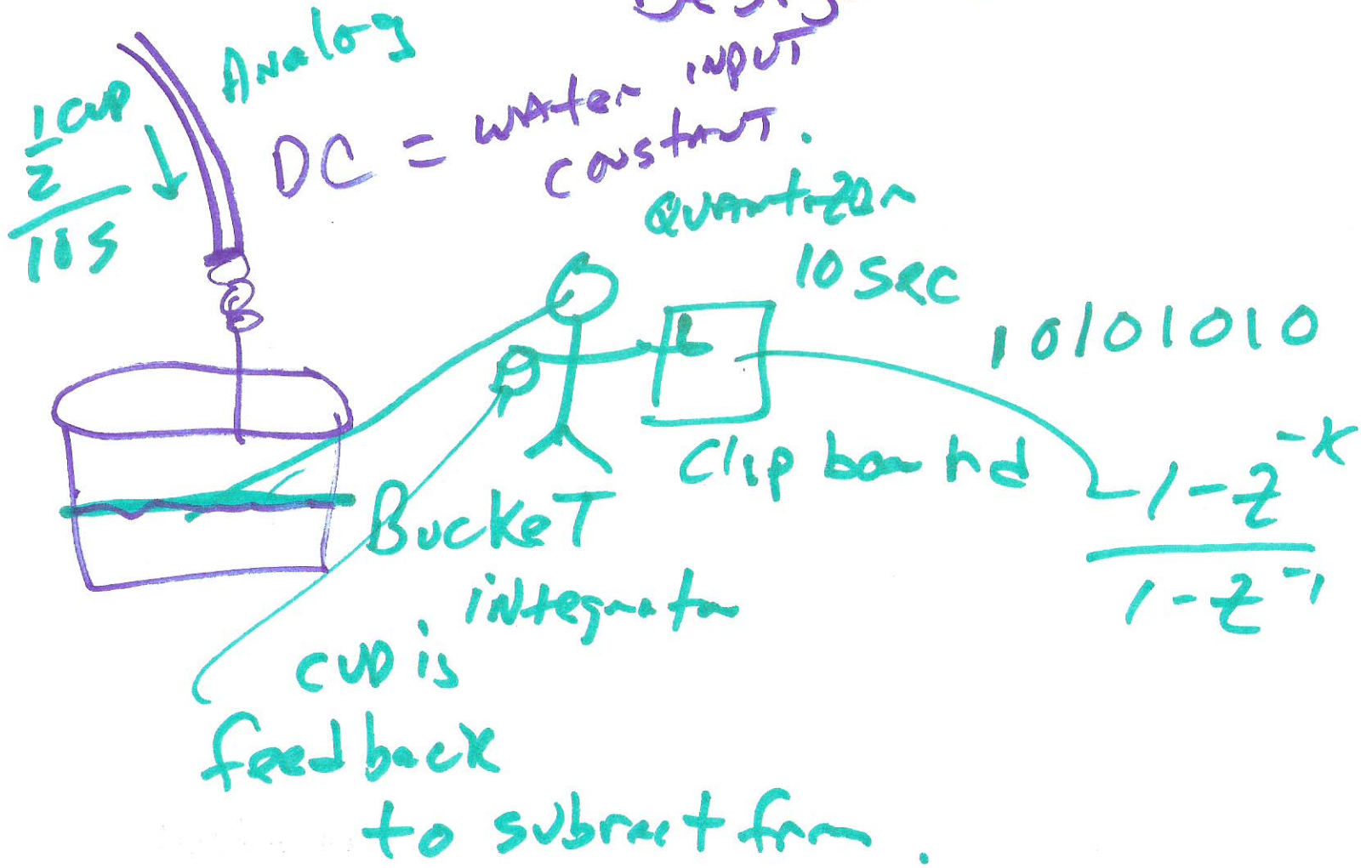


Ch. 6

Data Converter

Design Basics




1)


Level	time	Y/N ^{Y/N}	Level
5 cups	0	1	4 cups .61
4 cups	10	0, 4.61	4.61
4.61	20	1, 5.22	4. 22 22
4.22	30	0, 4.83	4.83
4.83	40	1, 5.44	4.44
4.44	50	0, 5.05	4.05
4.05	60	0, 4.66	4.66
4.66	70	1, 5.27	4.27
4.27	80	0, 4.88	4.88
4.88	90	1, 5.49	4.49
4.49	100	1, 5.10	4.1

$\frac{7}{11}$ 1 cup

2)

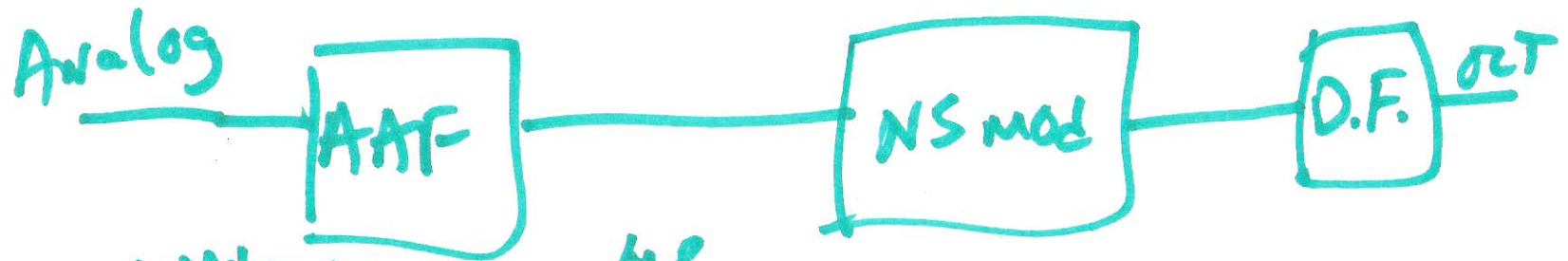

Water 10v_R

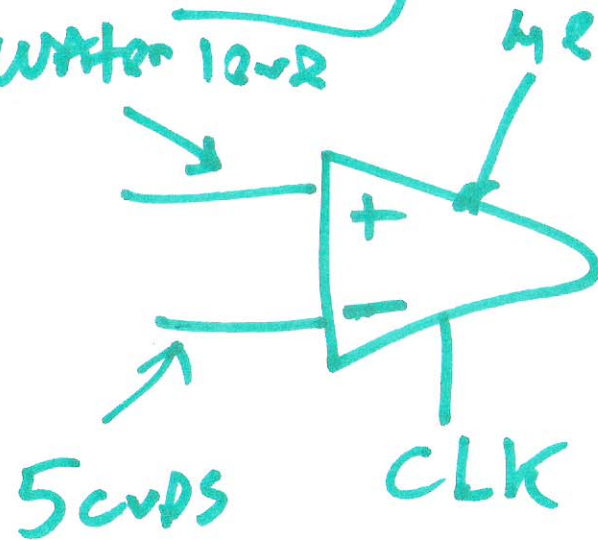


1-bit quantizer
10v_{DD}

$$V_{LSB} = V_{DD}$$

$$0 \rightarrow 11 \quad (-1)$$

$$1 \rightarrow 01 \quad (+1)$$

3)

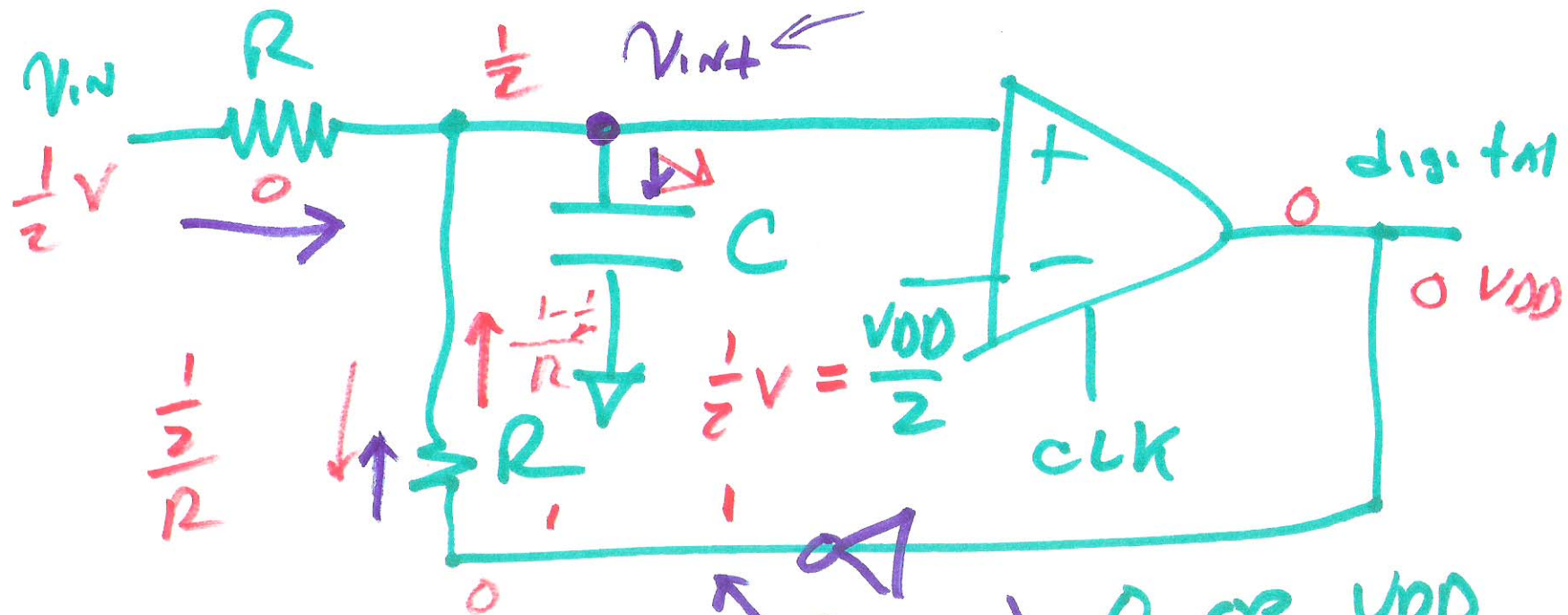

$$\frac{1}{j\omega C} \left(\frac{V_{in} - V_{int}}{R} + \frac{-V_{int} - V_{int}}{R} \right) = V_{int}$$

0 or VDD
 101010
 +1 -1 +1 -1
 0 = V_{en}

$$V_{int} \left(1 + \frac{2}{j\omega RC} \right) = \frac{V_{in}}{j\omega RC} \Rightarrow \frac{-V_{int}}{j\omega RC}$$

4)

$$V_{OUT} = V_{in} (j\omega RC + 2) + V_{in}$$

$$A(f) = \frac{1}{2 + j\omega RC}$$

$$V_{OUT} = \frac{1}{3 + j\omega RC} \cdot V_{in}(f)$$

5)