

CASCADED MODULATORS

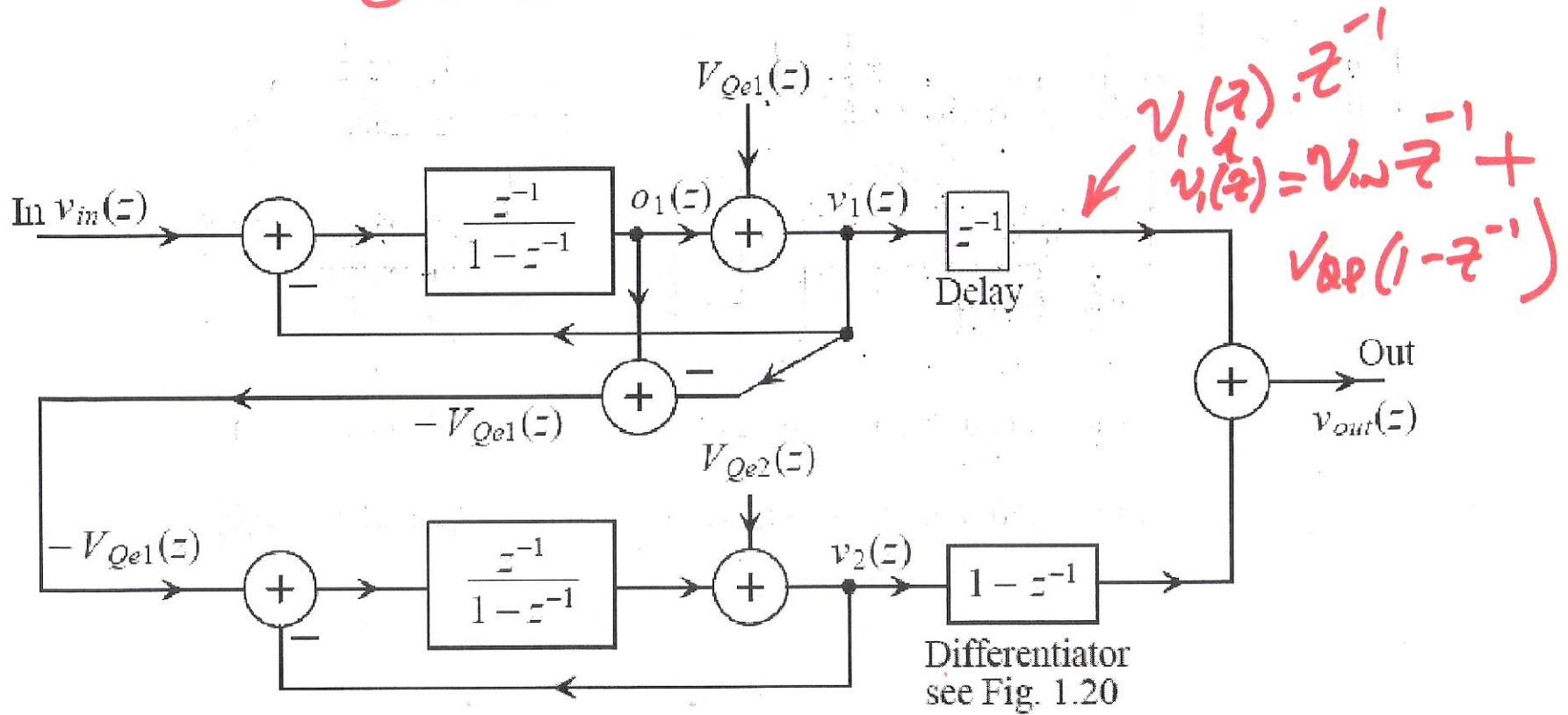


Figure 7.53 Second-order (1-1) cascaded modulator.


$$(1 - z^{-1})(V_2(z)) = (-V_{out}(z)z^{-1} + V_{Qe}(z)(1 - z^{-1}))$$


$$V_{\text{eff}}(z) = V_{in} z^{-2} + z^{-1}(1-z^{-1}) V_{Qe}(z)$$

$$+ (1-z^{-1}) z^{-1} (-V_{Qe}(z)) + (1-z^{-1}) V_{Qe}(z)(1-z^{-1})$$

$$= V_{in} z^{-2} + (1-z^{-1})^2 V_{Qe}(z)$$

Second-order
noise shaping

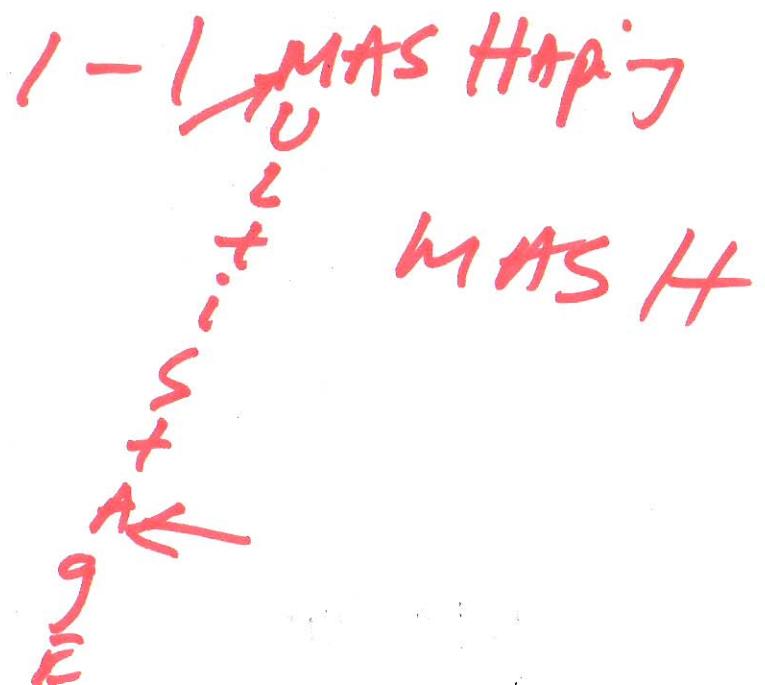

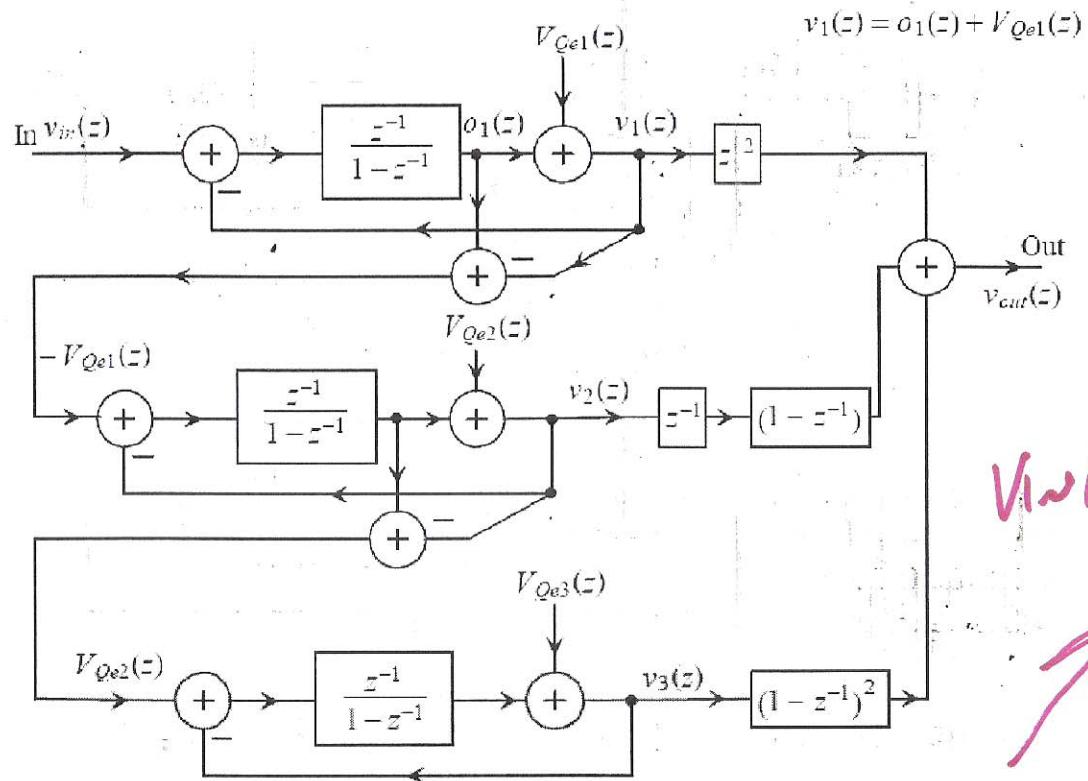

H1-1

$$V_{in}(z) z^{-3} (1 - z^{-1})^3 V_{ao}$$

Figure 7.54 Third-order (1-1-1) cascaded modulator.

$$\begin{aligned}
 v_{out}(z) &= z^{-2} \left(z^{-1} v_m(z) + V_{ao1}(z) (1 - z^{-1}) + \right. \\
 &\quad z^{-1} (1 - z^{-1}) \left(z^{-1} V_{ao1}(z) + V_{ao2}(z) (1 - z^{-1}) \right) \\
 &\quad \left. + (1 - z^{-1})^2 \left[(V_{ao2}(z)) \cancel{(z^{-1})} + V_{ao3}(z) (1 - z^{-1}) \right] \right)
 \end{aligned}$$

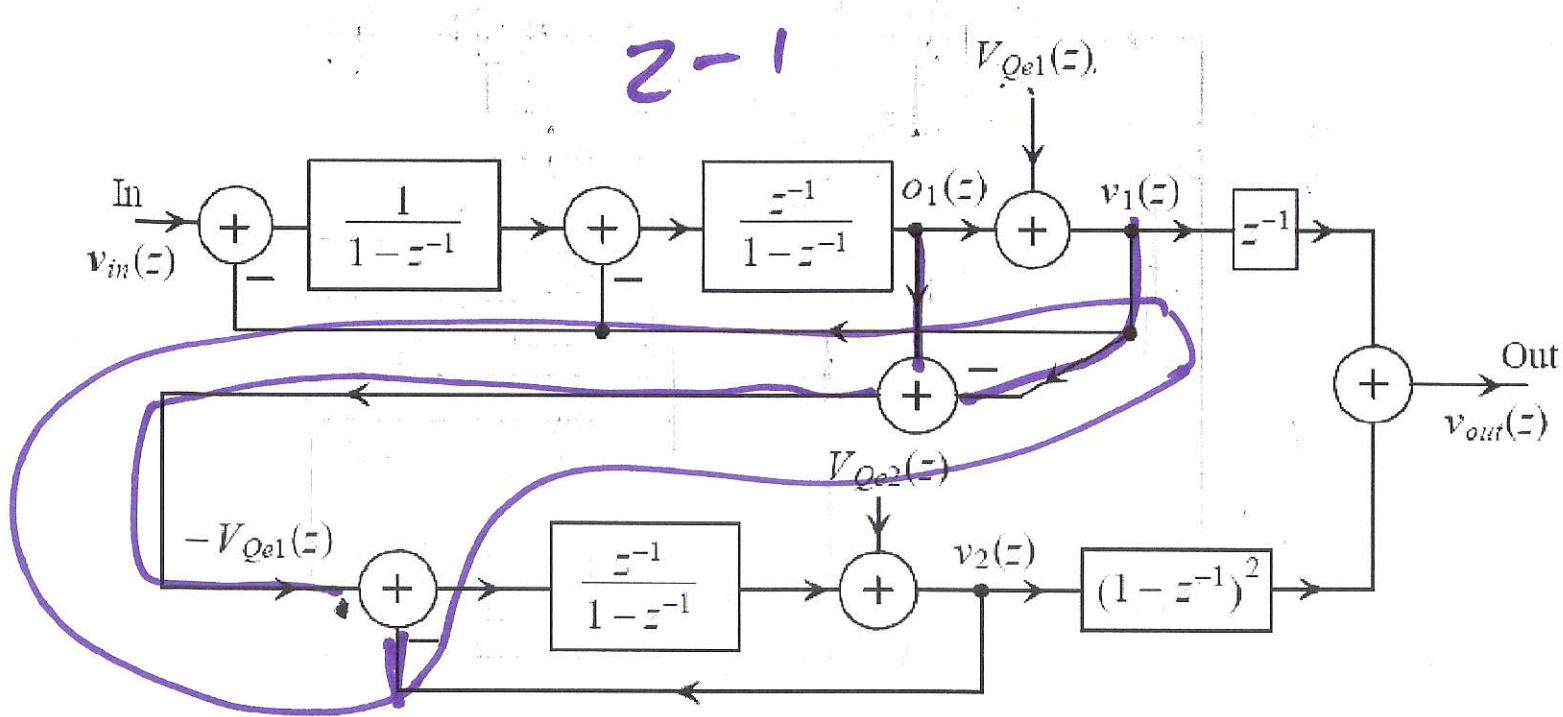


Figure 7.55 Third-order (2-1) cascaded modulator.

$$\begin{aligned}
 v_{out}(z) &= v_{in}(z) \cdot z^{-2} + z^{-1}(1-z^{-1})^2 V_{Qe1}(z) \\
 &\quad + (1-z^{-1})^2 z^{-1} (-V_{Qe1}(z)) + V_{Qe2}(1-z^{-1})^3 \\
 &= v_{in}(z) z^{-2} + V_{Qe1}(z)(1-z^{-1})^3
 \end{aligned}$$

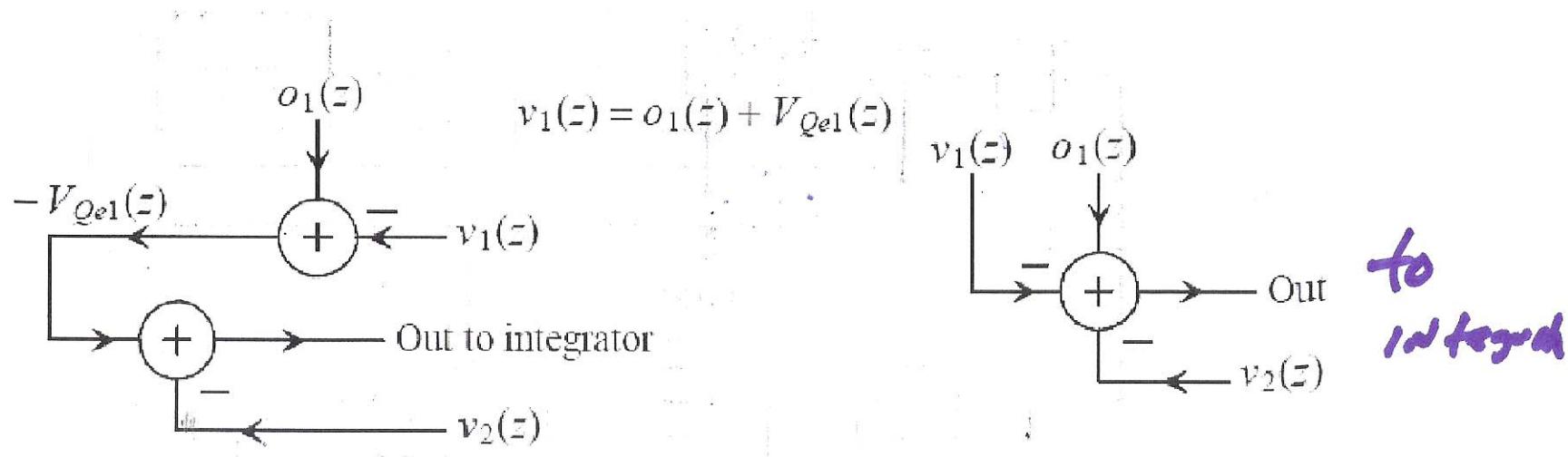


Figure 7.56 Showing implementation of the dual summing block as a single block

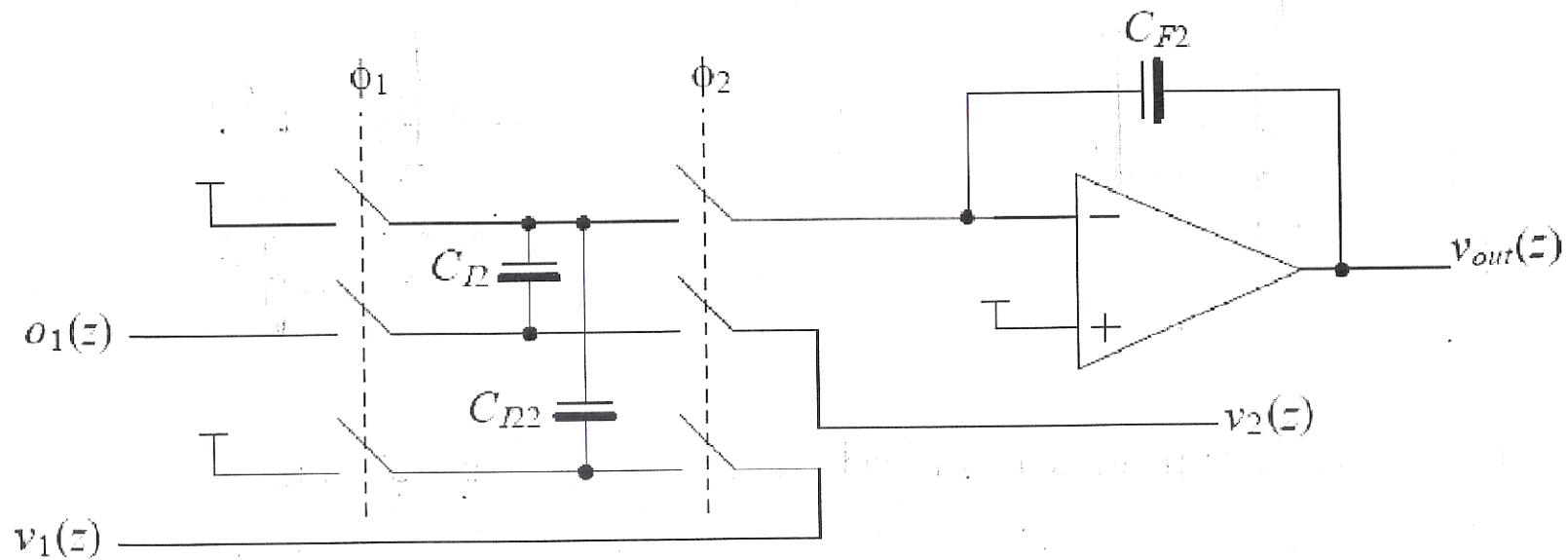


Figure 7.57 Implementing the dual summing block for a cascaded modulator.

