

Problem 20.1

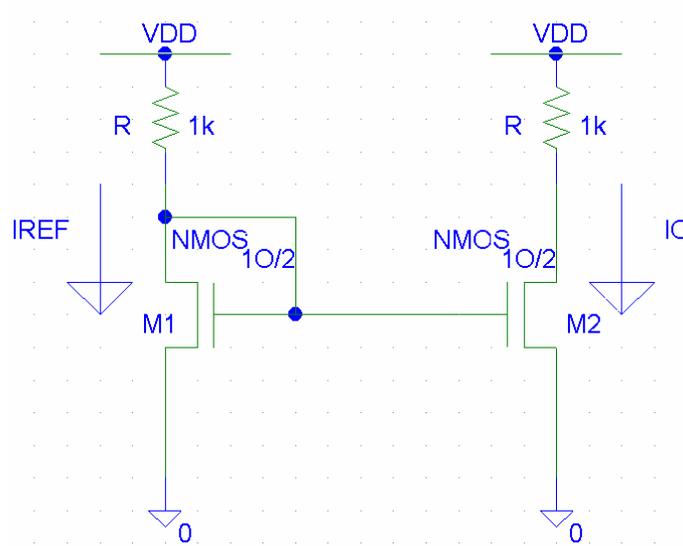


Figure 1.

Since the Drain Resistors and M1 and M2 are the same size, it can be said that:

$$V_{DS1} = V_{GS1} = V_{GS2} = V_{DS2}$$

Since, M1 is diode connected, and a current I_{REF} is running through it, M1 is in saturation, and:

$$I_{REF} = \frac{K P_N}{2} * \frac{W_1}{L_1} * (V_{GS1} - V_{TH_N})^2$$

And from Figure 1,

$$I_{REF} = \frac{(V_{DD} - V_{GS1})}{100K}$$

Setting these two equal and solving for V_{GS1} gives,

$$30 * V_{GS1}^2 - 47 * V_{GS1} + 14.2 = 0 \Rightarrow V_{GS1} = 1.15V \text{ OR } .409V .$$

For M1 to be in Saturation V_{GS1} must equal 1.15V. Putting this value into the equation for I_{REF} , gives:

$$I_{REF} = \frac{V_{DD} - V_{GS1}}{R} = \frac{5 - 1.15}{100K} = 38\mu A$$

If we don't concern ourselves with channel length modulation:

$$\Rightarrow \frac{I_O}{I_{REF}} = \frac{W_1}{W_2} \Rightarrow I_O = \frac{10\mu}{10\mu} * 38\mu A = 38\mu A \quad (\text{EQ.20.4})$$

These results are verified with the following SPICE netlist and Figure 2.

```
*** hw_20_1

.control
destroy all
run
LET IREF=VREF#BRANCH
let Io=Vo#branch
plot IREF Io
.endc

.option scale=1u
*.dc Vo 0.1 10 1m
.tran 1ns 1us

VDD    VDD    0      DC    5
VREF   VR1   VGS1   DC    0
Vo     vo    vd2    DC    0

R1     VDD    VR1    100k
R2     VDD    VO     100K

M1     VGS1  VGS1  0  0  NMOS L=2 W=10
M2     VD2   VGS1  0  0  NMOS L=2 W=10
**models excluded
```

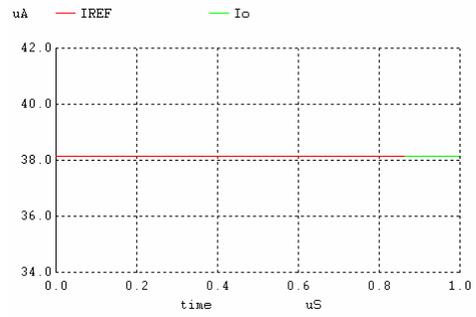


Figure 2

Problem 20.2 Solution by Robert J. Hanson, CNS

Problem Statement:

Repeat Problem 20.1 for when M2 has $V_{DS2}=V_{DS1}=V_{GS1}$. Can M1 and M2 be replaced with a single MOSFET? If so how and what size? If not why?

From the figure for Problem 20.2 we see that $W/L=10/2$ for both MOSFETs. We also know that $V_{DS1}=V_{GS1}=V_{DS2}=V_{GS2}$. We also know that this is a long channel process and $V_{DD}=5V$, $V_{THN}=0.8V$ for NMOS devices, CLM $\Lambda=0.01$, and $K_{PN}=120\mu$ and R is given as $100k$.

Since the same current flows in the resistor as the sum of both MOSFETs (the MOSFETs are in parallel with each other and in series with a resistor).

We have 2 diodes in saturation so the I_D equation in saturation will be used.

$$(5-V_{GS1})/R = K_{PN}/2 * W/L * (V_{GS1}-V_{THN})^2 * (1+\Lambda(V_{DS}-V_{DS,SAT}))$$

Here $V_{GS1}=V_{DS}=V_{GS}$, $V_{DS,SAT}=V_{GS}-V_{THN}$ and Since $I_R=I_{M1}+I_{M2}=2I_{M1}=2I_{M2}$

Substituting gives:

$$(5-V_{GS})/100k = 2 * (120\mu/2) * 10/2 * (V_{GS}-0.8)^2 * (1+0.01 * (V_{GS}-(V_{GS}-V_{THN})))$$

$$(5-V_{GS})/100k = 2 * (120\mu/2) * 10/2 * (V_{GS}-0.8)^2 * (1+0.01 * V_{THN})$$

$$(5-V_{GS})/100k = 2 * (120\mu/2) * 10/2 * (V_{GS}-0.8)^2 * (1+0.01 * 0.8)$$

$$(5-V_{GS})/100k = 604.8\mu * (V_{GS}-0.8)^2$$

By quadratic equation: $V_{GS} = [95.768 \pm \sqrt{95.768^2 - 4 * 60.48 * 33.71}] / (2 * 60.48)$

Therefore $V_{GS}=1.055V$ or $0.528V$ (less than V_{THN} so this is not the correct answer)

→ $V_{GS}=1.055V$

Plug Back into I equation and $I_R=39.3 \mu A$

Spice simulation uses the following net list:

```
*** Homework Problem 20.1 RJHANSON ***
.control
destroy all
run

print vmeas1#branch vmeas2#branch VGS1
.endc
.option scale=1u
```

```

.op

*** My Voltages ***
VDD   VDD   0     DC   5
VMEAS1 VR   VGS1  DC   0
VMEAS2 VS1  0     DC   0

*** My Devices in the Circuit ***
R1     VDD   VR   100K
M1     VGS1 VGS1 VS1  0     NMOS L=2 W=10
M2     VGS1 VGS1 0     0     NMOS L=2 W=10

*** These are the MOSFET Models***
.MODEL NMOS NMOS LEVEL = 3
+TOX = 200E-10  NSUB = 1E17  GAMMA = 0.5
+PHI = 0.7      VTO = 0.8    DELTA = 3.0
+UO  = 650      ETA  = 3.0E-6 THETA = 0.1
+KP  = 120E-6   VMAX = 1E5    KAPPA = 0.3
+RSH = 0        NFS  = 1E12   TPG  = 1
+XJ  = 500E-9   LD   = 100E-9
+CGDO = 200E-12 CGSO = 200E-12 CGBO = 1E-10
+CJ   = 400E-6  PB   = 1      MJ   = 0.5
+CJSW = 300E-12 MJSW = 0.5
*
.MODEL PMOS PMOS LEVEL = 3
+TOX = 200E-10  NSUB = 1E17  GAMMA = 0.6
+PHI = 0.7      VTO = -0.9   DELTA = 0.1
+UO  = 250      ETA  = 0      THETA = 0.1
+KP  = 40E-6    VMAX = 5E4    KAPPA = 1
+RSH = 0        NFS  = 1E12   TPG  = -1
+XJ  = 500E-9   LD   = 100E-9
+CGDO = 200E-12 CGSO = 200E-12 CGBO = 1E-10
+CJ   = 400E-6  PB   = 1      MJ   = 0.5
+CJSW = 300E-12 MJSW = 0.5

.end

```

And the output $I_R=39.3 \mu\text{A}$ (Pretty good calculation by hand)

Now if we are to establish the same I_R with 1 MOSFET it must have 2x the W to allow 2x current flow. Following is the SPICE simulation result for the same circuit as above with $W/L=20/2$.


$I_R=39.4 \mu\text{A}$
 $V_{GS1}=1.059$

It is possible to get the equivalent I_R using only 1 MOSFET, however, the circuit designer needs to be aware of what they are designing and what it is to be used for to optimize ones designs. This merely illustrates that by changing the W of an NMOS device that the same I_R could be obtained after eliminating M2 from the circuit. Rjh


Show the SPICE simulations for the PMOS devices in Ex. 20.1.

Using Table 9.1 values, we know that for a PMOS in saturation, that $V_{sg} = 1.15V$ in order to have a current of $20\mu A$ flowing. Therefore, the resistor size needed can be calculated by the following equation:

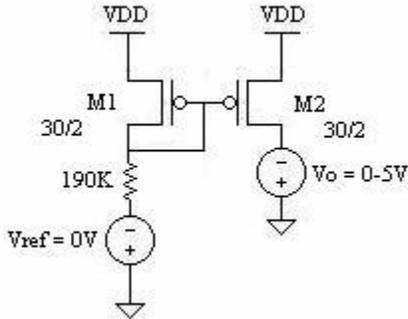$I_{ref} = (V_{DD} - V_{sg})/R$. Setting $I_{ref} = 20\mu A$ and solving for R we get $R \sim 190K\Omega$. Below is the circuit used to show the SPICE simulation.



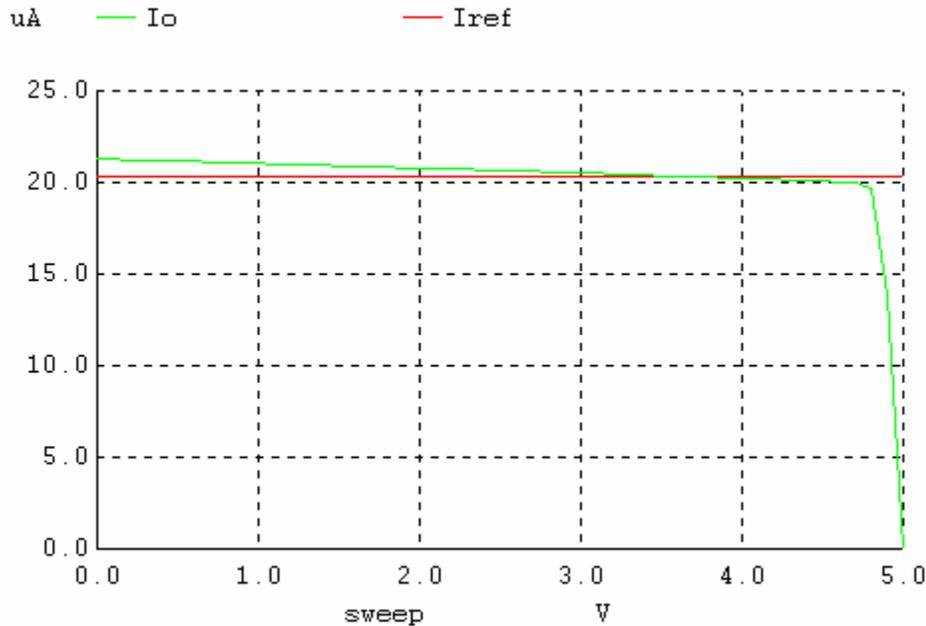Note V_{ref} is a dummy voltage (0V) only needed to monitor the current through M1. Below is the SPICE simulation for the above circuit sweeping V_o from 0 to 5V.



As V_o increases, I_o decreases due to the finite output resistance due to channel length modulation. Note that at 3.85V, V_{sd} for M2 is equal to V_{sd} of M1 and the two currents are equal. As V_o continues to increase the transistor moves into the triode region and begins to shut off. Below is the netlist for the above circuit.

```

*** Problem 20_3                Homework #2    Russell Benson

.control
destroy all
run

** Display Data **
let Iref = vref#branch
let Io = vo#branch

plot Iref Io
plot vsgl
.endc

.option scale=lu

** only need operating point analysis
.dc    Vo    0    5    .1

** Voltages
VDD    VDD    0    DC    5
Vo     Vo     0    DC    0
Vref   Vref   0    DC    0

** Resistors
R1     VD1    Vref   190000

** Transistors
M1     VD1    VD1    VDD    VDD    PMOS L=2 W=30
M2     VDD    VD1    Vo     VDD    PMOS L=2 W=30

.MODEL NMOS NMOS LEVEL = 3
+ TOX   = 200E-10      NSUB   = 1E17      GAMMA  = 0.5
+ PHI   = 0.7          VTO    = 0.8        DELTA  = 3.0
+ UO    = 650          ETA     = 3.0E-6     THETA  = 0.1
+ KP    = 120E-6       VMAX   = 1E5        KAPPA  = 0.3
+ RSH   = 0            NFS     = 1E12      TPG    = 1
+ XJ    = 500E-9       LD      = 100E-9
+ CGDO  = 200E-12     CGSO   = 200E-12   CGBO   = 1E-10
+ CJ    = 400E-6       PB      = 1          MJ      = 0.5
+ CJSW  = 300E-12     MJSW   = 0.5
*

.MODEL PMOS PMOS LEVEL = 3
+ TOX   = 200E-10      NSUB   = 1E17      GAMMA  = 0.6
+ PHI   = 0.7          VTO    = -0.9      DELTA  = 0.1
+ UO    = 250          ETA     = 0          THETA  = 0.1
+ KP    = 40E-6        VMAX   = 5E4       KAPPA  = 1
+ RSH   = 0            NFS     = 1E12      TPG    = -1
+ XJ    = 500E-9       LD      = 100E-9
+ CGDO  = 200E-12     CGSO   = 200E-12   CGBO   = 1E-10
+ CJ    = 400E-6       PB      = 1          MJ      = 0.5
+ CJSW  = 300E-12     MJSW   = 0.5

.end

```


Problem 20.4)

Solution:




We want to show, using SPICE, that the following equation is valid:

$$\frac{I_o}{I_{ref}} \approx 1 - \frac{2\Delta V_{thn}}{V_{GS} - V_{thn}}$$

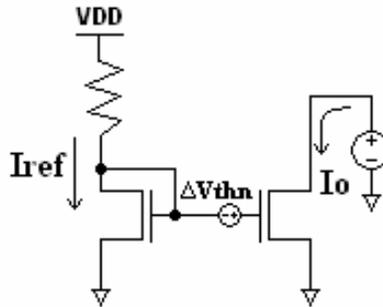Using the following circuit we'll use three different values for V_{GS} and simulate.



VGS=	<i>0.9V</i>	<i>1.05V</i>	<i>1.2V</i>
Io/Iref= (hand calculated)	<i>0.8</i>	<i>0.92</i>	<i>0.95</i>
Io/Iref= (simulated)	<i>0.85</i>	<i>0.97</i>	<i>0.99</i>

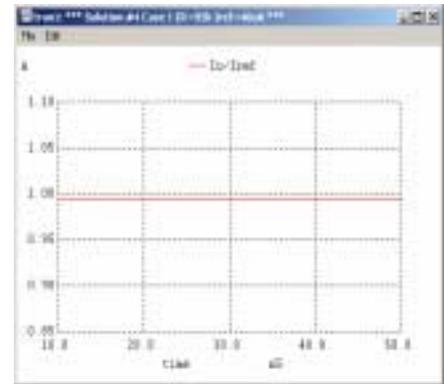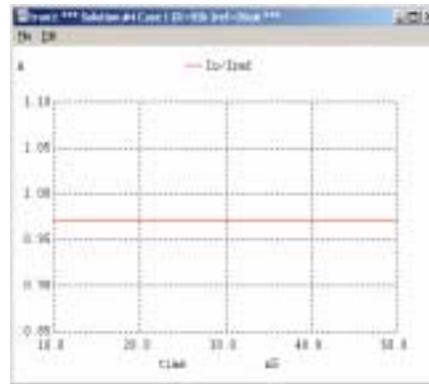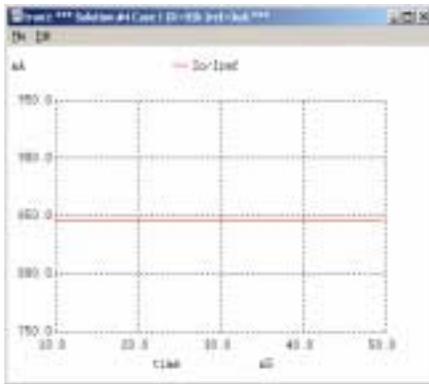

The values obtained from the sims differ slightly from the calculated values, this is due to the higher order terms being ignored in Eq. 20.8. We can see from the sims, and Eq. 20.8, increasing V_{GS} will minimize threshold voltage mismatches.

*** Solution #4 Case 1 (R=95k Iref=3uA) ***

```
.control
destroy all
run
let Io=-VI#branch
let Iref=-VDD#branch
plot Io/Iref
plot Io Iref
.endc
```

```
VDD VDD 0 DC 5
```

```
VI VI 0 DC 0.9
```

```
Vth VG1 VG2 10m
```

```
R1 VDD VG1 95k
```

```
*R1 VDD VG1 197.5k
```

```
*R1 VDD VG1 1.367MEG
```

```
M1 VG1 VG1 0 0 NMOS W=10u L=2u
```

```
M2 VI VG2 0 0 NMOS W=10u L=2u
```

*** Control Statements ***

```
*.OPTION ABSTOL=1u ITL4=100 RELTOL=0.01 VNTOL=.1mv
```

```
.tran .01n 50n 10n
```

Problem 20.5


Question:

Show, using simulations and hand-calculations, that by using a larger value of $V_{DS,sat}$ when designing bias circuit results in the MOSFETs entering the triode region earlier.

Solution:

By definition, $V_{DS,sat}$ is the V_{DS} at which the MOSFET transitions from the triode region to the saturation region of operation, when $V_{GS} > V_{THN}$. So, we would expect the MOSFET to enter the triode region earlier when designing with a higher $V_{DS,sat}$. For long-channel operation, $V_{DS,sat} = V_{GS} - V_{THN}$.

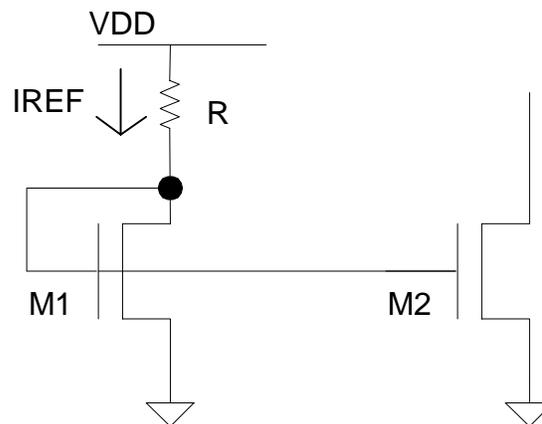Using the following circuit, it can be shown that using a larger $V_{DS,sat}$ in the design will cause the MOSFETs to enter the triode region earlier.



For long channel operation in saturation, neglecting channel-length modulation,

$$I_{REF} = KP_N \cdot \frac{W}{2L} (V_{GS} - V_{THN})^2 = KP_N \cdot \frac{W}{2L} (V_{DS,sat})^2$$

Solving for W yields,

$$W = \frac{2 \cdot I_{REF} \cdot L}{KP_N \cdot (V_{DS,sat})^2}$$


For the first design, we will use a $V_{DS,sat}=0.25V$.

Solving for W using values of $I_{REF}=20\mu A$, $L=2\mu m$, $KP_N=120\mu A/V^2$, and $V_{DS,sat}=0.25V$, results in $W=11\mu m$.

Also, we need to find the value of the resistor that will work with this circuit.

$$R = \frac{V_{DD} - V_{GS}}{I_{REF}} = \frac{5 - 1.05}{20\mu A} = 197.5k\Omega$$

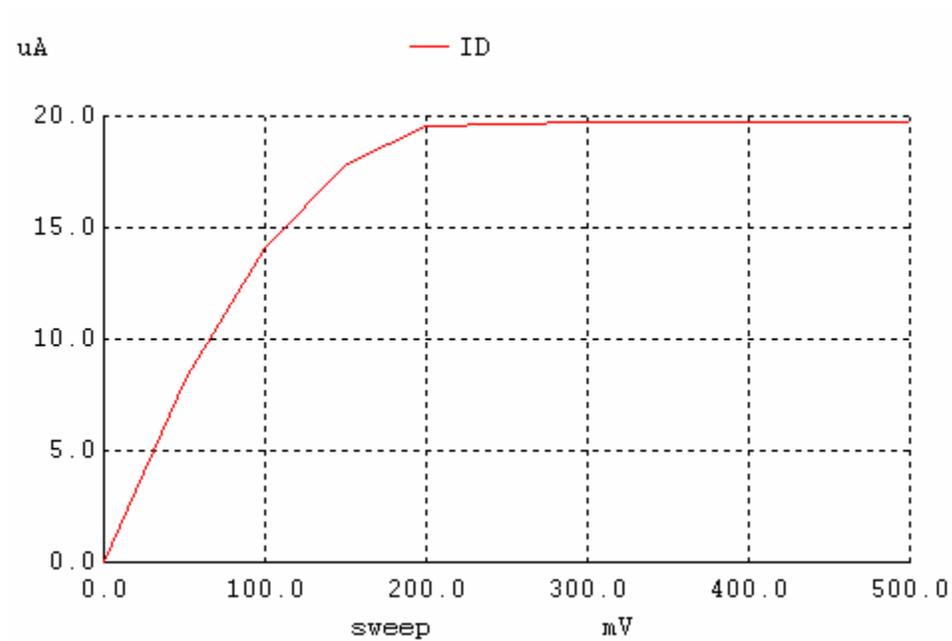Using the values of $W=11\mu m$ and $R=197.5k$ yields the following SPICE results. In this design, the M2 enters the triode region around $V_{DS}=200mV$.



Plot for design using $V_{DS,sat} = 0.25V$

For the second design, we will use a $V_{DS,sat}=0.15V$.

Remember,


$$W = \frac{2 \cdot I_{REF} \cdot L}{K P_N \cdot (V_{DS,sat})^2}$$

Solving for W using values of $I_{REF}=20\mu A$, $L=2\mu m$, $K P_N=120\mu A/V^2$, and $V_{DS,sat}=0.25V$, results in $W=30\mu m$.

Also, we need to find the value of the resistor that will work with this circuit.

$$R = \frac{V_{DD} - V_{GS}}{I_{REF}} = \frac{5 - 0.95}{20\mu A} = 192.5k\Omega$$

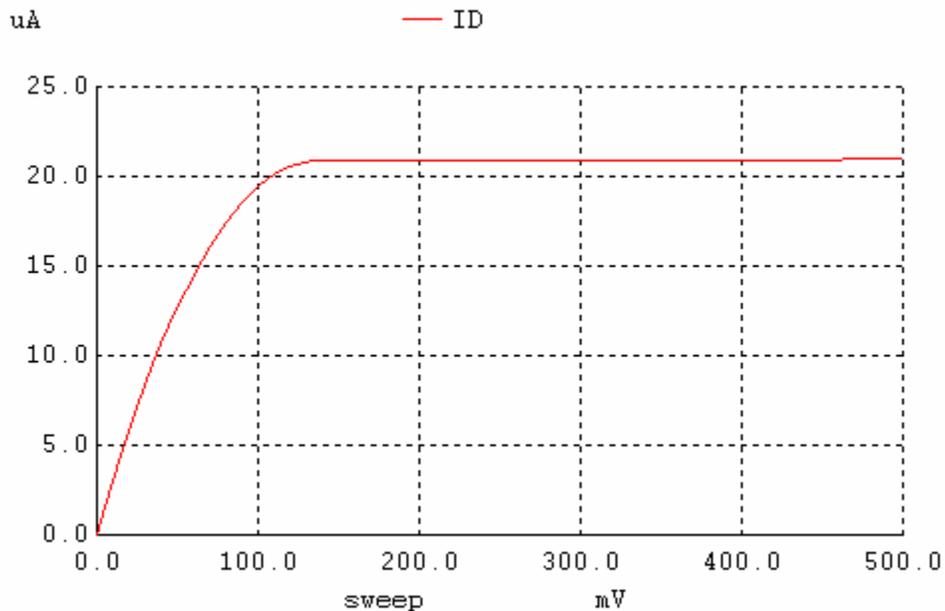Using the values of $W=30\mu m$ and $R=192.5k$ yields the following SPICE results. For this design, M2 enters the triode region around 120mV. Therefore, designing with a higher $V_{DS,sat}$ results in the MOSFET entering the triode region earlier.



Plot for design using $V_{DS,sat} = 0.15V$

SPICE netlists are shown on the following pages.

* EE511 Problem 20.5a

```
.control
destroy all
run
let ID=-Vd2#branch
plot ID
.endc
```

```
.options scale=1u
.DC Vd2 0 0.5 0.05

Vdd Vdd 0 DC 5
Vd2 Vd2 0 DC 0

M1 Vg1 Vg1 0 0 nmos W=11 L=2
M2 Vd2 Vg1 0 0 nmos W=11 L=2
R1 Vdd Vg1 197.5k
```

```
.MODEL NMOS NMOS LEVEL = 3
+ TOX = 200E-10 NSUB = 1E17 GAMMA = 0.5
+ PHI = 0.7 VTO = 0.8 DELTA = 3.0
+ UO = 650 ETA = 3.0E-6 THETA = 0.1
+ KP = 120E-6 VMAX = 1E5 KAPPA = 0.3
+ RSH = 0 NFS = 1E12 TPG = 1
+ XJ = 500E-9 LD = 100E-9
+ CGDO = 200E-12 CGSO = 200E-12 CGBO = 1E-10
+ CJ = 400E-6 PB = 1 MJ = 0.5
+ CJSW = 300E-12 MJSW = 0.5
*
```

```
.MODEL PMOS PMOS LEVEL = 3
+ TOX = 200E-10 NSUB = 1E17 GAMMA = 0.6
+ PHI = 0.7 VTO = -0.9 DELTA = 0.1
+ UO = 250 ETA = 0 THETA = 0.1
+ KP = 40E-6 VMAX = 5E4 KAPPA = 1
+ RSH = 0 NFS = 1E12 TPG = -1
+ XJ = 500E-9 LD = 100E-9
+ CGDO = 200E-12 CGSO = 200E-12 CGBO = 1E-10
+ CJ = 400E-6 PB = 1 MJ = 0.5
+ CJSW = 300E-12 MJSW = 0.5
```

```
.end
```

* EE511 Problem 20.5b

```
.control
destroy all
run
let ID=-Vd2#branch
plot ID
.endc
```

```

.options scale=1u
.DC      Vd2      0      0.5      0.005

Vdd      Vdd      0      DC      5
Vd2      Vd2      0      DC      0

M1       Vg1      Vg1      0      0      nmos    W=30 L=2
M2       Vd2      Vg1      0      0      nmos    W=30 L=2
R1       Vdd      Vg1      192.5k

```

```

.MODEL NMOS NMOS LEVEL = 3
+ TOX = 200E-10      NSUB = 1E17      GAMMA = 0.5
+ PHI = 0.7          VTO = 0.8        DELTA = 3.0
+ UO = 650           ETA = 3.0E-6      THETA = 0.1
+ KP = 120E-6        VMAX = 1E5        KAPPA = 0.3
+ RSH = 0            NFS = 1E12        TPG = 1
+ XJ = 500E-9        LD = 100E-9
+ CGDO = 200E-12     CGSO = 200E-12     CGBO = 1E-10
+ CJ = 400E-6        PB = 1           MJ = 0.5
+ CJSW = 300E-12    MJSW = 0.5
*

```

```

.MODEL PMOS PMOS LEVEL = 3
+ TOX = 200E-10      NSUB = 1E17      GAMMA = 0.6
+ PHI = 0.7          VTO = -0.9       DELTA = 0.1
+ UO = 250           ETA = 0          THETA = 0.1
+ KP = 40E-6         VMAX = 5E4        KAPPA = 1
+ RSH = 0            NFS = 1E12        TPG = -1
+ XJ = 500E-9        LD = 100E-9
+ CGDO = 200E-12     CGSO = 200E-12     CGBO = 1E-10
+ CJ = 400E-6        PB = 1           MJ = 0.5
+ CJSW = 300E-12    MJSW = 0.5

```

```

.end

```

Problem 20.6:

In Ex. 20.2 how does the gate voltage of M1/M2 change as V_{DD} is decreased? How does the V_{SG} change? Use SPICE to verify your answers.

Solution:

The following graph shows the I_o variation vs. V_{DD} for the circuit if Fig 20.11. It behaves as expected because once V_{DD} is large enough to supply a decent gate overdrive voltage V_{ovn} and force both M1 and M2 to operate in the saturation region.

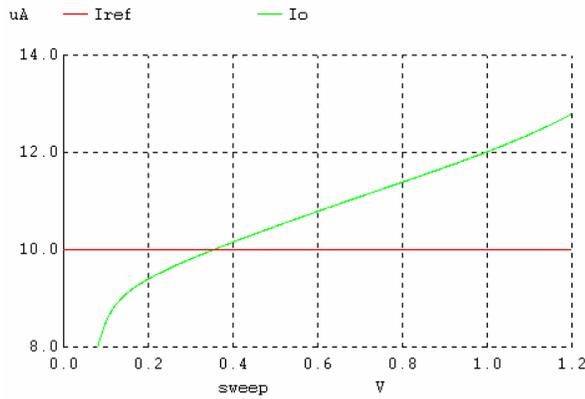


Figure 1. I_o and I_{ref} vs. V_{DD}

Since the I_{REF} current source is forcing M1 to provide a constant V_{SG} across M1 and M2, we would expect that V_{SG} would not change across V_{DD} . Figure 2 plots the gate voltage of M1 and M2 (V_{D1}) vs. V_{DD} . Notice that at any given point on the graph that $V_{DD} - V_{D1} = 350\text{mV}$. It is also apparent from the figure that V_{D1} (gate voltage of M1 and M2) linearly increases with V_{DD} .

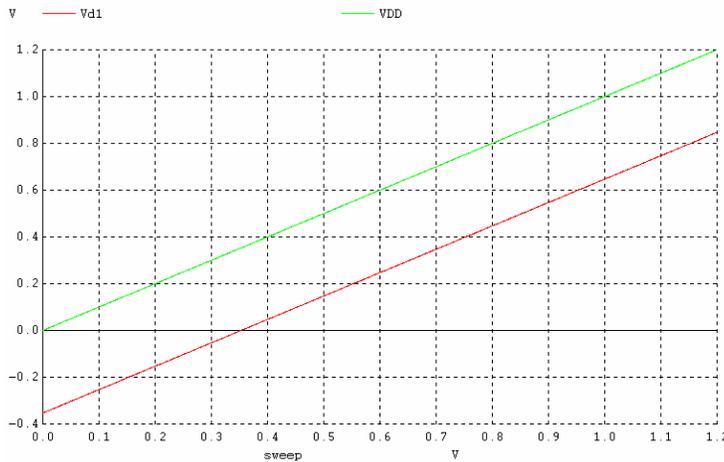


Figure 2. V_{D1} vs. V_{DD}

Netlist:

*** Problem 20.6 CMOS: Circuit Design, Layout, and Simulation ***

```
.control
destroy all
run
let Iref=Vmeas#branch
let Io=Vo#branch
plot Iref Io ylimit 8u 14u
plot Vd1 VDD
.endc
```

```
.option scale=50n
.dc VDD 0.0 1.2 1m
```


```
VDD  VDD  0      DC    1
Vo   Vo   0      DC    0
Vmeas Vmeas 0      DC    0
```

```
Iref  VD1  Vmeas DC    10u
M1    VD1  VD1   VDD   VDD   PMOS L=2 W=100
M2    Vo   VD1   VDD   VDD   PMOS L=2 W=100
```

* BSIM4 models

```
.model pmos pmos level = 14
.end
```

Problem 20.7

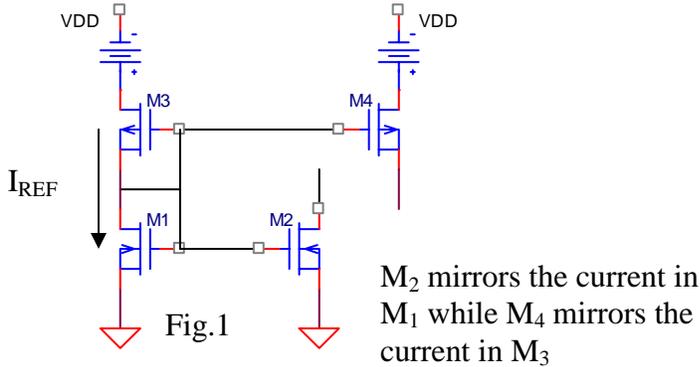

Assuming the long channel behavior we have

$$V_{DD} = V_{SG3} + V_{GS1}$$

$$V_{DD} = \sqrt{\frac{2 \cdot I_{REF}}{K_{P_P} \frac{w_3}{l_3}}} + V_{THP} + \sqrt{\frac{2 \cdot I_{REF}}{K_{P_N} \frac{w_1}{l_1}}} + V_{THN}$$

Thinking M₃ as a resistor in fig.1 to mirror the current in M₁ we solve for the size of M₃.

If minimum lengths MOSFETs are used we have L= 1μm and substituting the values from table 9.1 we get

$$5 = \sqrt{\frac{2.20}{40 \cdot \frac{w_3}{l_3}}} + 0.9 + \sqrt{\frac{2.20}{120 \cdot \frac{10}{1}}} + 0.8$$

$$\frac{w_3}{l_3} \approx 0.1 \quad \Rightarrow \quad \frac{w_3}{l_3} \approx \frac{10}{100}$$

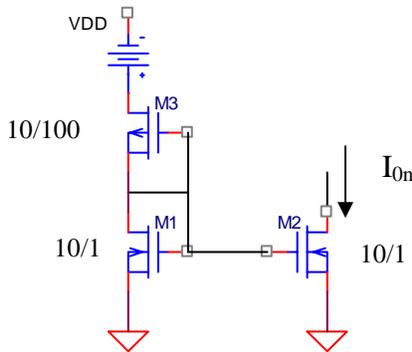


Fig.2 thinking M₃ (PMOS) as resistor

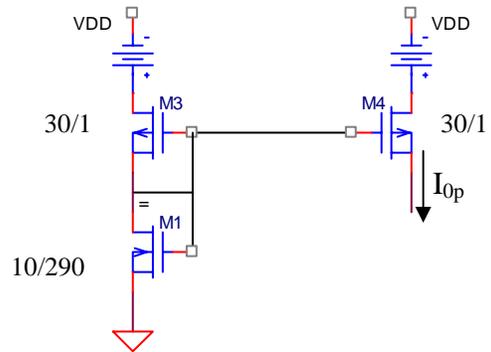


Fig.3 thinking M₁ (NMOS) as resistor

Thinking M_1 as a resistor in fig.1 to mirror the current in M_3 we solve for the size of M_1 ($L=1\mu\text{m}$)

$$5 = \sqrt{\frac{2.20}{40 \cdot \frac{30}{1}}} + 0.9 + \sqrt{\frac{2.20}{120 \cdot \frac{w_1}{l_1}}} + 0.8$$

$$\frac{w_1}{l_1} \approx 0.0342 \Rightarrow \frac{w_1}{l_1} \approx \frac{10}{290}$$

SIMULATIONS

SOURCE CODE

```
.control
destroy all
run
let Iop=Vop#branch
let Ion=Von#branch
plot Iop
plot Ion
.endc

.option scale=1u
.dc VDD 4.5 5.5 1m


VDD VDD 0 DC 5
Vop Vop 0 DC 0
Von VDD Von DC 0

M1n Vbiasn Vbiasn 0 0 NMOS L=1 W=10
M2n Vbiasn Vbiasn VDD VDD PMOS L=100 W=10


M1p Vbiasp Vbiasp 0 0 NMOS L=290 W=10
M2p Vbiasp Vbiasp VDD VDD PMOS L=1 W=30

Mn Von Vbiasn 0 0 NMOS L=1 W=10

Mp Vop Vbiasp VDD VDD PMOS L=1 W=30
```

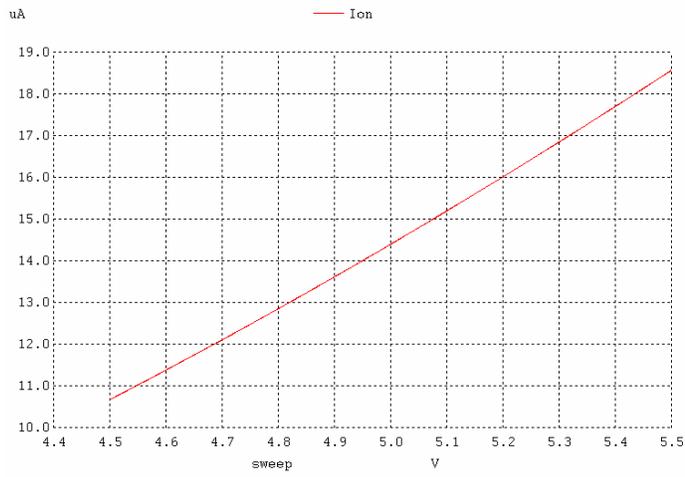

Thinking M_3 (PMOS) as resistor

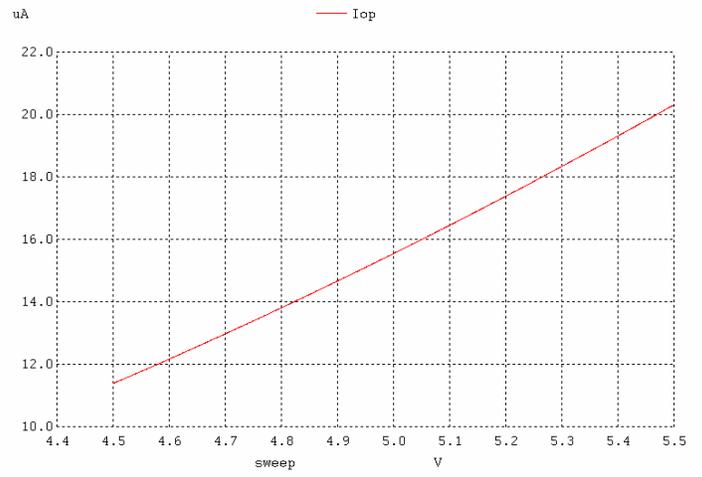

Thinking M_1 (NMOS) as resistor

Problem 20.8


The main portion of the circuit that could cause this anomaly is the 'Start Up Circuit'. There are two possible stable conditions in which the voltage reference beta multiplier might be operating...

- (1) The normal stable condition for which the circuit was designed.
- (2) When the gates of M3/M4 are at V_{DD} and the gates of M1/M2 are at 0(zero).

Refer to figure 20.14 for circuit.

When the gates of M3/M4 are at V_{DD} and the gates of M1/M2 are at 0(zero). When in this state the gate of MSU1 is at ground and so it is off. The gate of MSU2 would be somewhere around V_{thp} (because long L Pmos would have large drop across it) which would turn on MSU3. The function of MSU3 is to discharge the voltage on the gates of M3/M4 to the gates of M1/M2. Thus the circuit comes back to the desired operating point for which it was designed. In other words it can be said that the voltage at the PMOS gates leaks through the resistor (MSU3) to charge the capacitors at the gates of M1/M2. Thus the gate terminal of M1 increases and turns on the Mosfet MSU1, which would pull gate of MSU3 to ground and turn it off. But when the length of MSU2 is decreased there would a large voltage at the gate of MSU3, which MSU1 can't pull it to ground in order to turn it off because of which MSU3 would be always on and I_{ref} would be increasing with V_{DD} .

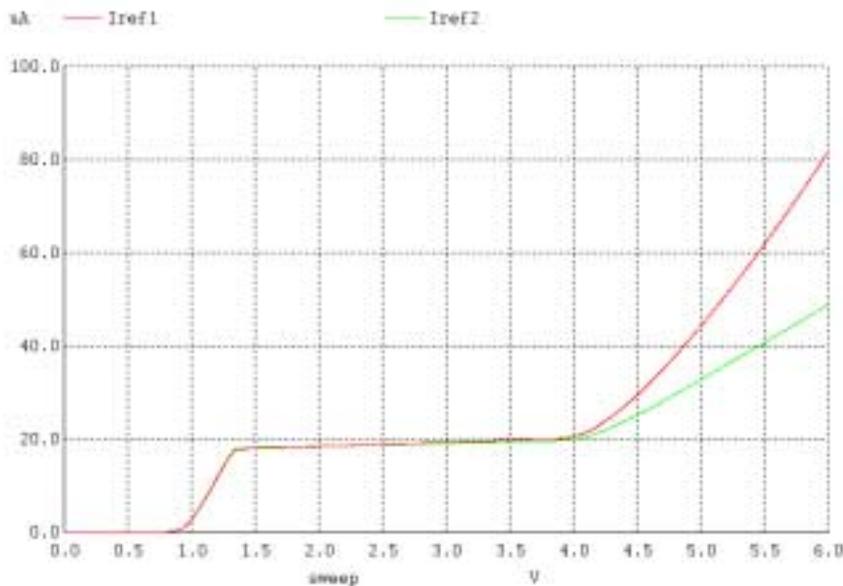Simulation Results obtained when MSU2 length is decreased to 10um.



```

.control
destroy all
run
let Iref1=Vmeas1#branch
let Iref2=Vmeas2#branch
plot Iref1 Iref2
.endc
.option scale=1u
.dc VDD 0 6 1m

```

```

VDD      VDD  0      DC    5
Vop      Vop  0      DC    0
Von      VDD  Von    DC    0
Vmeas1   Vmeas1  0      DC    0
Vmeas2   Vmeas2  0      DC    0

```

```

M1 Vbiasn Vbiasn Vmeas1  0      NMOS L=2 W=10
M2 Vbiasp Vbiasn Vr      0      NMOS L=2 W=40
M3 Vbiasn Vbiasp VDD    VDD    PMOS L=2 W=30
M4 Vbiasp Vbiasp VDD    VDD    PMOS L=2 W=30

```

```

Rbias    Vr      vmeas2  6.5k

```


```

MSU1     Vsur  Vbiasn 0      0      NMOS L=2 W=10
MSU2     Vsur  Vsur   VDD    VDD    PMOS L=10 W=10
MSU3     Vbiasp Vsur  Vbiasn 0      NMOS L=1 W=10

```

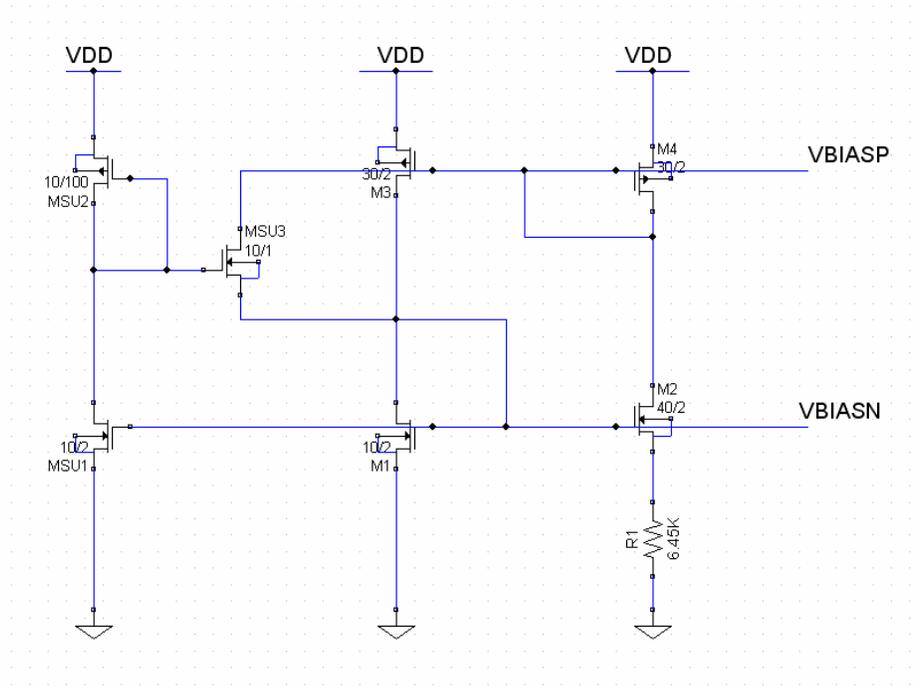PROBLEM 20.9

To estimate the value of voltage across resistor in the circuit below by hand calculations.



Let's first estimate the value of resistor for a bias current of $20\mu\text{A}$.

Since the resistor is connected to source, we can see from the circuit that the gate to source voltage of M1 is the sum of voltage drop across the resistor R_1 and gate to source voltage of M2.

$$\text{i.e. } V_{GS1} = V_{GS2} + I_{REF} \cdot R_1 \text{ -----(1)}$$

For long channel we can write V_{GS} to be

$$V_{GS} = \sqrt{\frac{2 \cdot I_D \cdot L}{K P_n W}} + V_{THN}$$

The MOSFET M2 is scaled such that the excess voltage is dropped across the resistor R_1 , i.e. $W_2 = K \cdot W_1$. Since width of M2 is increased it requires less V_{GS} to conduct the same I_{REF} , and excess voltage drop occurs across the resistor R_1 .

Therefore eq(1) can be written as

$$\sqrt{\frac{2 \cdot I_{REF} \cdot L_1}{K P_n W_1}} + V_{THN} = \sqrt{\frac{2 \cdot I_{REF} \cdot L_2}{K P_n \cdot K \cdot W_2}} + V_{THN} + I_{REF} \cdot R_1$$

Solving for I_{REF} we get

$$I_{REF} = \frac{2}{R^2 K P_n \frac{W_1}{L_1}} \left(1 - \frac{1}{\sqrt{K}} \right)^2$$

Solving for R_1 , we can rewrite the above equation as

$$R_1 = \sqrt{\frac{2}{I_{REF} K P_n \frac{W_1}{L_1}}} \left(1 - \frac{1}{\sqrt{K}}\right)$$

If we bias the transistor M1 with a reference current of $20\mu\text{A}$ and Choosing $K=4$ i.e. $W_2= 4.W_1$ and solving our circuit for R_1 by substituting the values of K, P_n, W_1, L_1 we get

$$R_1 = \sqrt{\frac{2}{20\mu\text{A} \cdot 120 \frac{\mu\text{A}}{\text{V}^2} \frac{10}{2}}} \left(1 - \frac{1}{\sqrt{4}}\right) = 6.45\text{K}\Omega$$

Having determined the value of resistor then the voltage drop across it is given by $I_{REF} \times R_1$

$$20\mu\text{A} \cdot 6.45\text{K}\Omega = 0.129\text{V}$$

From simulations :


Voltage drop across the resistor = 0.1279V

Voltage drop across the gate and source of M2 = 0.945V

Voltage drop across the gate and source of M1 = 1.070V

$$\therefore V_{GS1} = V_{GS2} + I_{REF} \cdot R_1$$

$$1.07 = 0.945 + 0.1279$$

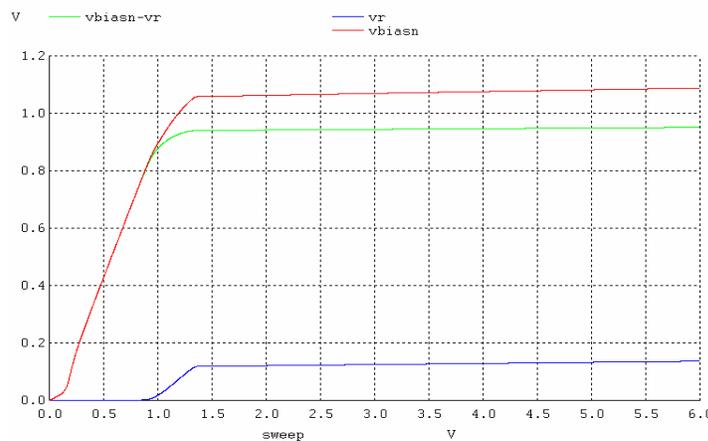

NOTE:

For a particular value of $K = 4$ we can also call this β multiplier circuit as constant g_m bias circuit because the value of R then becomes

$$R = \sqrt{\frac{2}{I_{REF} K P_n \frac{W_1}{L_1}}} \left(1 - \frac{1}{\sqrt{4}}\right) = \sqrt{\frac{1}{2 \cdot I_{REF} K P_n \frac{W_1}{L_1}}} = \frac{1}{g_m}$$

Problem 10)

The reference circuit in Fig. 20.22 provides improved current reference for short channel devices. To see the stability of this circuit with changes in VDD, we couple a 50mv square wave signal at 100 MHz to VDD. So we have a square wave VDD oscillating between 1 and 1.05v at 100MHz.

Net list

```

*prob20.10*
.control
destroy all
run
let Iref1=Vmeas1#branch
let Iref2=Vmeas2#branch
plot Iref1
plot Iref2
.endc
.option scale=50n
.tran .1n 400n

VDD VDD 0 DC 1 pulse 1 1.05 0 0 0 5n 10n
Vop Vop 0 DC 0
Von VDD Von DC 0
Vmeas1 Vmeas1 0 DC 0
Vmeas2 Vmeas2 0 DC 0



M1 Vbiasn Vbiasn Vmeas1 0 NMOS L=2 W=50
M2 Vreg Vreg Vr 0 NMOS L=2 W=200
M3 Vbiasn Vbiasp VDD VDD PMOS L=2 W=100
M4 Vreg Vbiasp VDD VDD PMOS L=2 W=100
Rbias Vr vmeas2 5.5k

*amplifier
MA1 Vamp Vreg 0 0 NMOS L=2 W=50
MA2 Vbiasp Vbiasn 0 0 NMOS L=2 W=50
MA3 Vamp Vamp VDD VDD PMOS L=2 W=100
MA4 Vbiasp Vamp VDD VDD PMOS L=2 W=100
Mcp VDD Vbiasp VDD VDD PMOS L=100 W=100
Mc n 0 Vbiasn 0 0 NMOS L=100 W=100

*start-up stuff
MSU1 Vsur Vbiasn 0 0 NMOS L=2 W=50
MSU2 Vsur Vsur VDD VDD PMOS L=20 W=10
MSU3 Vbiasp Vsur Vbiasn 0 NMOS L=1 W=10

* BSIM4 models
.model nmos nmos level = 14
-----
.model pmos pmos level = 14
-----
.end


```

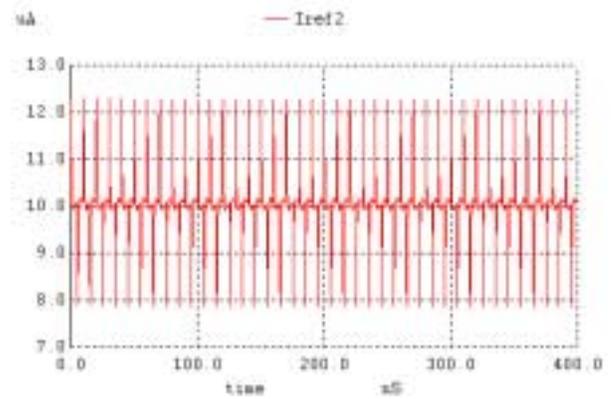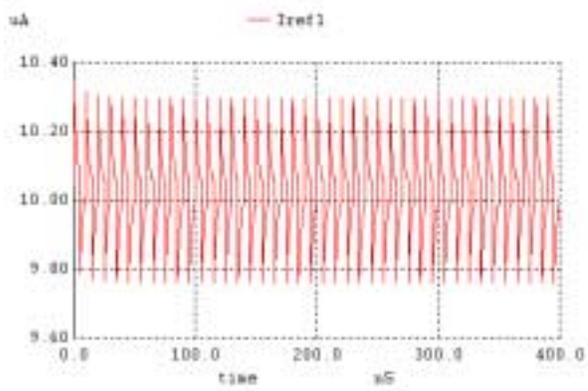


We can observe the effects of high-frequency noise causing huge variations in Iref1 and Iref2. So the reference circuit is very unstable with changes in VDD.

Effect of size of MCP and MCN

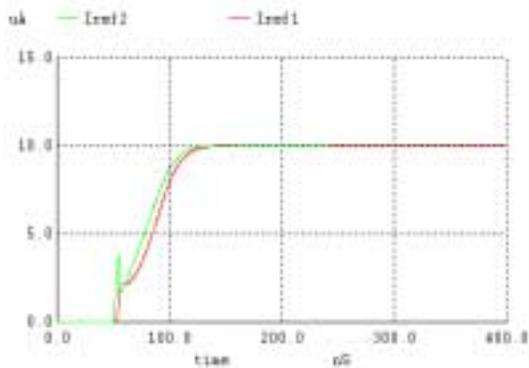To see the effect of size of MCP and MCN, let's reduce both sizes from 100/100 to 100/2. We can clearly see that reducing the size of MCP and MCN makes the circuit unstable.



Size – 100/100

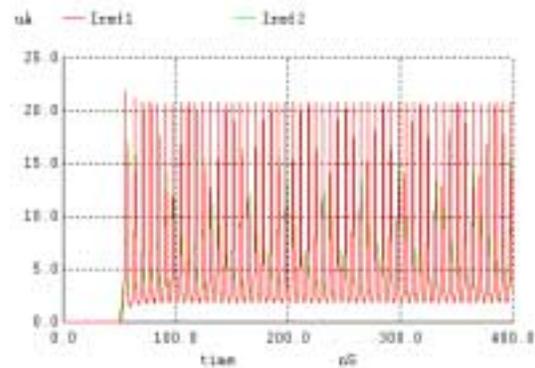

Size – 100/2

20.11

If we assume, as we did in Example 20.4, that dV_{SG}/dT is approximately equal to dV_{THP}/dT , the answer is basically -0.6 mV per degree C.

No lengthy derivations are needed.

Problem 20.12

I used the beta-multiplier in Fig 20.22 (Pg 20.17) except I changed the value of the resistor to 1.67K which I calculated by substituting values used in Table 9.2 in Equation 20.38(Pg 20.22)

The equation is as follows:

$$R = \frac{2}{(-.6E - 3 * 120E - 6 * 50 / 2)} \left[1 - \frac{1}{2} \right] \left[2E - 3 + \left(\frac{-1.5}{300} \right) \right]$$

R=1.67K which I used in my simulations for Fig 20.22

SPICE STATEMENTS

*** Problem 20.12 CMOS: Circuit Design, Layout, and Simulation ***

```
.control
destroy all
set temp=0
run
set temp=25
run
set temp=50
run
set temp=75
run
set temp=100
run
plot tran1.vbiasn tran2.vbiasn tran3.vbiasn tran4.vbiasn tran5.vbiasn
.endc

.option scale=50n
.tran 1m 1

VDD VDD 0 DC 1
*Vop Vop 0 DC 0
*Von VDD Von DC 0
Vmeas1 Vmeas1 0 DC 0
Vmeas2 Vmeas2 0 DC 0

M1 Vbiasn Vbiasn Vmeas1 0 NMOS L=2 W=50
M2 Vreg Vreg Vr 0 NMOS L=2 W=200
M3 Vbiasn Vbiasp VDD VDD PMOS L=2 W=100
M4 Vreg Vbiasp VDD VDD PMOS L=2 W=100

Rbias Vr vmeas2 1.67k RMOD
```


```
.model RMOD R TC1=0.002
```

```
*amplifier
```

```
MA1 Vamp Vreg 0 0 NMOS L=2 W=50  
MA2 Vbiasp Vbiasn 0 0 NMOS L=2 W=50  
MA3 Vamp Vamp VDD VDD PMOS L=2 W=100  
MA4 Vbiasp Vamp VDD VDD PMOS L=2 W=100
```

```
*start-up stuff
```
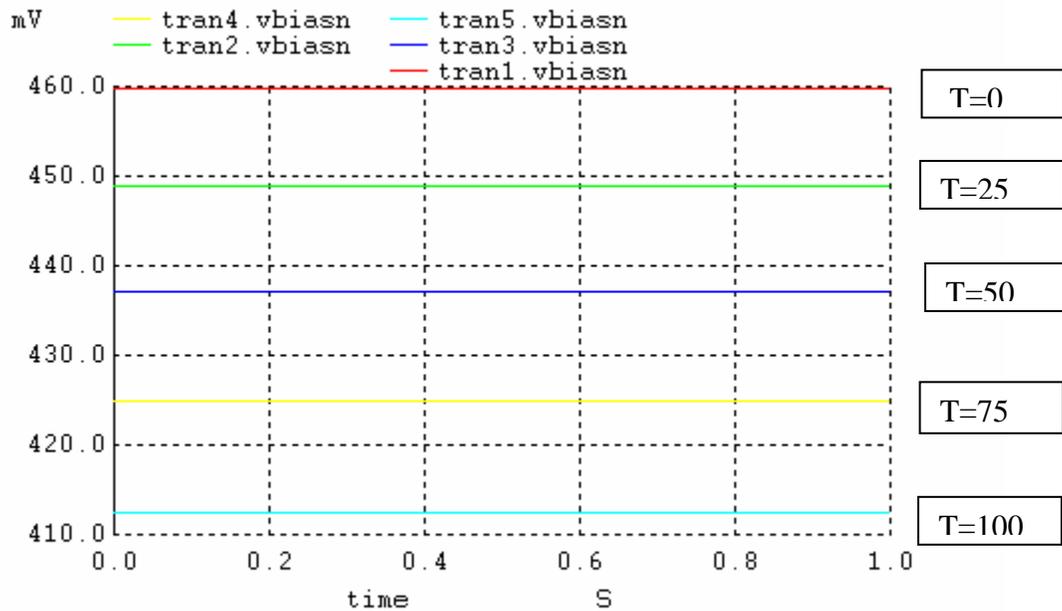
```
MSU1 Vsur Vbiasn 0 0 NMOS L=2 W=50  
MSU2 Vsur Vsur VDD VDD PMOS L=20 W=10  
MSU3 Vbiasp Vsur Vbiasn 0 NMOS L=1 W=10
```



The variation is around $-50\text{mV}/100\text{C}$ or $500\mu\text{V}/\text{C}$

Because we do not consider the effect of velocity saturation at lower temperatures the long channel equations can be used for the calculations.

Problem Solution for 20.13 :

Including threshold offset voltage in equation 20.42 we have:

$$V_{gs1} = n V_t \ln[(I_{ref} L_1)/(I_{do} W_1)] + V_{thn} + \Delta V_{thn} \text{ and}$$

$$V_{gs2} = n V_t \ln[(I_{ref} L_1)/(I_{do} K W_1)] + V_{thn}$$

$$\text{Now } I_{ref} = (V_{gs1} - V_{gs2})/R$$

$$I_{ref} = [n V_t \ln(K) + \Delta V_{thn}] / R$$

Using value for $K=4$ and $n=1$ and we obtain

$$I_{ref} = (1/R) (35\text{mV} + \Delta V_{thn})$$

If we want to tolerate 30% of current change it means we can tolerate $\Delta V_{thn} = 10.5$ mV change in threshold voltage. Figure 1 shows simulation results for beta multiplier ($I_{ref}=10$ nA) including threshold voltage mismatch. From the figure we can see that at 30% tolerance of current (13 nA) we have a threshold voltage mismatch at about 10 mV.



Figure 1: WinSpice simulation results for Beta multiplier with threshold voltage mismatch form 0 to 40 mV.

Problem 20.14)

Before applying a test voltage, we can estimate the output resistance by plotting the DC current versus the voltage. From this plot, the output resistance is the inverse of the slope of I_D . Using spice to plot r_o ($r_o = 1/\text{deriv}(I_D)$) we find that r_o is approximately 164k ohms. These two plots are seen below in figures 1 & 2.

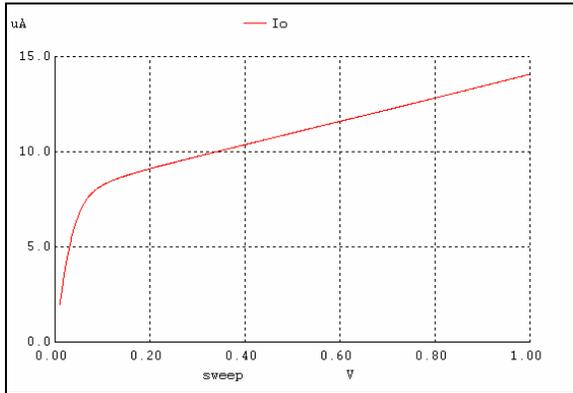


Figure 1: I_o vs V_o .

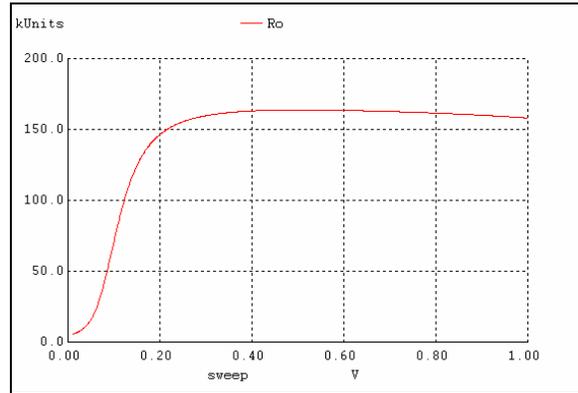


Figure 2: r_o vs V_o .

Next we apply the AC test voltage. In this case $r_o = \frac{v_T}{i_T}$. Using spice, the output resistance is about 158k ohms as seen in figure 3 below. (The AC test voltage must be placed in series with the DC voltage source.)

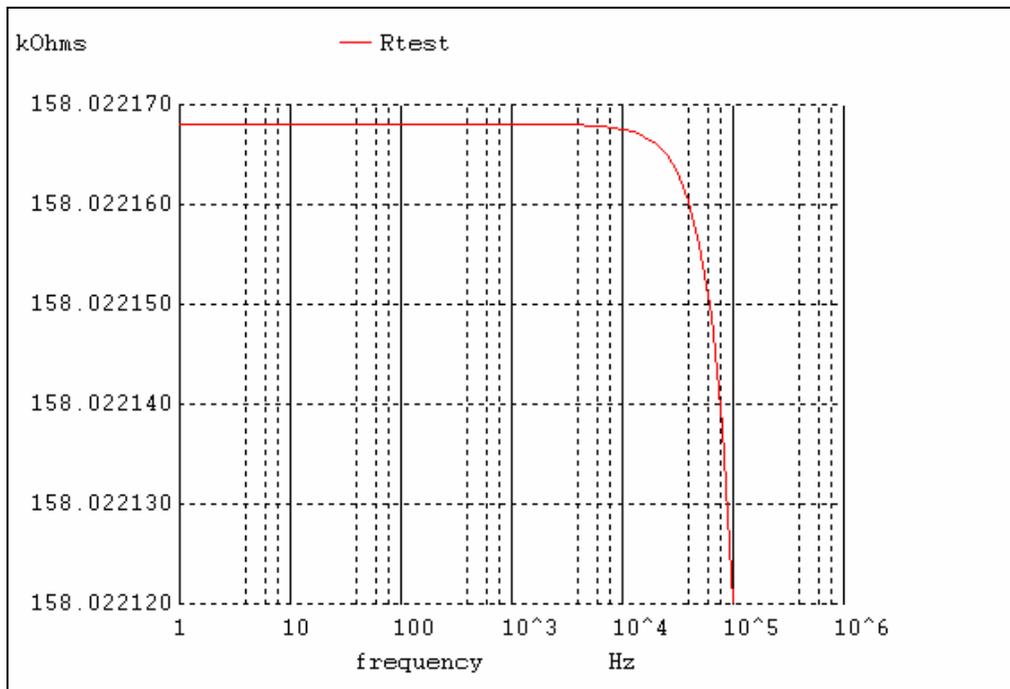


Figure 3: r_o as a function of v_T/i_T (ac).

*** Problem 20.14 ***

```
.control
destroy all
run
let Itest = abs(Vtest#branch)
plot Itest
let Rtest = (Vtest/Itest)
plot Rtest
.endc

.option scale=50n
.ac DEC 10 1 100K

VDD VDD 0 DC 1
Vo Vo Vtest DC 1 AC 0
Vtest Vtest 0 DC 0 AC 10m

X1 VDD Vbiasp Vbiasn bmrefs
M1 Vo Vbiasn 0 0 NMOS L=2 W=50

.subckt bmrefs VDD Vbiasp Vbiasn
M1 Vbiasn Vbiasn 0 0 NMOS L=2 W=50
M2 Vreg Vreg Vr 0 NMOS L=2 W=200
M3 Vbiasn Vbiasp VDD VDD PMOS L=2 W=100
M4 Vreg Vbiasp VDD VDD PMOS L=2 W=100

Rbias Vr 0 5.5k

*amplifier
MA1 Vamp Vreg 0 0 NMOS L=2 W=50
MA2 Vbiasp Vbiasn 0 0 NMOS L=2 W=50
MA3 Vamp Vamp VDD VDD PMOS L=2 W=100
MA4 Vbiasp Vamp VDD VDD PMOS L=2 W=100

*start-up stuff
MSU1 Vsur Vbiasn 0 0 NMOS L=2 W=50
MSU2 Vsur Vsur VDD VDD PMOS L=20 W=10
MSU3 Vbiasp Vsur Vbiasn 0 NMOS L=1 W=10
.ends
```

Figure 4: Netlist used when applying a test voltage to find r_o .

20.15. Find the voltages on the drain, gate, and source terminals of M1 – M4 in Figure 20.29 using the data in Table 9.1.

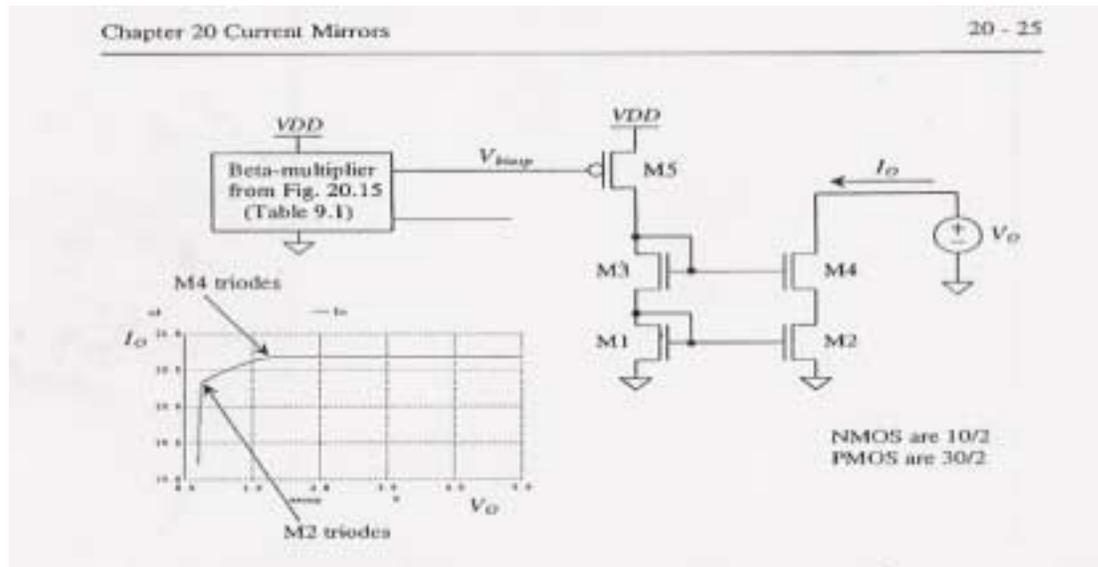



Figure 20.29

V_{biasp} is at $V_{DD} - 1.15V$ which sets the V_{SG} of M5 at 1.15V and I_{D} for M5 at 20uA since it is a 30/2 PMOS (Table 9.1). Since both M1 and M2 are connected in a diode configuration with 20uA of current, their V_{GS} voltages will be 1.05V. This sets the gate voltage for M1 and M2 at 1.05V and the gate voltage of M3 and M4 and the drain voltages of M5 and M3 at 2.1V. The drain voltage of M2 and the source voltage of M4 will be 1.05V or a V_{GS} voltage (1.05V) below the gate voltage of M4. To keep M4 operating in the saturation region, the V_{DS} for M4 must be greater than or equal to a V_{DSSAT} voltage (0.25V). The drain of M4 will be greater than or equal to 1.3V and the IV plot for this node is shown in the graph in Figure 20.29.

Simulation results had V_{biasp} at 3.85V, gate voltage of M1 and M2 at 1.08V, and the gate voltage of M3 and M4 at 2.4V. The V_{GS} of M3 and M4 are slightly higher than the table values due to the body effect because the bulk is more negatively biased than the source. The drain of M2 is at 1.08V and the IV plot for the drain of M4 is shown in Figure 20.29. The drain of M4 must be greater than or equal to 1.29V to remain in saturation.

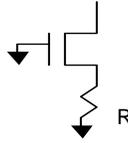20.16)

If the MOSFET below is operating in the saturation region determine the small-signal resistance looking into its drain



Apply a test voltage v_t to the drain of the MOSFET then calculate the current (i_t) in the MOSFET. Then solve for v_t/i_t .

$$i_t = V_{GS} gm + \frac{V_t + V_{GS}}{r_o}$$

$$V_{GS} = -i_t R$$

$$i_t = -i_t R \cdot gm + \frac{V_t - i_t R}{r_o}$$

$$i_t - \frac{V_t}{r_o} = -i_t R \cdot gm - \frac{i_t R}{r_o}$$

$$-\frac{V_t}{i_t} = -R \cdot gm \cdot r_o - R - r_o$$

$$\frac{V_t}{i_t} = +R \cdot gm \cdot r_o + R + r_o$$

$$R_o = \frac{V_t}{i_t} = r_o(1 + gmR) + R \approx r_o(1 + gmR)$$

20.17) To calculate the size of the MWS transistor when the transistor M3 enters the triode region using long channel values in figure 20.38.

We know the $I_{d3} = 20\mu\text{A}$, and the $V_{d3} = V_{gs}$, so when the transistor is in triode we have

$$I_{d3} = K_{Pn} * (W/L) * [(V_{gs} - V_{thn})V_{ds} - ((V_{ds}^2)/2)]$$

We know all the values except for V_{gs} , so solving the above equation by substituting values from Table 9.1, we get

$$V_{gs} = 1.6\text{V}$$

Now using this value of V_{gs} we find the size of MWS transistor

$$W_{mws}/L_{mws} = 1/5 \text{ (approx.)}$$

So we take a value of **10/10 or 10/9 for the W/L for the MWS transistor.**

On the sim, I calculated the value of the o/p resistance for $w=7$ and $w=10$ to show how this affects the o/p resistance.

Netlist

*** Hw 20.17_a CMOS: Circuit Design, Layout, and Simulation ***

```
.control
destroy all
```

```
run
```

```
let Io=-Vo#branch
```

```
let ro=1/deriv(Io)
```

```
let Id3=vdummy#branch
```

```
let rd3=1/deriv(Id3)
```

```
plot ro
```

```
plot Io
```

```
.endc
```

```
.option scale=1u
```

```
.dc Vo 0.25 5 1m
```

```
VDD VDD 0 DC 5
```

```
Vo Vo 0 DC 0
```

```
vdummy vd5b vd3 DC 0
```

```
X1 VDD Vbiasp Vbiasn bmrefl
```

```
M1 Vd1 Vd3 0 0 NMOS L=2 W=10
```

```
M2 Vd2 Vd3 0 0 NMOS L=2 W=10
```

```
M3 Vd3 Vg3 Vd1 0 NMOS L=2 W=10
```

```
MWS Vg3 Vg3 0 0 NMOS L=7 W=10
```

```
M4 Vo Vg3 Vd2 0 NMOS L=2 W=10
```

```
M5a Vg3 Vbiasp VDD VDD PMOS L=2 W=30
```

```
M5b Vd5b Vbiasp VDD VDD PMOS L=2 W=30
```

```
.subckt bmrefl VDD Vbiasp Vbiasn
```

```
M1 Vbiasn Vbiasn 0 0 NMOS L=2 W=10
```

```
M2 Vbiasp Vbiasn Vr 0 NMOS L=2 W=40
```

```

M3  Vbiasn Vbiasp VDD  VDD  PMOS L=2 W=30
M4  Vbiasp Vbiasp VDD  VDD  PMOS L=2 W=30

```

```



Rbias Vr    0    6.5k

```


```

MSU1 Vsur  Vbiasn 0    0    NMOS L=2 W=10
MSU2 Vsur  Vsur   VDD  VDD  PMOS L=100 W=10
MSU3 Vbiasp Vsur  Vbiasn 0    NMOS L=1 W=10
.ends

```

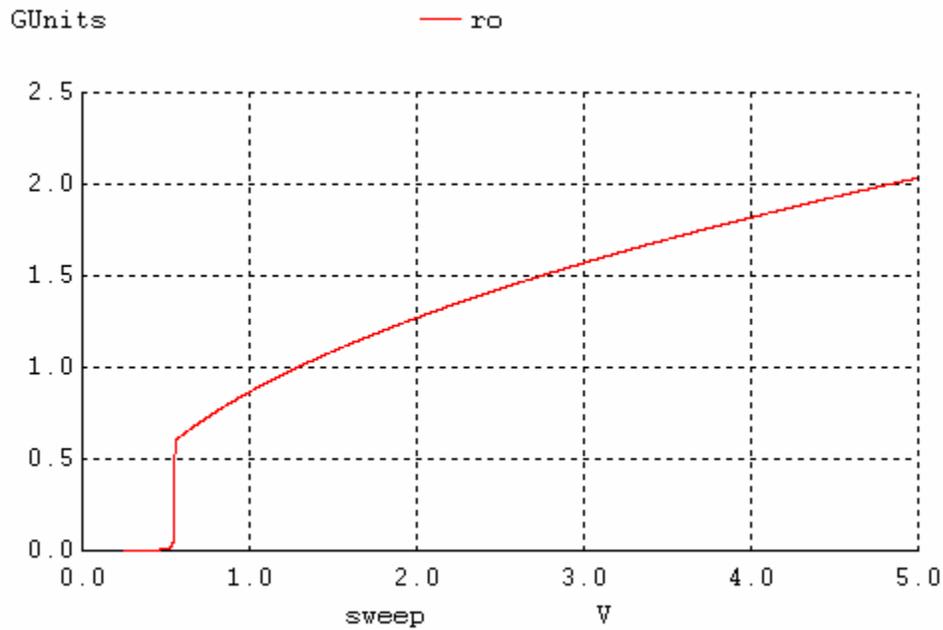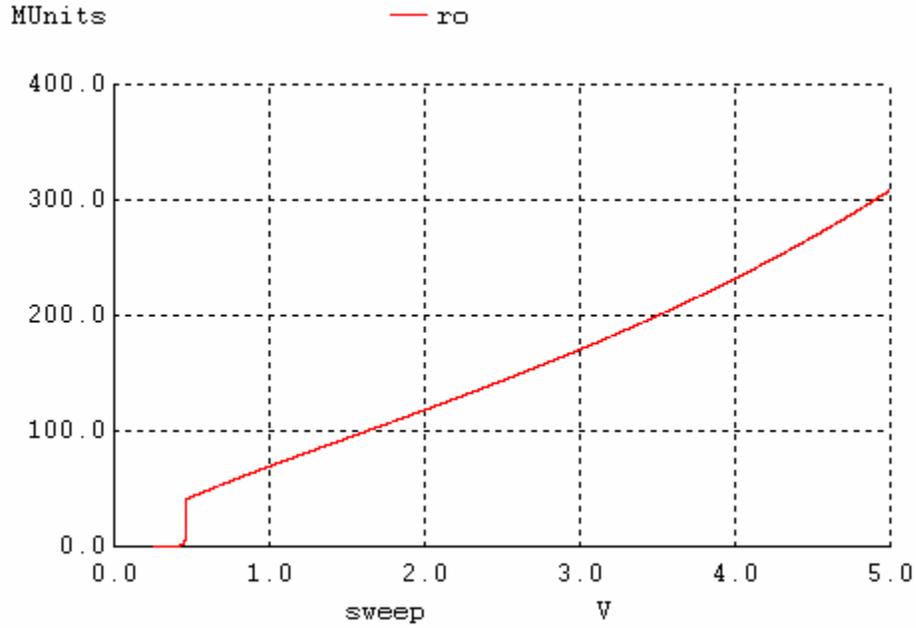

20.18 Solution:

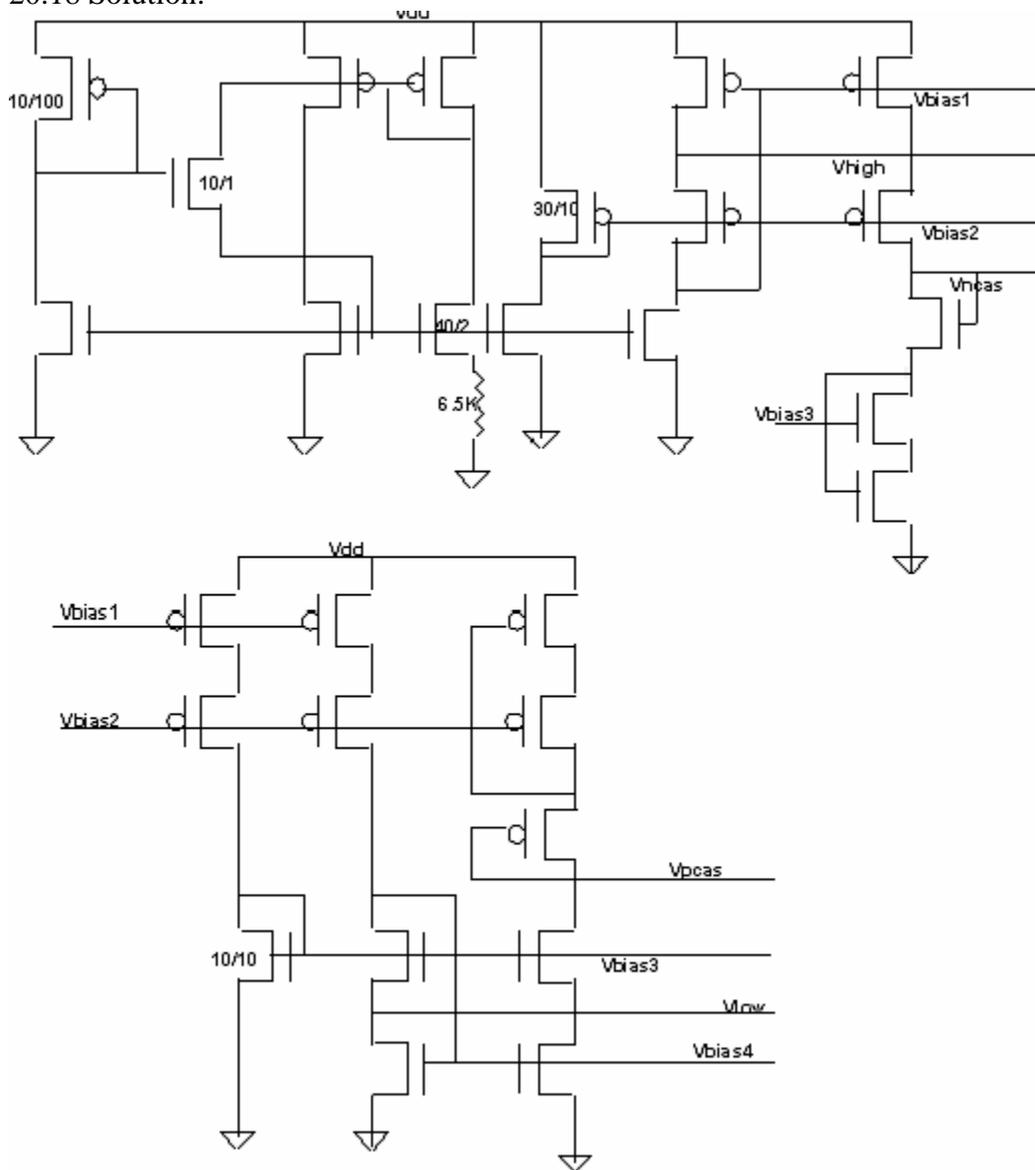

From above figure in order to keep circuit in saturation

$$\begin{aligned}
 V_{bias1} &= V_{dd} - V_{sgp} &= 5 - 1.15 &= 3.58\text{v} \\
 V_{high} &= V_{dd} - V_{sdsat} &= 5 - 0.25 &= 4.75\text{v} \\
 V_{bias2} &= V_{dd} - (V_{sgp} + V_{sdsat}) &= 5 - 1.4 &= 3.6\text{v} \\
 V_{ncas} &= V_{gsn} + V_{gsn} &= 1.05 + 1.05 &= 2.1\text{v} \\
 V_{pcas} &= V_{dd} - (V_{sgp} + V_{sgp}) &= 5 - 2.3 &= 2.7\text{v} \\
 V_{bias3} &= V_{gsn} + V_{dssat} &= 1.05 + 0.25 &= 1.3\text{v} \\
 V_{low} &= V_{dssat} &= &= 0.25\text{v} \\
 V_{bias4} &= V_{gs} &= &= 1.05\text{v}
 \end{aligned}$$

```

*** Assign 20.18  CMOS: Circuit Design, Layout, and Simulation ***
.control
destroy all
run
print vbias1 vhigh vbias2 vncas vpcas vbias3 vlow vbias4
.endc
.option scale=1u rshunt=1e9
.op
VDD  VDD  0      DC    5
Vop  Vop   0      DC    5
Xbias VDD  Vbias1 Vbias2 Vbias3 Vbias4 Vhigh Vlow Vncas Vpcas bias
M2P  Vdp2 Vbias1      VDD  VDD  PMOS L=2 W=30
M4P  Vop  Vbias2      Vdp2 VDD  PMOS L=2 W=30
.subckt bias VDD Vbias1 Vbias2 Vbias3 Vbias4 Vhigh Vlow Vncas Vpcas
MN1  Vbias2      Vbiasn      0      0      NMOS L=2 W=10
MN2  Vbias1      Vbiasn      0      0      NMOS L=2 W=10
MN3  Vncas Vncas vn1  0      NMOS L=2 W=10
MN4  vn1  Vbias3      vn2  0      NMOS L=2 W=10
MN5  vn2  vn1  0      0      NMOS L=2 W=10
MN6  Vbias3      Vbias3      0      0      NMOS L=10 W=10
MN7  Vbias4      Vbias3      Vlow  0      NMOS L=2 W=10
MN8  Vlow Vbias4      0      0      NMOS L=2 W=10
MN9  Vpcas Vbias3      vn3  0      NMOS L=2 W=10
MN10 vn3  Vbias4      0      0      NMOS L=2 W=10

MP1  Vbias2      Vbias2      VDD  VDD  PMOS L=10 W=30
MP2  Vhigh Vbias1      VDD  VDD  PMOS L=2 W=30
MP3  Vbias1      Vbias2      Vhigh VDD  PMOS L=2 W=30
MP4  vp1  Vbias1      VDD  VDD  PMOS L=2 W=30
MP5  Vncas Vbias2      vp1  VDD  PMOS L=2 W=30
MP6  vp2  Vbias1      VDD  VDD  PMOS L=2 W=30
MP7  Vbias3      Vbias2      vp2  VDD  PMOS L=2 W=30
MP8  vp3  Vbias1      VDD  VDD  PMOS L=2 W=30
MP9  Vbias4      Vbias2      vp3  VDD  PMOS L=2 W=30
MP10 vp4  vp5  VDD  VDD  PMOS L=2 W=30
MP11 vp5  Vbias2      vp4  VDD  PMOS L=2 W=30
MP12 Vpcas Vpcas vp5  VDD  PMOS L=2 W=30

MBM1 Vbiasn      Vbiasn      0      0      NMOS L=2 W=10
MBM2 Vbiasp      Vbiasn      Vr     0      NMOS L=2 W=40
MBM3 Vbiasn      Vbiasp      VDD  VDD  PMOS L=2 W=30
MBM4 Vbiasp      Vbiasp      VDD  VDD  PMOS L=2 W=30

Rbias Vr     0      6.5k

MSU1 Vsur Vbiasn      0      0      NMOS L=2 W=10
MSU2 Vsur Vsur  VDD  VDD  PMOS L=100 W=10
MSU3 Vbiasp      Vsur  Vbiasn      0      NMOS L=1 W=10
.ends

```

Simulation Outputs:

DC Operating Point ...100%

vbias1 = 3.840356e+00

vhigh = 4.678606e+00

vbias2 = 3.430383e+00

vncas = 2.414760e+00

vpcas = 2.412956e+00

vbias3 = 1.493566e+00

vlow = 3.238476e-01

vbias4 = 1.086655e+00

Figure 20.44, Problem 20.19
In the figure below both P-channel transistors are 30/2 size initially.
The circuit is designed to mirror 20ua with V_{sg} of 1.15V.



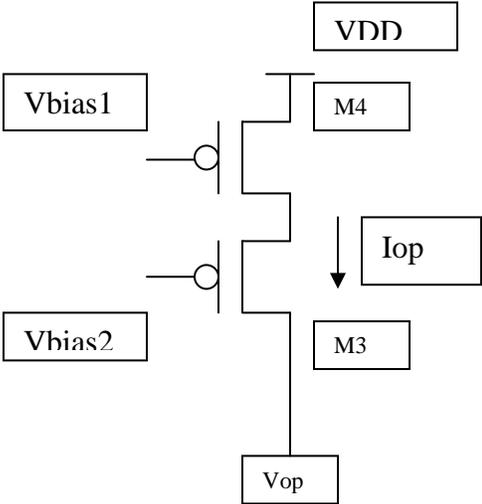
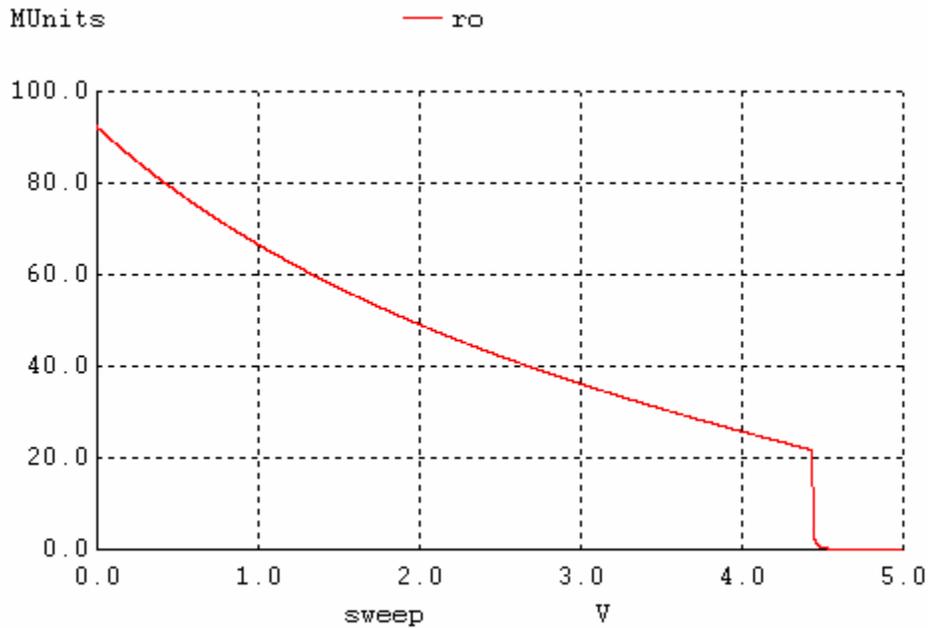


Figure 20.44

Case1: Reduce the size of M3, say 15/2

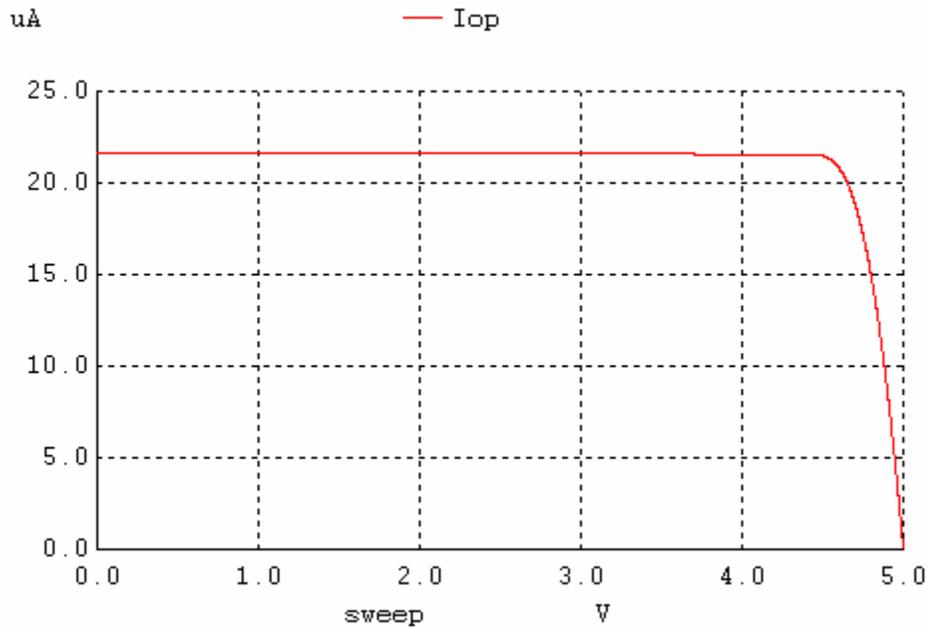When we reduce the size of the transistor M3, the source voltage of M3 will go up and so does V_{gs3} and V_{ds3} . since I_d is proportional to $1/L$ and proportional to V_{ds}^2 the overall current will be constant (since the transistors are in saturation). However since V_{gs} has increased the transistor M3 will enter in saturation earlier.





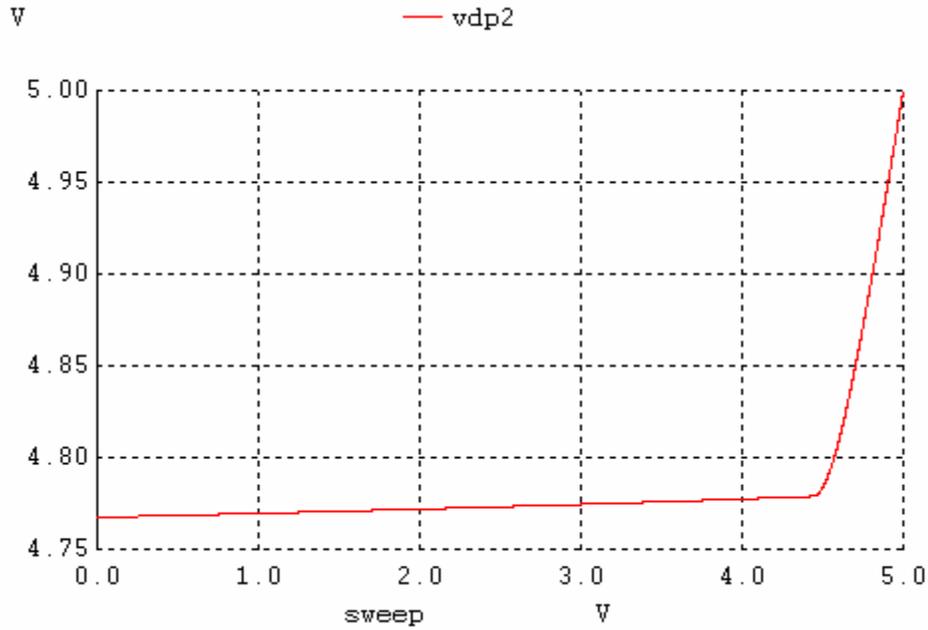


In Vdp2 plot, for 15/2 device, we see the source voltage of the transistor is varying with changing V_{op} which is causing the output resistance of the cascode to vary with varying V_{op} .

Case2: Increase the size of M3, say 60/2

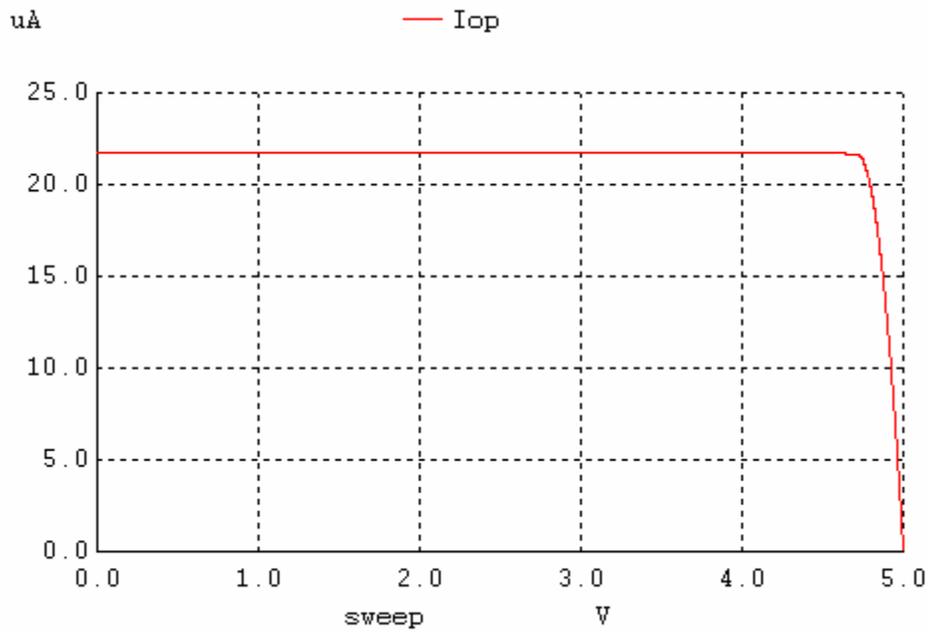When we increase the size of the transistor M3, the source voltage will decrease. since I_d is proportional to $1/L$ and proportional to V_{ds}^2 , the overall current will be constant. However since V_{gs} has decreased the transistor M3 will enter in saturation later.



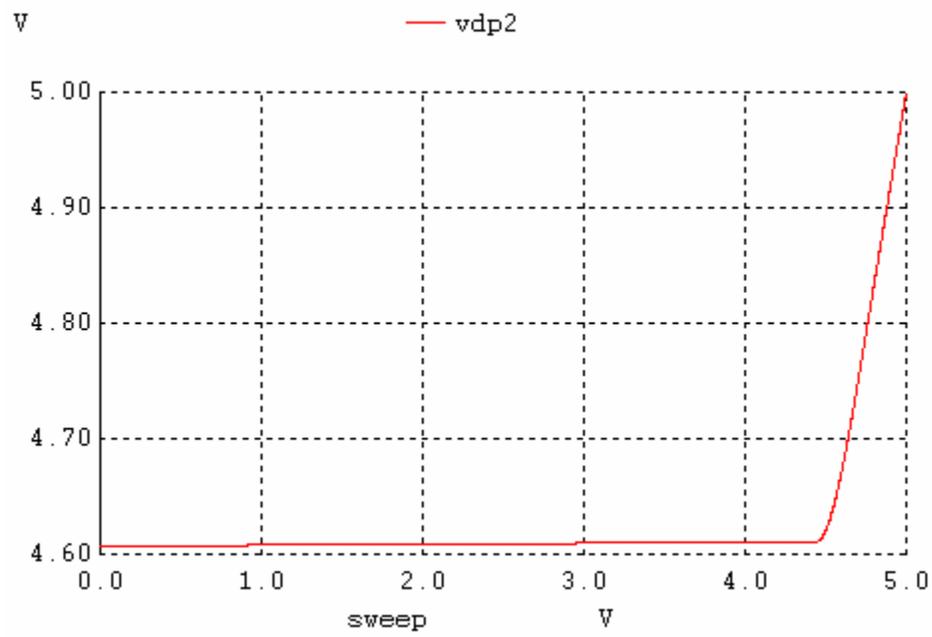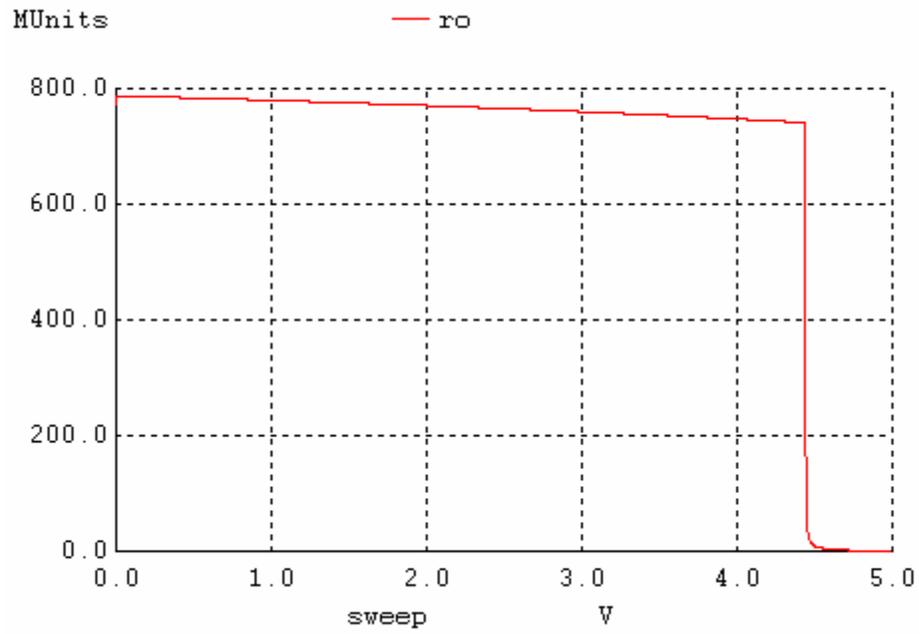

Vdp2 plots are source voltage of M3.

*** Figure 20.44_PMOS CMOS: Circuit Design, Layout, and Simulation ***

```
.control
destroy all
run
let Iop=Vop#branch
let ro=abs(1/deriv(Iop))
plot ro
plot Iop ylimit 0 25u
.endc
```

```
.option scale=1u rshunt=1e9
.dc vop 0 5 1m
```

```
VDD VDD 0 DC 5
Vop Vop 0 DC 2.5
```

```
Xbias VDD Vbias1 Vbias2 Vbias3 Vbias4 Vhigh Vlow Vncas Vpcas bias
```

```
M2P Vdp2 Vbias1 VDD VDD PMOS L=2 W=30
M4P Vop Vbias2 Vdp2 VDD PMOS L=2 W=15
```

```
.subckt bias VDD Vbias1 Vbias2 Vbias3 Vbias4 Vhigh Vlow Vncas Vpcas
```

```
MN1 Vbias2 Vbiasn 0 0 NMOS L=2 W=10
MN2 Vbias1 Vbiasn 0 0 NMOS L=2 W=10
MN3 Vncas Vncas vn1 0 NMOS L=2 W=10
MN4 vn1 Vbias3 vn2 0 NMOS L=2 W=10
MN5 vn2 vn1 0 0 NMOS L=2 W=10
MN6 Vbias3 Vbias3 0 0 NMOS L=10 W=10
MN7 Vbias4 Vbias3 Vlow 0 NMOS L=2 W=10
MN8 Vlow Vbias4 0 0 NMOS L=2 W=10
MN9 Vpcas Vbias3 vn3 0 NMOS L=2 W=10
MN10 vn3 Vbias4 0 0 NMOS L=2 W=10
```

```
MP1 Vbias2 Vbias2 VDD VDD PMOS L=10 W=30
MP2 Vhigh Vbias1 VDD VDD PMOS L=2 W=30
MP3 Vbias1 Vbias2 Vhigh VDD PMOS L=2 W=30
MP4 vp1 Vbias1 VDD VDD PMOS L=2 W=30
MP5 Vncas Vbias2 vp1 VDD PMOS L=2 W=30
MP6 vp2 Vbias1 VDD VDD PMOS L=2 W=30
MP7 Vbias3 Vbias2 vp2 VDD PMOS L=2 W=30
MP8 vp3 Vbias1 VDD VDD PMOS L=2 W=30
MP9 Vbias4 Vbias2 vp3 VDD PMOS L=2 W=30
MP10 vp4 vp5 VDD VDD PMOS L=2 W=30
```

```

MP11 vp5 Vbias2 vp4 VDD PMOS L=2 W=30
MP12 Vpcas Vpcas vp5 VDD PMOS L=2 W=30

MBM1 Vbiasn Vbiasn 0 0 NMOS L=2 W=10
MBM2 Vbiasp Vbiasn Vr 0 NMOS L=2 W=40
MBM3 Vbiasn Vbiasp VDD VDD PMOS L=2 W=30
MBM4 Vbiasp Vbiasp VDD VDD PMOS L=2 W=30

```

```
Rbias Vr 0 6.5k
```

```

MSU1 Vsur Vbiasn 0 0 NMOS L=2 W=10
MSU2 Vsur Vsur VDD VDD PMOS L=100 W=10
MSU3 Vbiasp Vsur Vbiasn 0 NMOS L=1 W=10

```

```
.ends
```

```

.MODEL NMOS NMOS LEVEL = 3
+ TOX = 200E-10 NSUB = 1E17 GAMMA = 0.5
+ PHI = 0.7 VTO = 0.8 DELTA = 3.0
+ UO = 650 ETA = 3.0E-6 THETA = 0.1
+ KP = 120E-6 VMAX = 1E5 KAPPA = 0.3
+ RSH = 0 NFS = 1E12 TPG = 1
+ XJ = 500E-9 LD = 100E-9
+ CGDO = 200E-12 CGSO = 200E-12 CGBO = 1E-10
+ CJ = 400E-6 PB = 1 MJ = 0.5
+ CJSW = 300E-12 MJSW = 0.5
*

```

```

.MODEL PMOS PMOS LEVEL = 3
+ TOX = 200E-10 NSUB = 1E17 GAMMA = 0.6
+ PHI = 0.7 VTO = -0.9 DELTA = 0.1
+ UO = 250 ETA = 0 THETA = 0.1
+ KP = 40E-6 VMAX = 5E4 KAPPA = 1
+ RSH = 0 NFS = 1E12 TPG = -1
+ XJ = 500E-9 LD = 100E-9
+ CGDO = 200E-12 CGSO = 200E-12 CGBO = 1E-10
+ CJ = 400E-6 PB = 1 MJ = 0.5
+ CJSW = 300E-12 MJSW = 0.5


```

```
.end
```

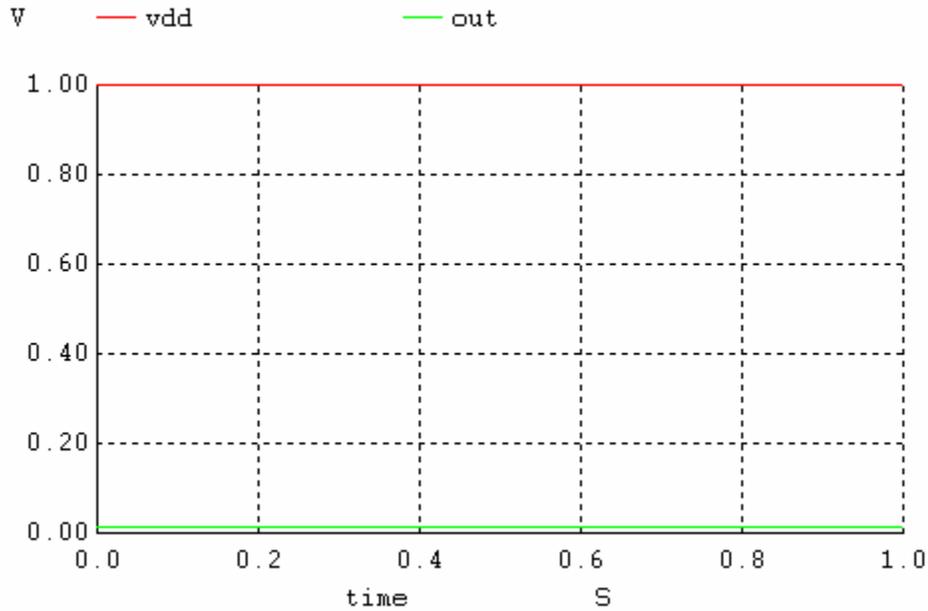
Problem 20.20

Should the voltage labeled “Out” in Fig. 20.49 be at a specific value? Why or Why not.

No, it doesn't need to be at a specific value. It will be pulled towards either VDD or GND depending on whether MOP or MON is stronger.



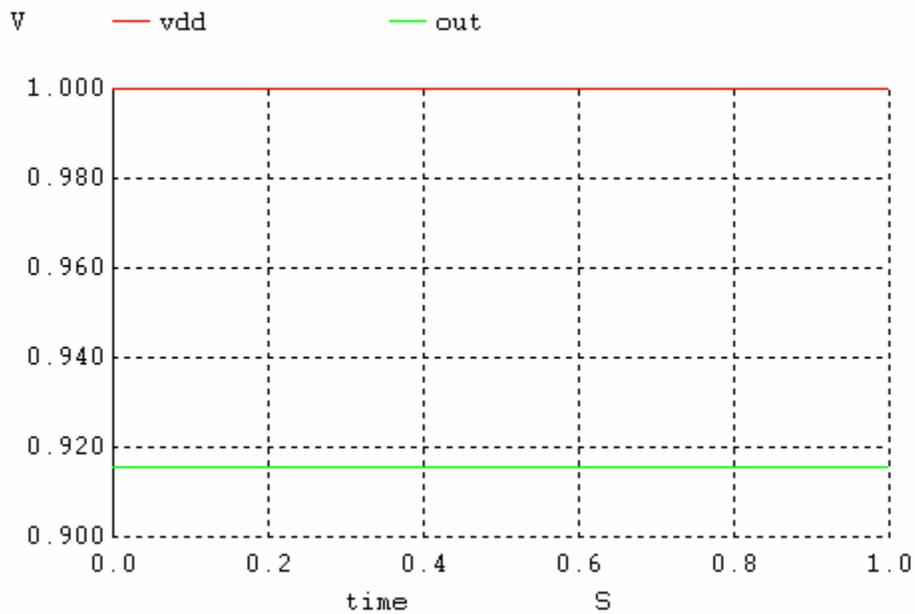Plot where NMOS is stronger (NMOS W=500, PMOS W=1000)



Plot where PMOS is stronger (NMOS W=100, PMOS W=5000)

Changing the W/L ratios of MON and MOP will effect the current through stage 2 which is expected but it won't effect the reference current in stage 1.