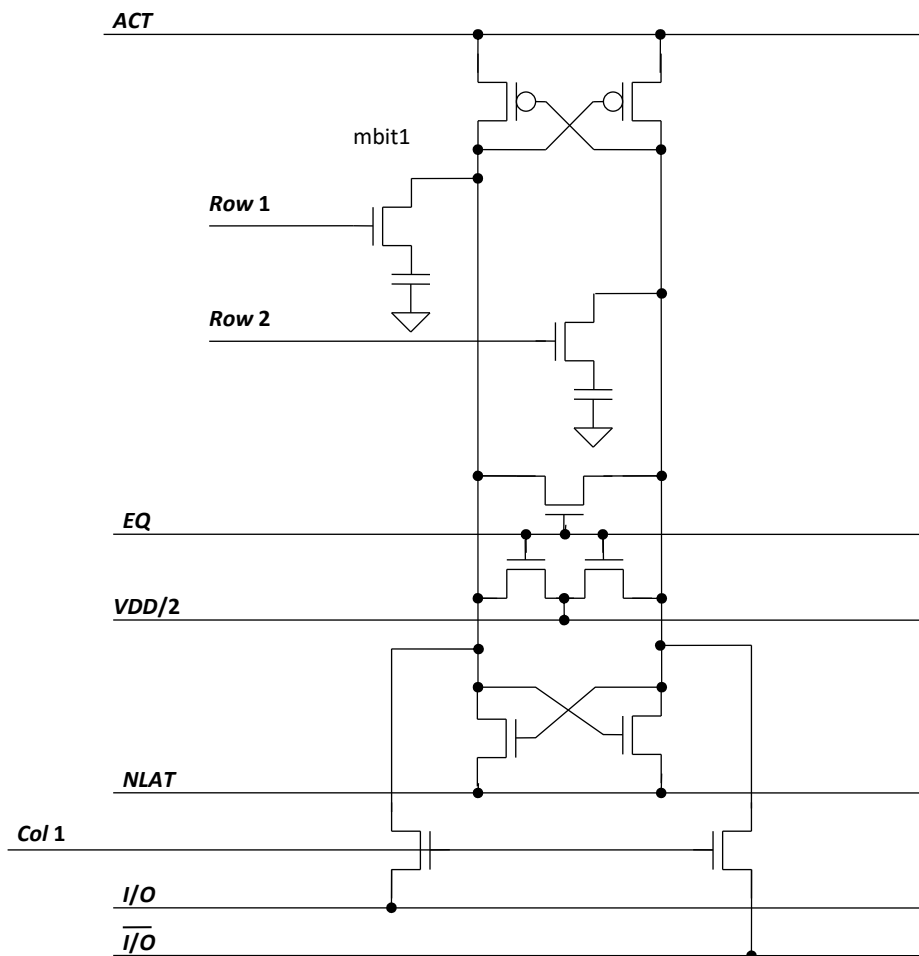


ECG 721 Memory Circuit Design, Midterm exam

Practice, University of Nevada, Las Vegas

Name: _____

- Show your work to get credit.
 - Open book and closed notes.
 - Do all work on these test sheets only (no extra paper).
1. On the back of this piece of paper sketch the waveforms, using a common time axis but several y-axes to make things clear, we would have if we write a 0 to mbit1 in the circuit seen below. State all assumptions. (15 points)



4. Is it possible to have only an n-well in a Flash memory technology? If so how and if not why? Use cross-sectional views to illustrate your understanding. (15 points)

5. Derive the relationship between V_R and V_I for the DSM circuit seen in Fig. 17.36. Is it bad if $V_R > V_I$? Why or why not? (20 points)

6. Show how to design a negative charge pump (voltage generator) that outputs a voltage less than $-2V_{DD}$. Comment on your design and, of course, show a schematic. (20 points)