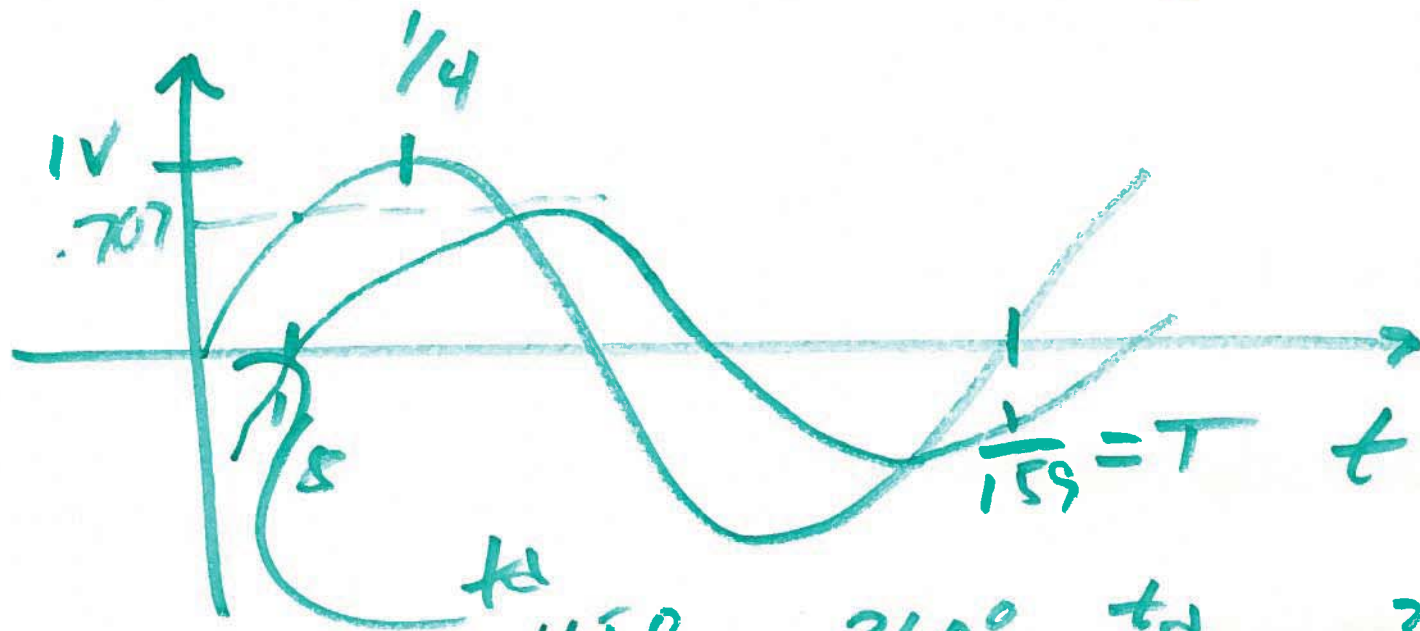


EE220 circuits 1

Lecture 26

Dec. 4, 2017

$$\phi = 45^\circ = 360$$



$$\phi = 45^\circ = 360^\circ \cdot \frac{t_d}{T} = 360^\circ \cdot t_d \cdot 159$$


17

Quiz #17 EE 220 Fall 2017 Name: _____

Closed book and notes.

Show your work for credit!

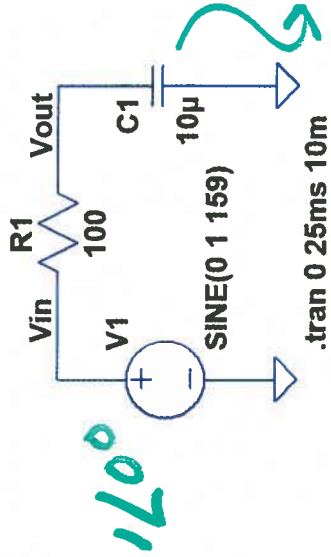1. Using phasors determine V_{out} in the following circuit and plot, along with V_{in} , on the same plot. (5 points)



$$V_{out} = 1 \angle 0^\circ \cdot \frac{0 + j(-100)}{100 + j(-100)}$$

$$= -j \cdot 100$$

$$f(-j) = f(x) \text{ even! } \frac{j \cdot 2\pi \cdot 159 \cdot 10^{-4}}{j \cdot 2\pi \cdot 159 \cdot 10^{-4}} = 100(0 + j(-1))$$

100(0 + j(-1))


$$V_{out} = \frac{1 \angle 0^\circ \cdot 100(0 + j(-1))}{100(1 + j(-1))}$$

$$= \frac{1 \angle 0^\circ \cdot 1 \angle -90^\circ}{1 + j(-1)}$$

$$|V_{out}| = \frac{1}{\sqrt{1^2 + (-1)^2}} = \frac{1}{\sqrt{2}} = 0.707$$



$$\angle V_{out} = 90^\circ - \tan^{-1} \frac{-1}{1} = 90^\circ + \tan^{-1} \frac{1}{1} = 90^\circ + 45^\circ = 135^\circ$$

2/2

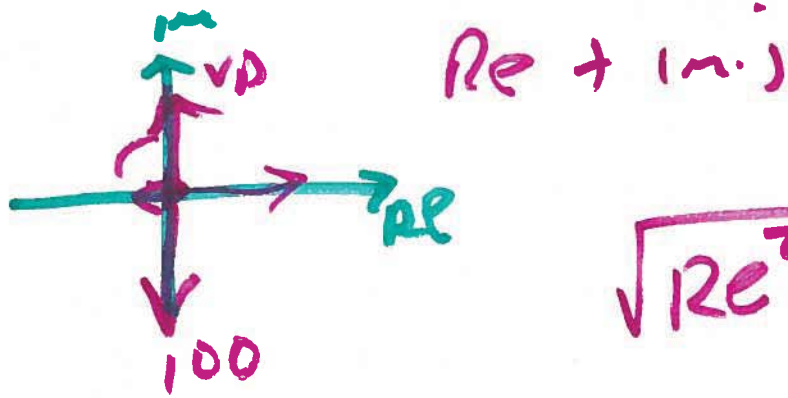

$$V(j\omega) = I(j\omega) \cdot \frac{1}{j\omega C} \tan^{-1} \frac{Im}{Re}$$

$0 + j(-100)$
 Z_C
 Reactance

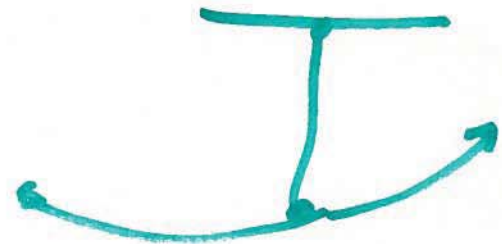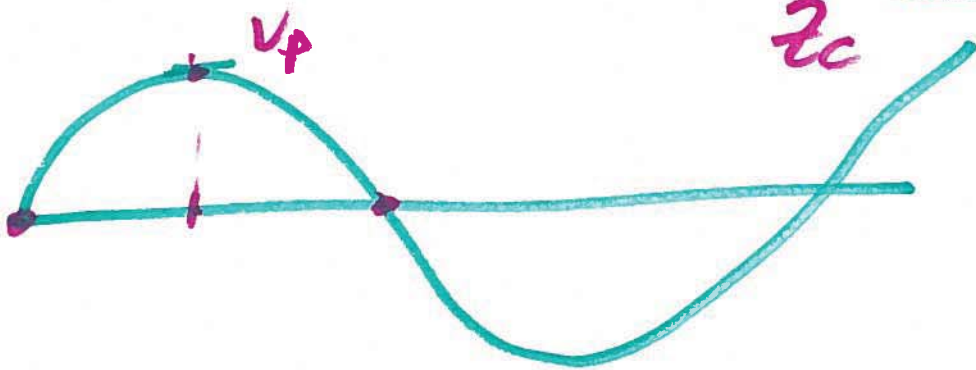

impedance = Res + Reactance

3)


$$-17 \text{ dB} = 20 \log V_{\text{RT}}$$


$$V_{\text{RT}} = 10^{-17/20} = .141 \text{ V}$$

$$1 \text{ kHz} = f$$

$$f = \frac{1}{T} \quad -81^\circ = 360^\circ \cdot \frac{t_d}{1 \text{ ms}} = 360 \cdot t_d \cdot 1 \text{ kHz}$$
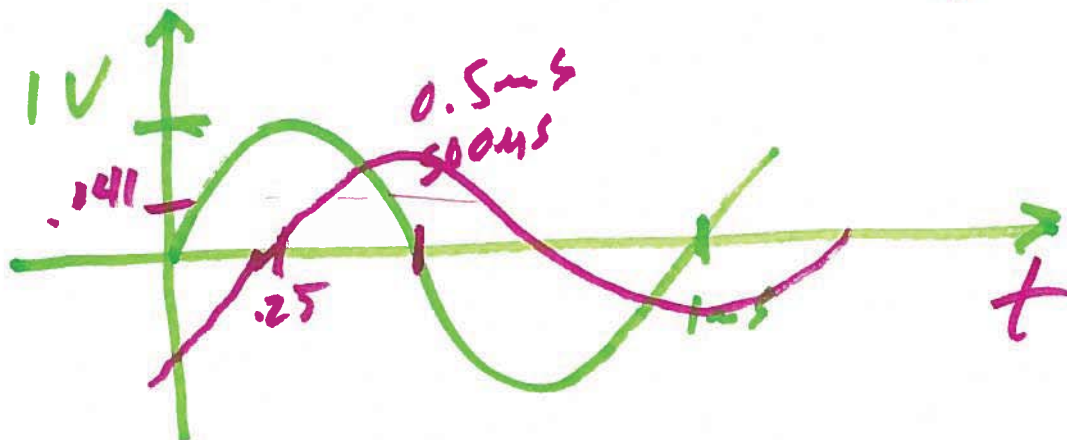
$$t_d = \frac{81}{360} \cdot 1 \text{ ms} = 225 \mu\text{s} = 0.225 \text{ ms}$$



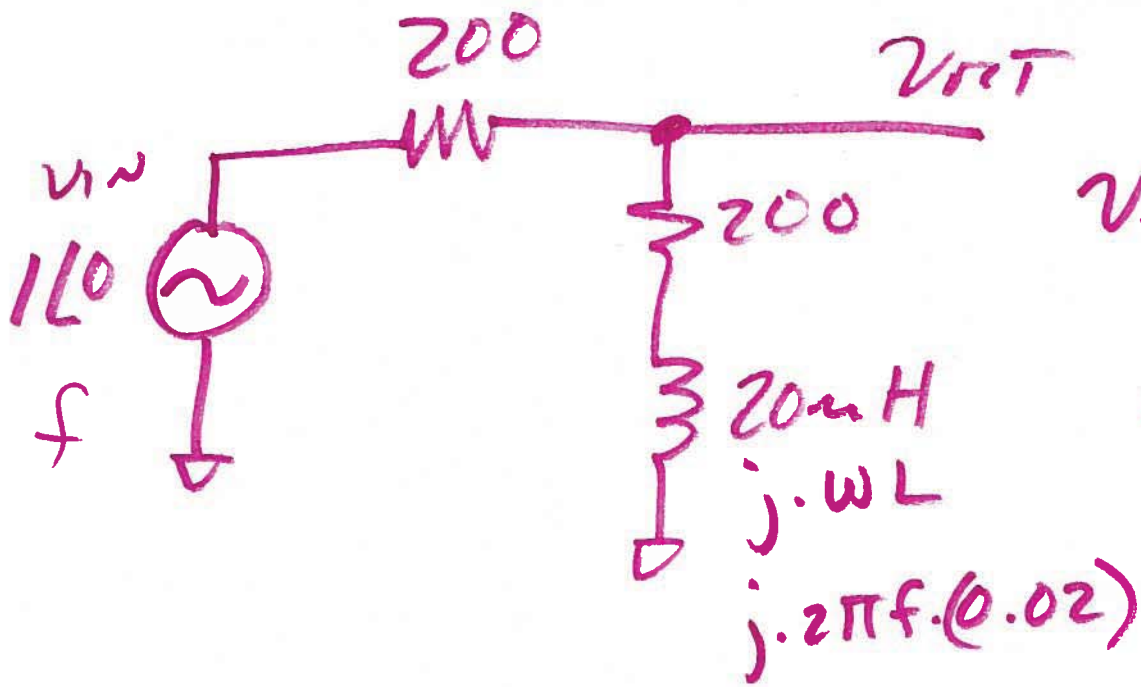

$$u_{nT} = u_w \cdot \frac{200 + j\omega L}{200 + 200 + j\omega L}$$

$$\frac{u_{nT}}{u_w} = \frac{200 + j \cdot 2\pi f \cdot (0.02)}{400 + j \cdot 2\pi \cdot f \cdot (0.02)}$$

$$200 \pm \frac{200}{j \cdot 2\pi f \cdot (0.02)} = 0$$

$$f_z = \frac{200}{2\pi \cdot (0.02)} = 1.59 \text{ kHz}$$


$$400 = 2\pi f_p \cdot (0.02)$$

$$f_p = \frac{400}{2\pi \cdot (0.02)} = 3.18 \text{ kHz}$$


5)

$$f_z = 1.59 \text{ kHz}$$

$$f_p = 3.18 \text{ kHz}$$

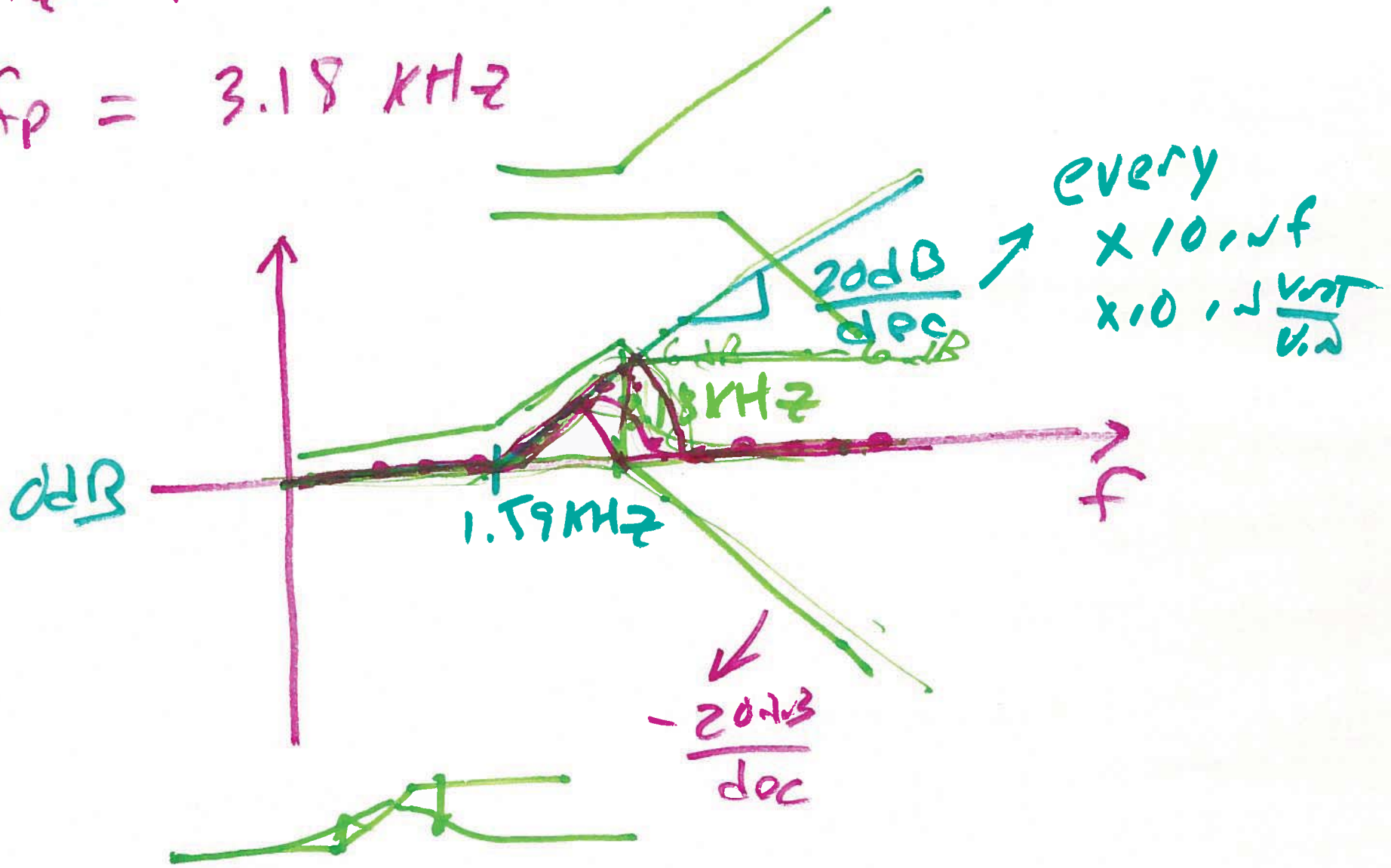

b)

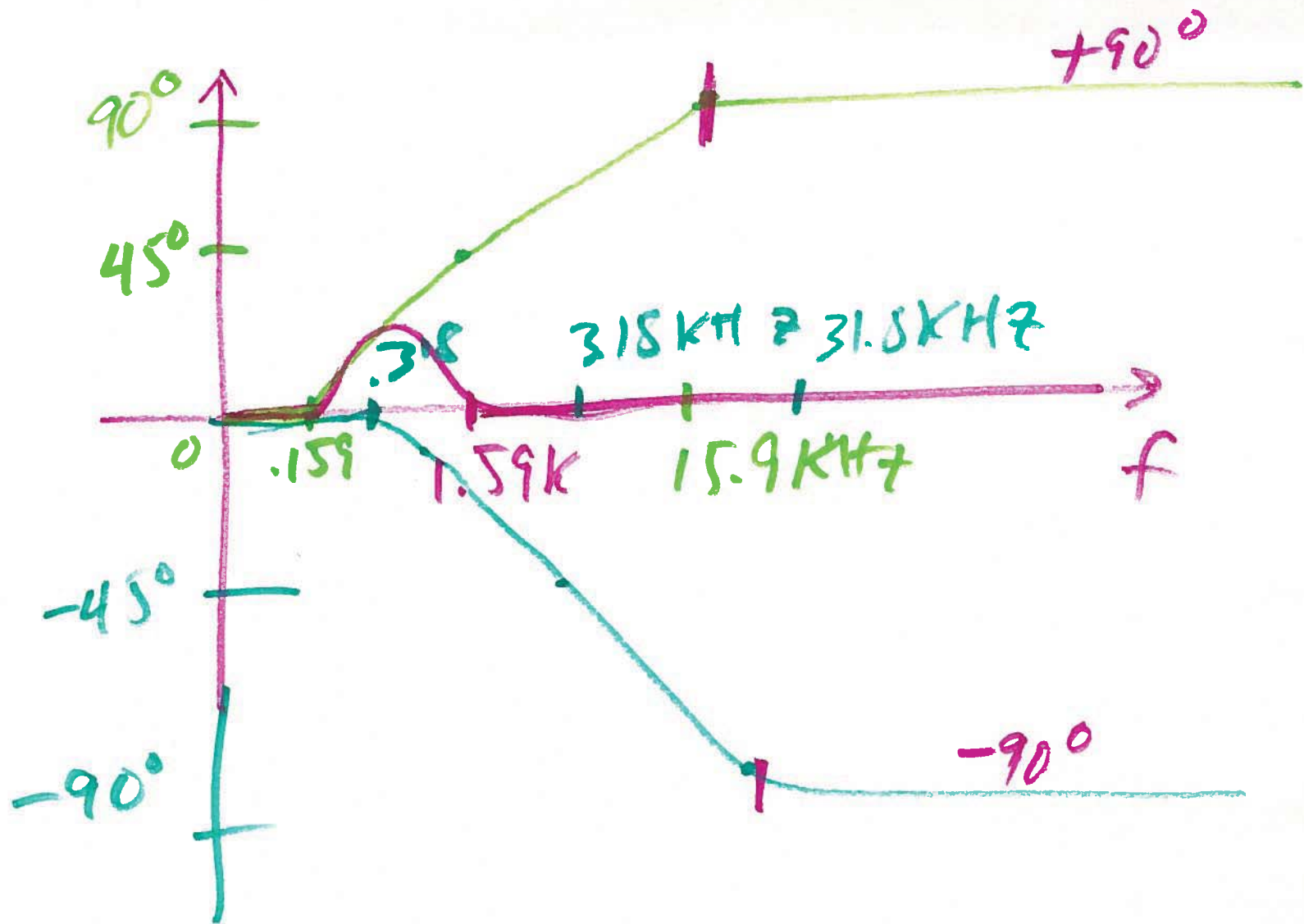

$$\frac{v_{IT}}{v_{i0}} = \frac{200 \left(1 + j2\pi f \frac{0.02}{200} \right)}{400 \left(1 + j2\pi f \cdot \frac{0.02}{400} \right)}$$

$$f_z = \frac{1}{2\pi \cdot \frac{0.02}{200}} \Rightarrow \frac{1}{f_z} = 2\pi \cdot \frac{0.02}{200}$$

$$f_p = \frac{1}{2\pi \cdot \frac{0.02}{400}} \Rightarrow \frac{1}{f_p} = 2\pi \cdot \frac{0.02}{400}$$

$$\frac{1}{2} \cdot \frac{1 + j \frac{f}{f_z}}{1 + j \frac{f}{f_p}}$$