


$g_m = 20 \mu A/V$ $\frac{w}{L} = \frac{500 \mu}{5 \mu}$ $k_{pn} = 9.38 \times 10^{-6}$ $V_{THN} = 1.2$
 $k_{pp} = 4.8 \times 10^{-6}$ $V_{THP} = 1.75$

NMOS

$$g_m = \sqrt{2 k_{pn} \frac{w}{L} I_D}$$

$$20 \mu = \sqrt{2 \cdot 9.38 \times 10^{-6} \frac{500 \mu}{5 \mu} I_D}$$

$$I_D = 213 nA$$

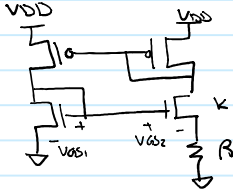

$$V_{GS1} = V_{GS2} + I_D R$$

$$\sqrt{\frac{2 I_D}{k_{pn} \frac{w}{L}}} + V_{THN} = \sqrt{\frac{2 I_D}{k_{pn} \frac{w}{L}}} + V_{THP} + I_D R$$

$$\left(1 - \frac{1}{\sqrt{k}}\right) \sqrt{\frac{2 I_D}{k_{pn} \frac{w}{L}}} = I_D R$$

$$\left(1 - \frac{1}{\sqrt{k}}\right)^2 \frac{2 I_D}{k_{pn} \frac{w}{L}} = I_D^2 R^2$$

$$R^2 = \left(1 - \frac{1}{\sqrt{k}}\right)^2 \frac{2}{I_D k_{pn} \frac{w}{L}}$$

$$R = \left(1 - \frac{1}{\sqrt{k}}\right) \sqrt{\frac{2}{I_D k_{pn} \frac{w}{L}}} \quad \text{let } k=4$$

$$R = \sqrt{\frac{1}{2 I_D k_{pn} \frac{w}{L}}} \Rightarrow \frac{1}{R} = g_m = 20 \mu = \sqrt{2 I_D k_{pn} \frac{w}{L}}$$


$R = \frac{1}{20 \mu} = 50 k$

Min V_{DD} for V_{biasn} to stabilize

$$V_{GS} + V_{GSsat} + V_{GS}$$


$$= 1.2 + 0 + 1.75$$
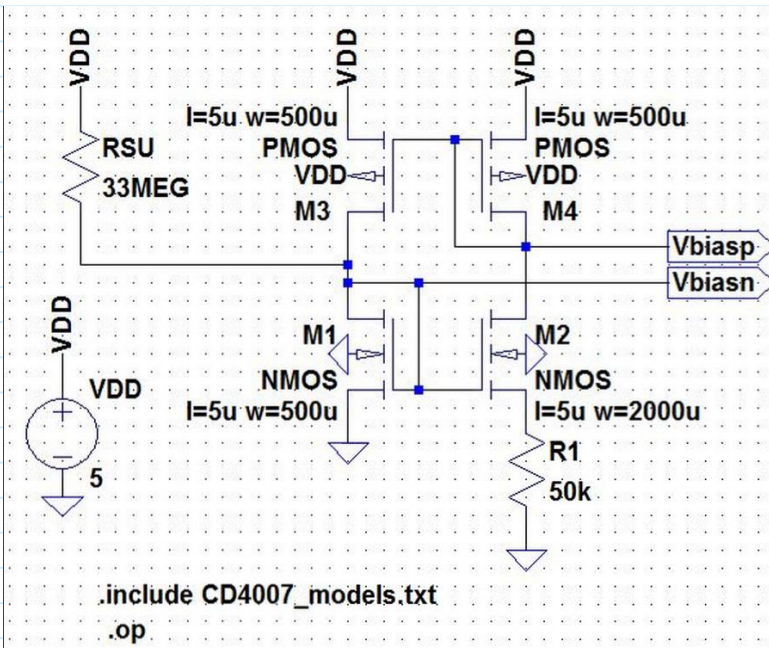
$$= 2.95 \Rightarrow \text{min } V_{DD}$$




P2

Thursday, April 16, 2015 11:23 PM

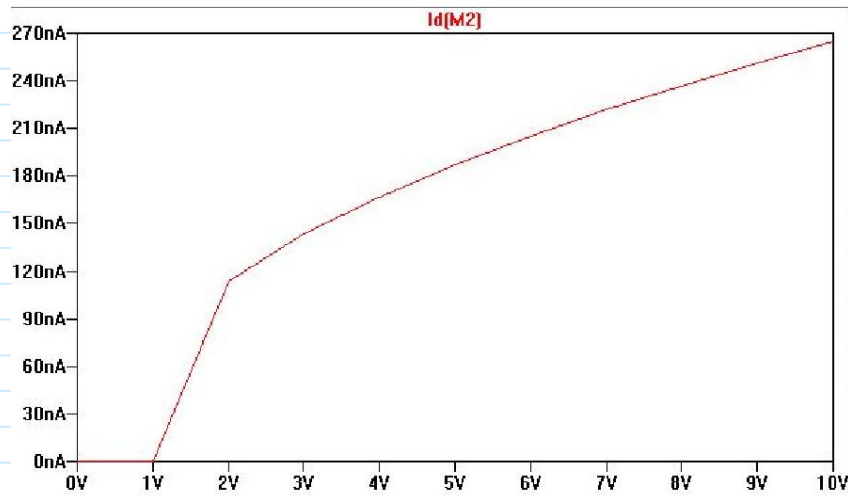

ID

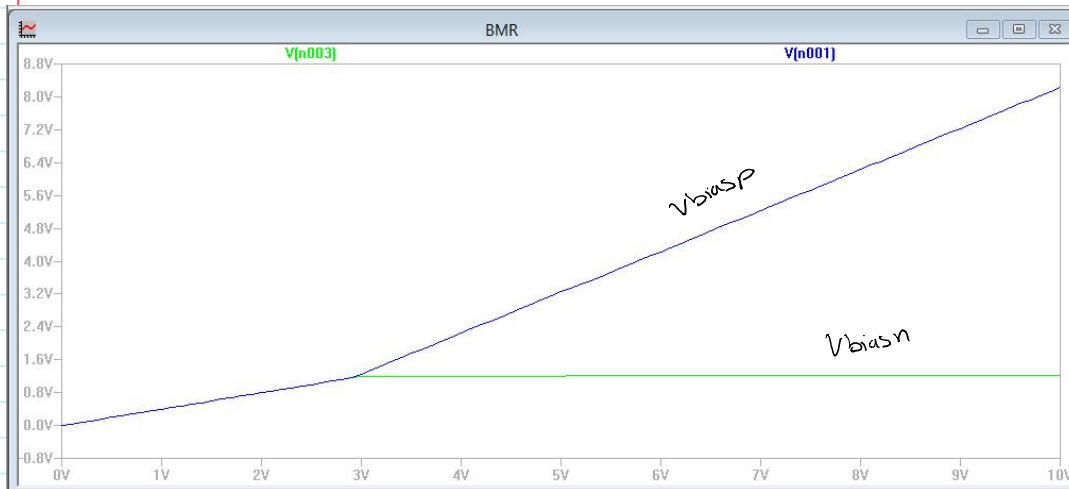We can see that our BMR from simulations rounds out at around 180-250nA. One of the possible reasons for this may be because that we are using a resistor as a startup and the resistor will steal some current from the mirror.



Vbiasn and Vbiasp

From the figure above, we can see that Vbiasn stays constant after the minimum VDD voltage (~3V) and Vbiasp follows VDD after that same minimum VDD voltage.